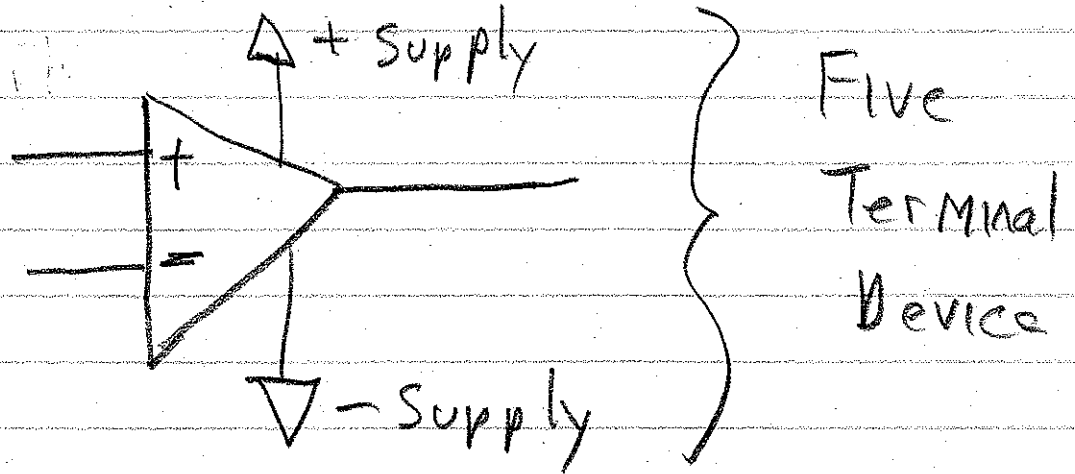


11/07/2006


G. 081

①

Op Amp



Our Usual View

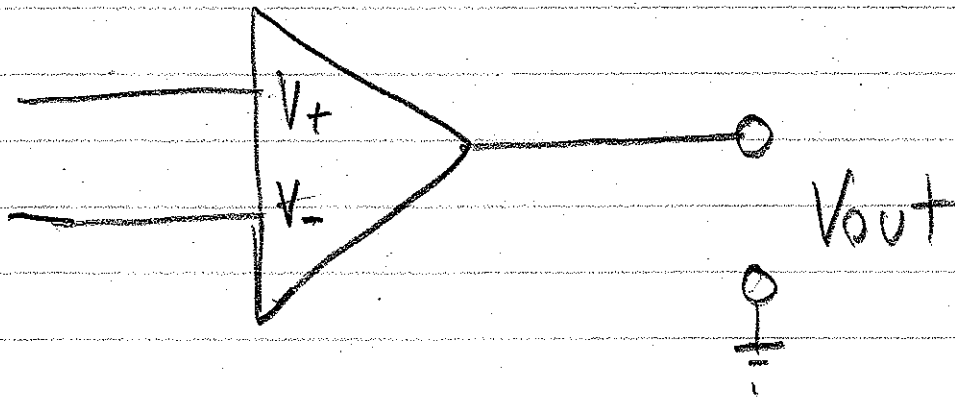


2

Simple Model

The output of the op-amp adjusts so as to make the V_+ input and the V_- input nearly equal

* And no current flows into the V_+ and V_- terminals

Simple Circuit Follower

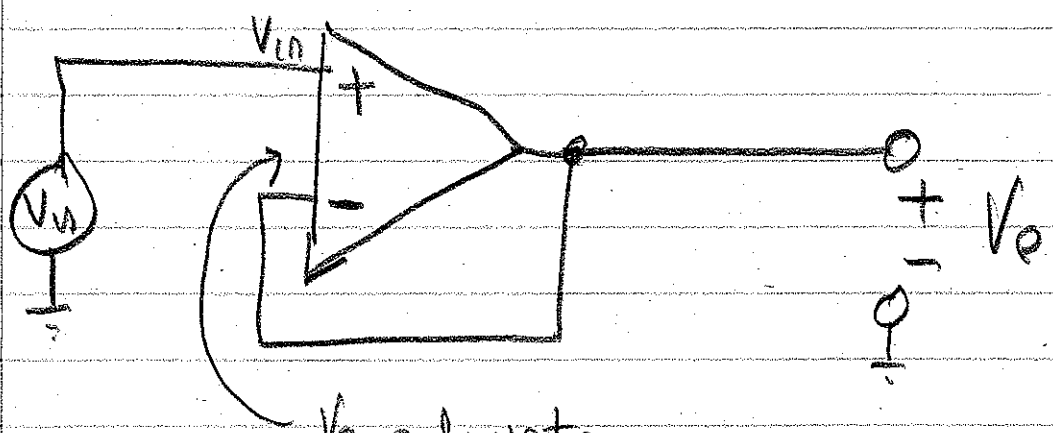


V_o adjusts
to make $V_- = V_+$

$$\Rightarrow V_o = V_{in}$$

3


An Aside on Motors

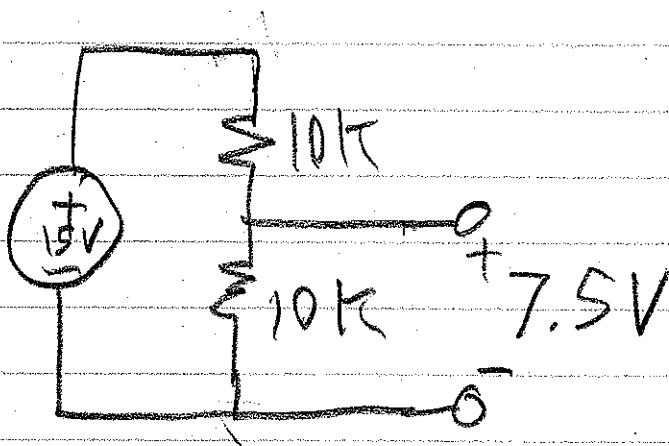Suppose one has a 15V supply
can one create 7.5V using
a resistor divider?




Yes!

When Driving a motor does

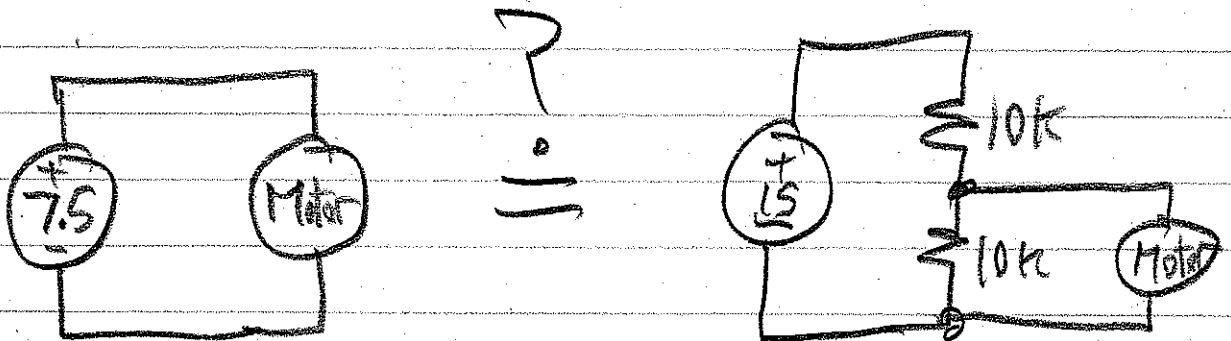


No

the motor "loads" the
divider

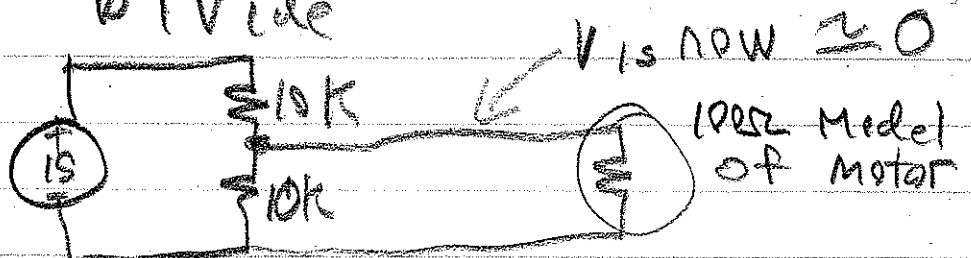


Use a op-amp Follower

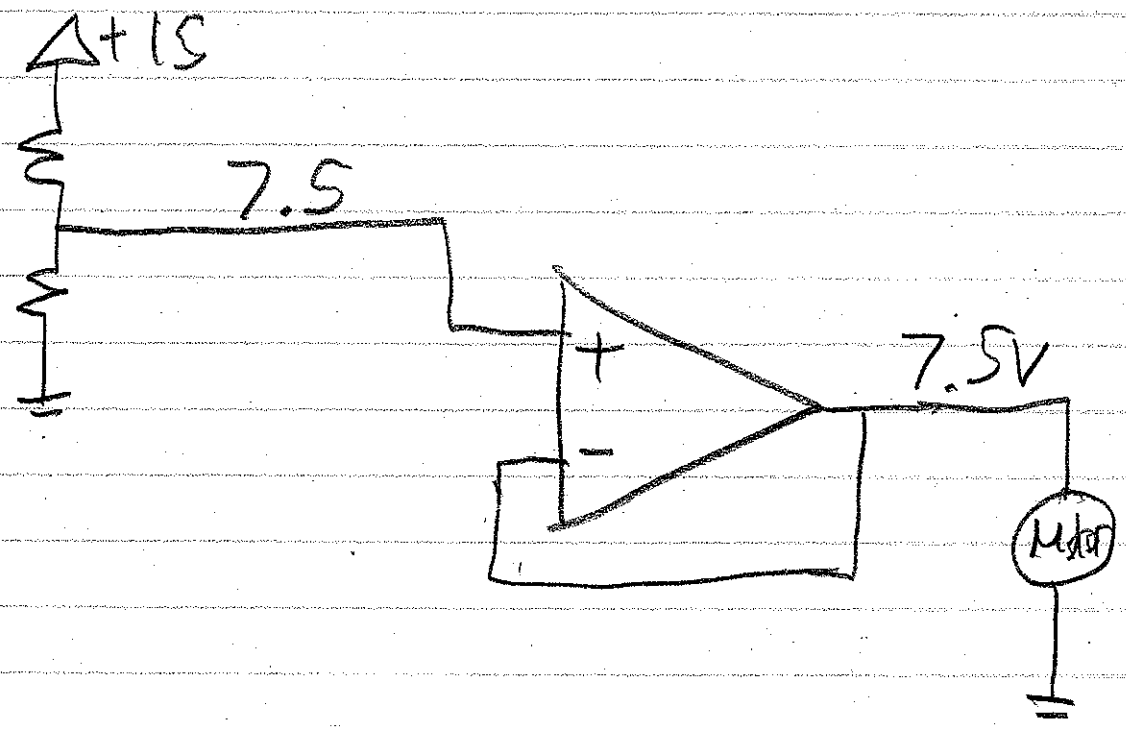

Why does follower help?


Need a better Model of op-amp!

More Detailed Op-amp Model

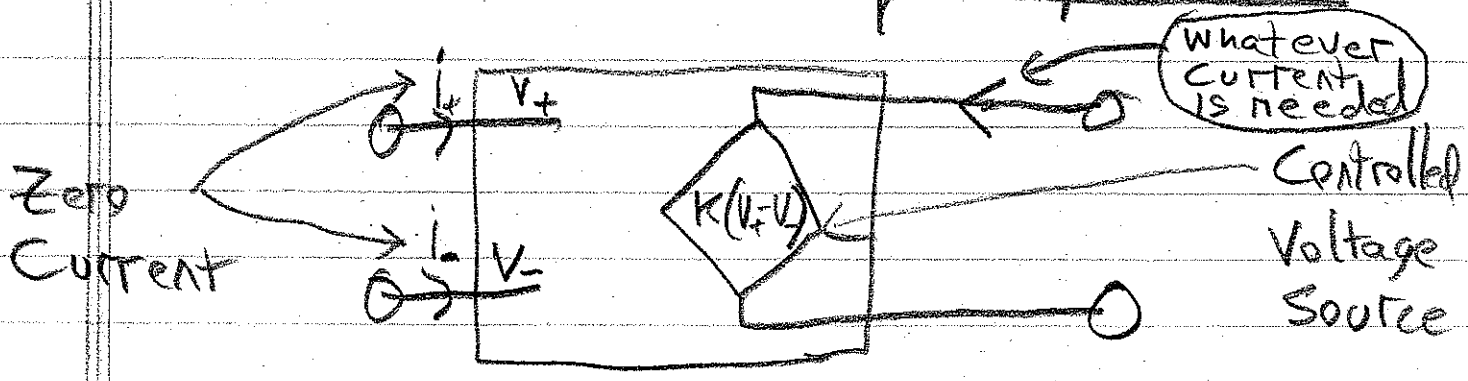

5

Follower

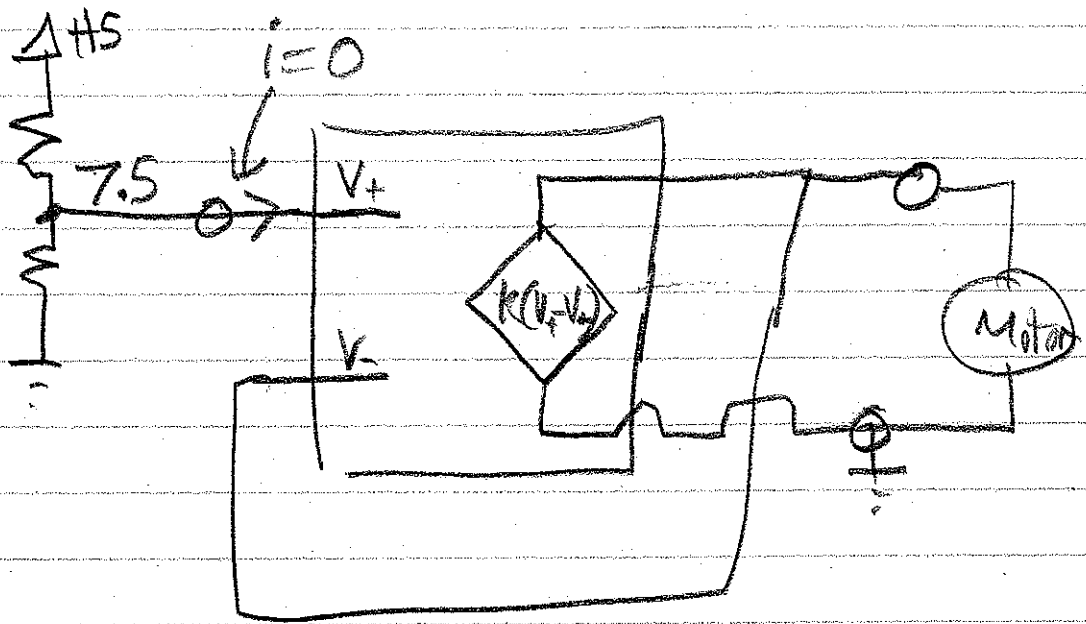


$$V_o = K (V_+ - V_-)$$

$$V_o = K (7.5 - V_o) \Rightarrow V_o = \frac{K}{K+1} 7.5$$

≈ 1 for large K


6

Simple Model is great for Design

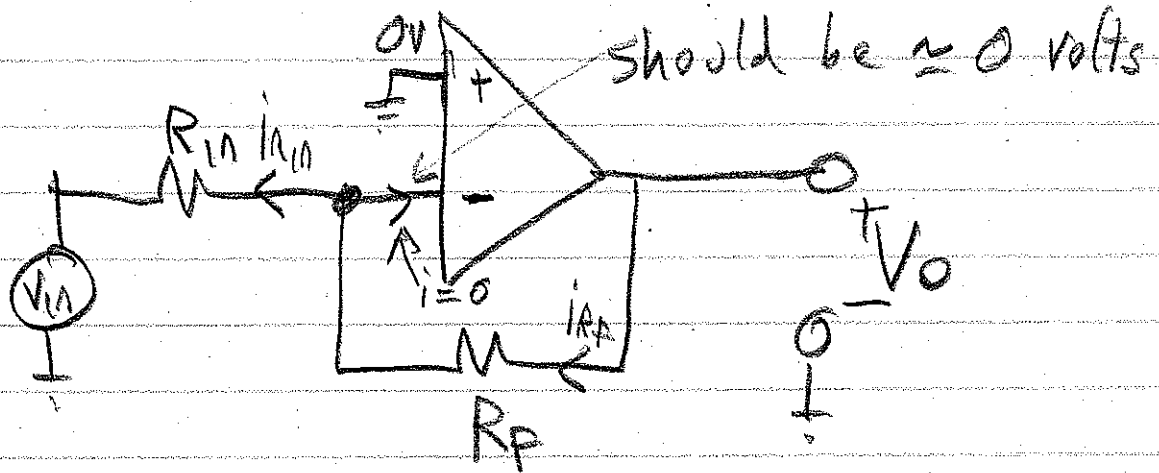

$$\frac{V_o - 0}{R_F} = i_{R_F} = i_{R_{in}} = \frac{0 - V_{in}}{R_{in}}$$
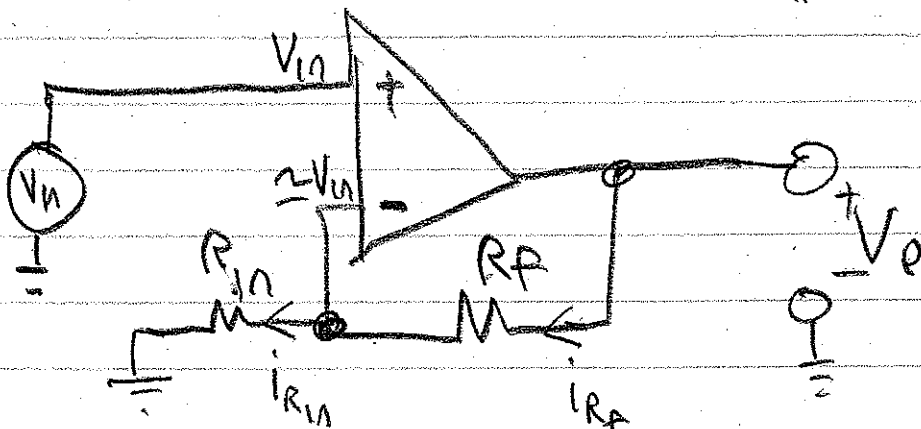
$$\Rightarrow V_o = -\frac{R_F}{R_{in}} V_{in}$$




$$\frac{V_o - V_{in}}{R_F} = \frac{V_{in} - 0}{R_{in}} \Rightarrow V_o = \left(1 + \frac{R_F}{R_{in}}\right) V_{in}$$

7

More Complicated Circuits


Summer (Inverting)

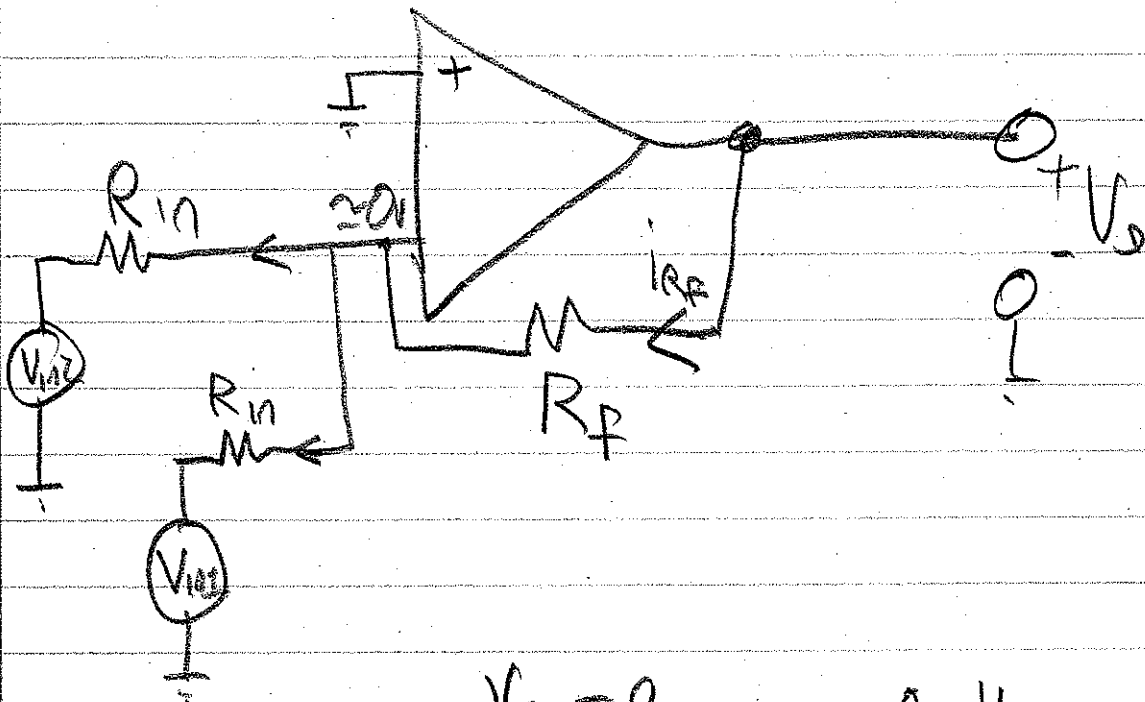

$$\frac{V_o - 0}{R_F} = \frac{0 - V_{in2}}{R_{in}} + \frac{0 - V_{in1}}{R_{in}}$$


$$V_o = - \frac{R_F}{R_{in}} (V_{in1} + V_{in2})$$

Level Shifter

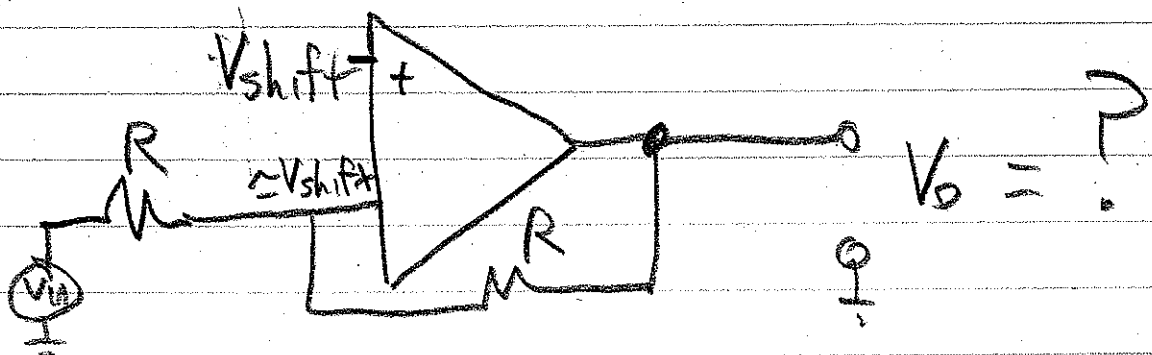

8

Non-inverting Amp Using Detailed Model

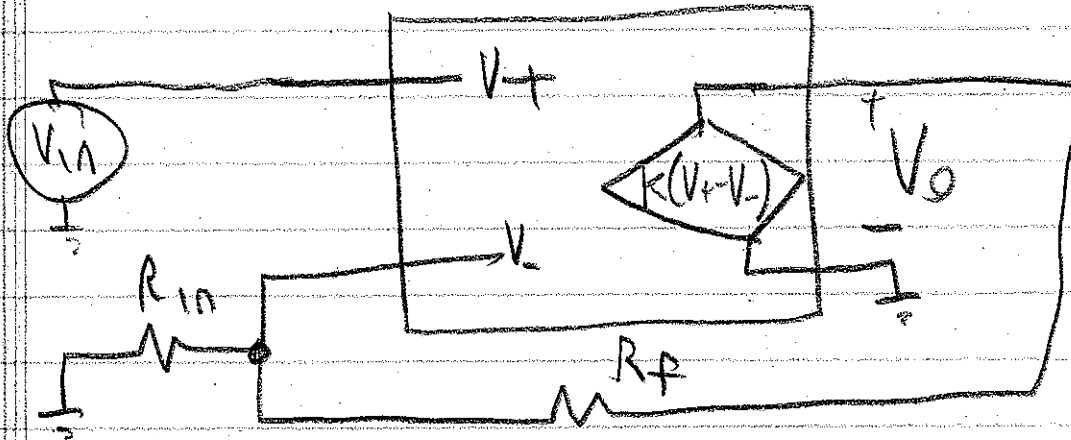

$$V_o = K (V_+ - V_-)$$

$\uparrow = V_o \frac{R_{in}}{R_{in} + R_f}$

$$V_o = K \left(V_{in} - \left(\frac{R_{in}}{R_{in} + R_f} \right) V_o \right)$$

$$\left(1 + K \frac{R_{in}}{R_{in} + R_f} \right) V_o = K V_{in}$$


$$V_o = \frac{K}{1 + K \frac{R_{in}}{R_{in} + R_f}} V_{in}$$

$= 1 + \frac{R_f}{R_{in}} \quad \text{if } K \text{ large}$


9

Question About Followers

"Good" Follower


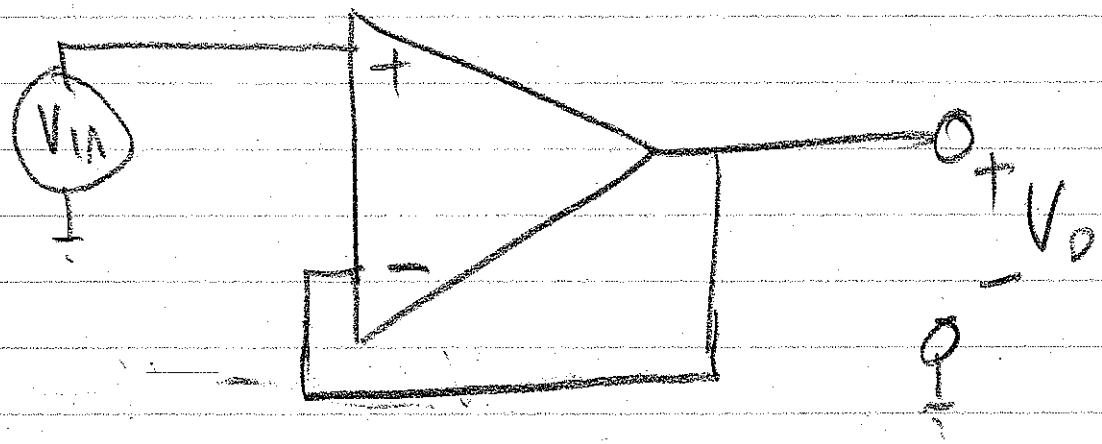


"Bad" Follower


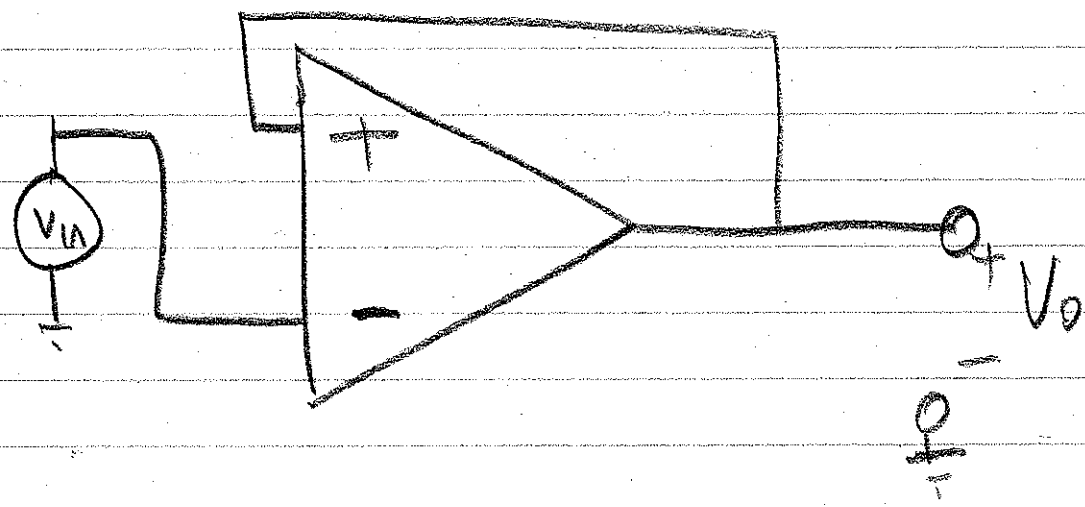


10

Simple Model

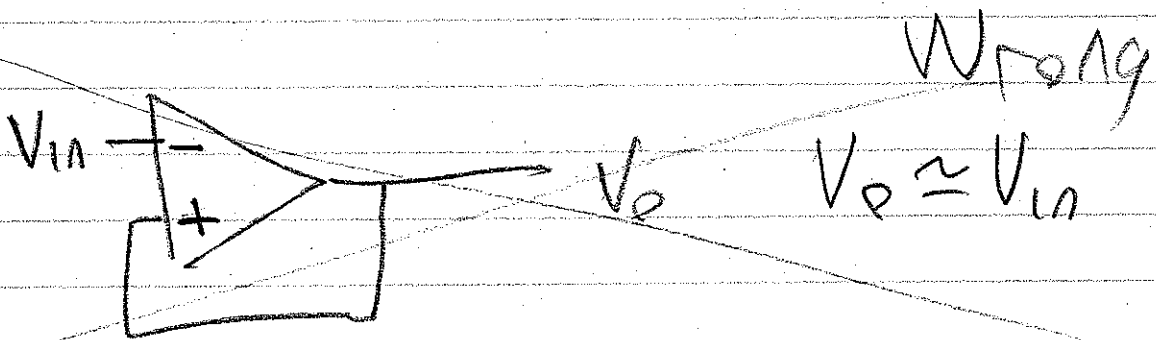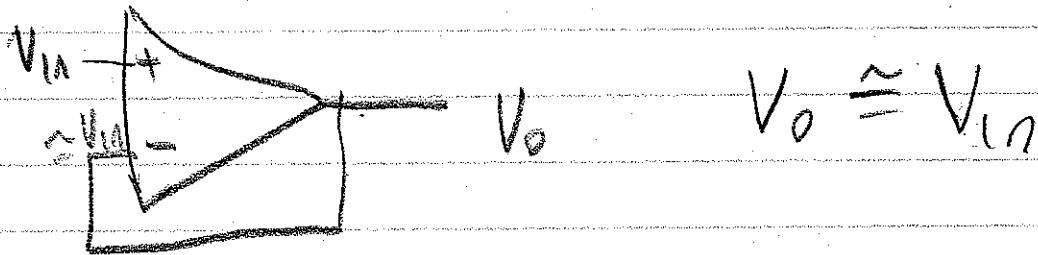



More Detailed Model

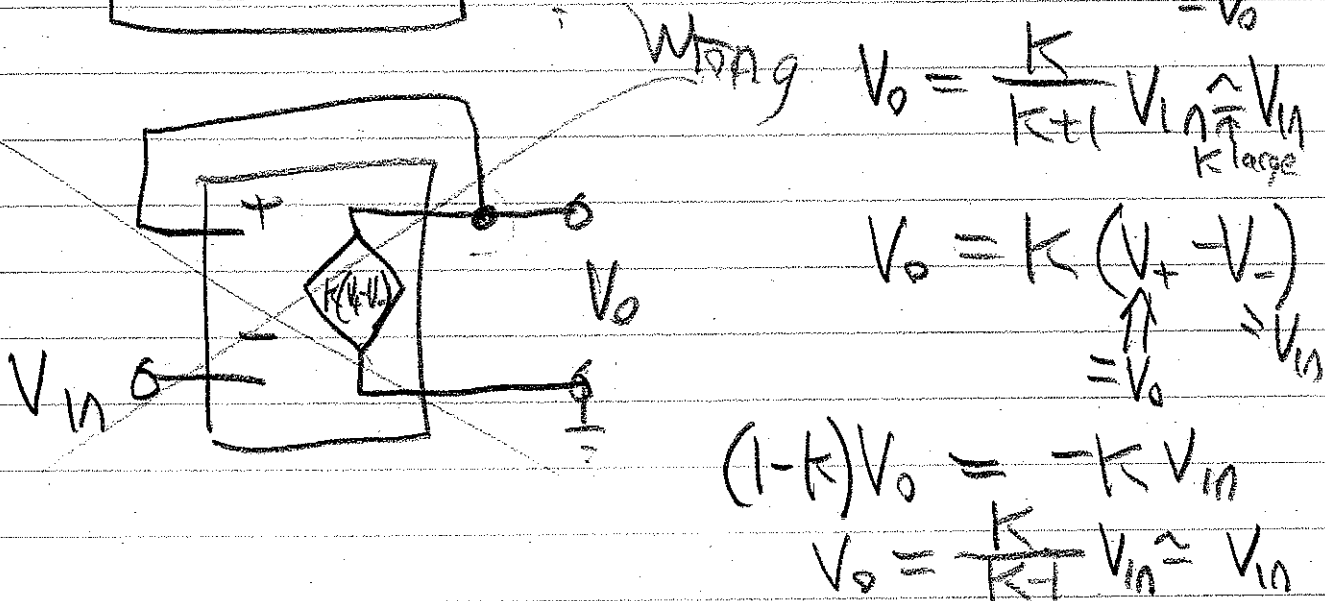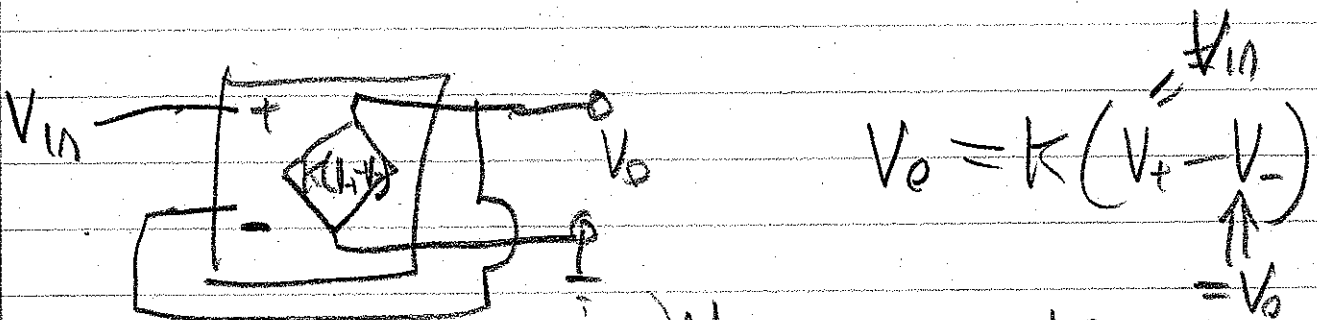

(11)

More Detailed Op amp model

What to Model

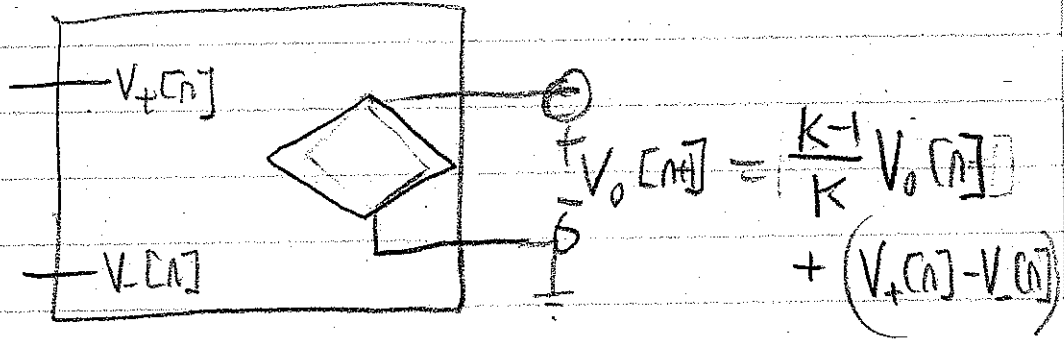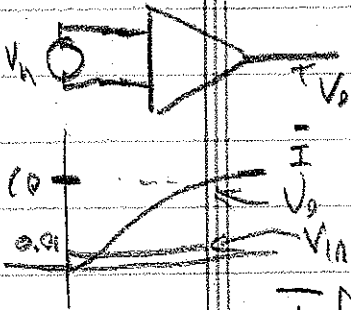

TF $K = 1000$

$$V_o[n] = \frac{999}{1000} V_o[n] + (V_+[n] - V_-[n])$$

What if $V_+[n] - V_-[n] = 0.1 \forall n$

If $V_o[0] = 0$

$$V_o[n] = \sum_{k=0}^{n-1} \left(\frac{999}{1000} \right)^{n-k} (V_+[k] - V_-[k])$$

$$V[1] = (V_+[0] - V_-[0])$$

$$V[2] = \frac{999}{1000} (V_+[0] - V_-[0]) + (V_+[1] - V_-[1])$$

⋮

12

Eventually

$$V_o[n] = V_o[n-1] = V[*] \text{ (for large } n)$$

$$V[*] - \frac{999}{1000} V[*] = 0.01$$

$$= \frac{1}{1000} V[*] = 0.01$$

$$V[*] = 1000$$

New Back to the question



$$V[n] = \frac{999}{1000} V[n-1] + (V_+[n-1] - V[n-1])$$

$$V[n] = -\frac{1}{1000} V[n-1] + V_+[n-1]$$

Net freq < 1



$$V[n] = \frac{999}{1000} V[n-1] + V_+[n-1]$$

$$V[n] = \frac{1.999}{1000} V[n-1] - V[n-1]$$

Net freq > 1