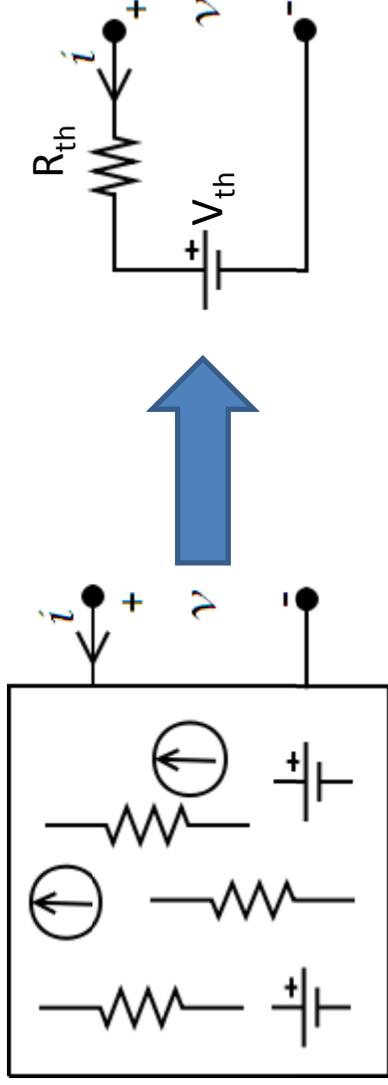


# 6.01 Review Session

Thevenin Equivalent Circuits


# What is Thevenin's Theorem?

- Any electrical network comprised of a combination of **linear** circuit elements (i.e. **voltage sources, current sources, resistors**) can be replaced by a single voltage source,  $V_{th}$ , and a single resistor,  $R_{th}$ .




# How can we get away with this?

- Linearity

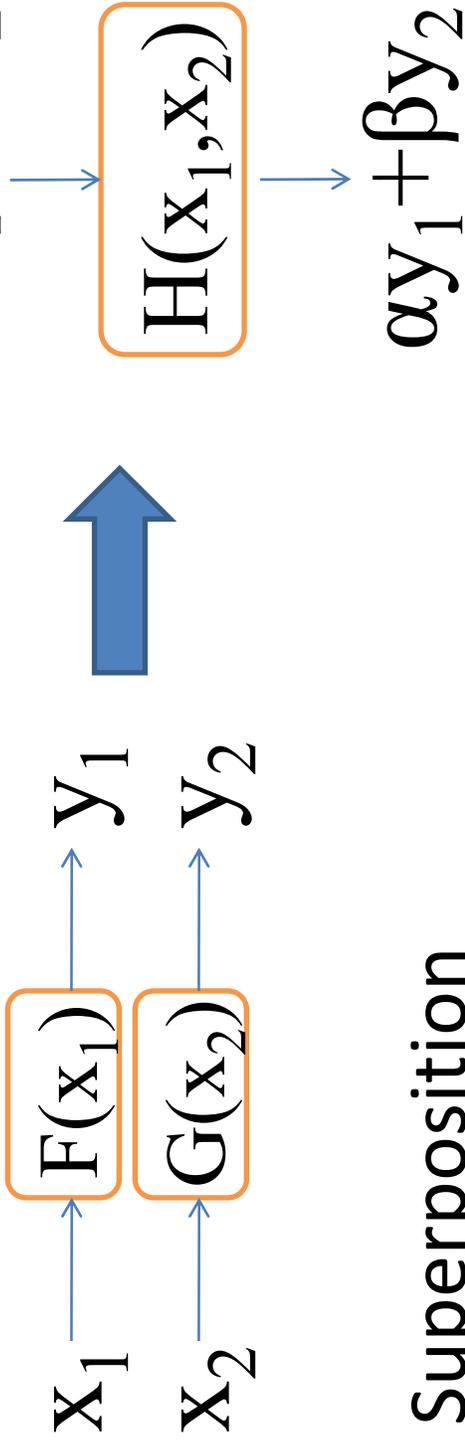


- Superposition

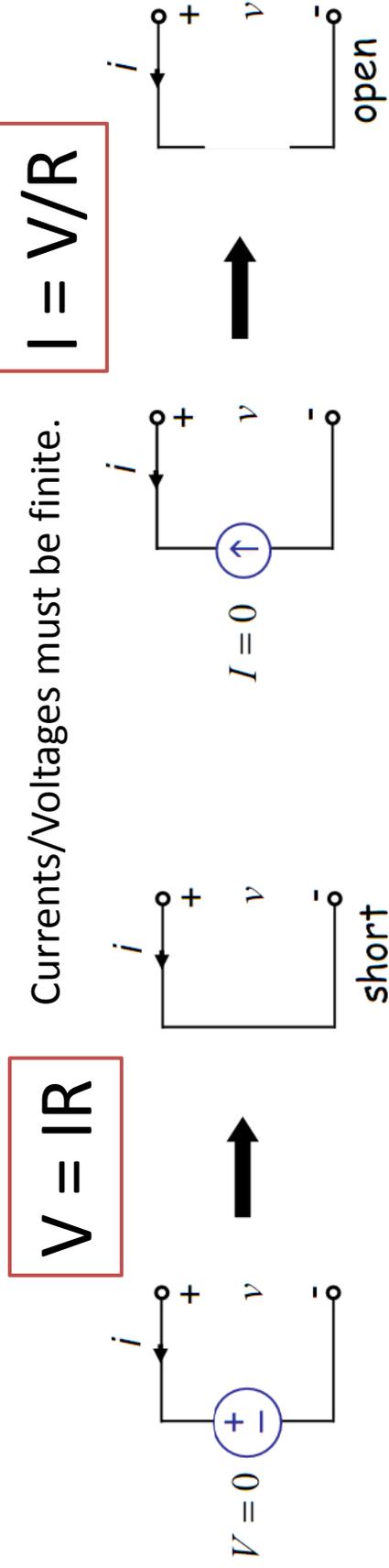– The output of a circuit comprised of independent sources is determined by summing the responses to each source alone.





# Example #1

Solve for voltage at  $e$ .

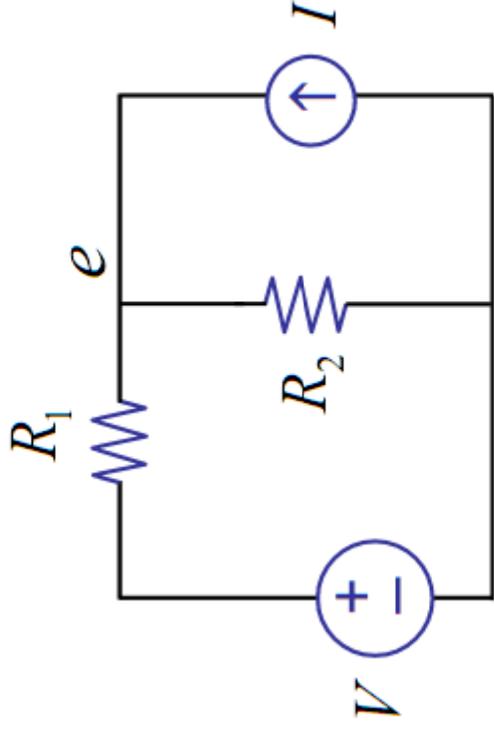

# Solution

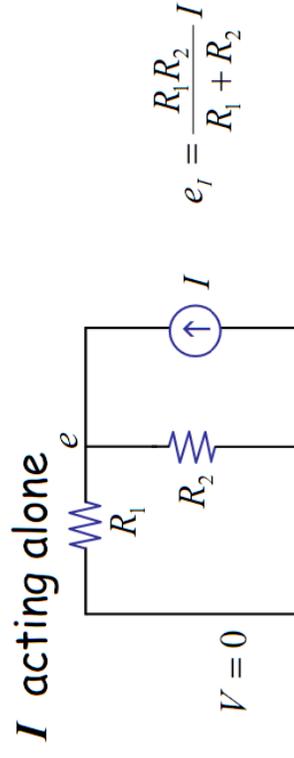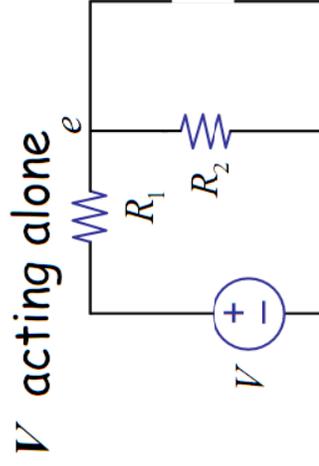


**sum  $\longrightarrow$  superposition**

$$e = e_V + e_I = \frac{R_2}{R_1 + R_2} V + \frac{R_1 R_2}{R_1 + R_2} I$$

$$e = a_1 V_1 + a_2 V_2 + \dots + b_1 I_1 + b_2 I_2 + \dots$$

**Linear!**

Consider

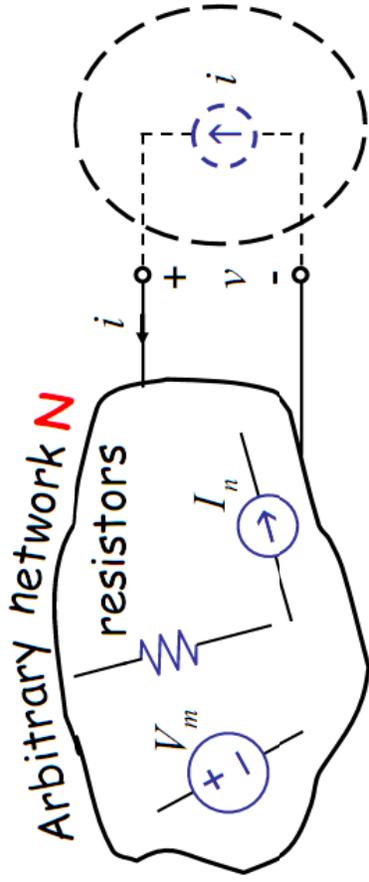

By superposition

$$v = \sum_m \alpha_m V_m + \sum_n \beta_n I_n + Ri$$

no units      no resistance units      All

also independent of external & excitement & behaves like a resistor


By setting

$$\forall_n I_n = 0, \forall V_m = 0, \forall V_m = 0, \forall I_n = 0, \forall I_n = 0, \forall V_m = 0$$

independent of external excitation and behaves like a voltage " $v_{TH}$ "

"Arbitrary network N" is indistinguishable

from:

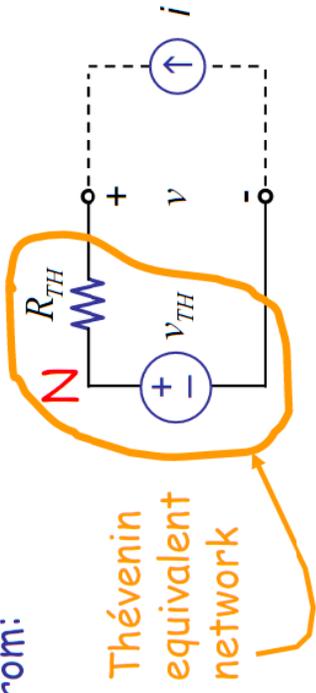


$v_{TH}$  → open circuit voltage at terminal pair (a.k.a. port)

$R_{TH}$  → resistance of network seen from port ( $V_m$ 's,  $I_n$ 's set to 0)


$$v = v_{TH} + R_{TH}i$$

## Example #2

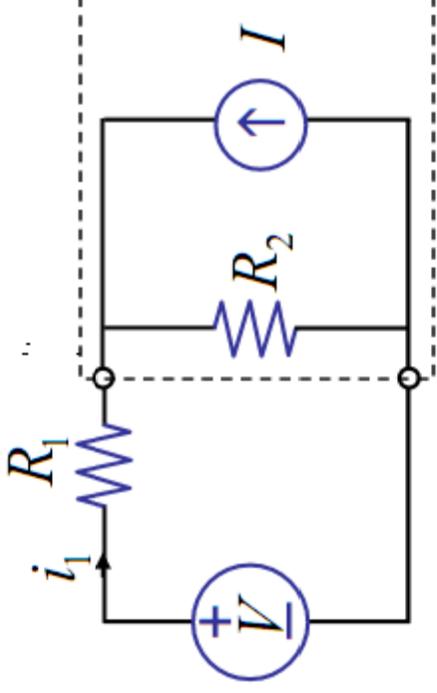



Solve for the Thevenin equivalent of  
the boxed area.

# Solution

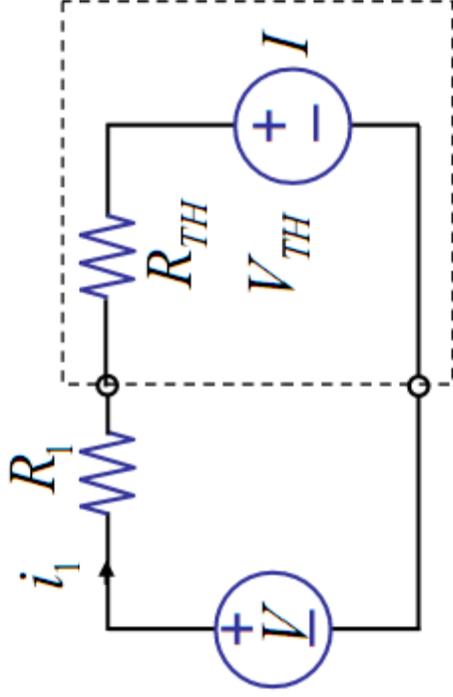

$$V_{TH} : V_{TH} = IR_2$$


$$R_{TH} : R_{TH} = R_2$$

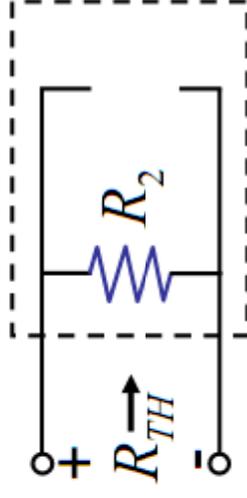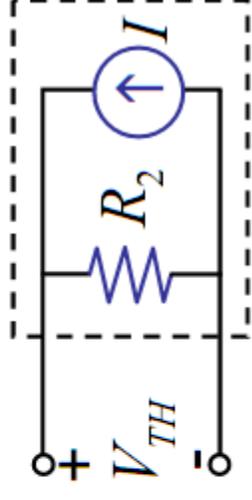

$$i_1 = \frac{V - V_{TH}}{R_1 + R_{TH}}$$
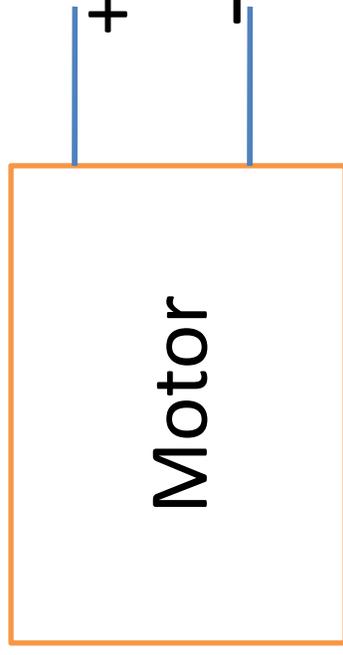
## Example #3

Using a multimeter, you measure the resistance of the motor (while it's off) to be 10 Ohms. Then, you measure the current through the running motor (15 V power supply) to be 100 mA. Draw the Thevenin equivalent circuit for the motor.



# Solution

Because we measured the resistance at the motor terminals without any sources, the Thevenin resistance value is  $R_{th} = 10 \text{ Ohms}$ . The  $100 \text{ mA}$  of current we measured implies that there is a  $1 \text{ V}$  potential drop across  $R_{th}$ . Therefore, there must be a back-EMF of  $14 \text{ V}$  to produce this potential drop. This gives us a  $V_{th}$  of  $14 \text{ V}$  for the running motor.

