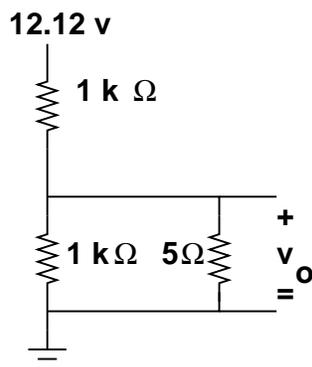


MASSACHUSETTS INSTITUTE OF TECHNOLOGY  
Department of Electrical Engineering and Computer Science  
6.01—Introduction to EECS I  
Spring Semester, 2008

Sections 1 and 2 NanoQuiz For Week 9

NAME: \_\_\_\_\_

1. For the resistive circuit below, what is the voltage  $V_o$ ?



2. For the op-amp circuit below, what is the output voltage  $v_o$ ?

