

Major topics of 6.01

- Controlling complexity
 - abstraction and modularity
- Interacting with the real world
 - models
- Coping with error and incomplete information
 - reasoning about uncertainty


PCAP framework for Python


	Procedures	Data
Primitives	+, *, ==	numbers, strings
Combination	if, f(g(x))	lists, objects
Abstraction	def	ADTs, classes
Patterns	higher-order fns	polymorphism, inheritance


PCAP framework for signals and systems

Primitives	signal
Combination	adder, gain, delay
Abstraction	system function
Patterns	feedback

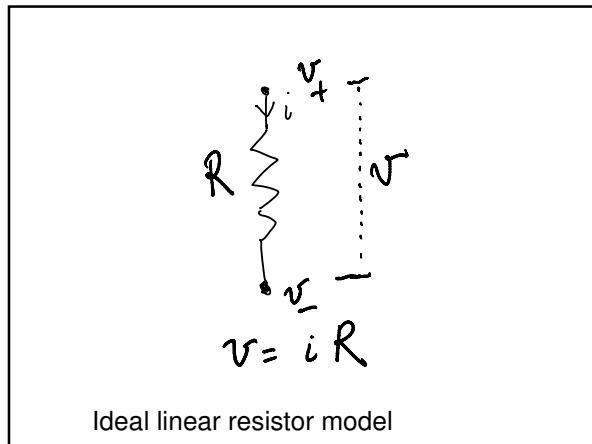
6.01: Circuit abstraction, modeling, op-amps




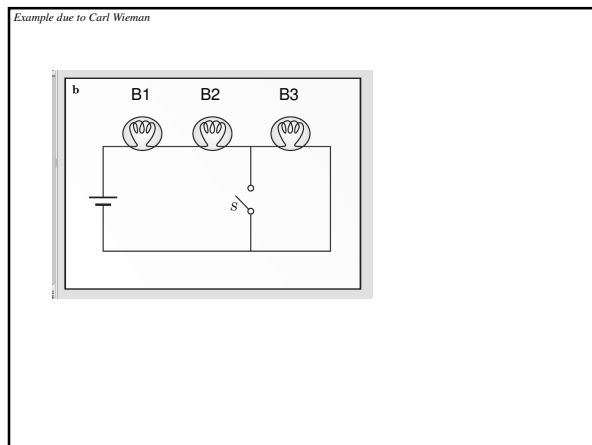


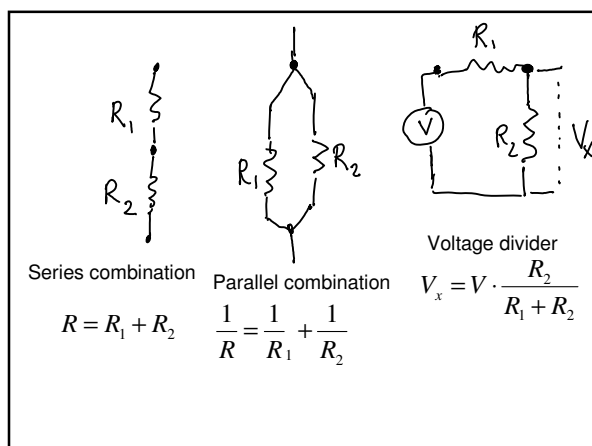

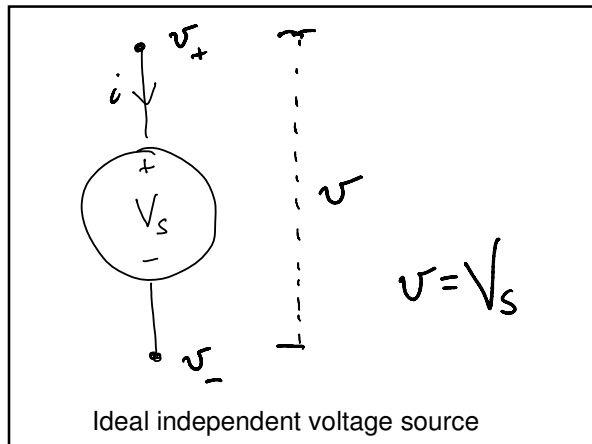6.01: Circuit abstraction, modeling, op-amps



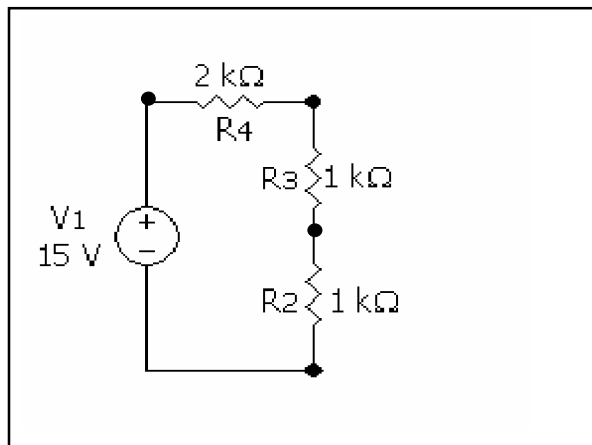

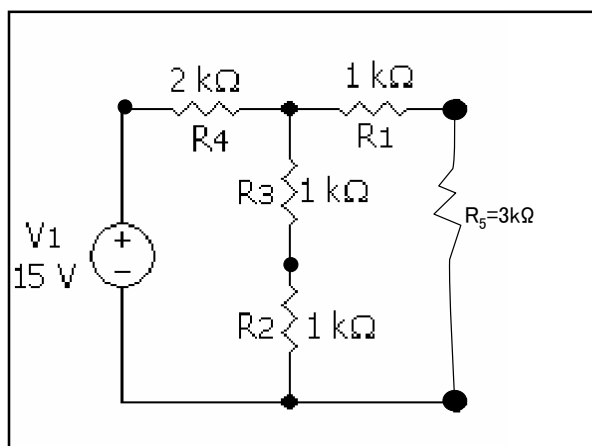

6.01: Circuit abstraction, modeling, op-amps

File Edit Format Run Options Windows Help

import CircuitDesign
reload(CircuitDesign)
from CircuitDesign import *

ex1 = Circuit([Vsrc(15,'n1','gnd'),
 Resistor(2000,'n1','n2'),
 Resistor(1000,'n2','n3'),
 Resistor(1000,'n3','gnd'),
 Resistor(1000,'n2','n4'),
 Resistor(3000,'n4','gnd')])

ex1.solve()

Ln 3 Col 0

Using the circuit solver

Python Shell


File Edit Debug Options Windows Help

gnd = 3.14339452167e-030
i_n1_gnd_1 = -0.0045
i_n1_n2_2 = 0.0045
i_n2_n3_3 = 0.003
i_n2_n4_5 = 0.0015
i_n3_gnd_4 = 0.003
i_n4_gnd_6 = 0.0015
n1 = 15.0
n2 = 6.0
n3 = 3.0
n4 = 4.5
>>>

Ln 69 Col 10

Different styles of computational models

- Functional models
 - Sytems are described as collections of mathematical functions with inputs and outputs
- Object models
 - Things are described as collections of objects that have behavior and internal state
- Constraint models
 - Systems are described as collections of the constrains that must hold among their components. There are no “inputs” and “outputs”, just constraints that must be satisfied.

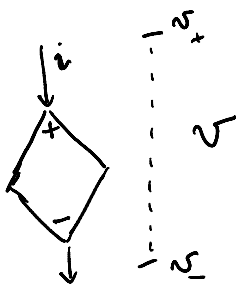

$$v = f \left[\begin{matrix} \text{various} \\ \text{circuit} \\ \text{quantities} \end{matrix} \right]$$

* For 6.01, we'll assume f is a linear function.

Dependent voltage source

PCAP framework for circuits

Primitives	Resistors, sources, 2-terminal devices (assume all linear)
Combination	Wire parts together at the terminals
Abstraction	
Patterns	

"Modeling and Monitoring of Cardiovascular Dynamics in the Intensive Care Unit"
Tushar Parlikar, Thomas Heldt, George Verghese, 2005

- For the SPCVM, applying the cycle-averaging technique, we obtain a circuit with dependent voltage and current sources:

$$\langle V_1(t) \rangle_0 = \langle g_1(t) V_3(t) \rangle_0 + \langle (1 - s_1(t)) V_2(t) \rangle_0 \approx \langle s_1(t) \rangle_0 \langle V_3(t) \rangle_0 + \langle (1 - \langle s_1(t) \rangle_0) \rangle_0 \langle V_2(t) \rangle_0 + K_1$$


$$\langle V_2(t) \rangle_0 \approx \langle s_2(t) \rangle_0 \langle V_3(t) \rangle_0 + \langle (1 - \langle s_2(t) \rangle_0) \rangle_0 \langle V_1(t) \rangle_0 + K_2$$

1-port

Apply a voltage and measure the current. The 1-port is completely described by the relation of the between the voltage and the current. **It doesn't matter what's in the box, so long as the relation holds.**

Analogy with software:
An abstract data type is described by its operations.

Thévenin model

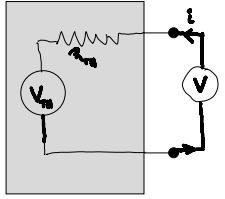



Any 1-port made up of linear resistors and sources, when viewed from the terminals, is **completely electrically equivalent** to a network composed of a single resistor and a single voltage source.

$$v = V_{TH} + iR_{TH}$$

Open circuit voltage

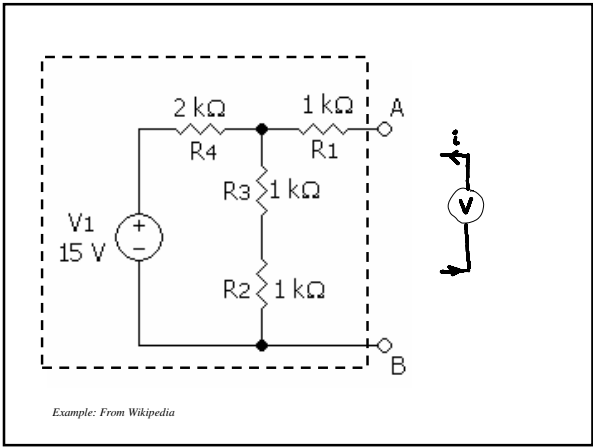
Resistance seen from the terminals what all independent sources are suppressed




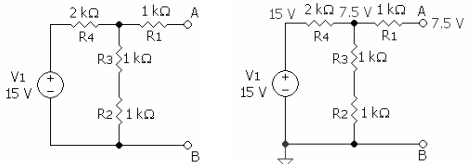


The voltage at the terminals is 7.5V, so V_{TH} is 7.5V

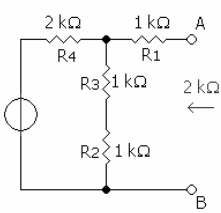6.01: Circuit abstraction, modeling, op-amps



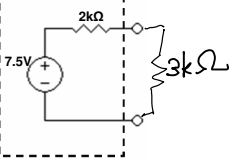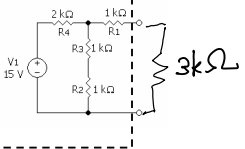The resistance seen from the terminals is $2k\Omega$, so R_{TH} is $2k\Omega$





$v = 7.5 \times \frac{3}{3+2} = 7.5 \times \frac{3}{5} = 4.5$


PCAP framework for circuits


Primitives	Resistors, sources, 2-terminal devices (assume all linear)
Combination	Wire parts together at the terminals
Abstraction	1-port (Thévenin model)
Patterns	

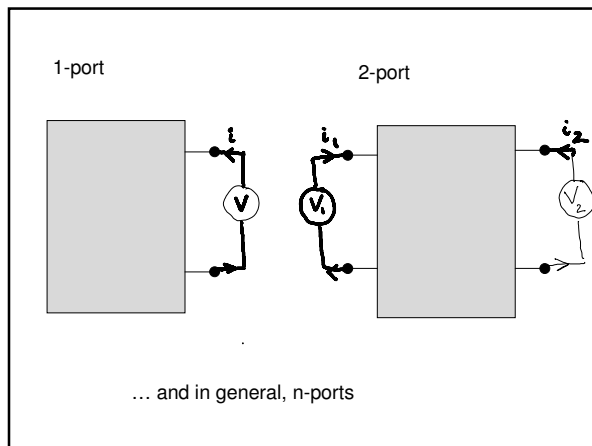
6.01: Circuit abstraction, modeling, op-amps




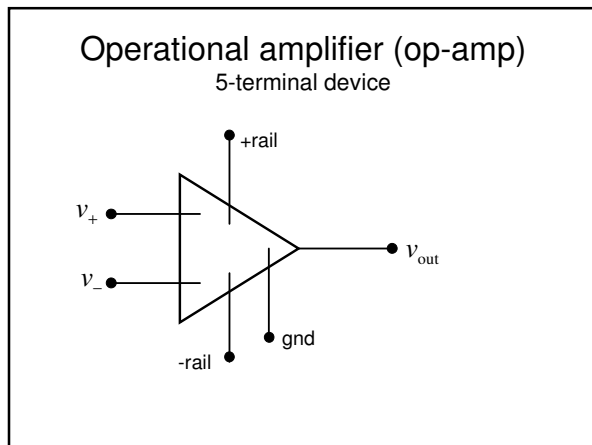

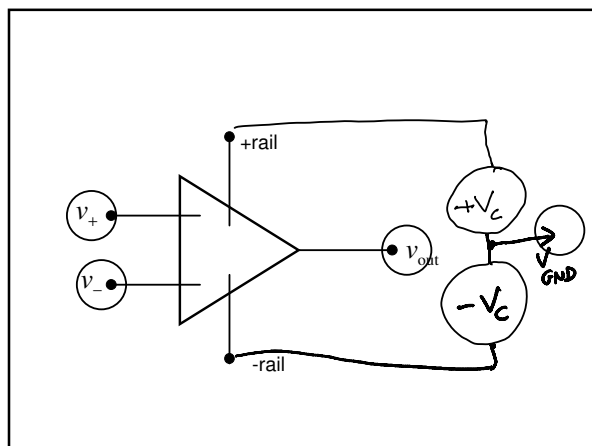

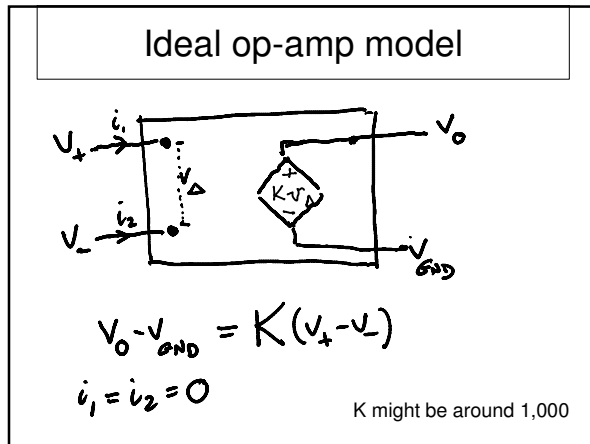


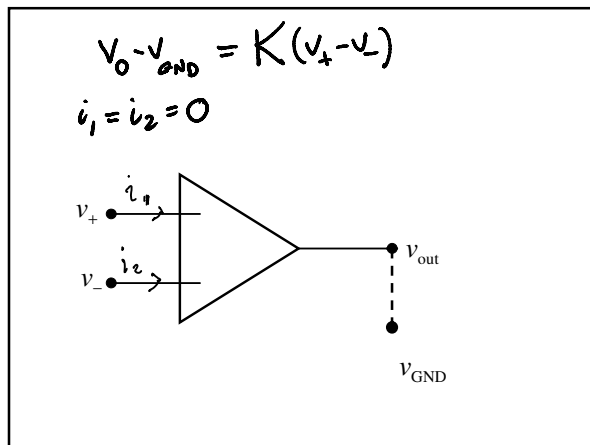

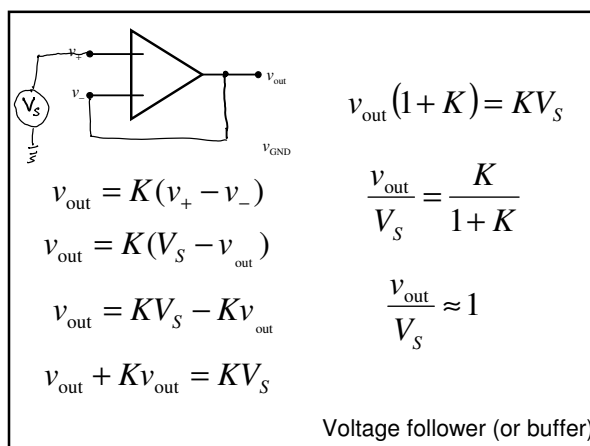

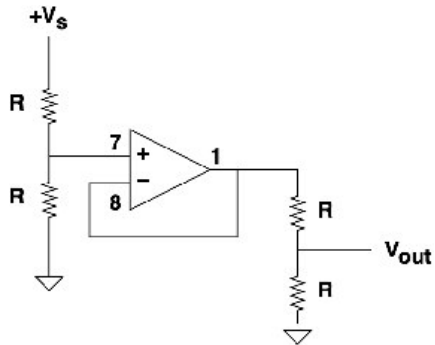
6.01: Circuit abstraction, modeling, op-amps

Using a buffer to cascade voltage dividers in lab last week



An even simpler op-amp model (K infinite)

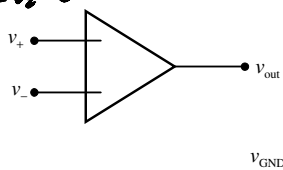
$$V_o - V_{out} = K(V_+ - V_-)$$
$$i_1 = i_2 = 0$$



- Draws no current, that is, $i_1 = i_2 = 0$
- If K is very large, and V_{out} is finite, then $V_+ = V_-$

Inverting amplifier

6.01: Circuit abstraction, modeling, op-amps




- $\frac{v_o - v_{in}}{R_F} = \frac{v_{in}}{R_1}$
- $R_1 v_o - R_1 v_{in} = R_F v_{in}$
- $R_1 v_o = (R_1 + R_F) v_{in}$
- $\frac{v_o}{v_{in}} = \frac{R_F + R_1}{R_1}$

$\frac{v_o - v_{in}}{R_F} = \frac{v_{in}}{R_1}$

$v_{-} = v_{+} = v_{in}$

Non-inverting amplifier

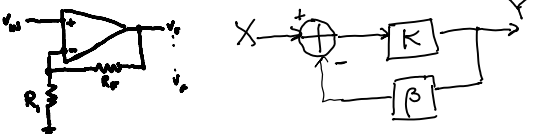



$\frac{v_o}{v_{in}} = \frac{R_F + R_1}{R_1}$

$\frac{Y}{X} = \frac{K}{1 + \beta K}$

$\approx \frac{1}{\beta} \quad K \gg 0$

$\beta = \frac{R_1}{R_1 + R_F}$

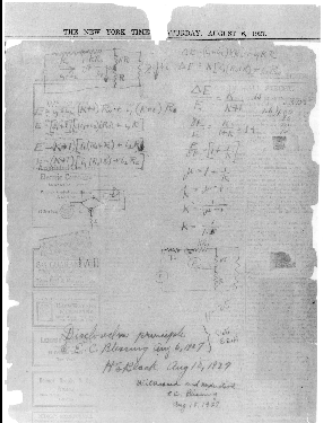



Harold S. Black (1898-1983)
Inventor of the negative feedback amplifier (1927)
