
 


# D-Register Timing - I

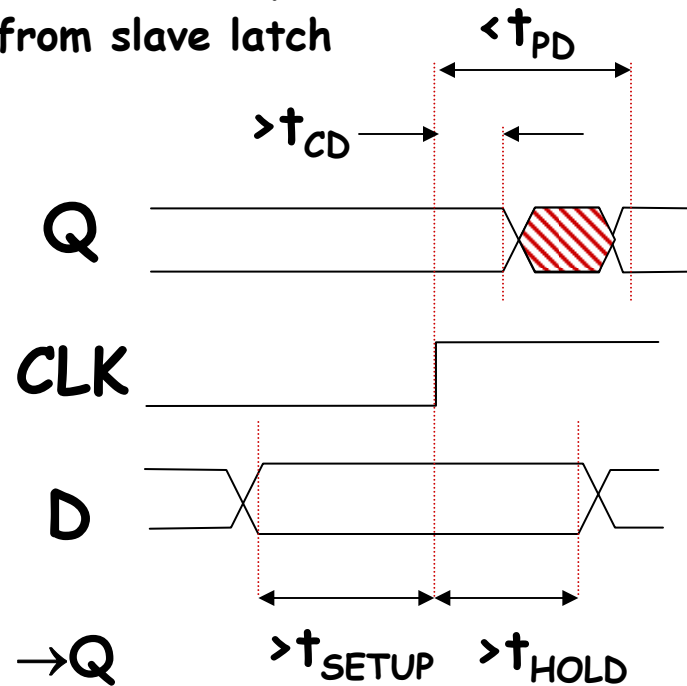

Values determined from slave latch



$t_{PD}$ : maximum propagation delay, CLK  $\rightarrow$  Q

$t_{CD}$ : minimum contamination delay, CLK  $\rightarrow$  Q

$t_{SETUP}$ : setup time



*guarantee that D has propagated through feedback path before master closes*

$t_{HOLD}$ : hold time

*guarantee master is closed and data is stable before allowing D to change*

Values determined from master latch

# D-Register Timing - II

  


$$t_1 = t_{CD,reg1} + t_{CD,1} > t_{HOLD,reg2}$$

$$t_2 = t_{PD,reg1} + t_{PD,1} < t_{CLK} - t_{SETUP,reg2}$$

Questions for register-based designs:

- how much time for useful work (i.e. for combinational logic delay)?
- does it help to guarantee a minimum  $t_{CD}$ ? How about designing registers so that  $t_{CD,reg} > t_{HOLD,reg}$ ?
- what happens if CLK signal doesn't arrive at the two registers at exactly the same time (a phenomenon known as "clock skew")?

# Sequential Circuit Timing

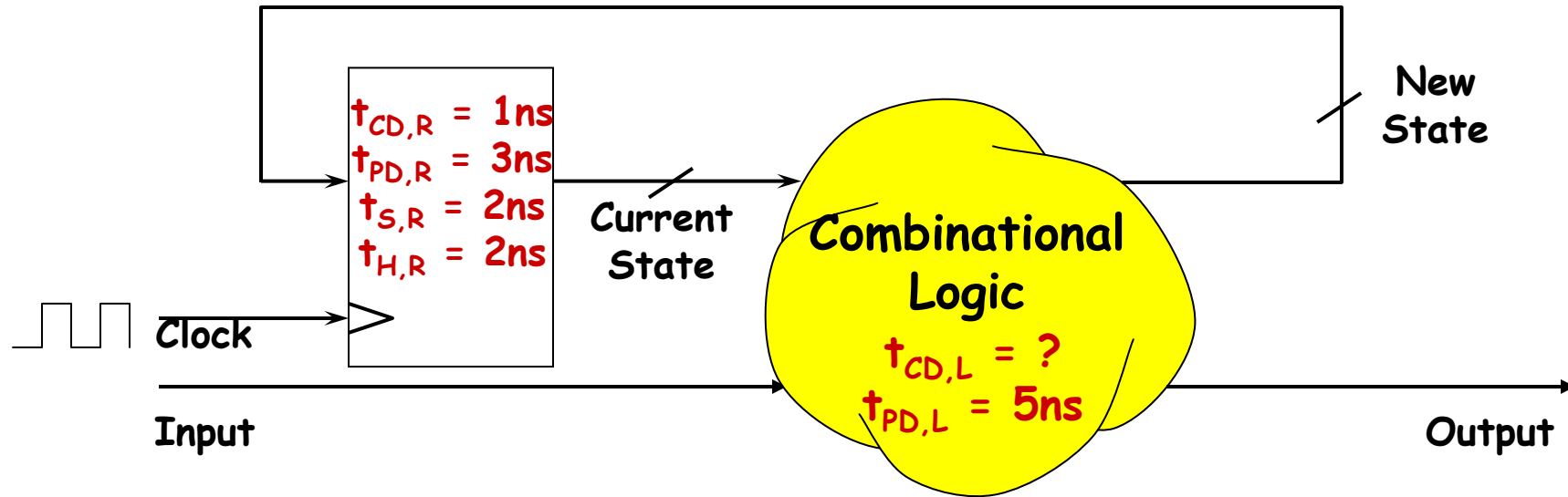

## Questions:


- Constraints on  $T_{CD}$  for the logic?  $> 1\text{ ns}$
- Minimum clock period?  $> 10\text{ ns } (T_{PD,R} + T_{PD,L} + T_{S,R})$
- Setup, Hold times for Inputs?
  - $T_S = T_{PD,L} + T_{S,R}$
  - $T_H = T_{H,R} - T_{CD,L}$

# The Sequential always Block

- Edge-triggered circuits are described using a sequential always block

 
## Combinational

```
module combinational(a, b, sel,
                    out);
    input a, b;
    input sel;
    output out;
    reg out;
    always @ (a or b or sel)
    begin
        if (sel) out = a;
        else out = b;
    end
endmodule
```


 
## Sequential

```
module sequential(a, b, sel,
                 clk, out);
    input a, b;
    input sel, clk;
    output out;
    reg out;
    always @ (posedge clk)
    begin
        if (sel) out <= a;
        else out <= b;
    end
endmodule
```



# Importance of the Sensitivity List

- The use of `posedge` and `negedge` makes an `always` block sequential (edge-triggered)
- Unlike a combinational `always` block, the sensitivity list **does** determine behavior for synthesis!

*D Flip-flop with **synchronous** clear*

```
module dff_sync_clear(d, clearb,
clock, q);
input d, clearb, clock;
output q;
reg q;
always @ (posedge clock)
begin
    if (!clearb) q <= 1'b0;
    else q <= d;
end
endmodule
```

`always` block entered only at  
each positive clock edge

*D Flip-flop with **asynchronous** clear*

```
module dff_async_clear(d, clearb, clock, q);
input d, clearb, clock;
output q;
reg q;
always @ (negedge clearb or posedge clock)
begin
    if (!clearb) q <= 1'b0;
    else q <= d;
end
endmodule
```

`always` block entered immediately  
when (active-low) `clearb` is asserted


Note: The following is **incorrect** syntax: `always @ (clear or negedge clock)`

If one signal in the sensitivity list uses `posedge`/`negedge`, then all signals must.

- **Assign any signal or variable from only one `always` block, Be wary of race conditions: `always` blocks execute in parallel**

# Simulation


- **DFF with Synchronous Clear**

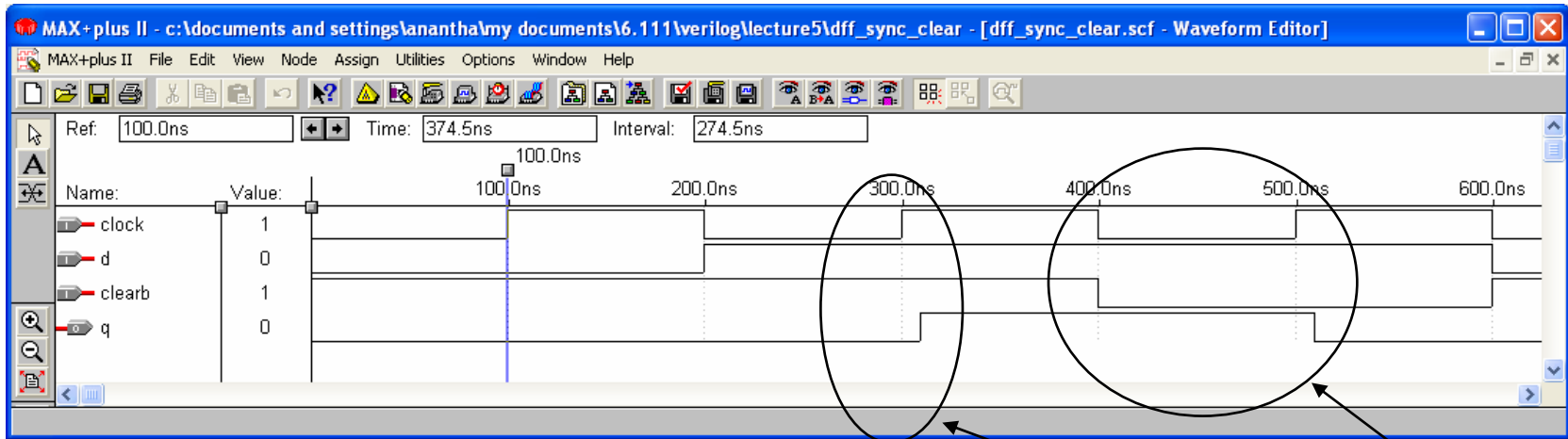

$t_{c-q}$

Clear on Clock Edge

- **DFF with Asynchronous Clear**

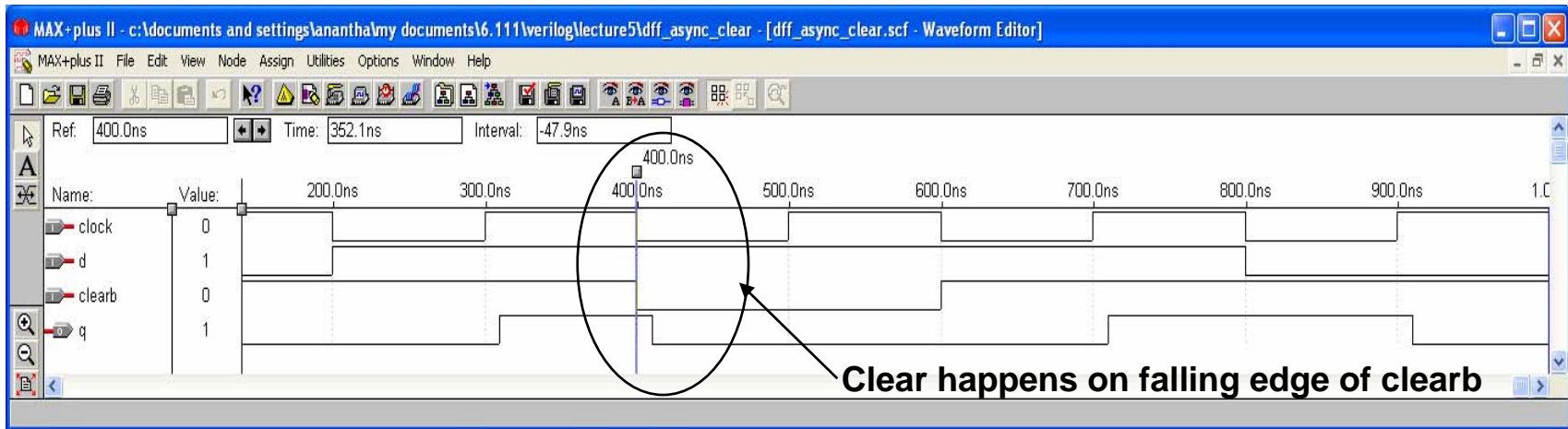

Clear happens on falling edge of clearb

# Blocking vs. Nonblocking Assignments

- Verilog supports two types of assignments within `always` blocks, with subtly different behaviors.

- **Blocking assignment:** evaluation and assignment are immediate

```
always @ (a or b or c)
```

```
begin
```

```
x = a | b;           1. Evaluate  $a | b$ , assign result to  $x$ 
```

```
y = a ^ b ^ c;      2. Evaluate  $a^b^c$ , assign result to  $y$ 
```

```
z = b & ~c;         3. Evaluate  $b \& (\sim c)$ , assign result to  $z$ 
```

```
end
```

- **Nonblocking assignment:** all assignments deferred until all right-hand sides have been evaluated (end of simulation timestep)

```
always @ (a or b or c)
```

```
begin
```

```
x <= a | b;          1. Evaluate  $a | b$  but defer assignment of  $x$ 
```


```
y <= a ^ b ^ c;      2. Evaluate  $a^b^c$  but defer assignment of  $y$ 
```

```
z <= b & ~c;         3. Evaluate  $b \& (\sim c)$  but defer assignment of  $z$ 
```

```
end                 4. Assign  $x$ ,  $y$ , and  $z$  with their new values
```

- Sometimes, as above, both produce the same result. Sometimes, not!

# Assignment Styles for Sequential Logic

 

- Will nonblocking and blocking assignments both produce the desired result?

```
module nonblocking(in, clk, out);  
  input in, clk;  
  output out;  
  reg q1, q2, out;  
  always @ (posedge clk)  
  begin  
    q1 <= in;  
    q2 <= q1;  
    out <= q2;  
  end  
endmodule
```


```
module blocking(in, clk, out);  
  input in, clk;  
  output out;  
  reg q1, q2, out;  
  always @ (posedge clk)  
  begin  
    q1 = in;  
    q2 = q1;  
    out = q2;  
  end  
endmodule
```


 
# Use Nonblocking for Sequential Logic


```
always @ (posedge clk)
begin
  q1 <= in;
  q2 <= q1;
  out <= q2;
end
```

“At each rising clock edge,  $q1$ ,  $q2$ , and  $out$  simultaneously receive the old values of  $in$ ,  $q1$ , and  $q2$ .”



```
always @ (posedge clk)
begin
  q1 = in;
  q2 = q1;
  out = q2;
end
```

 
“At each rising clock edge,  $q1 = in$ .  
After that,  $q2 = q1 = in$ .  
After that,  $out = q2 = q1 = in$ .  
Therefore  $out = in$ .”




- Blocking assignments do not reflect the intrinsic behavior of multi-stage sequential logic
- **Guideline: use nonblocking assignments for sequential always blocks**

# Simulation

## ■ Non-blocking Simulation

 


## ■ Blocking Simulation

 

# Use Blocking for Combinational Logic

## Blocking Behavior

	a	b	c	x	y
(Given) Initial Condition	1	1	0	1	1
a changes; always block triggered	0	1	0	1	1
x = a & b;	0	1	0	0	1
y = x   c;	0	1	0	0	0

 

```

module blocking(a,b,c,x,y);
  input a,b,c;
  output x,y;
  reg x,y;

  always @ (a or b or c)
  begin
    x = a & b;
    y = x | c;
  end
endmodule

```

## Nonblocking Behavior

	a	b	c	x	y	Deferred
(Given) Initial Condition	1	1	0	1	1	
a changes; always block triggered	0	1	0	1	1	
x <= a & b;	0	1	0	1	1	x<=0
y <= x   c;	0	1	0	1	1	x<=0, y<=1
Assignment completion	0	1	0	0	1	

```


module nonblocking(a,b,c,x,y);
  input a,b,c;
  output x,y;
  reg x,y;

  always @ (a or b or c)
  begin
    x <= a & b;
    y <= x | c;
  end
endmodule


```

- Nonblocking and blocking assignments will synthesize correctly. Will both styles simulate correctly?
- Nonblocking assignments do not reflect the intrinsic behavior of multi-stage combinational logic
- While nonblocking assignments can be hacked to simulate correctly (expand the sensitivity list), it's not elegant
- **Guideline: use blocking assignments for combinational always blocks**

# Implementation for on/off button

 

 
```
module onoff(button,light);  
  input button;  
  output light;  
  reg light;  
  always @ (posedge button)  
  begin  
    light <= ~light;  
  end  
endmodule
```


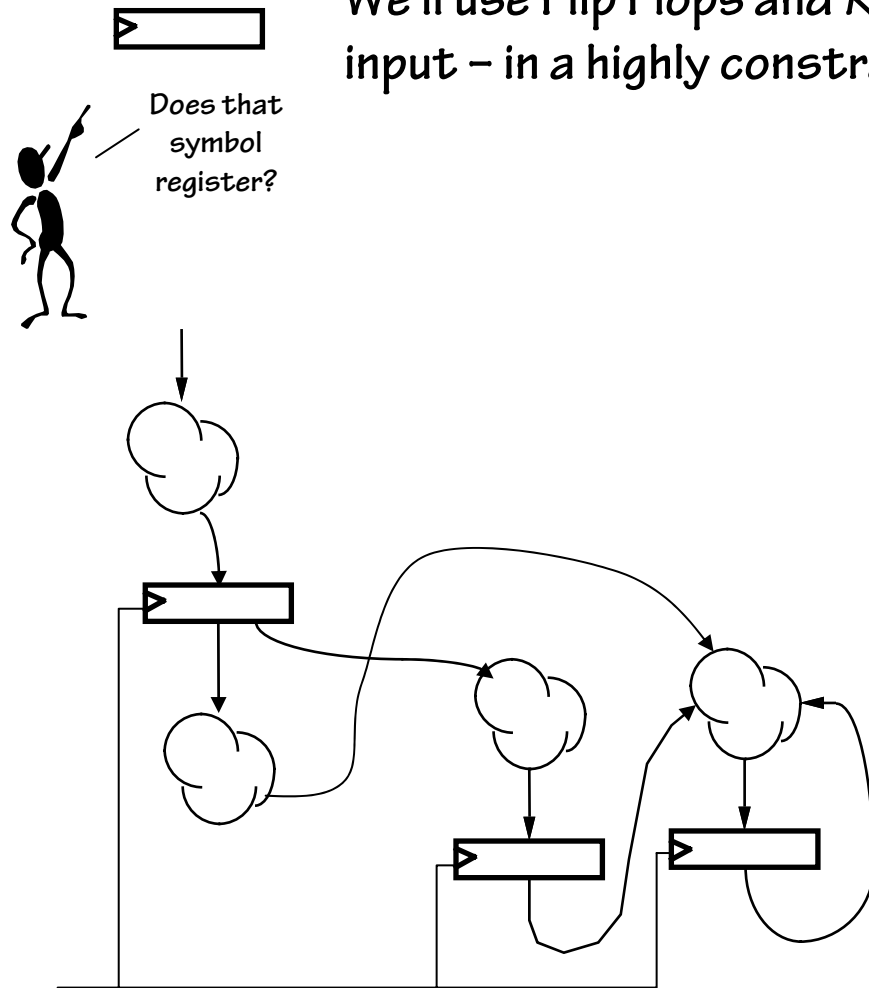
# Single-clock Synchronous Circuits

We'll use Flip Flops and *Registers* – groups of FFs sharing a clock input – in a highly constrained way to build digital systems:




## Single-clock Synchronous Discipline

- No combinational cycles
- Single clock signal shared among all clocked devices
- Only care about value of combinational circuits just before rising edge of clock
- Period greater than every combinational delay
- Change saved state after noise-inducing logic transitions have stopped!

# Clocked circuit for on/off button


```
module onoff(clk,button,light);  
  input clk,button;  
  output light;  
  reg light;  
  always @ (posedge clk)  
  begin  
    if (button) light <= ~light;  
  end  
endmodule
```

Does this work  
with a 1Mhz  
CLK?

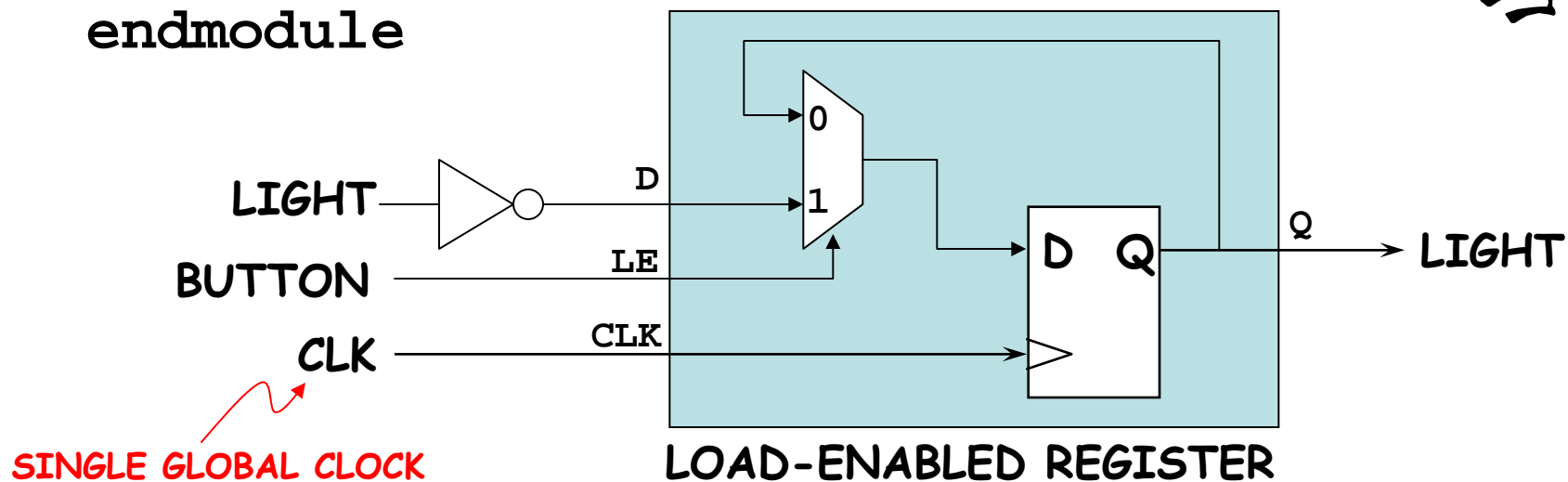


# Asynchronous Inputs in Sequential Systems

What about external signals?

 

*Can't guarantee setup and hold times will be met!*

 When an asynchronous signal causes a setup/hold violation...



Transition is missed on first clock cycle, but caught on next clock cycle.

Transition is caught on first clock cycle.



Output is metastable for an indeterminate amount of time.

**Q: Which cases are problematic?**
  
# Asynchronous Inputs in Sequential Systems

All of them can be, if more than one happens simultaneously within the same circuit.

*Idea: ensure that external signals directly feed exactly one flip-flop*




This prevents the possibility of I and II occurring in different places in the circuit, but what about metastability?


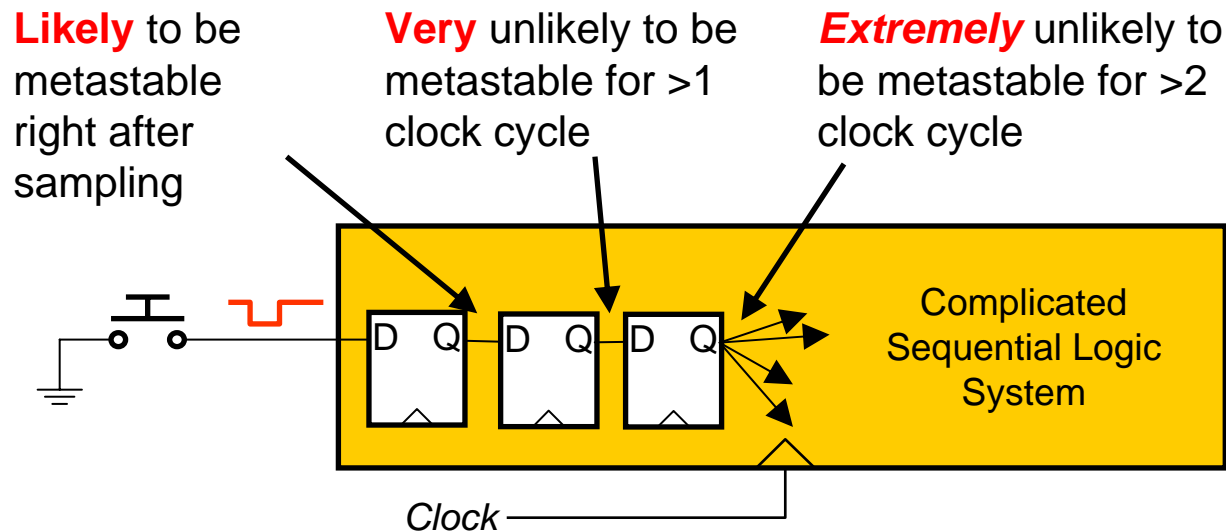
# Handling Metastability

- Preventing metastability turns out to be an impossible problem
- High gain of digital devices makes it likely that metastable conditions will resolve themselves quickly
- Solution to metastability: allow time for signals to stabilize




*How many registers are necessary?*

- Depends on many design parameters (clock speed, device speeds, ...)
- In 6.111, a pair of synchronization registers is sufficient
 
# Finite State Machines


- Finite State Machines (FSMs) are a useful abstraction for sequential circuits with centralized “states” of operation
- At each clock edge, combinational logic computes *outputs* and *next state* as a function of *inputs* and *present state*




# Two Types of FSMs

Moore and Mealy FSMs are distinguished by their output generation

## Moore FSM:

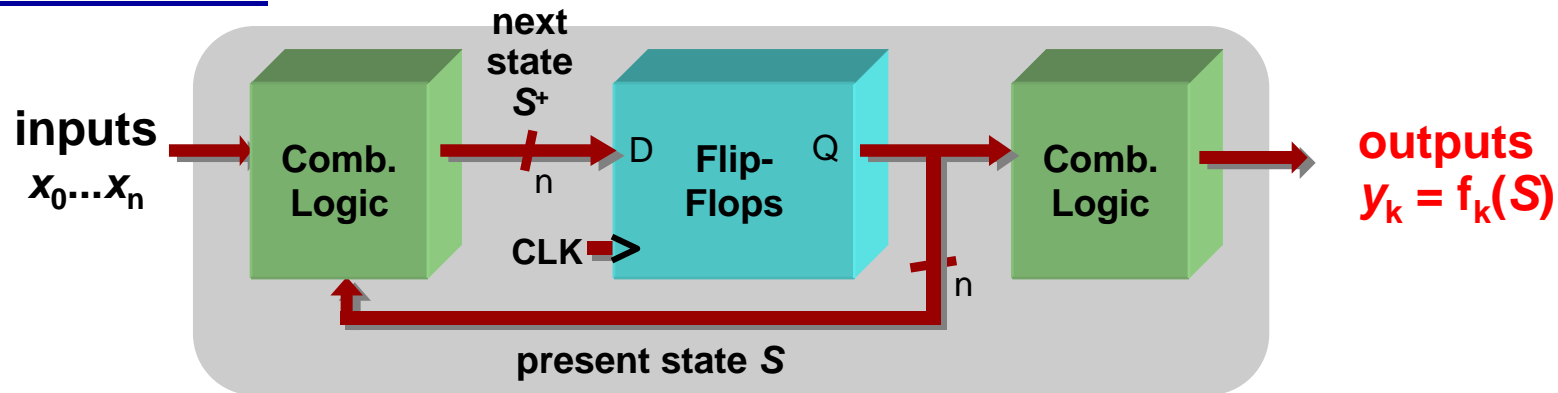


## Mealy FSM:

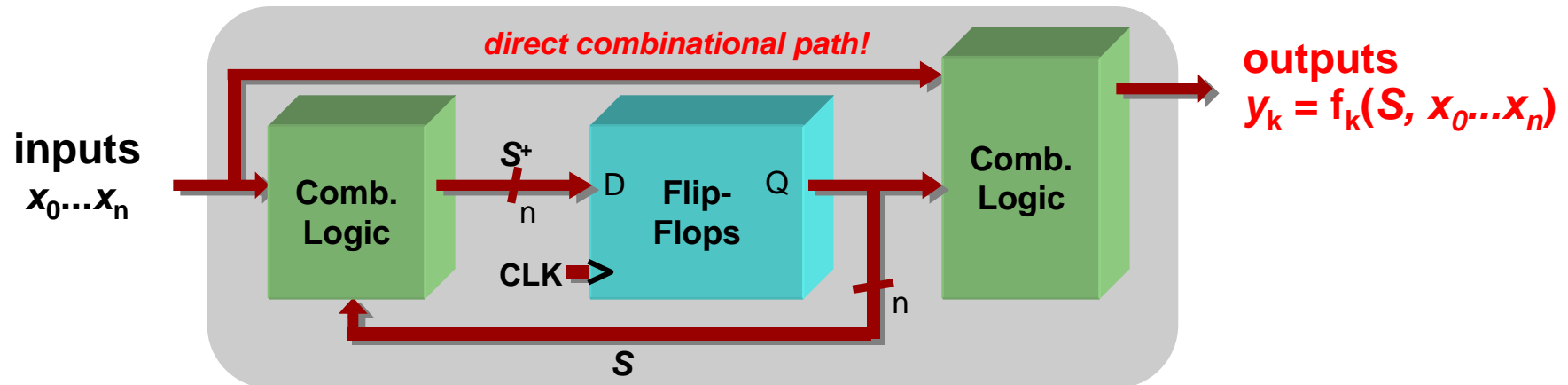

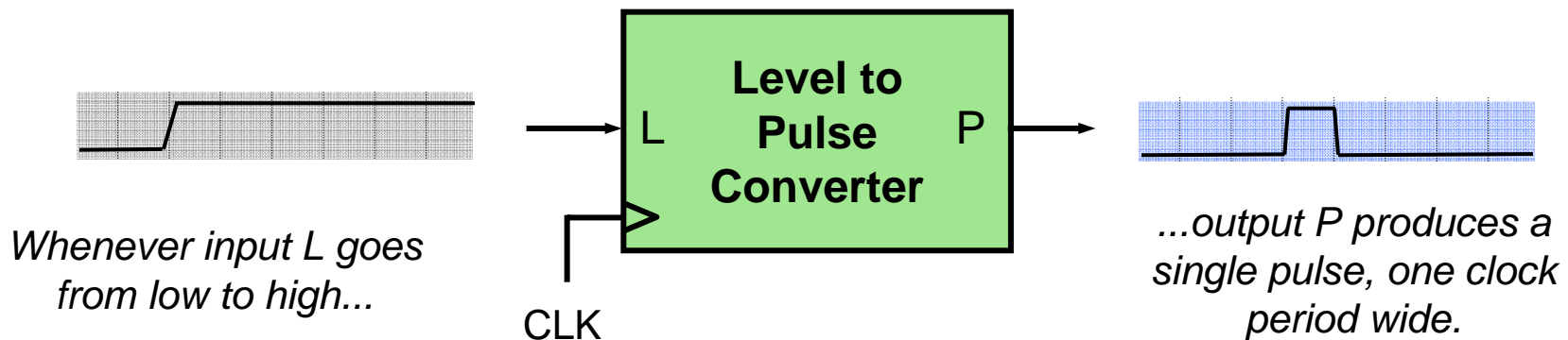
# On/off button done right!

- A **level-to-pulse converter** produces a single-cycle pulse each time its input goes high.
- In other words, it's a synchronous rising-edge detector.
- Sample uses:
  - Buttons and switches pressed by humans for arbitrary periods of time
  - Single-cycle enable signals for counters




# State Transition Diagrams

- Block diagram of desired system:

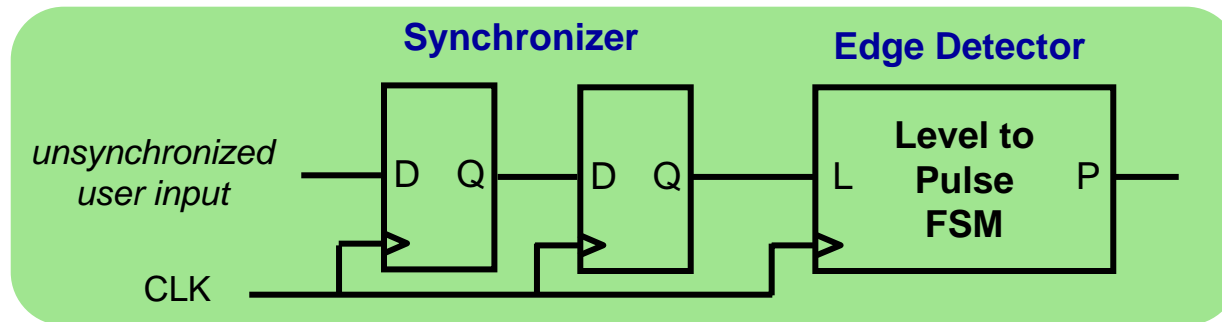


 - State transition diagram** is a useful FSM representation and design aid



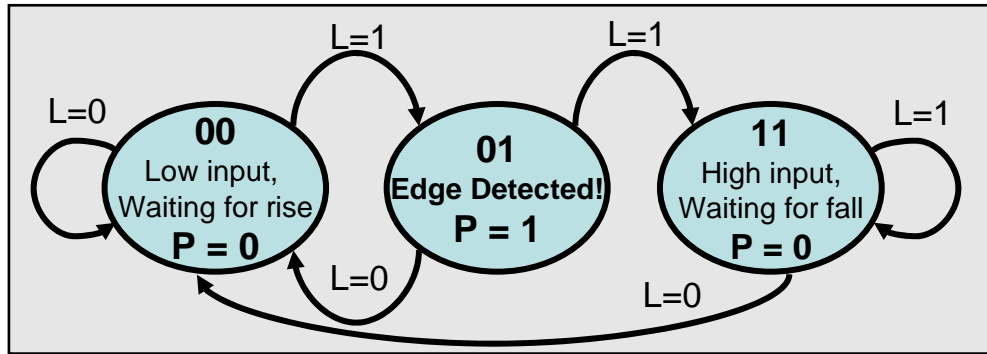
# Logic Derivation for a Moore FSM

Transition diagram is readily converted to a state transition table (just a truth table)




Current t State		In	Next State		Out
$S_1$	$S_0$	$L$	$S_1^+$	$S_0^+$	$P$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	1
1	1	0	0	0	0
1	1	1	1	1	0

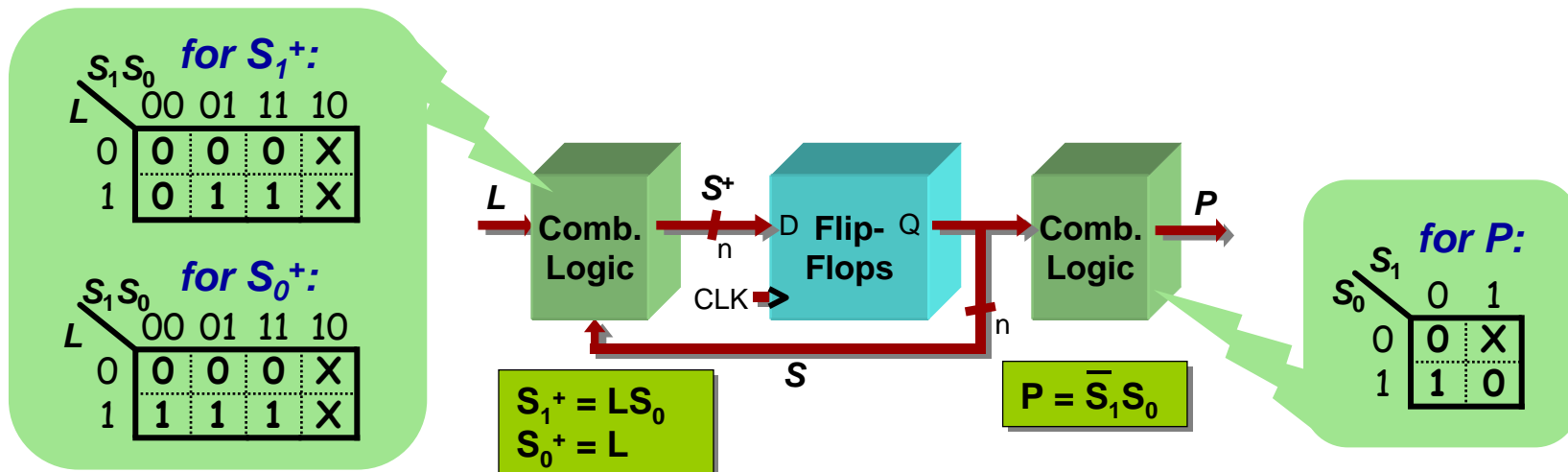
- Combinational logic may be derived using Karnaugh maps




# Moore Level-to-Pulse Converter

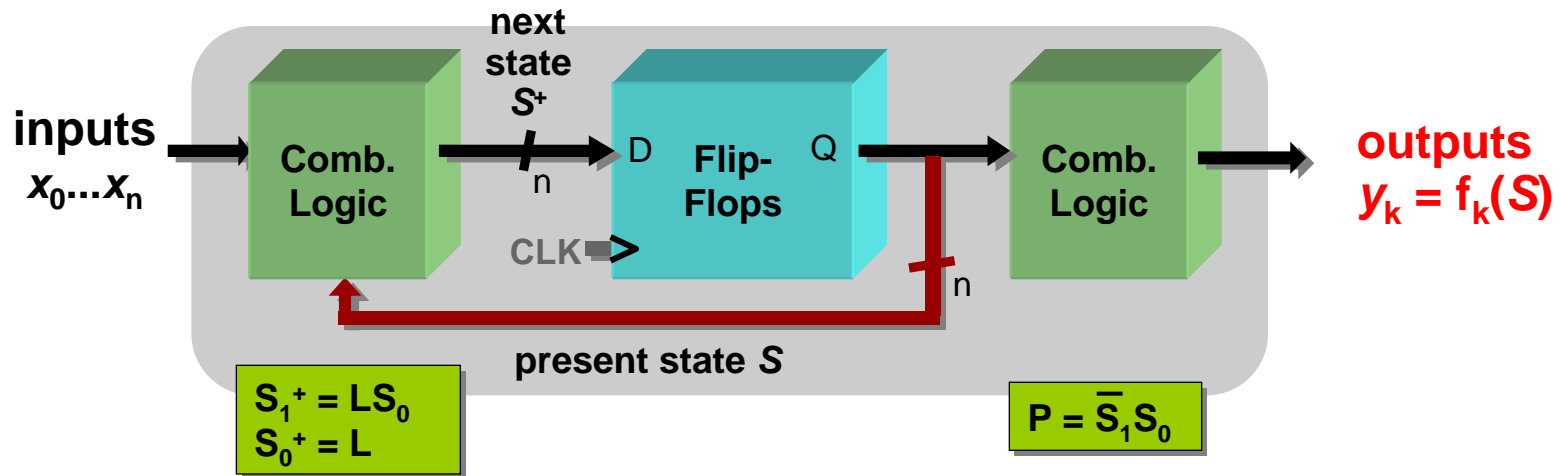

 
Moore FSM circuit implementation of level-to-pulse converter:



# Design of a Mealy Level-to-Pulse

 


 - Since outputs are determined by state *and* inputs, Mealy FSMs may need fewer states than Moore FSM implementations






# Mealy Level-to-Pulse Converter

 

Pres. State	In	Next State	Out
<b>S</b>	<b>L</b>	<b>S<sup>+</sup></b>	<b>P</b>
0	0	0	0
0	1	1	1
1	0	0	0
1	1	1	0

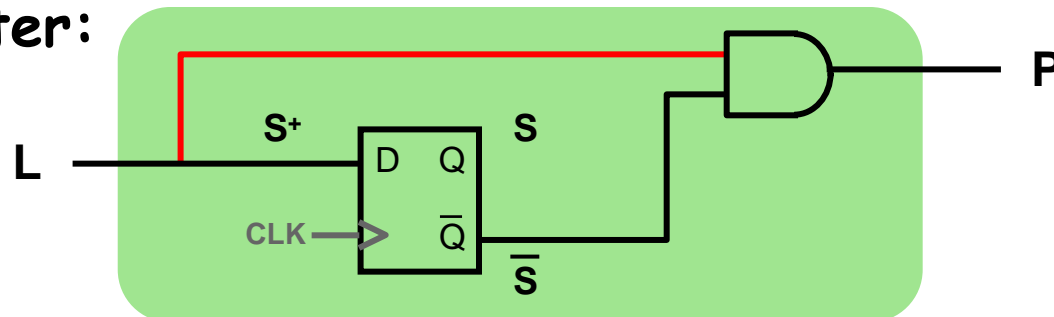Mealy FSM circuit implementation of level-to-pulse converter:




- FSM's state simply remembers the previous value of L
- Circuit benefits from the Mealy FSM's implicit single-cycle assertion of outputs during state transitions


# Moore/Mealy Trade-Offs

- Remember that the difference is in the output:
  - Moore outputs are based on state only
  - Mealy outputs are based on state *and input*
  - Therefore, Mealy outputs generally occur one cycle earlier than a Moore:

Moore: delayed assertion of P

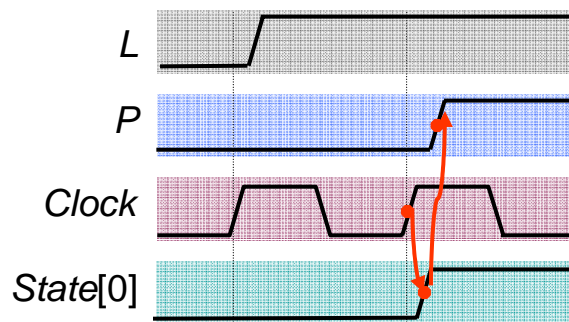

Mealy: immediate assertion of P

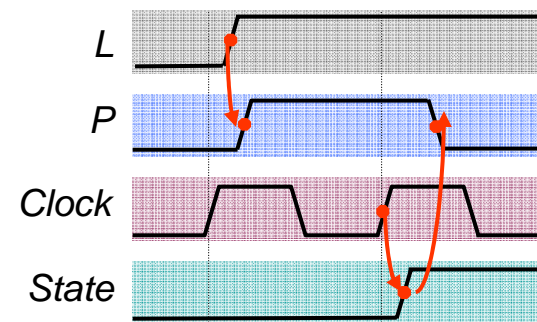


- Compared to a Moore FSM, a Mealy FSM might...
  - Be more difficult to conceptualize and design
  - Have fewer states

# FSM Timing Requirements


- Timing requirements for FSM are identical to any generic sequential system with feedback

## Minimum Clock Period

 

$$T > T_{pd,reg} + T_{pd,logic} + T_{su}$$

## Minimum Delay

 

$$T_{cd,reg} + T_{cd,logic} > T_{hold}$$

# Summary

- Use blocking assignments for combinational `always` blocks
- Use non-blocking assignments for sequential `always` blocks
- Synchronous design methodology usually used in digital circuits
  - Single global clocks to all sequential elements
  - Sequential elements almost always of edge-triggered flavor (design with latches can be tricky)