

# L08: Memory Basics and Timing

*Acknowledgement: Nathan Ickes, Rex Min*

J. Rabaey, A. Chandrakasan, B. Nikolic, “Digital Integrated Circuits: A Design Perspective”  
Prentice Hall, 2003 (Chapter 10)


# Memory Classification & Metrics

Read-Write Memory		Non-Volatile Read-Write Memory	Read-Only Memory (ROM)
Random Access	Non-Random Access	EPROM E <sup>2</sup> PROM	Mask-Programmed
SRAM DRAM	FIFO LIFO	FLASH	

## Key Design Metrics:


1. Memory Density (number of bits/ $\mu\text{m}^2$ ) and Size
2. Access Time (time to read or write) and Throughput
3. Power Dissipation

# Memory Array Architecture

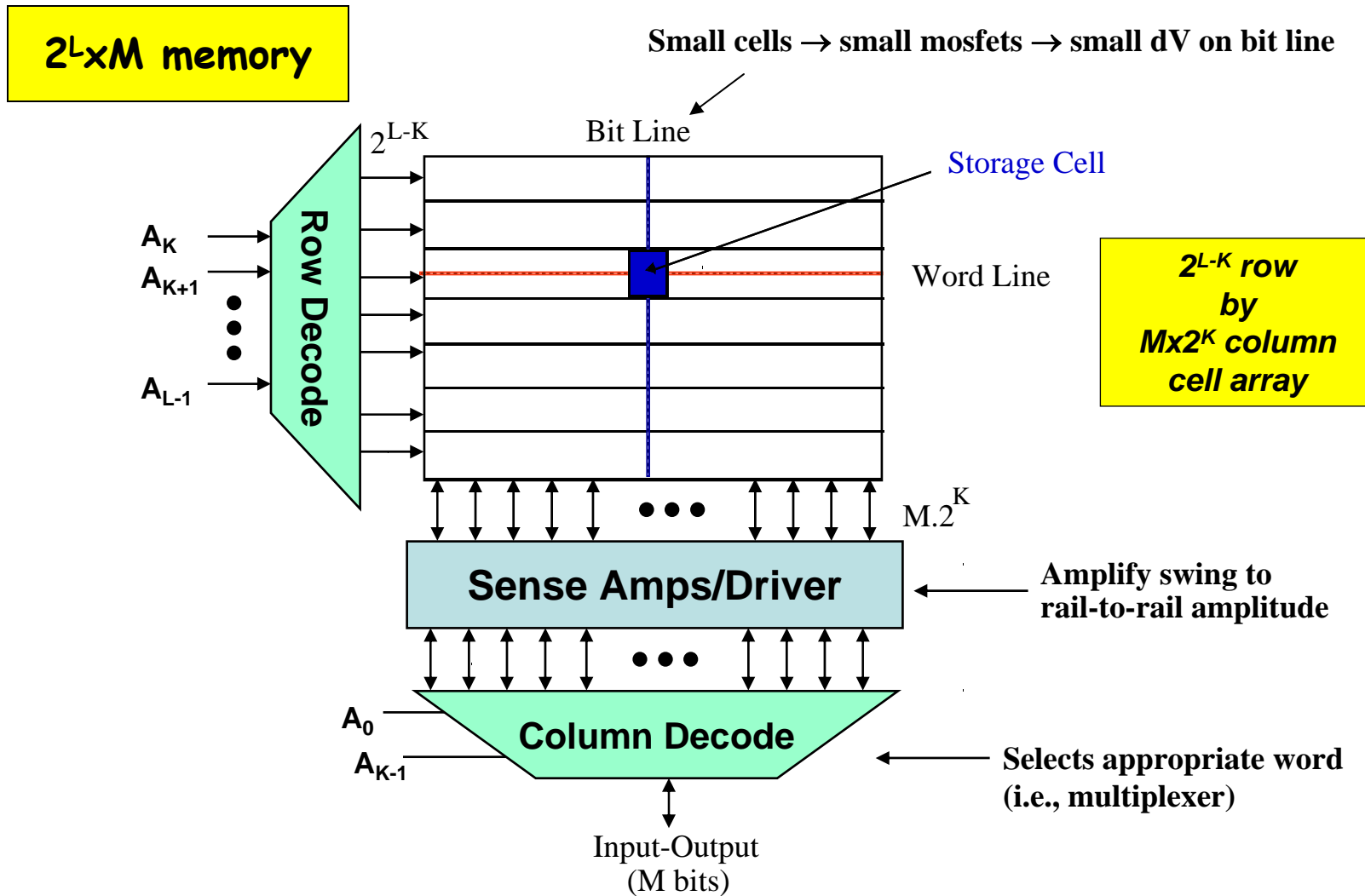


# Latch and Register Based Memory

## Positive Latch    Negative Latch

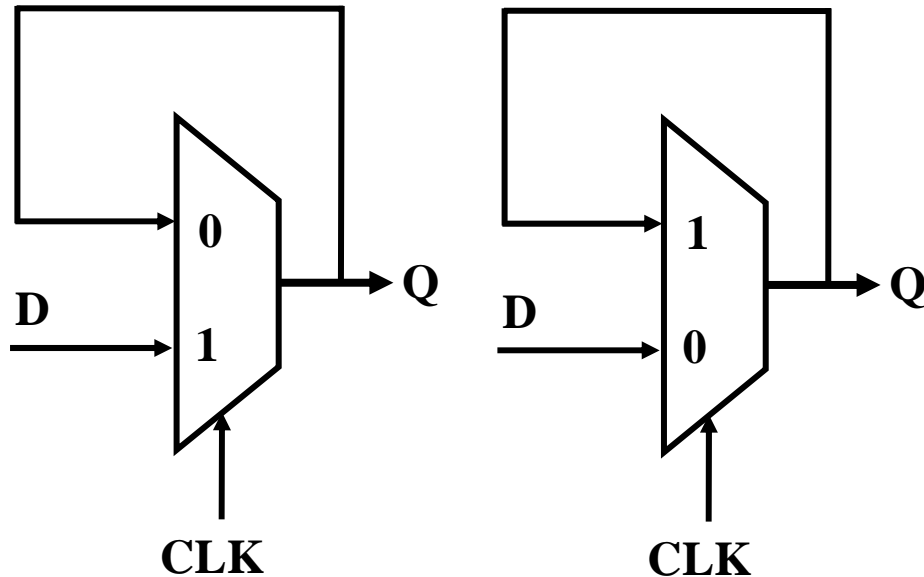


## Register Memory

 

- *Works fine for small memory blocks (e.g., small register files)*
- *Inefficient in area for large memories – **density is the key metric in large memory circuits***

***How do we minimize cell size?***

# Static RAM (SRAM) Cell (The 6-T Cell)

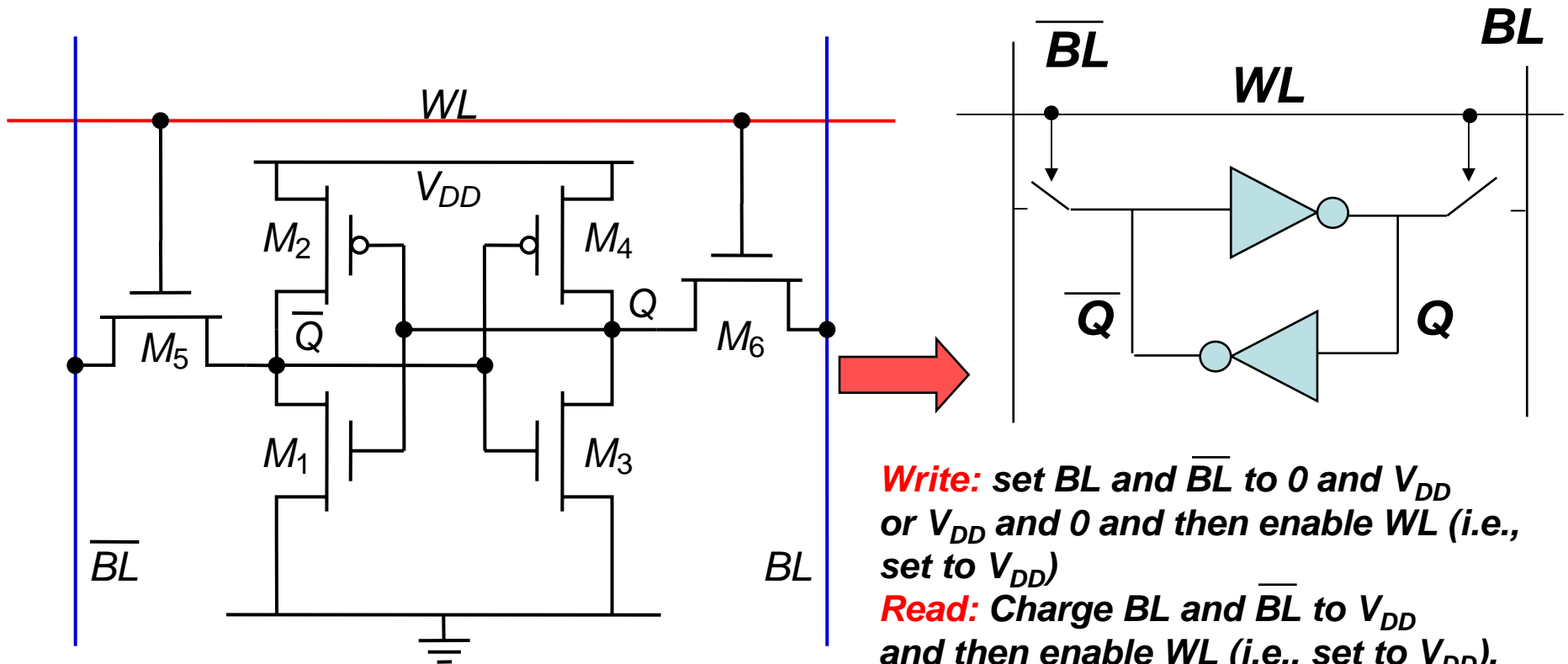


**Write:** set  $BL$  and  $\overline{BL}$  to 0 and  $V_{DD}$  or  $V_{DD}$  and 0 and then enable  $WL$  (i.e., set to  $V_{DD}$ )

**Read:** Charge  $BL$  and  $\overline{BL}$  to  $V_{DD}$  and then enable  $WL$  (i.e., set to  $V_{DD}$ ). Sense a small change in  $BL$  or  $\overline{BL}$

- **State held by cross-coupled inverters (M1-M4)**
- Retains state as long as power supply turned on
- Feedback must be overdriven to write into the memory


# Interacting with a Memory Device

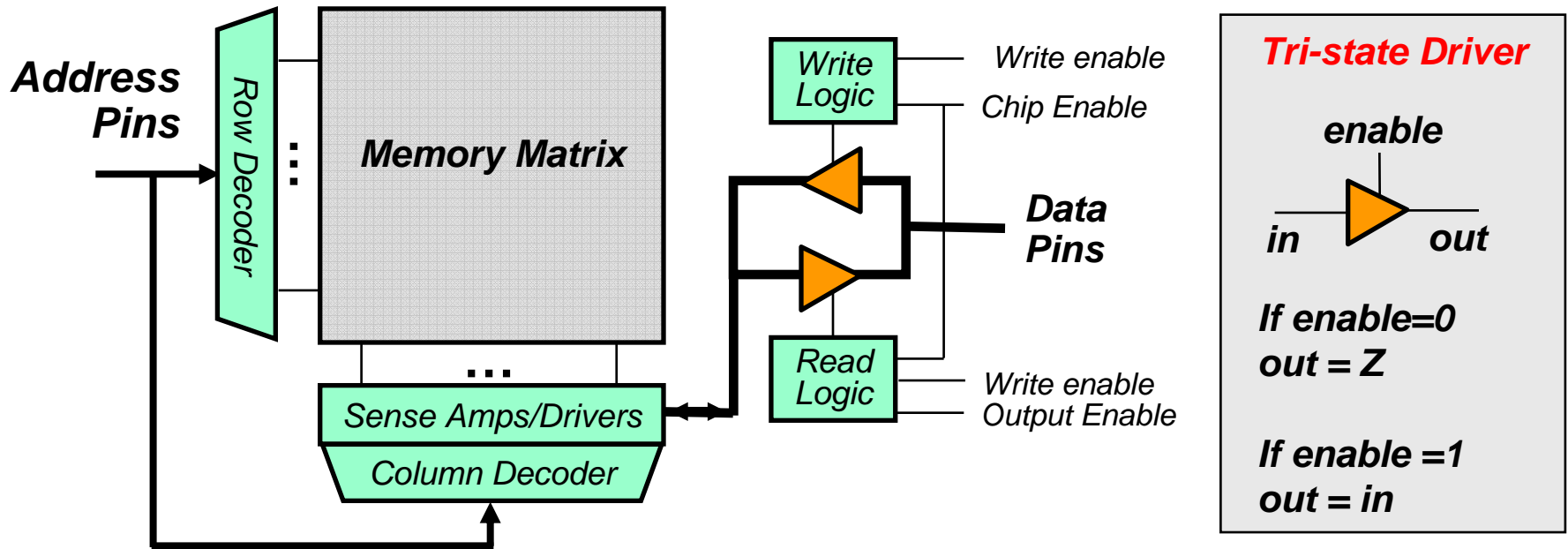

- **Address** pins drive row and column decoders
- **Data** pins are bidirectional and shared by reads and writes
- **Output Enable** gates the chip's tristate driver
- **Write Enable** sets the memory's read/write mode
- **Chip Enable/Chip Select** acts as a "master switch"

# MCM6264C 8K x 8 Static RAM

## On the outside:

 

Same (bidirectional) data bus used for reading and writing

## Chip Enables ( $\overline{E1}$ and $E2$ )

$\overline{E1}$  must be low and  $E2$  must be high to enable the chip


## Write Enable ( $\overline{W}$ )

When low (and chip is enabled), the values on the data bus are written to the location selected by the address bus


## Output Enable ( $\overline{G}$ )

When low (and chip is enabled), the data bus is driven with the value of the selected memory location


## On the inside:

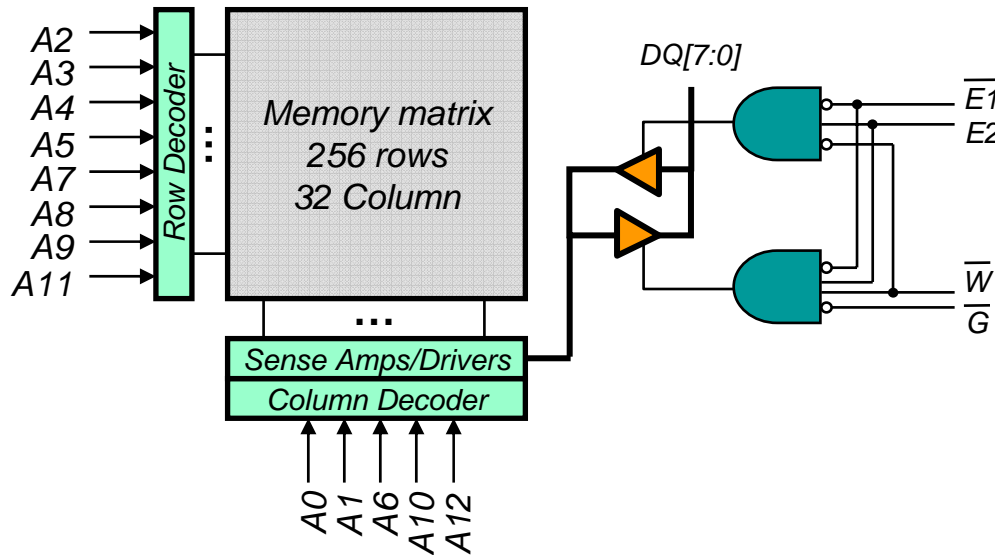

## Pinout

 


# Reading an Asynchronous SRAM

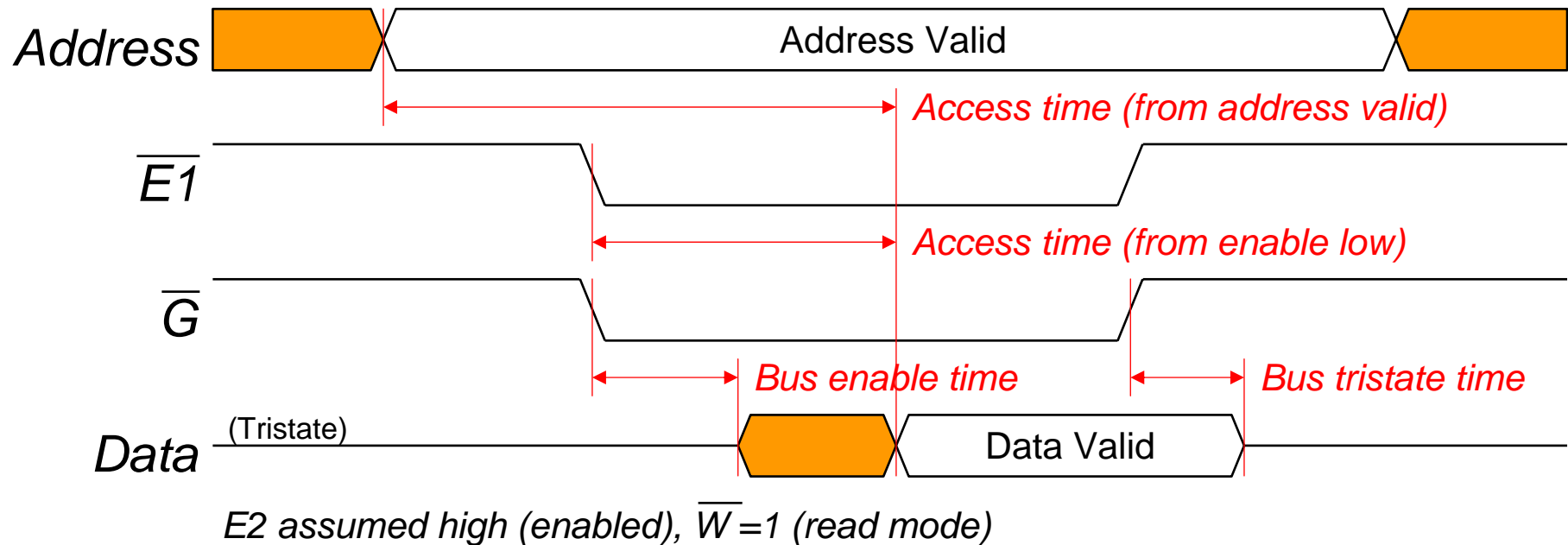

- Read cycle begins when all enable signals ( $\overline{E1}$ ,  $E2$ ,  $\overline{G}$ ) are active
- Data is valid after read access time
  - Access time is indicated by full part number: *MCM6264CP-12*  $\rightarrow$  12ns
- Data bus is tristated shortly after  $\overline{G}$  or  $\overline{E1}$  goes high




# Address Controlled Reads

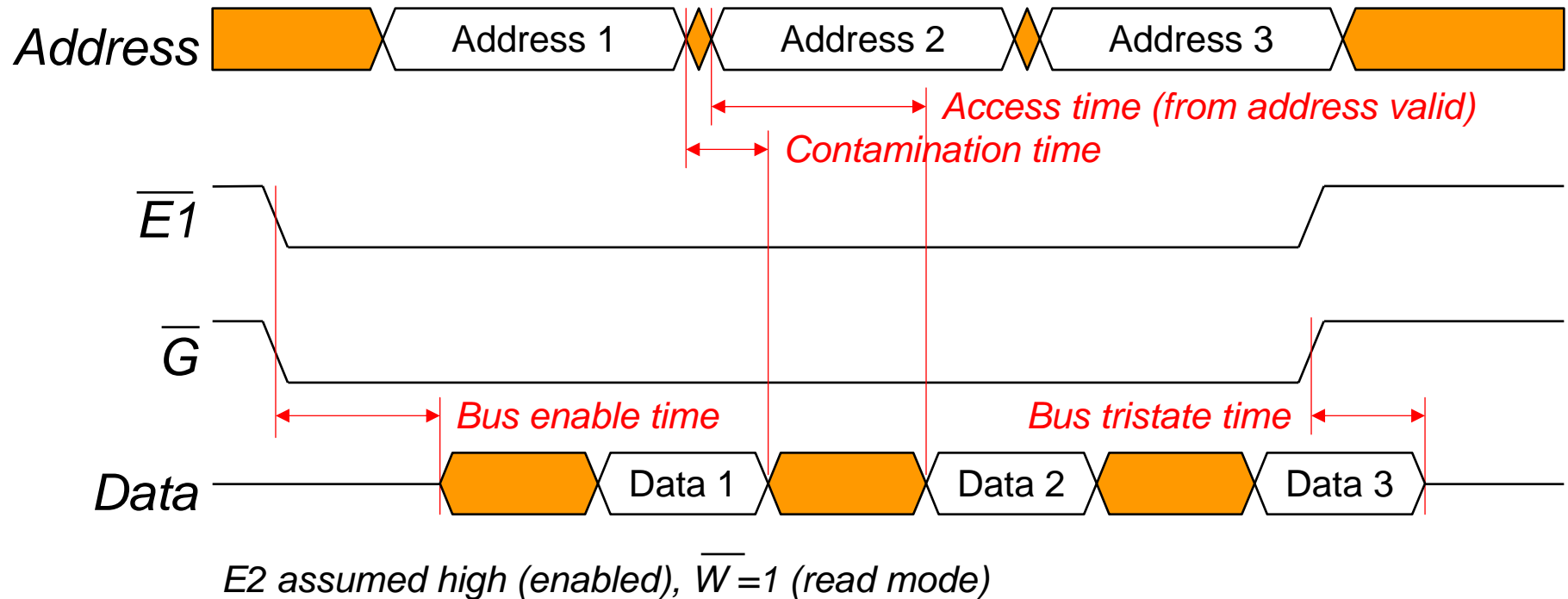

- Can perform multiple reads without disabling chip
- Data bus follows address bus, after some delay



# Writing to Asynchronous SRAM

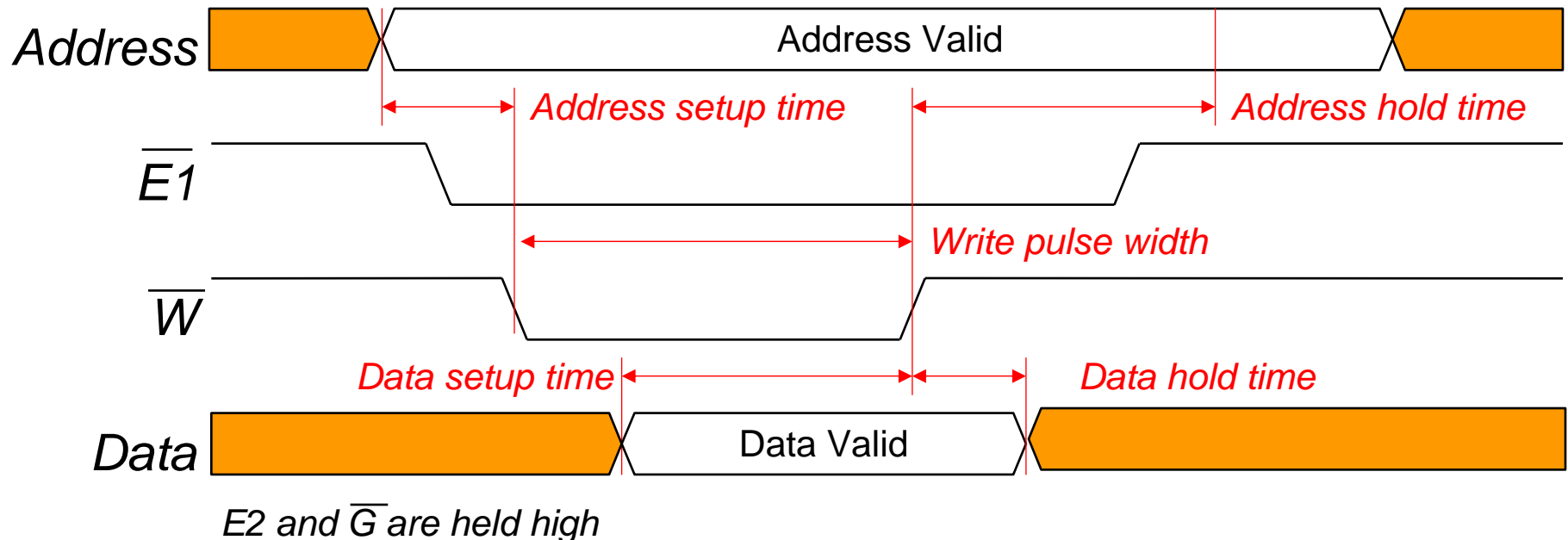


- Data latched when  $\overline{W}$  or  $\overline{E1}$  goes high (or E2 goes low)
  - Data must be stable at this time
  - Address must be stable before  $\overline{W}$  goes low
- Write waveforms are more important than read waveforms
  - Glitches to address can cause writes to random addresses!


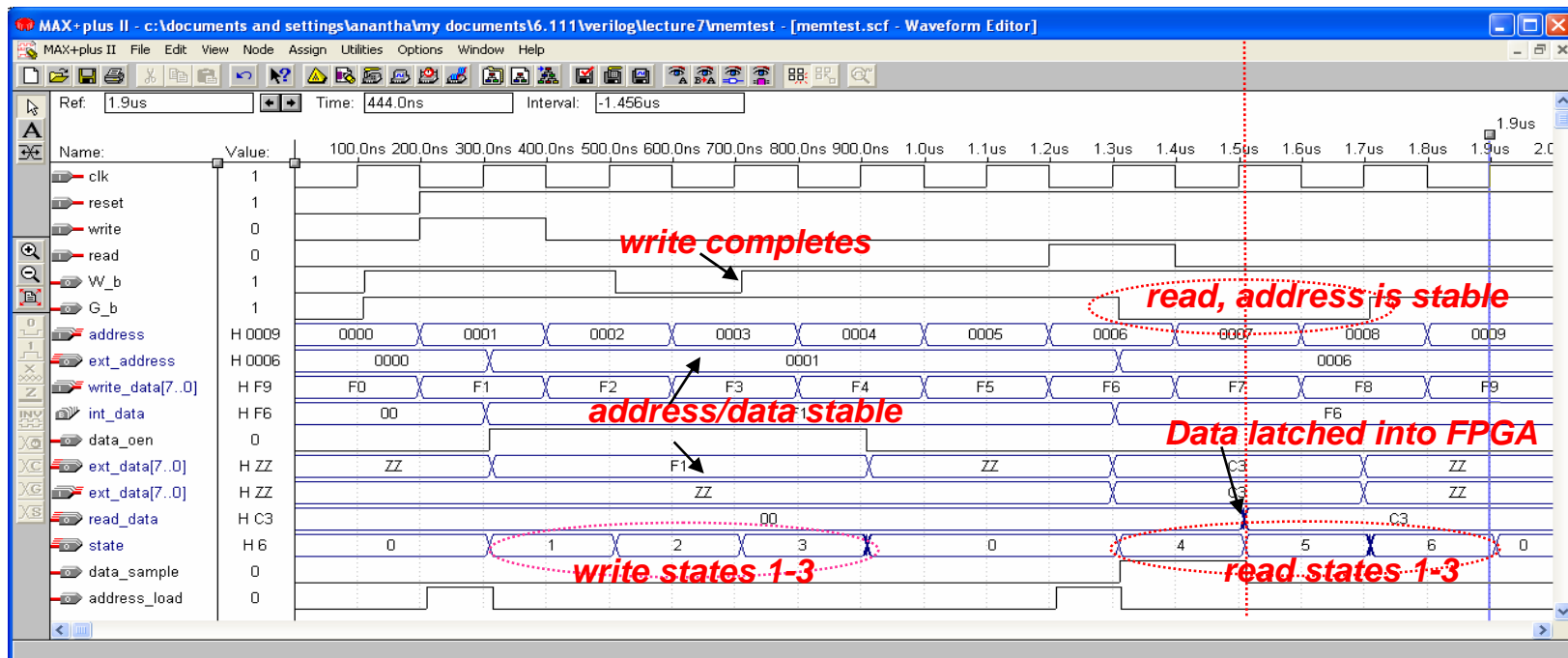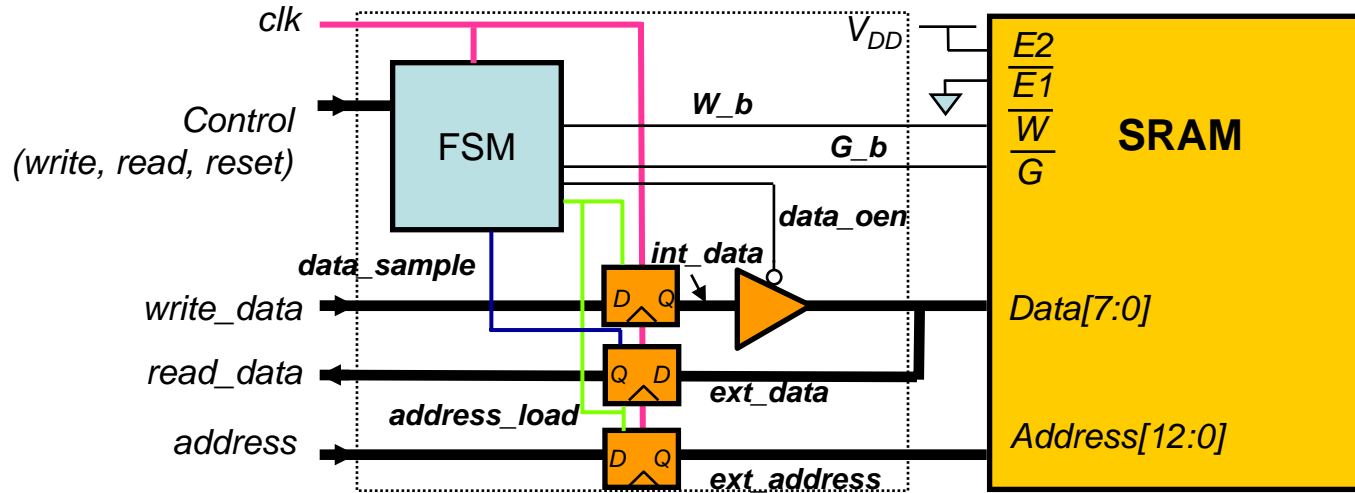
# Multi-Cycle Read/Write (less aggressive, recommended timing)



# Simulation from Previous Slide

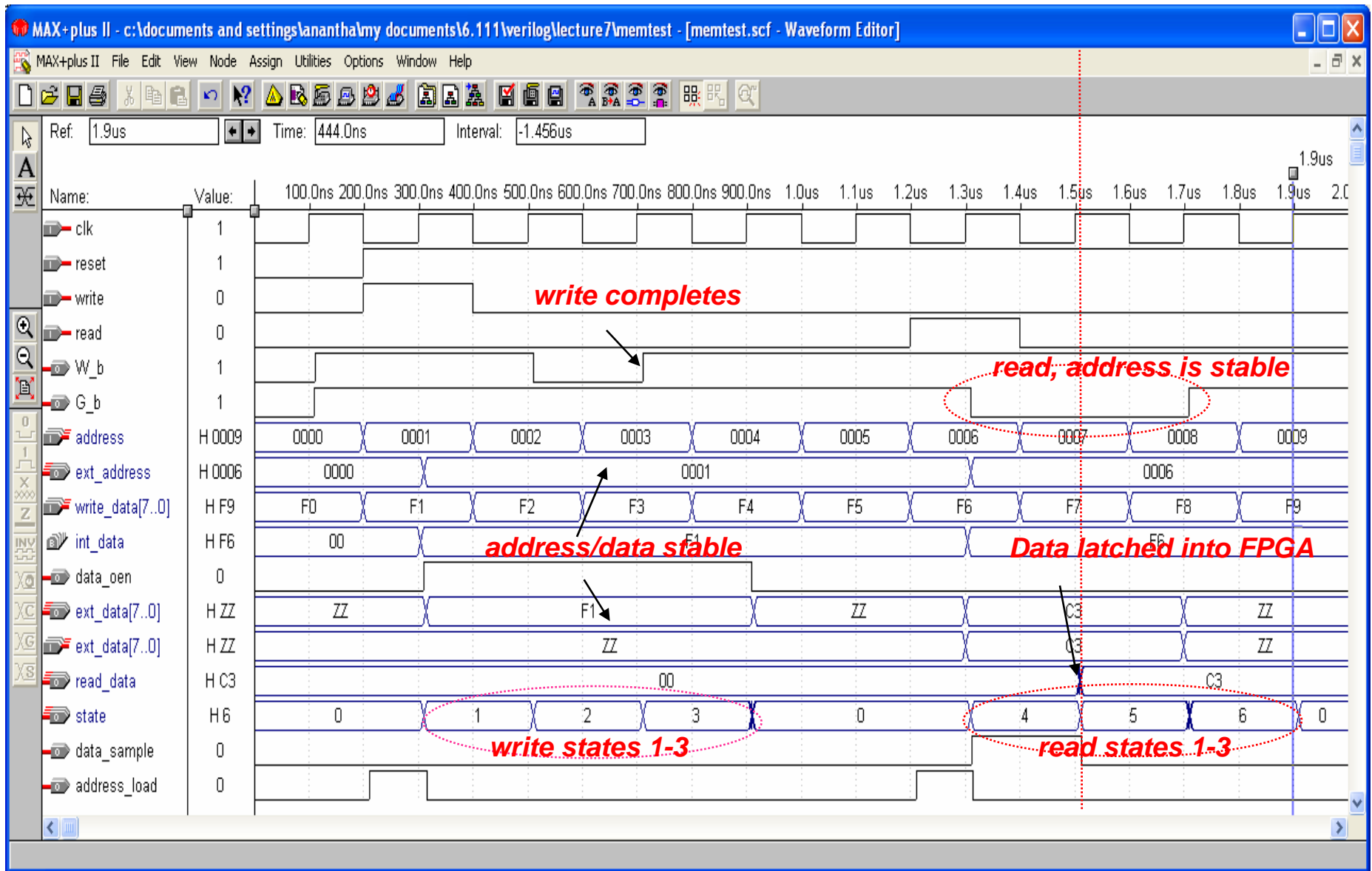

# Verilog for Simple Multi-Cycle Access

```
module memtest (clk, reset, G_b, W_b, address,
  ext_address, write_data, read_data, ext_data,
  read, write, state, data_oen, address_load,
  data_sample);
  input clk, reset, read, write;
  output G_b, W_b;
  output [12:0] ext_address;
  reg [12:0] ext_address;
  input [12:0] address;
  input [7:0] write_data;
  output [7:0] read_data;
  reg [7:0] read_data;
  inout [7:0] ext_data;
  reg [7:0] int_data;
  output [2:0] state;
  reg [2:0] state, next;
  output data_oen, address_load, data_sample;
  reg G_b, W_b, G_b_int, W_b_int, address_load,
  data_oen, data_oen_int, data_sample;

  wire [7:0] ext_data;
  parameter IDLE = 0;
  parameter write1 = 1;
  parameter write2 = 2;
  parameter write3 = 3;
  parameter read1 = 4;
  parameter read2 = 5;
  parameter read3 = 6;
```

1/4

```
// Sequential always block for state assignment
```

```
assign ext_data = data_oen ? int_data : 8'hz;
```

```
always @ (posedge clk)
```

```
begin
```

```
if (!reset) state <= IDLE;
```

```
else state <= next;
```

```
G_b <= G_b_int;
```

```
W_b <= W_b_int;
```

```
data_oen <= data_oen_int;
```

```
if (address_load) ext_address <= address;
```

```
if (data_sample) read_data <= ext_data;
```

```
if (address_load) int_data <= write_data;
```

```
end
```

```
// note that address_load and data_sample are not
```

```
// registered signals
```

2/4

# Verilog for Simple Multi-Cycle Access

```
// Combinational always block for next-state  
// computation
```

```
always @ (state or read or write) begin
```

```
    W_b_int = 1;  
    G_b_int = 1;  
    address_load = 0;  
    data_oen_int = 0;  
    data_sample = 0;
```

*Setup the  
Default values*

```
    case (state)
```

```
    IDLE:
```

```
        if (write) begin
```

```
            next = write1;  
            address_load = 1;  
            data_oen_int = 1;
```

```
        end
```

```
        else if (read) begin
```

```
            next = read1;  
            address_load = 1;  
            G_b_int = 0;
```

```
        end
```

```
        else next = IDLE;
```

```
    write1: begin
```

```
        next = write2;  
        W_b_int = 0;  
        data_oen_int = 1;  
    end
```

3/4

```
    write2: begin  
        next = write3;  
        data_oen_int = 1;  
    end  
    write3: begin  
        next = IDLE;  
        data_oen_int = 0;  
    end  
    read1: begin  
        next = read2;  
        G_b_int = 0;  
        data_sample = 1;  
    end  
    read2: begin  
        next = read3;  
    end  
    read3: begin  
        next = IDLE;  
    end  
    default: next = IDLE;  
endcase  
end  
endmodule
```

4/4


# Testing Memories

- **Common device problems**
  - **Bad locations: rare for individual locations to be bad**
  - **Slow (out-of-spec) timing(s): access incorrect data or violates setup/hold**
  - **Catastrophic device failure: e.g., ESD**
  - **Missing wire-bonds/devices (!): possible with automated assembly**
  - **Transient Failures: Alpha particles, power supply glitch**
- **Common board problems**
  - **Stuck-at-Faults: a pin shorted to  $V_{DD}$  or GND**
  - **Open Circuit Fault: connections unintentionally left out**
  - **Open or shorted address wires: causes data to be written to incorrect locations**
  - **Open or shorted control wires: generally renders memory completely inoperable**
- **Approach**
  - **Device problems generally affect the entire chip, almost any test will detect them**
  - **Writing (and reading back) many different data patterns can detect data bus problems**
  - **Writing unique data to every location and then reading it back can detect address bus problems**


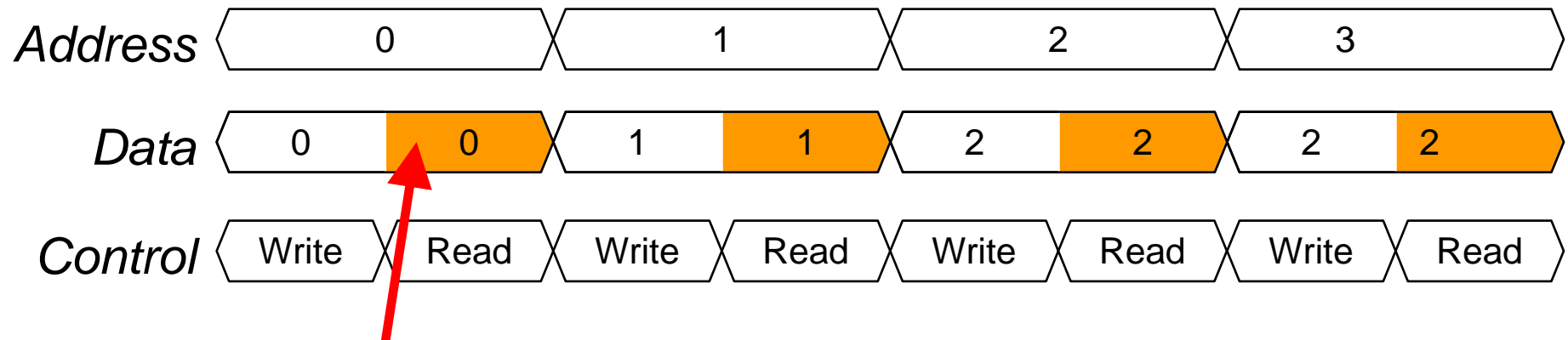
# An Approach

- **An idea that almost works**
  1. Write 0 to location 0
  2. Read location 0, compare value read with 0
  3. Write 1 to location 1
  4. Read location 1, compare value read with 1
  5. ...
- **What is the problem?**
  - **Suppose the memory was missing (or output enable was disconnected)**




***Data bus is undriven but wire capacitance briefly maintains the bus state: **memory appears to be ok!*****
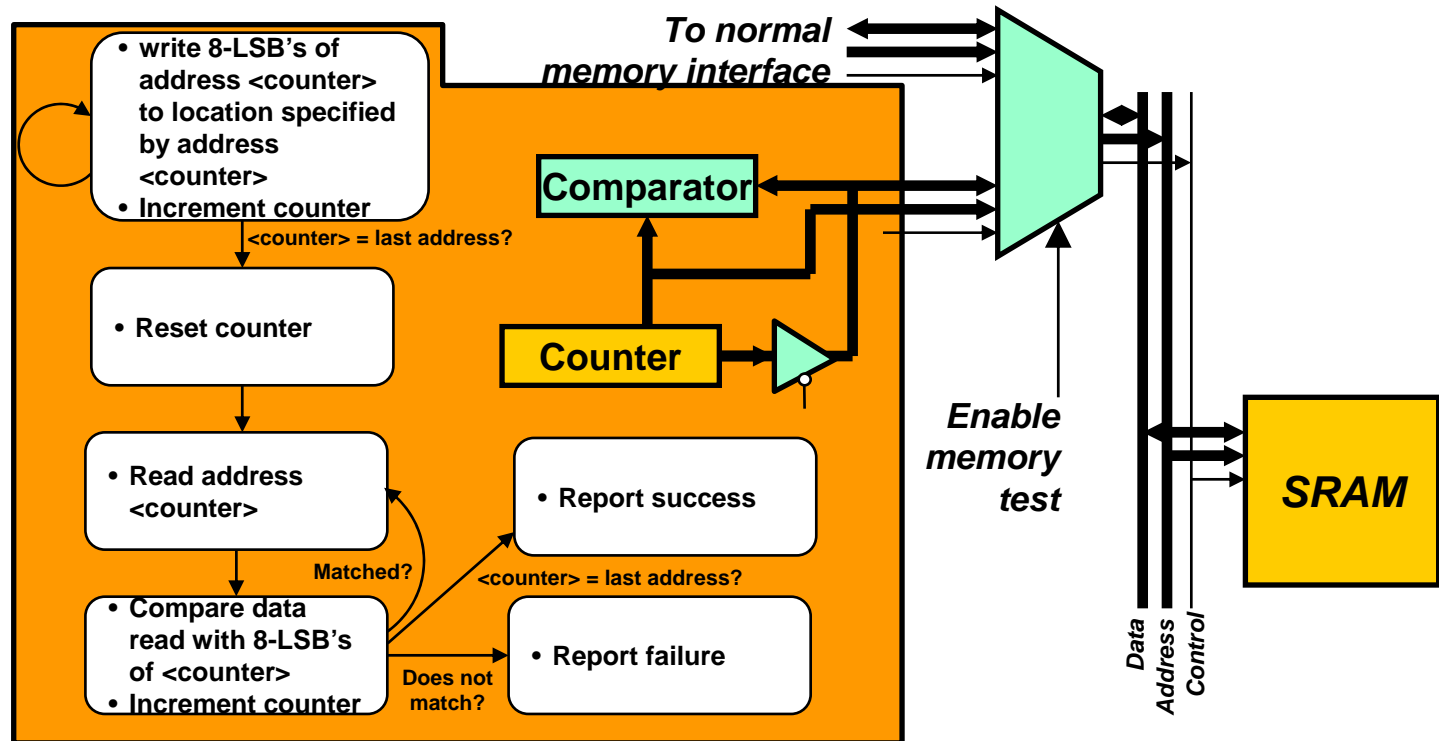
# A Simple Memory Tester


- Write to all locations, then read back all locations
  - Separates read/write to the same location with reads/writes of different data to different locations
  - (both data and address busses are changed between read and write to same location)

- Write 0 to address 0
- Write 1 to address 1
- ...
- Write ( $n \bmod 256$ ) to address  $n$
- Read address 0, compare with 0
- Read address 1, compare with 1
- ...
- Read address  $n$ , compare with ( $n \bmod 256$ )



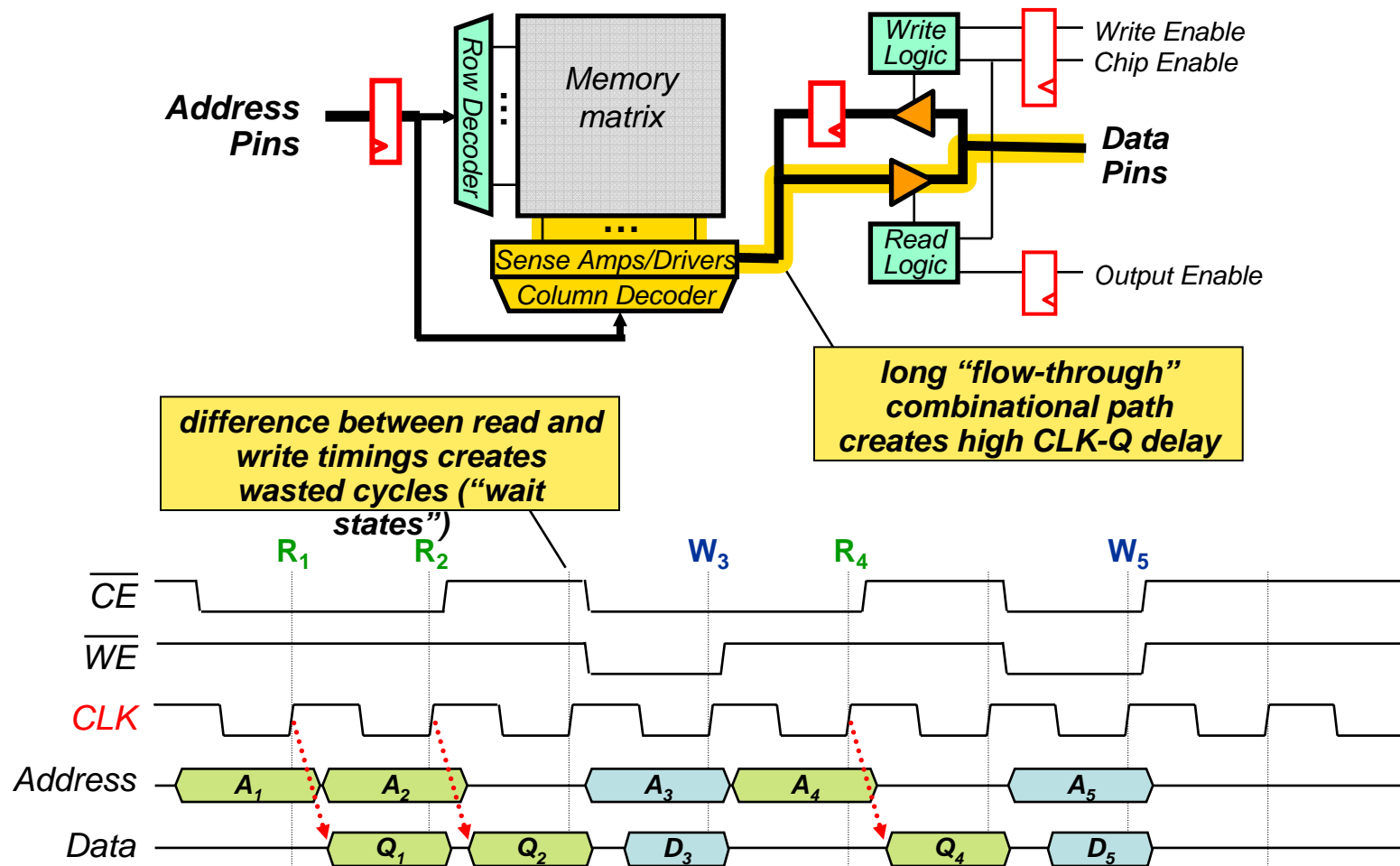
# Synchronous SRAM Memories

- **Clocking** provides input synchronization and encourages more reliable operation at high speeds



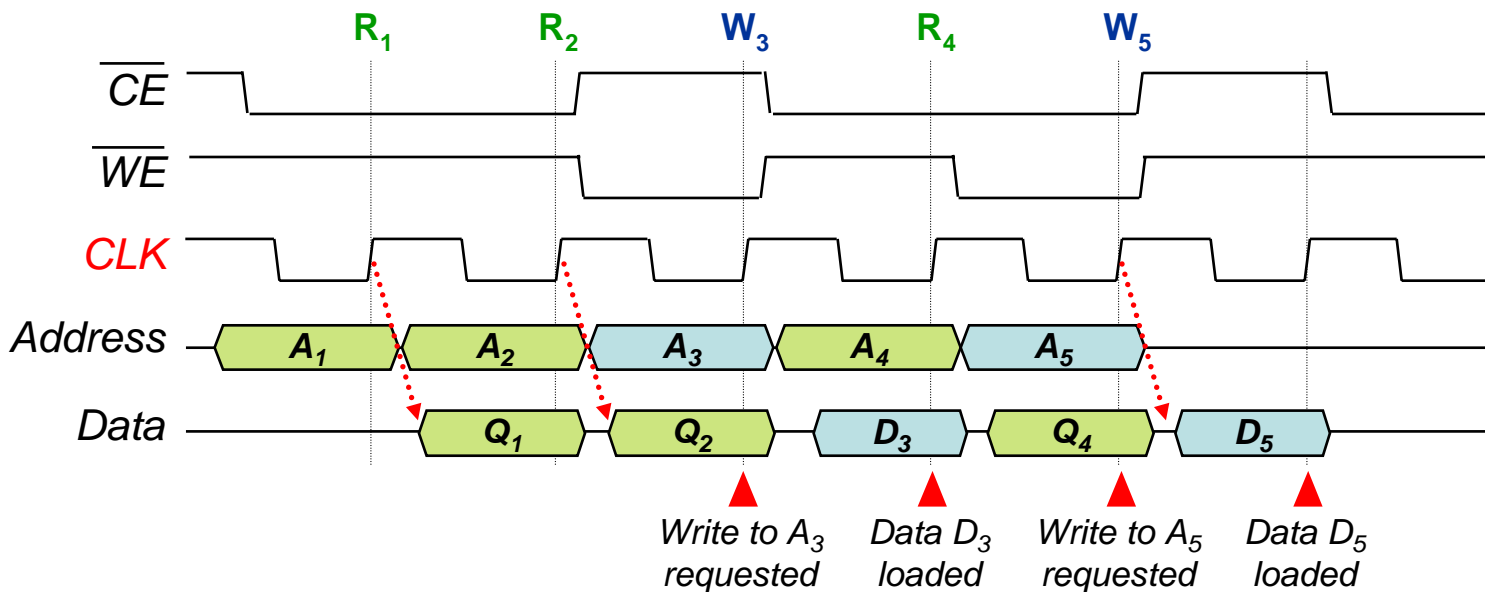
# ZBT Eliminates the Wait State

- The wait state occurs because:
  - On a read, data is available *after* the clock edge
  - On a write, data is set up *before* the clock edge
- ZBT (“zero bus turnaround”) memories **change the rules for writes**
  - On a write, data is set up **after** the clock edge (so that it is read on the following edge)
  - Result: no wait states, higher memory throughput



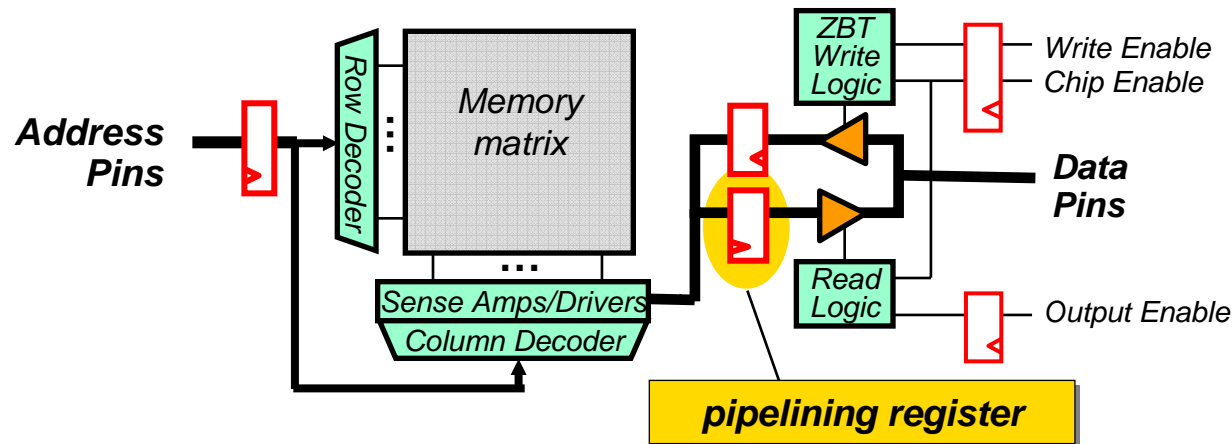
# Pipelining Allows Faster CLK



- Pipeline the memory by registering its output
  - Good: Greatly reduces CLK-Q delay, allows higher clock (more throughput)
  - Bad: Introduces an extra cycle before data is available (more latency)



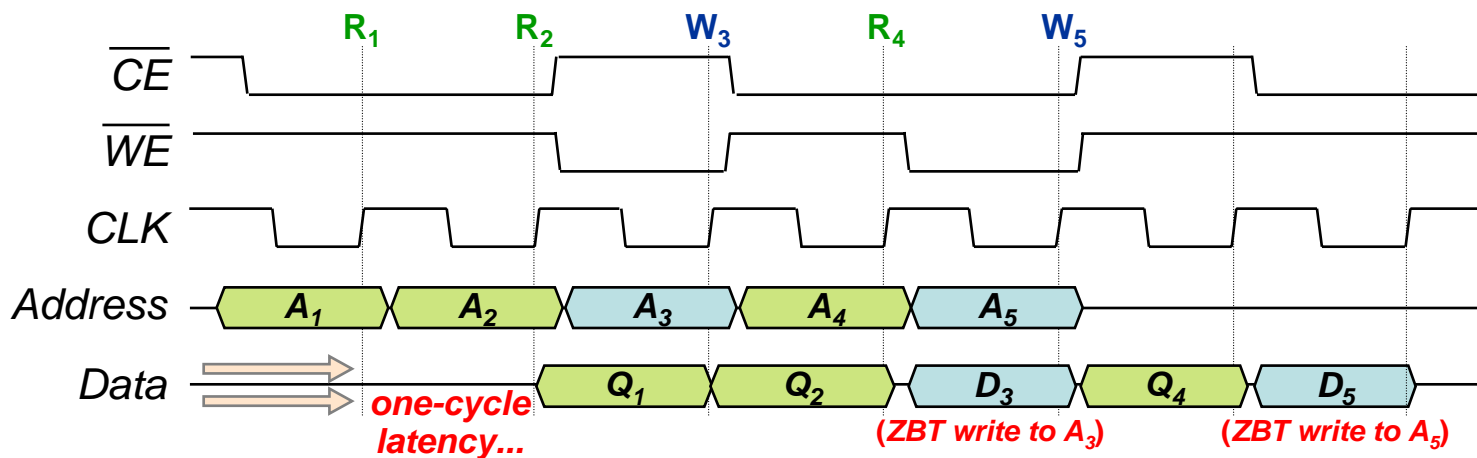As an example,  
see the **CY7C147X**  
ZBT Synchronous  
SRAM


 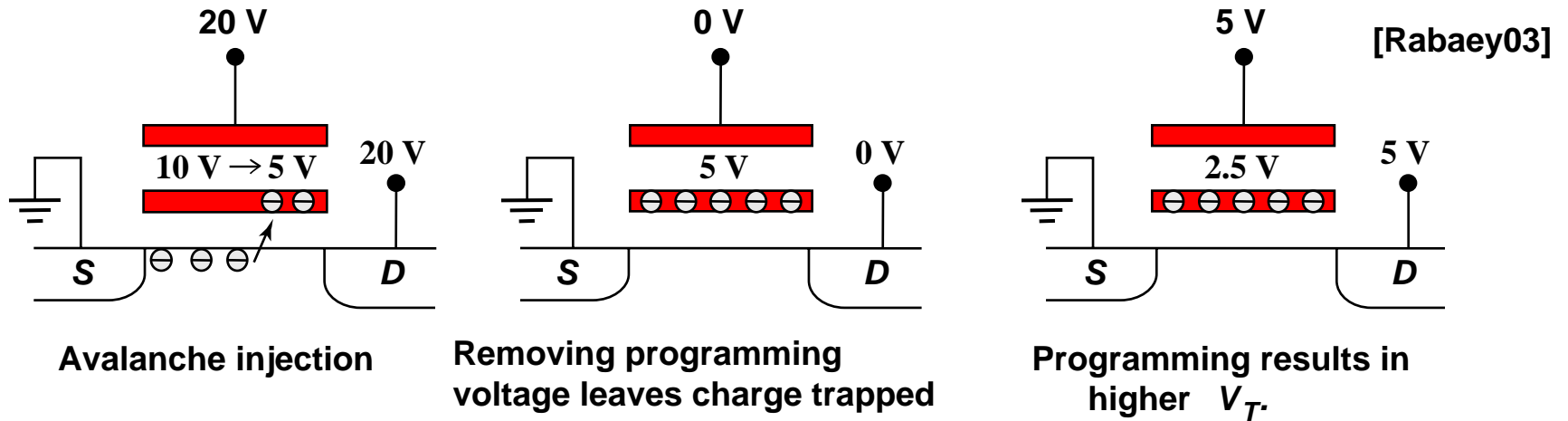
# EPRM Cell - The Floating Gate Transistor




## EPROM Cell

*Courtesy Intel*



**This is a non-volatile memory (retains state when supply turned off)**
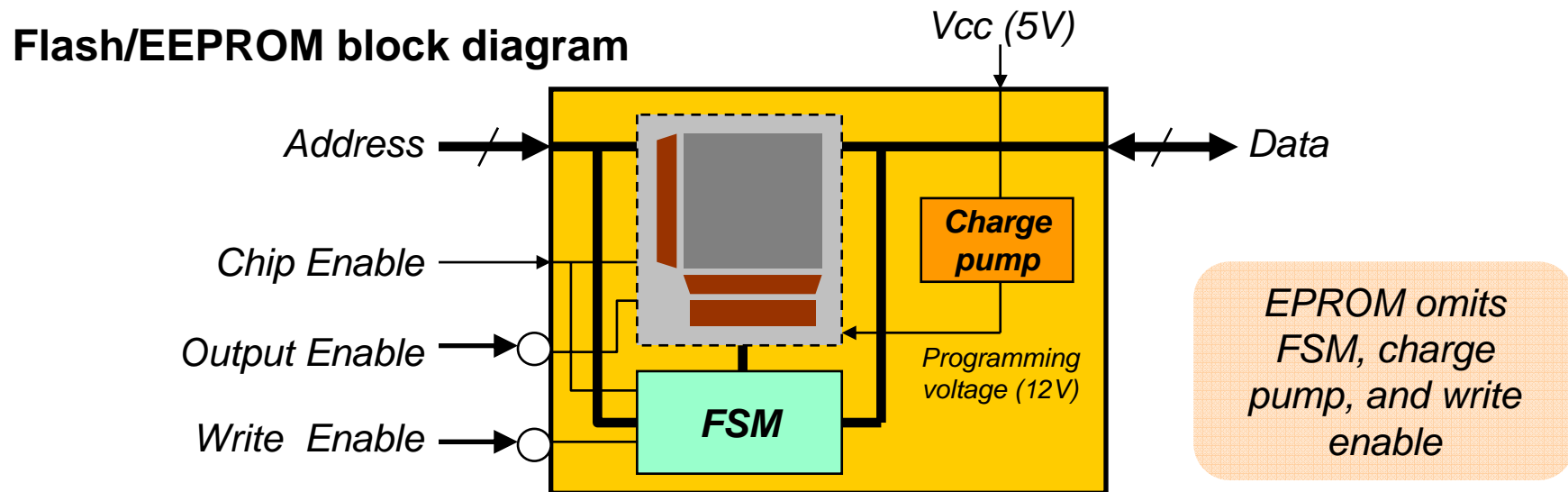
# Interacting with Flash and (E)EPROM


- Reading from flash or (E)EPROM is the same as reading from SRAM
- $V_{pp}$ : input for programming voltage (12V)
  - EPROM:  $V_{pp}$  is supplied by programming machine
  - Modern flash/EEPROM devices generate 12V using an on-chip charge pump
- EPROM lacks a write enable
  - Not in-system programmable (must use a special programming machine)
- For flash and EEPROM, write sequence is controlled by an internal FSM
  - Writes to device are used to send signals to the FSM
  - Although the same signals are used, one can't write to flash/EEPROM in the same manner as SRAM



# Dynamic RAM (DRAM) Cell

  

DRAM uses Special Capacitor Structures

 


**To Write:** set Bit Line (BL) to 0 or  $V_{DD}$  & enable Word Line (WL) (i.e., set to  $V_{DD}$ )

**To Read:** set Bit Line (BL) to  $V_{DD}/2$  & enable Word Line (i.e., set it to  $V_{DD}$ )

- DRAM relies on charge stored in a capacitor to hold state
- Found in all high density memories (one bit/transistor)
- Must be “refreshed” or state will be lost – high overhead





# Asynchronous DRAM Operation

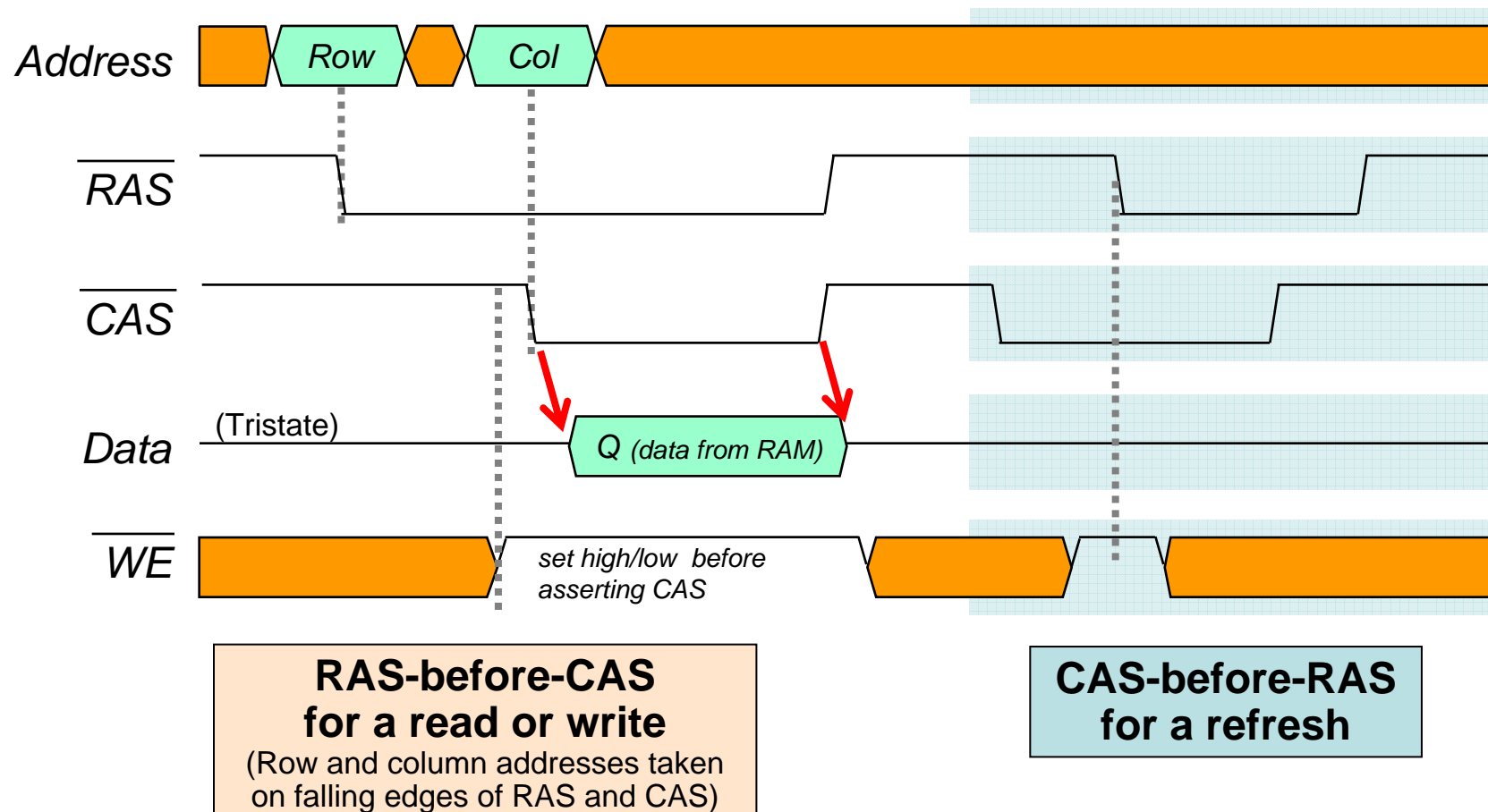

- **Clever manipulation of RAS and CAS after reads/writes provide more efficient modes: early-write, read-write, hidden-refresh, etc. (See datasheets for details)**
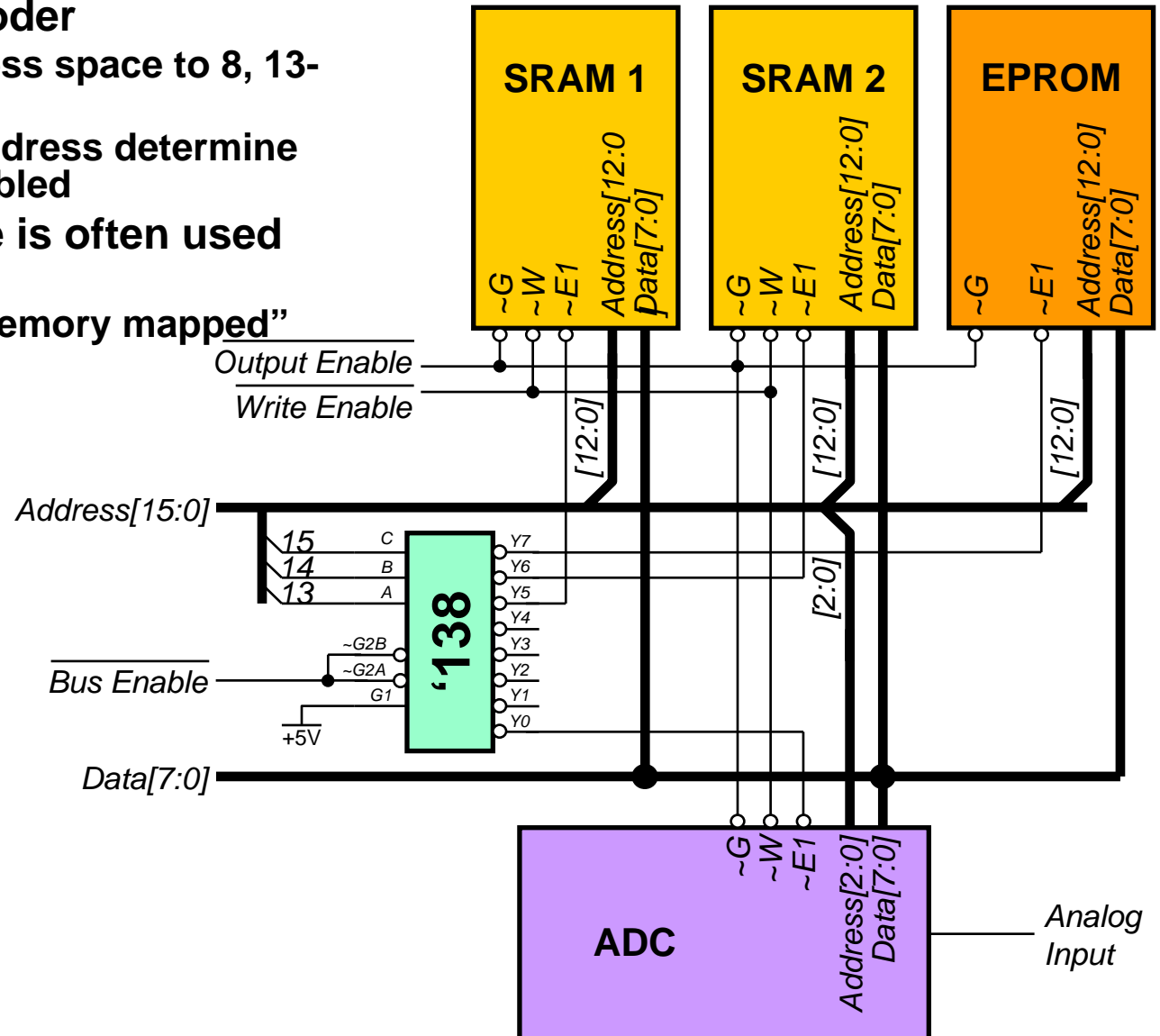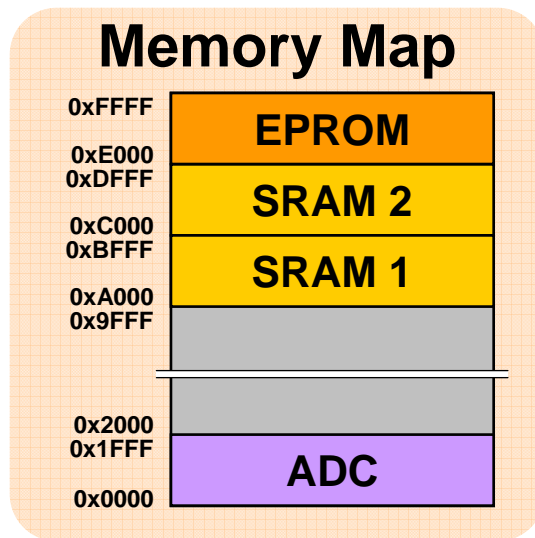
# Addressing with Memory Maps

- '138 is a 3-to-8 decoder
  - Maps 16-bit address space to 8, 13-bit segments
  - Upper 3-bits of address determine which chip is enabled
- SRAM-like interface is often used for peripherals
  - Referred to as “memory mapped” peripherals



# Key Messages on Memory Devices

- **SRAM vs. DRAM**
  - SRAM holds state as long as power supply is turned on. DRAM must be "refreshed" - results in more complicated control
  - DRAM has much higher density, but requires special capacitor technology.
  - FPGA usually implemented in a standard digital process technology and uses SRAM technology
- **Non-Volatile Memory**
  - Fast Read, but very slow write (EPROM must be removed from the system for programming!)
  - Holds state even if the power supply is turned off
- **Memory Internals**
  - Has quite a bit of analog circuits internally -- pay particular attention to noise and PCB board integration
- **Device details**
  - Don't worry about them, wait until 6.012 or 6.374

# You Should Understand Why...

- control signals such as *Write Enable* should be registered
- a multi-cycle read/write is safer from a timing perspective than the single cycle read/write approach
- it is a bad idea to enable two tri-states driving the bus at the same time
- an SRAM does not need to be “refreshed” while a DRAM requires refresh
- an EPROM/EEPROM/FLASH cell can hold its state even if the power supply is turned off
- a synchronous memory can result in higher throughput