


L11: Analog Building Blocks

(OpAmps, A/D, D/A)


Acknowledgement: Dave Wentzloff

Introduction to Operational Amplifiers


DC Model

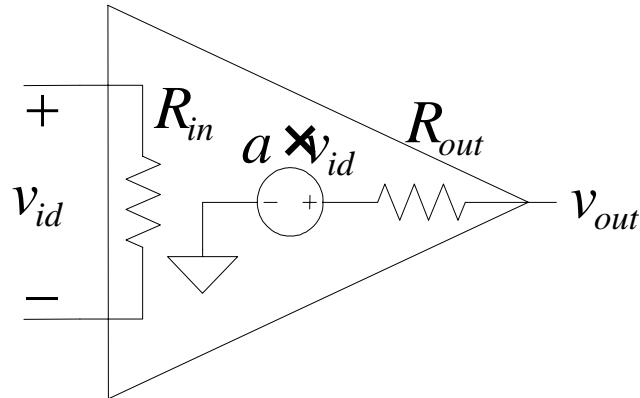


LM741 Pinout

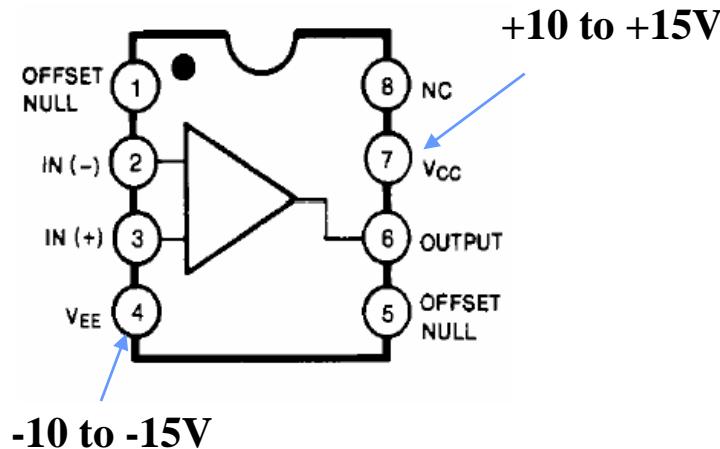

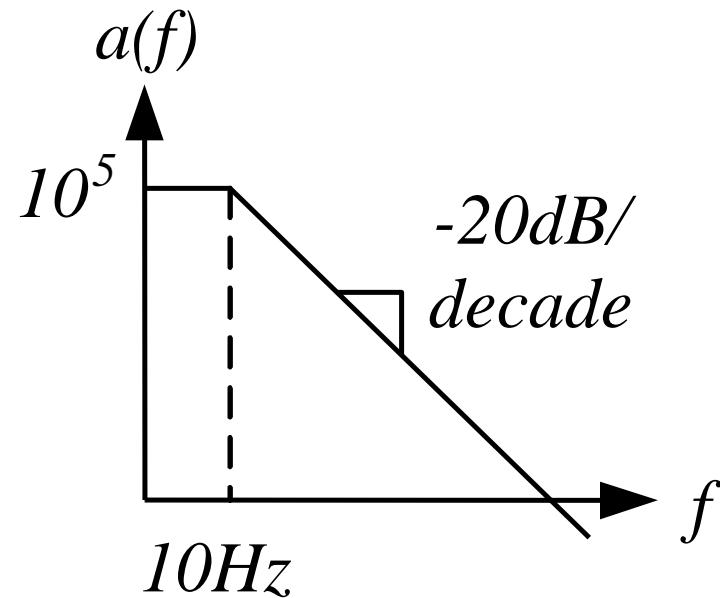- Typically very high input resistance $\sim 300K\Omega$
 - High DC gain ($\sim 10^5$)
 - Output resistance $\sim 75\Omega$
- $$V_{out} = a(f) \cdot V_{in}$$





The Inside of a 741 OpAmp

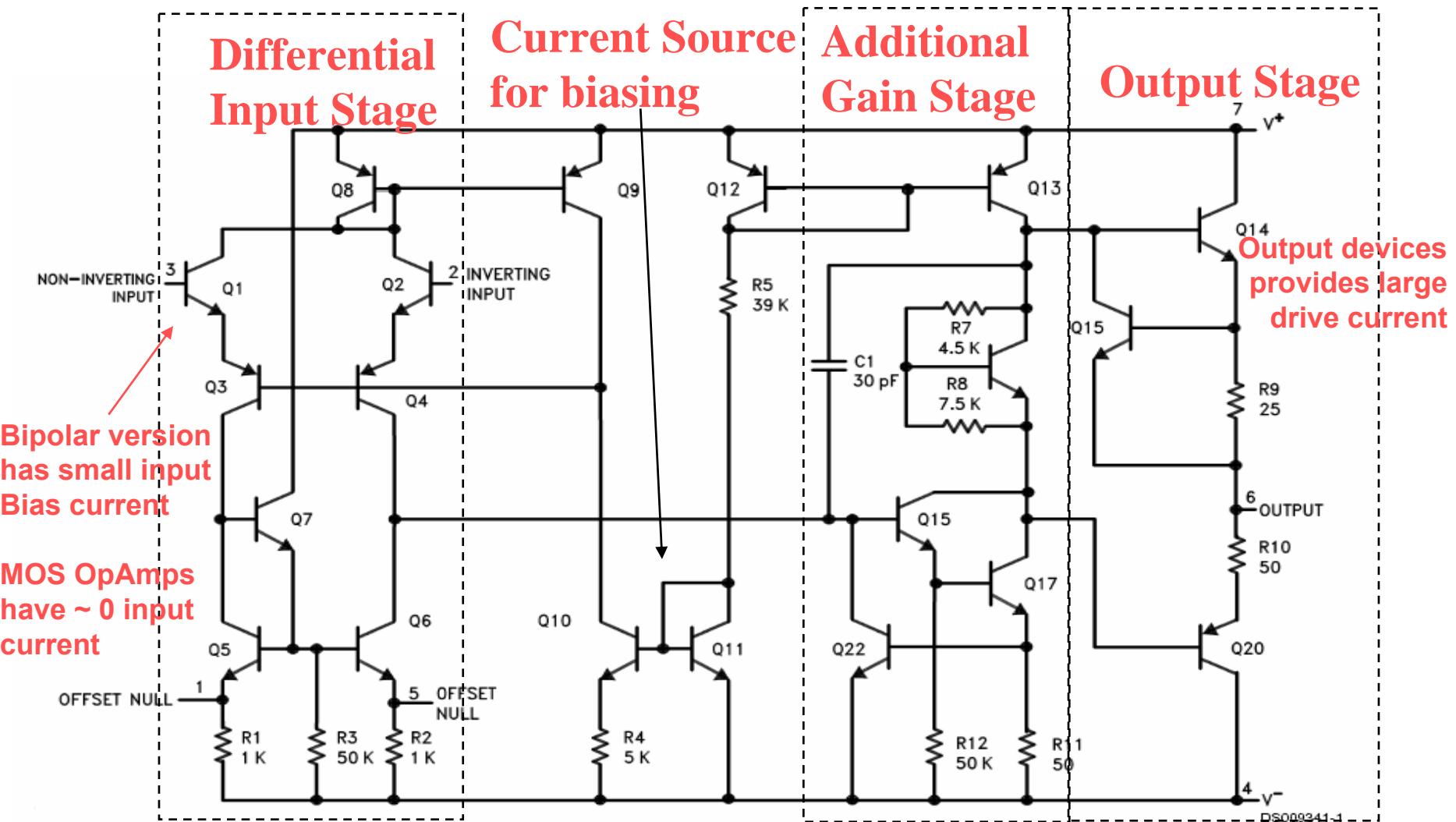


**Gain is Sensitive to Operating Condition
(e.g., Device, Temperature, Power supply voltage, etc.)**

Simple Model for an OpAmp

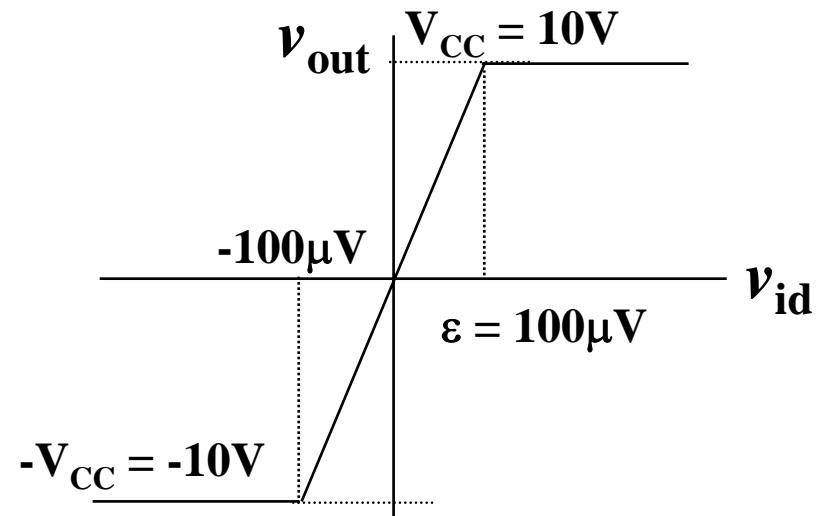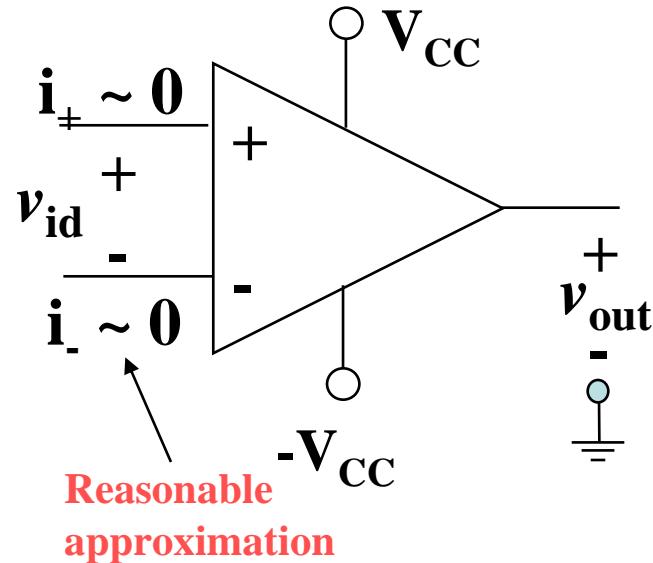


Linear Mode

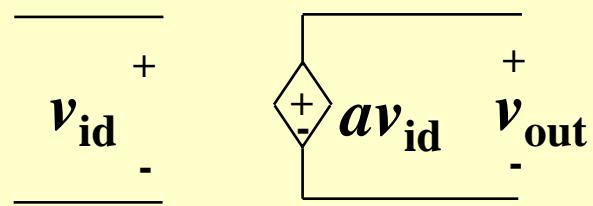


If $-V_{CC} < v_{out} < V_{CC}$

Negative Saturation

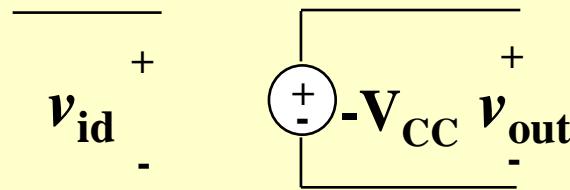

$v_{id} < -\varepsilon$


Positive Saturation

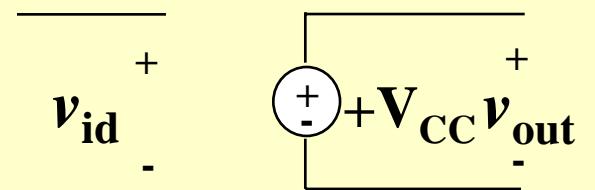

$v_{id} > \varepsilon$

Very small input range for “open loop” configuration

The Power of (Negative) Feedback

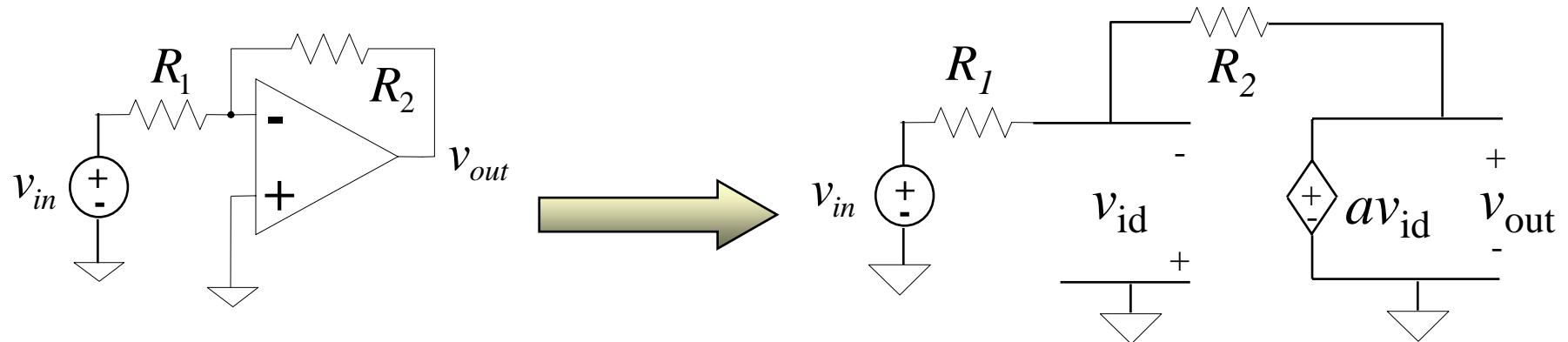


$$\frac{v_{in} + v_{id}}{R_1} + \frac{v_{out} + v_{id}}{R_2} = 0 \quad v_{id} = \frac{v_{out}}{a} \quad \frac{v_{in}}{R_1} = -\frac{v_{out}}{a} \left[\frac{1}{R_1} + \frac{a}{R_2} + \frac{1}{R_2} \right]$$

$$\frac{v_{out}}{v_{in}} = -\frac{R_2 a}{(1+a)R_1 + R_2} \approx -\frac{R_2}{R_1} \text{ (if } a \gg 1)$$

- Overall (closed loop) gain does not depend of open loop gain
- Trade gain for robustness
- Easier analysis approach: “virtual short circuit approach”
 - $v_+ = v_- = 0$ if OpAmp is linear


Basic OpAmp Circuits

Voltage Follower (buffer)

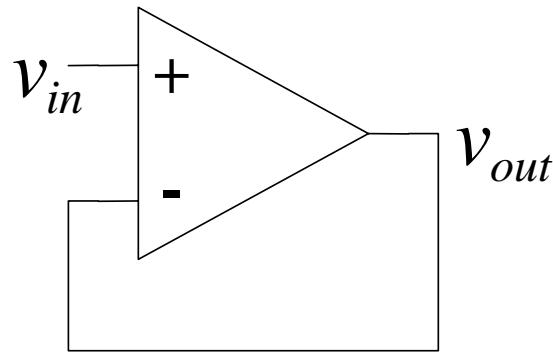


$$v_{out} \approx v_{in}$$

Differential Input

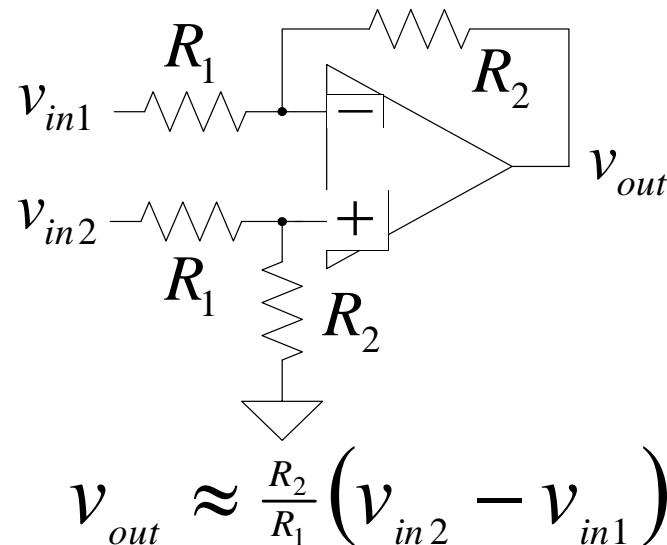


$$v_{out} \approx \frac{R_2}{R_1} (v_{in2} - v_{in1})$$

Non-inverting

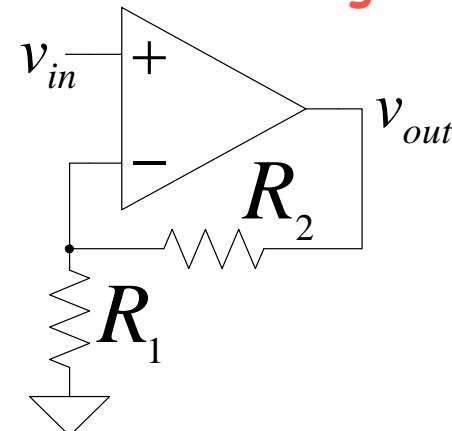

$$v_{out} \approx \frac{R_1 + R_2}{R_1} v_{in}$$

Integrator

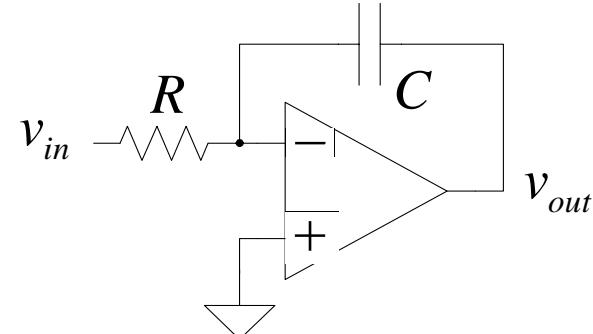

$$v_{out} \approx -\frac{1}{RC} \int_{-\infty}^t v_{in} dt$$


Use With Open Loop

Analog Comparator:

Is $V_+ > V_-$? The Output is a DIGITAL signal


Analog Comparator: Analog to TTL

LM 311 Needs Pull-Up


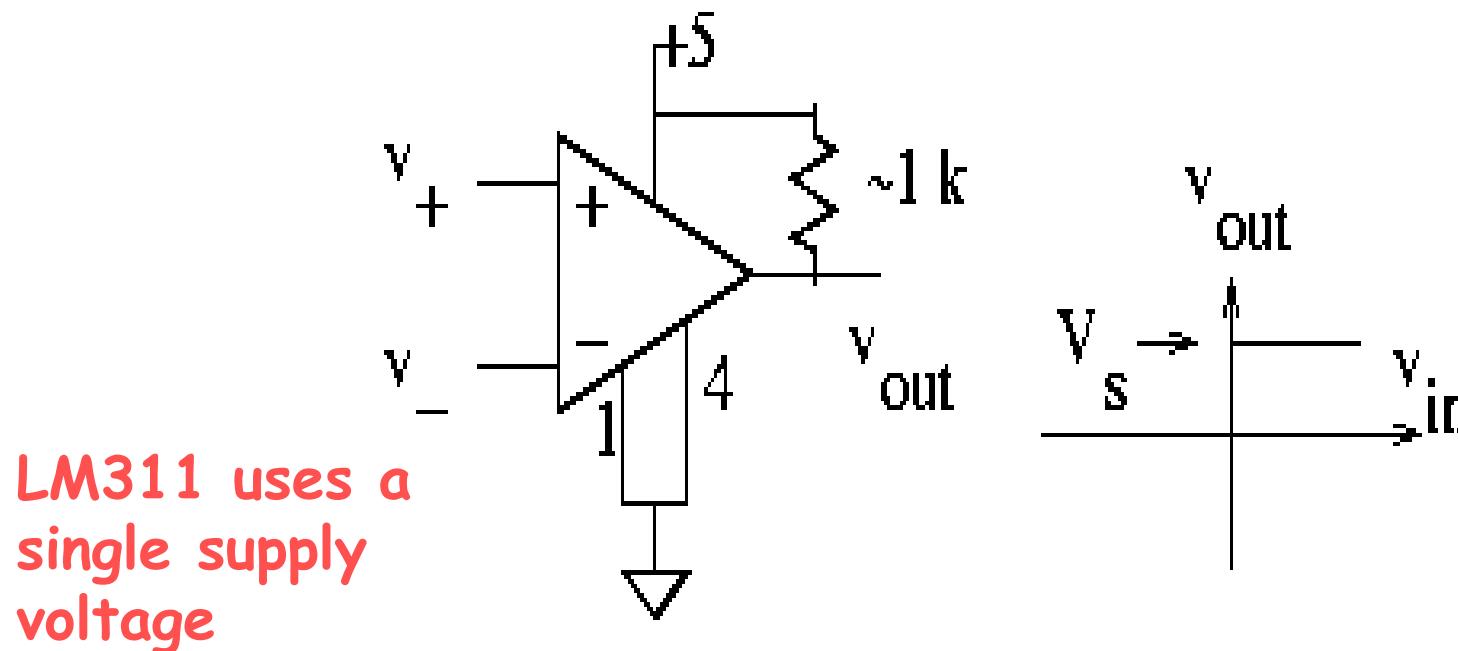


Data Conversion: Quantization Noise


A/D Conversion

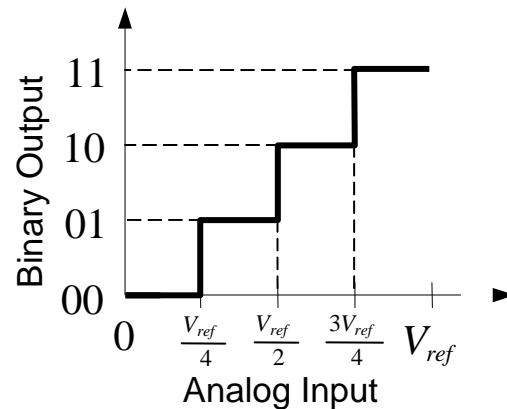

D/A Conversion

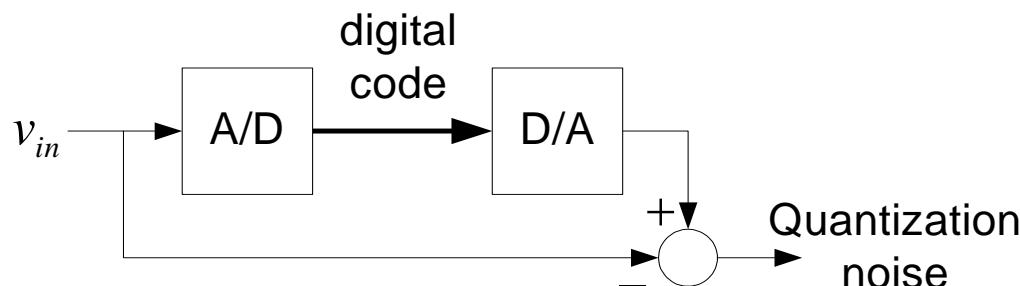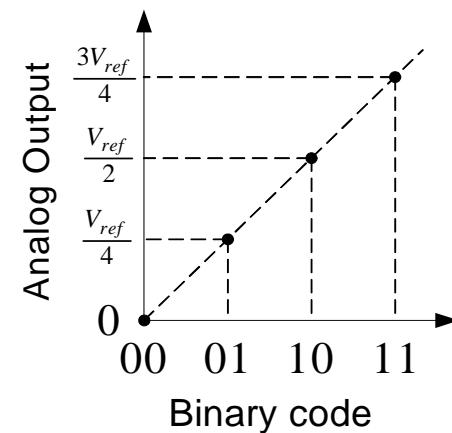


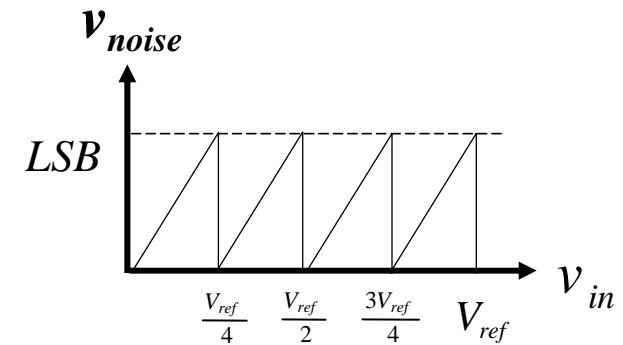- Quantization noise exists even with *ideal* A/D and D/A converters




Non-idealities in Data Conversion

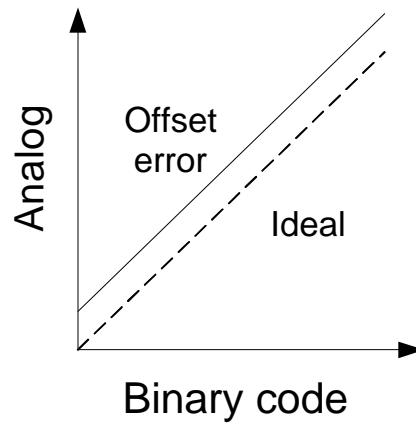
Offset - a constant voltage offset that appears at the output when the digital input is 0



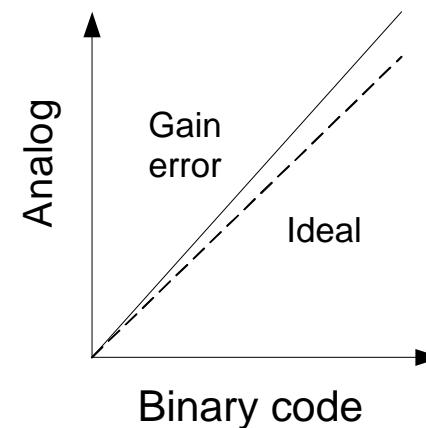
Gain error - deviation of slope from ideal value of 1



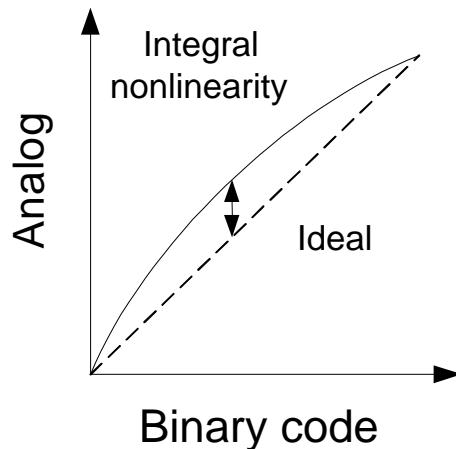
Integral Nonlinearity - maximum deviation from the ideal analog output voltage



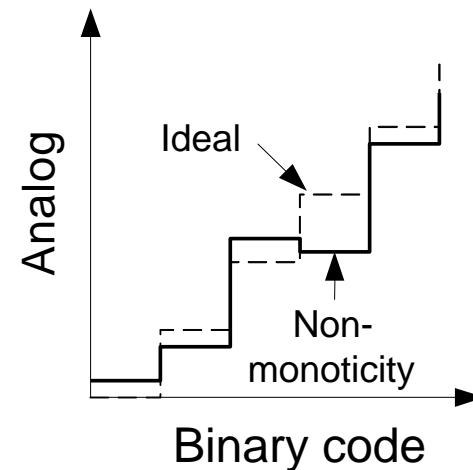Differential nonlinearity - the largest increment in analog output for a 1-bit change




R-2R Ladder DAC Architecture

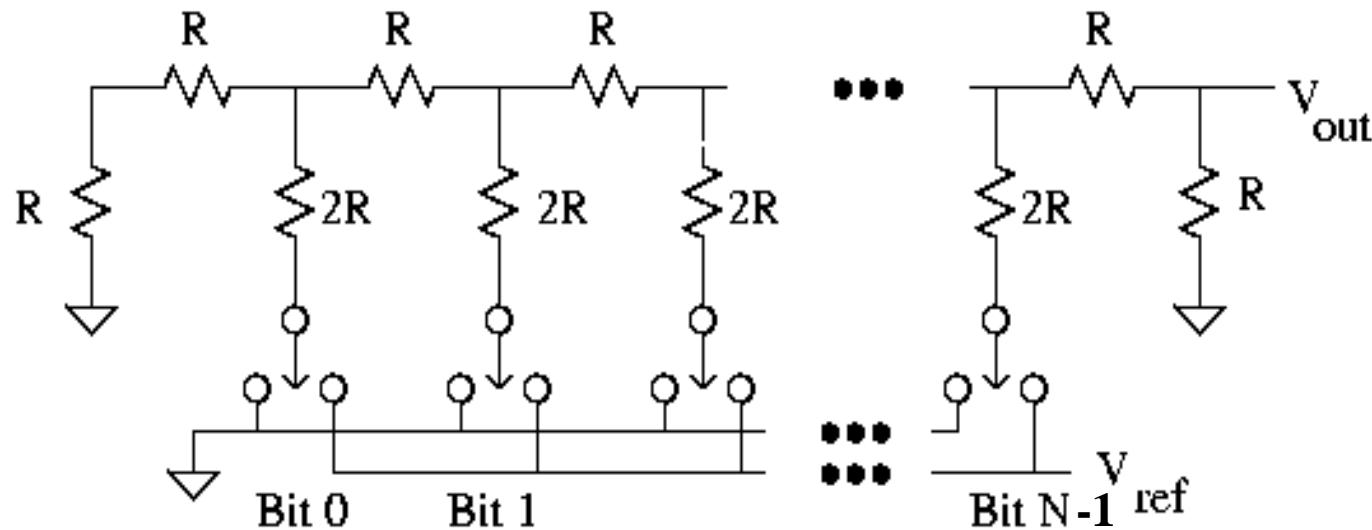

$$V_{out} = \frac{1}{6} V_{ref} [B_7 + \frac{1}{2}B_6 + \frac{1}{4}B_5 + \dots + \frac{1}{128}B_0]$$

- Note that the driving point impedance (resistance) is the same for each cell.
- R-2R Ladder achieves large current division ratios with only two resistor values

DAC (AD 558) Specs - Used in Lab 3

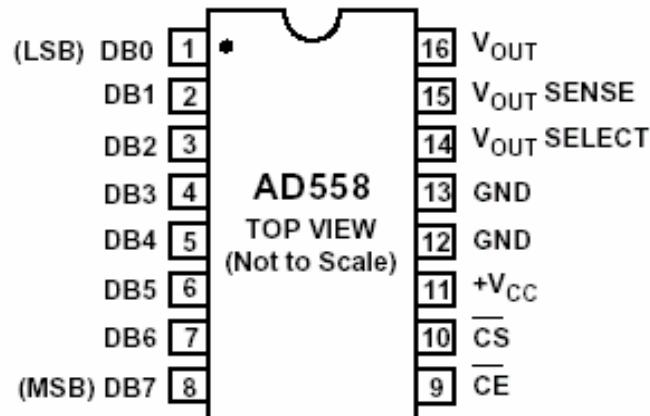

Input Logic Coding

Digital Input Code		Output Voltage		
Binary	Hexadecimal	Decimal	2.56 V Range	10.000 V Range
0000 0000	00	0	0	0
0000 0001	01	1	0.010 V	0.039 V
0000 0010	02	2	0.020 V	0.078 V
0000 1111	0F	15	0.150 V	0.586 V
0001 0000	10	16	0.160 V	0.625 V
0111 1111	7F	127	1.270 V	4.961 V
1000 0000	80	128	1.280 V	5.000 V
1100 0000	C0	192	1.920 V	7.500 V
1111 1111	FF	255	2.55 V	9.961 V

- 8-bit DAC
- Single Supply Operation: 5V to 15V
- Integrates required references (bandgap voltage reference)
- Uses a R-2R resistor ladder
- Settling time 1 μ s
- Programmable output range from 0V to 2.56V or 0V to 10V
- Simple Latch based interface

Chip Architecture and Interface

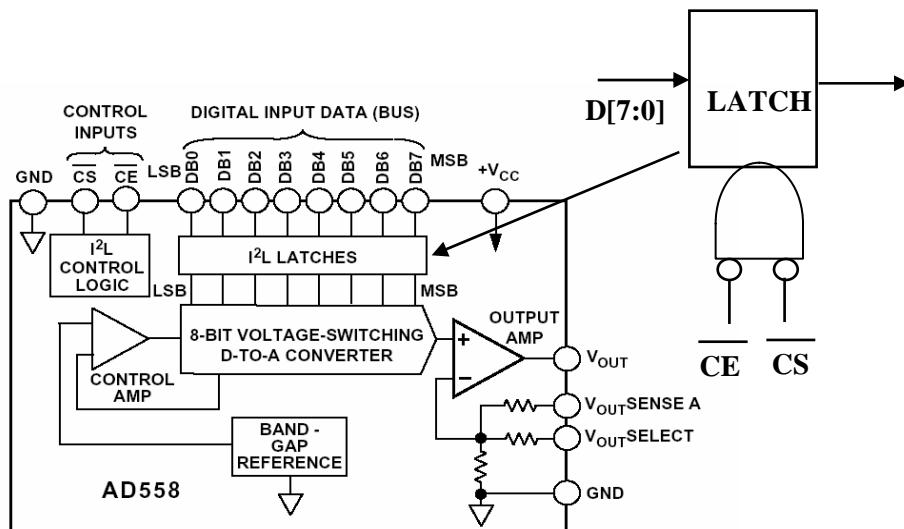



Table I. AD558 Control Logic Truth Table

Input Data	\overline{CE}	\overline{CS}	DAC Data	Latch Condition
0	0	0	0	"Transparent"
1	0	0	1	"Transparent"
0	g	0	0	Latching
1	g	0	1	Latching
0	0	g	0	Latching
1	0	g	1	Latching
X	1	X	Previous Data	Latched
X	X	1	Previous Data	Latched

NOTES

X = Does not matter.

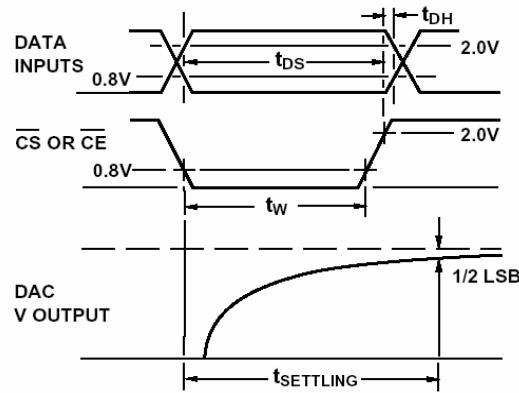g = Logic Threshold at Positive-Going Transition.



t_W = STORAGE PULSE WIDTH = 200ns MIN
 t_{DH} = DATA HOLD TIME = 10ns MIN
 t_{DS} = DATA SETUP TIME = 200ns MIN
 $t_{SETTLING}$ = DAC OUTPUT SETTLING TIME TO $\pm 1/2$ LSB

Outputs are noisy
 while input bits settle,
 so it is best to have inputs
 stable before latching
 the input data


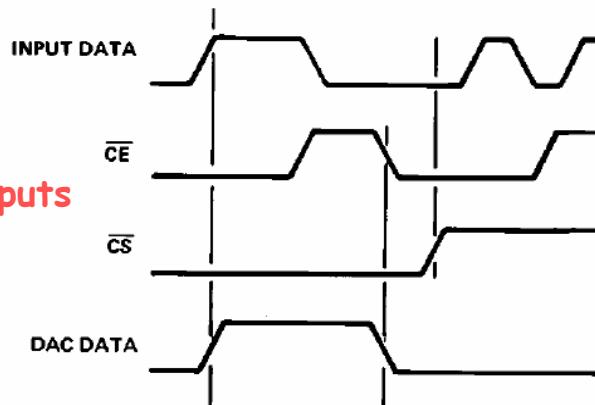


Figure 6. AD558 Control Logic Function

Setting the Voltage Range

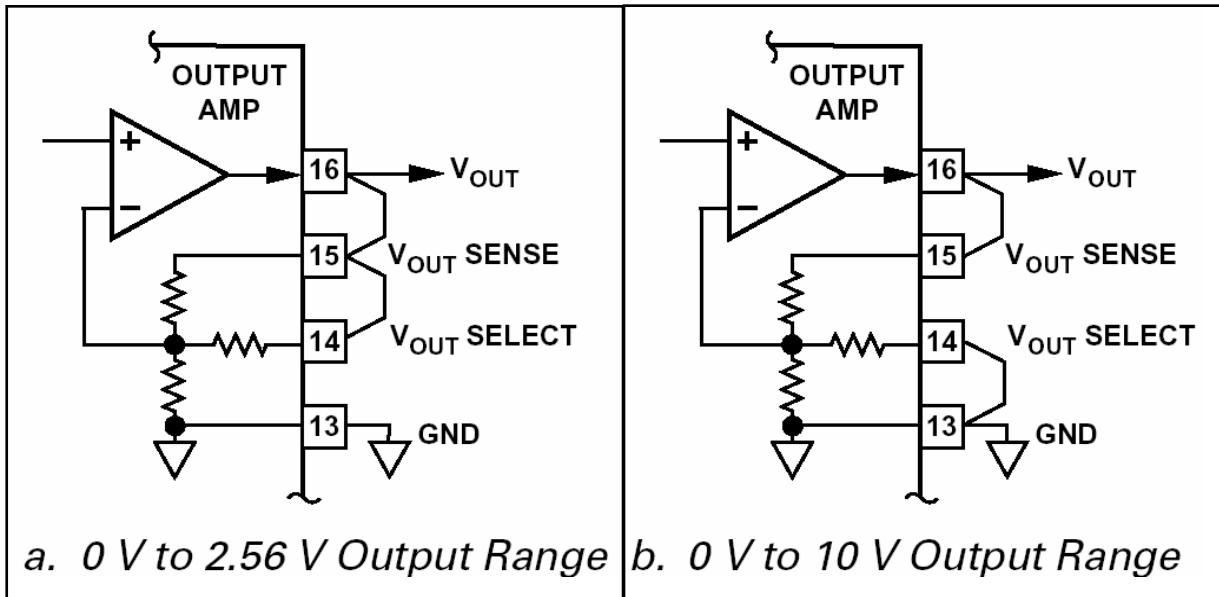

Very similar to a
non-inverting amp


Strap output for
different voltage
ranges

Input Logic Coding


Digital Input Code			Output Voltage	
Binary	Hexadecimal	Decimal	2.56 V Range	10.000 V Range
0000 0000	00	0	0	0
0000 0001	01	1	0.010 V	0.039 V
0000 0010	02	2	0.020 V	0.078 V
0000 1111	0F	15	0.150 V	0.586 V
0001 0000	10	16	0.160 V	0.625 V
0111 1111	7F	127	1.270 V	4.961 V
1000 0000	80	128	1.280 V	5.000 V
1100 0000	C0	192	1.920 V	7.500 V
1111 1111	FF	255	2.55 V	9.961 V

Convert data to
Offset binary

Another Approach: Binary-Weighted DAC

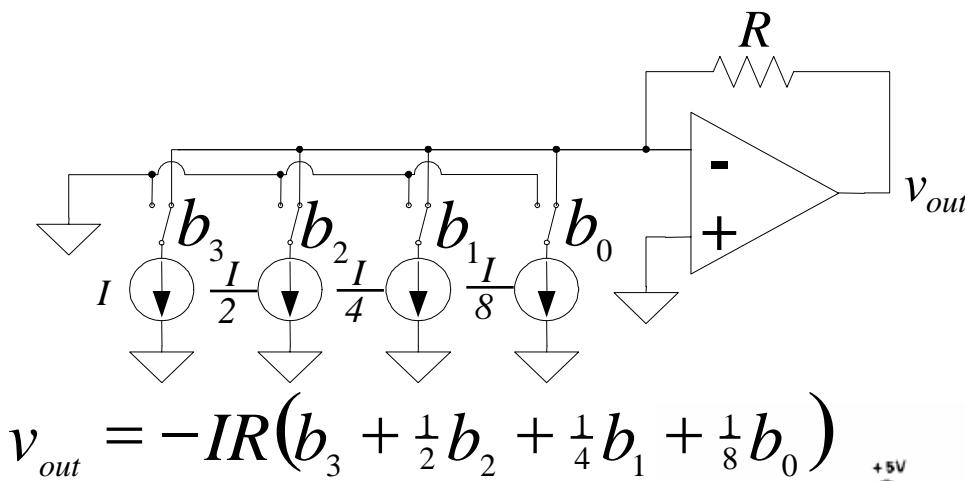


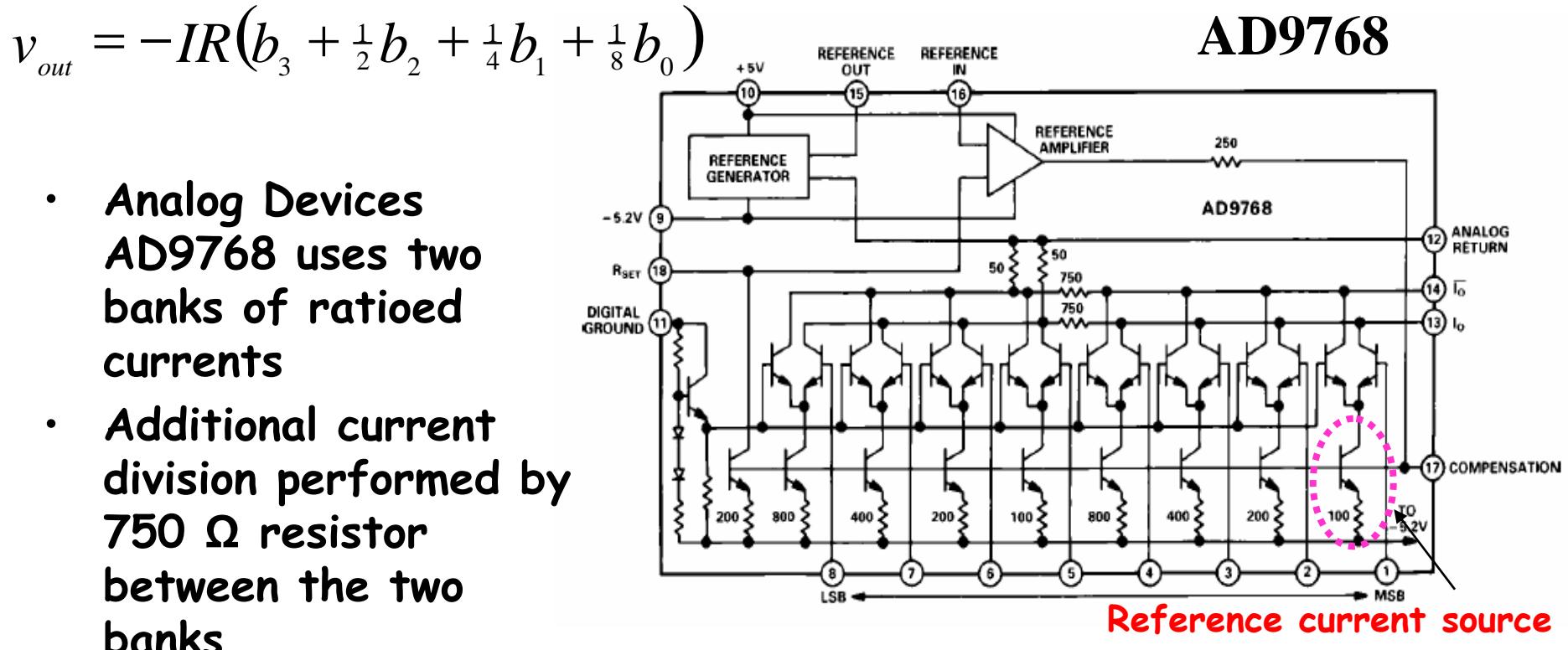- Switch binary-weighted currents
- MSB to LSB current ratio is 2^N




Glitching and Thermometer D/A

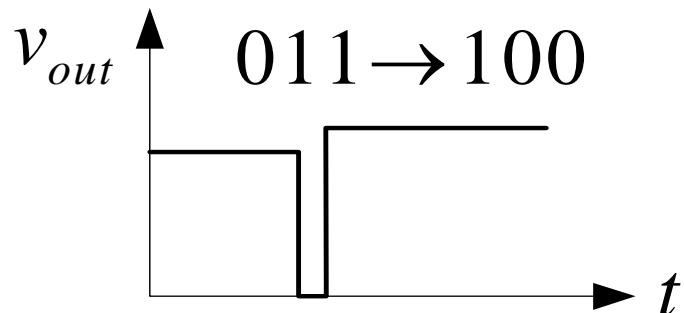- Glitching is caused when switching times in a D/A are not synchronized
- Example: Output changes from 011 to 100 - MSB switch is delayed
- Filtering reduces glitch but increases the D/A settling time
- One solution is a thermometer code D/A - requires $2^N - 1$ switches but no ratioed currents





Binary		Thermometer		
0	0	0	0	0
0	1	0	0	1
1	0	0	1	1
1	1	1	1	1

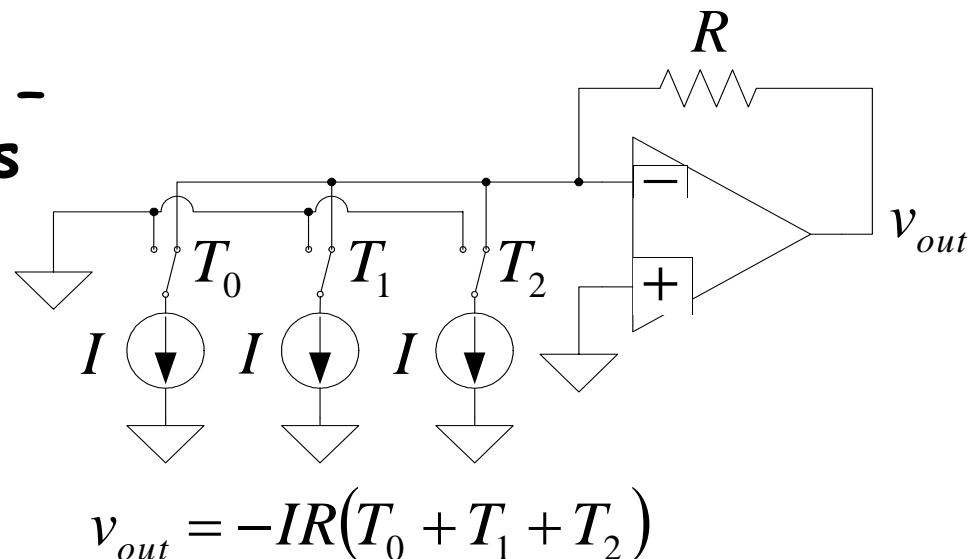


Successive-Approximation A/D

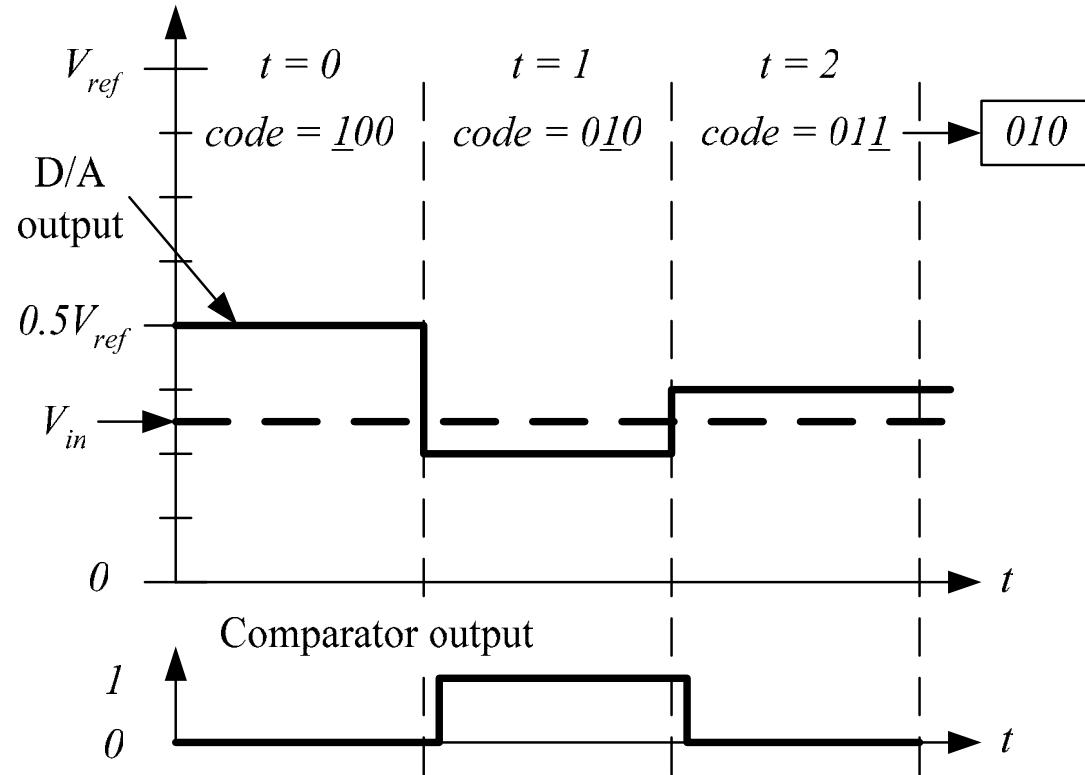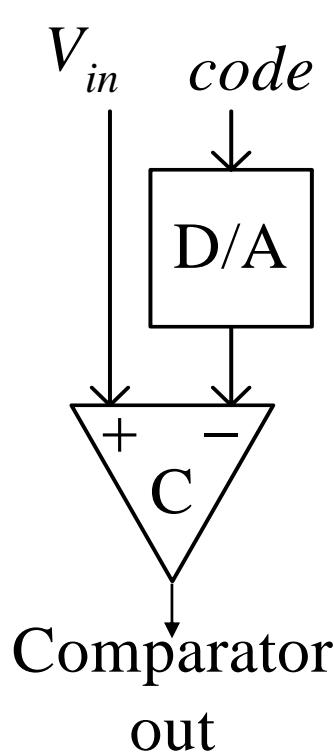- D/A converters are typically compact and easier to design. Why not A/D convert using a D/A converter and a comparator?
- D to A generates analog voltage which is compared to the input voltage
- If D to A voltage > input voltage then set that bit; otherwise, reset that bit
- This type of A to D takes a fixed amount of time proportional to the bit length




Successive-Approximation A/D

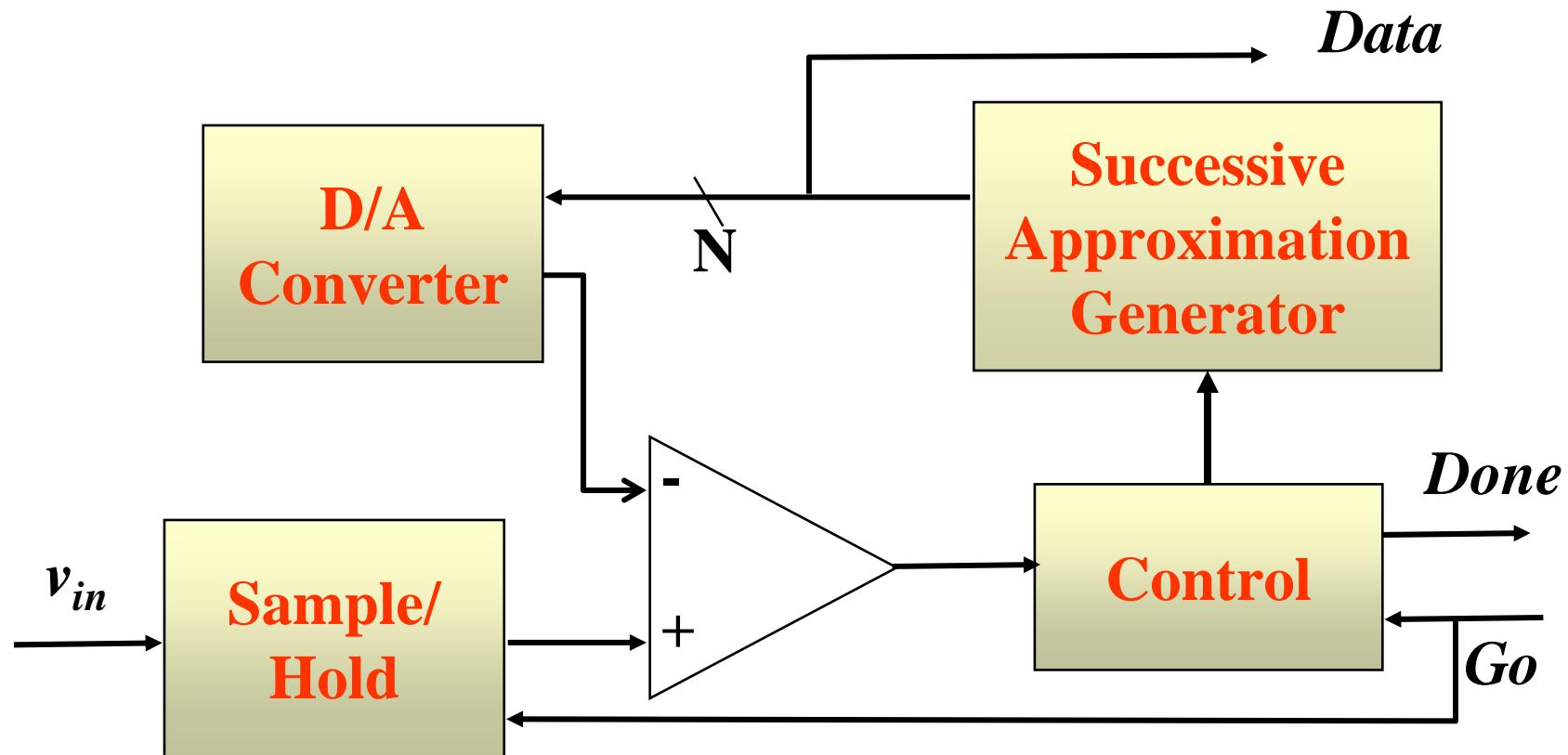

Serial conversion takes a time equal to $N(t_{D/A} + t_{comp})$


Successive-Approximation A/D (AD670) - Used in Lab 3

10μs conversion time

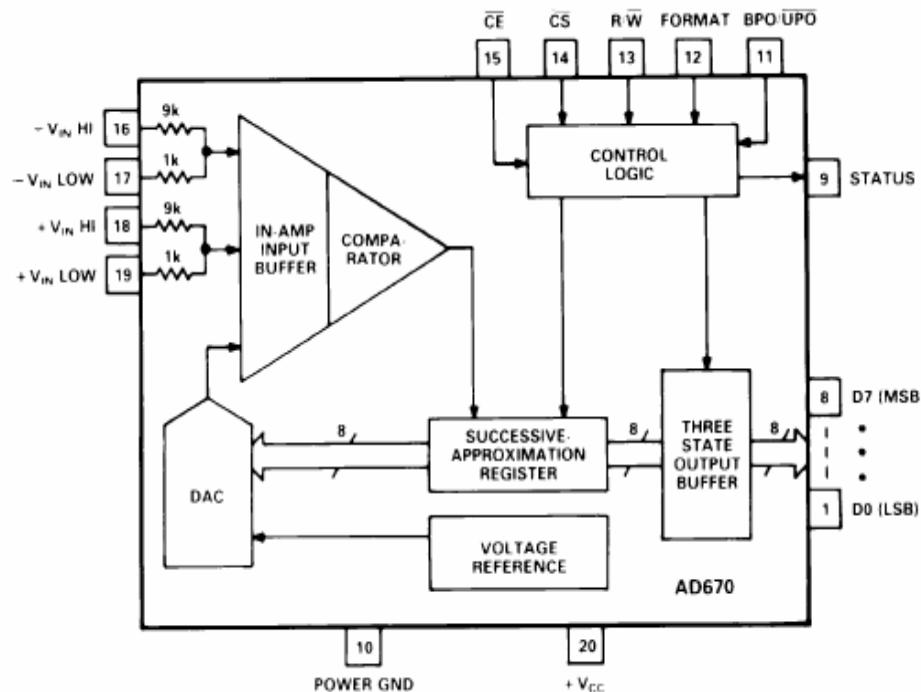


BPO/UPO	FORMAT	INPUT RANGE/ OUTPUT FORMAT
0	0	Unipolar/Straight Binary
1	0	Bipolar/Offset Binary
0	1	Unipolar/2s Complement
1	1	Bipolar/2s Complement

Unipolar (BPO = 0)

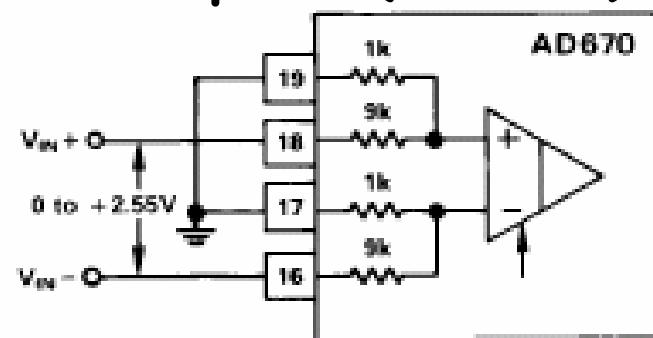

2a. 0 V to 2.55 V (10 mV/LSB)

Bipolar (BPO = 1)

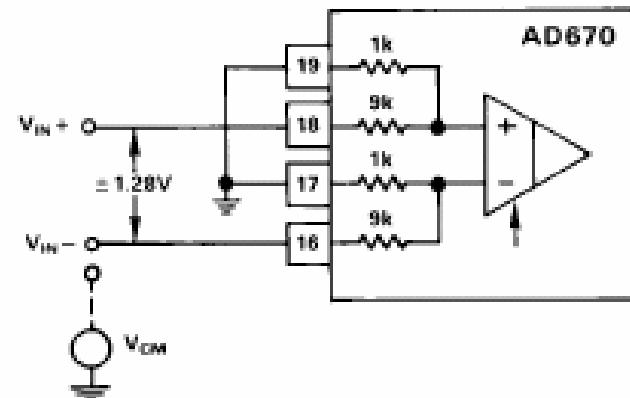

3a. ±1.28 V Range

AD670 operation

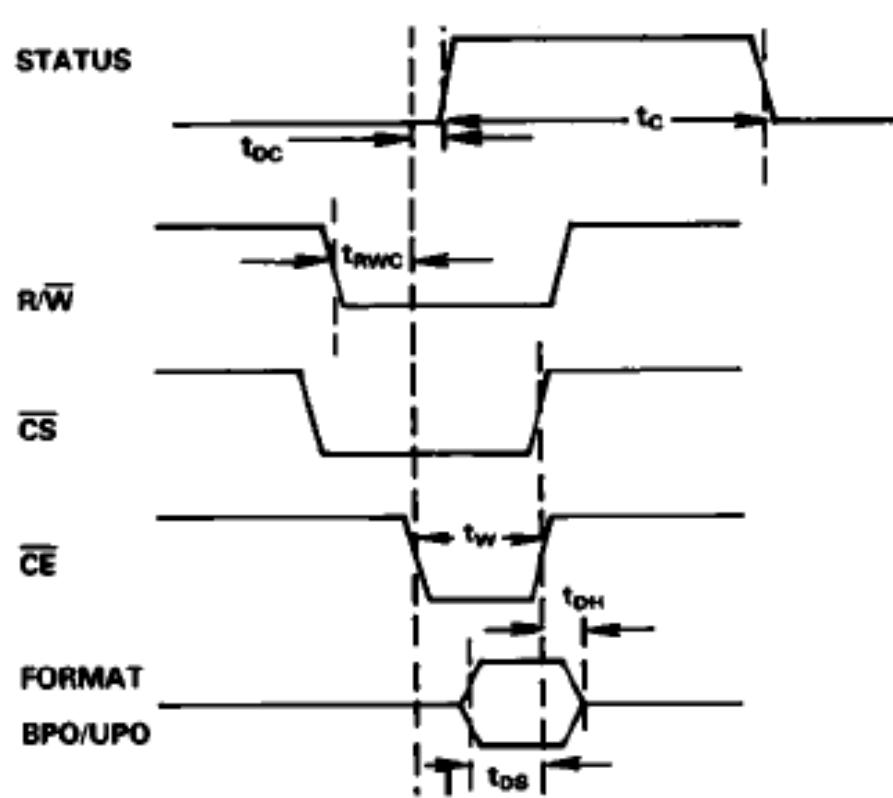


Figure 8. Write/Convert Start Timing


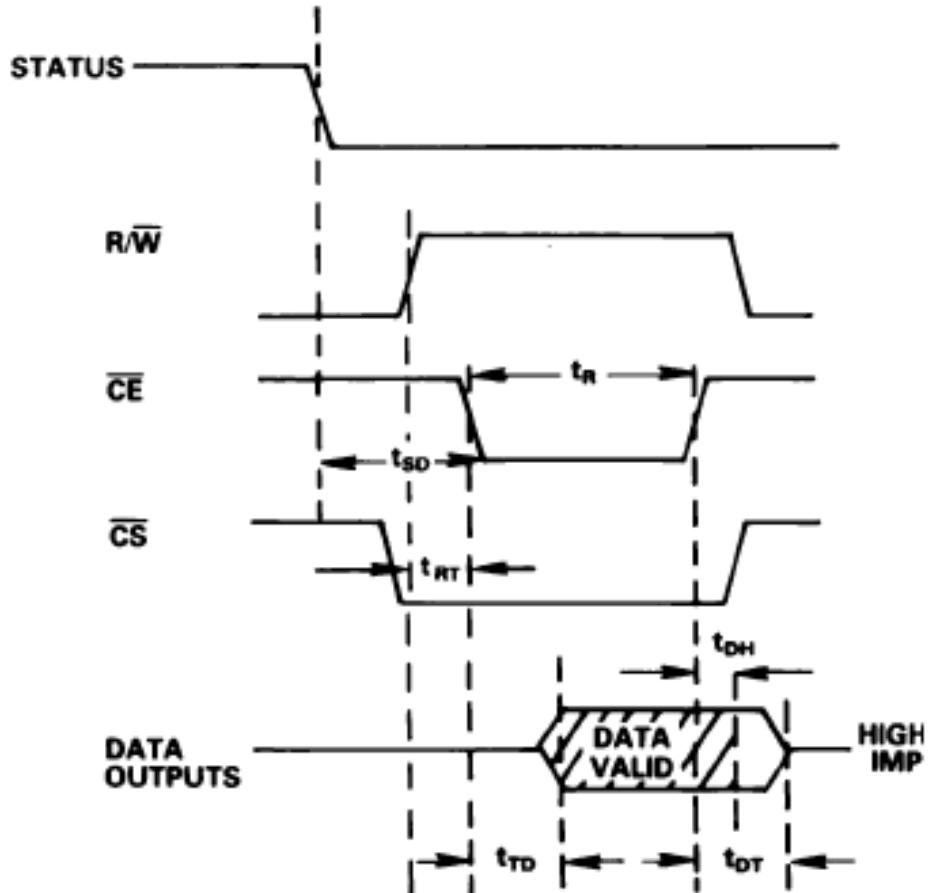


Figure 9. Read Cycle Timing

Simple A/D Interface FSM

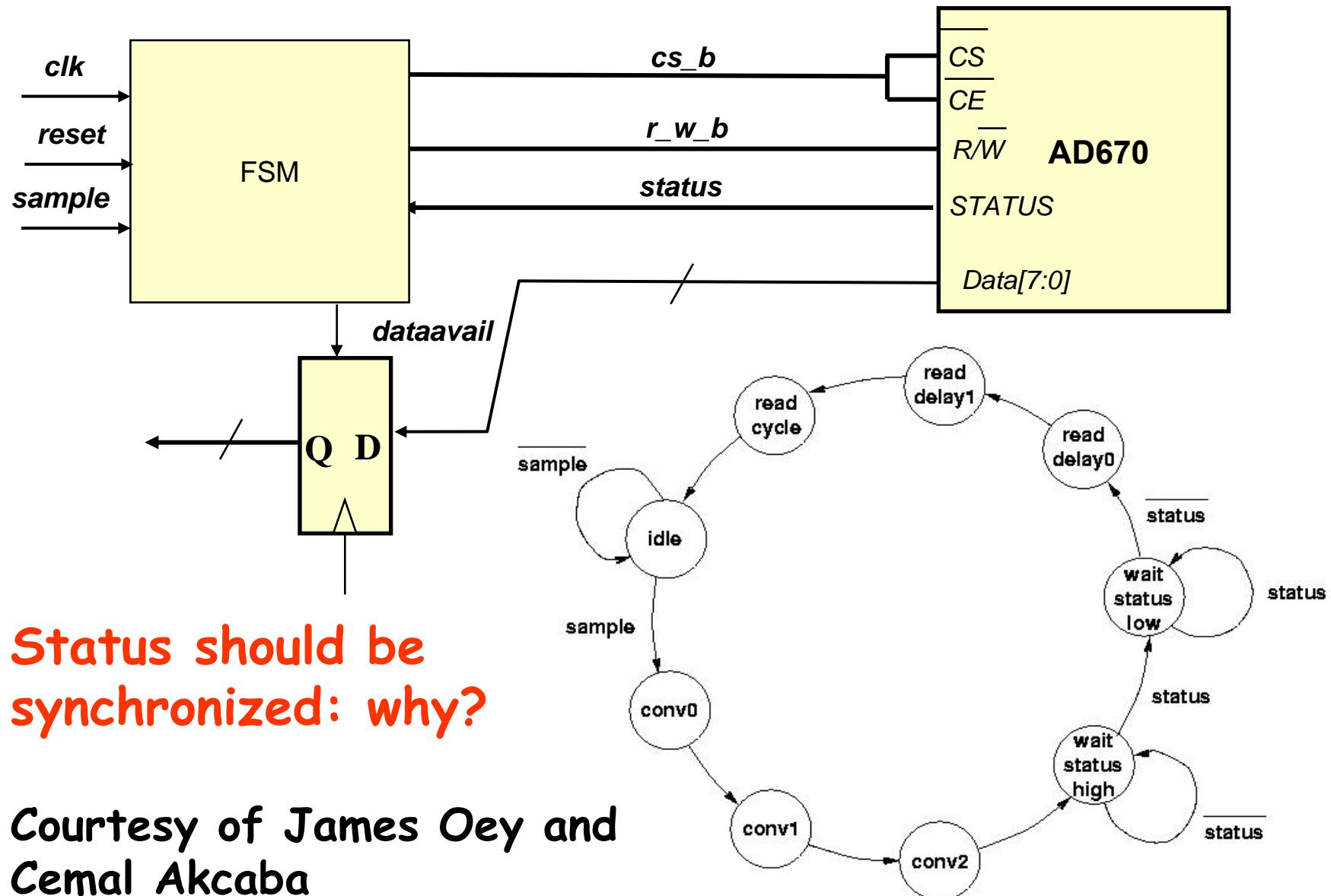

Status should be synchronized: why?

Courtesy of James Oey and
Cemal Akcaba

Example A/D Verilog Interface

```
module AD670 (clk, reset, sample,
dataavail, r_wbar, cs_bar, status, state);

// System Clk
input clk;
// Global Reset signal
// assume it is synchronized
input reset;

// User Interface
input sample;
output dataavail;

// A-D Interface
input status;
reg status_d1, status_d2;
output r_wbar, cs_bar;
output [3:0] state;

// internal state
reg [3:0] state;
reg [3:0] nextstate;
reg r_wbar_int, r_wbar;
reg cs_bar_int, cs_bar;
reg dataavail;
```

1/5

```
// State declarations.
parameter IDLE = 0;
parameter CONV0 = 1;
parameter CONV1 = 2;
parameter CONV2 = 3;
parameter WAITSTATUSHIGH = 4;
parameter WAITSTATUSLOW = 5;
parameter READDELAY0 = 6;
parameter READDELAY1 = 7;
parameter READCYCLE = 8;

always @ (posedge clk or negedge
reset)
begin
    if (!reset) state <=IDLE;
    else state <=nextstate;

    status_d1 <= status;
    status_d2 <= status_d1;

    r_wbar <= r_wbar_int;
    cs_bar <=cs_bar_int;
end
```

2/5

Example A/D Verilog Interface (cont.)

```
always @ (state or status_d2 or sample)
begin
    // defaults
    r_wbar_int = 1; cs_bar_int = 1;
    dataavail = 0;

    case (state)

        IDLE: begin
            if(sample) nextstate = CONV0;
            else nextstate = IDLE;
        end

        CONV0:
        begin
            r_wbar_int = 0;
            cs_bar_int = 0;
            nextstate = CONV1;
        end

        CONV1:
        begin
            r_wbar_int = 0;
            cs_bar_int = 0;
            nextstate = CONV2;
        end
    endcase
end
```

3/5

```
CONV2:
begin
    r_wbar_int = 0;
    cs_bar_int = 0;
    nextstate = WAITSTATUSHIGH;

end

WAITSTATUSHIGH:
begin
    cs_bar_int = 0;
    if (status_d2)
        nextstate = WAITSTATUSLOW;
    else nextstate = WAITSTATUSHIGH;
end

WAITSTATUSLOW:
begin
    cs_bar_int = 0;
    if (!status_d2)
        nextstate = READDELAY0;
    else nextstate = WAITSTATUSLOW;
end
```

4/5

Example A/D Verilog Interface (cont.)


```
READDELAY0:  
    begin  
        cs_bar_int = 0;  
        nextstate = READDELAY1;  
    end  
  
READDELAY1:  
    begin  
        cs_bar_int = 0;  
        nextstate = READCYCLE;  
    end  
  
READCYCLE:  
    begin  
        cs_bar_int = 0;  
        dataavail = 1;  
        nextstate = IDLE;  
    end  
  
    default: nextstate = IDLE;  
endcase // case(state)  
end // always  
endmodule // adcInterface
```

5/5


Simulation

On reset, present state goes to 0

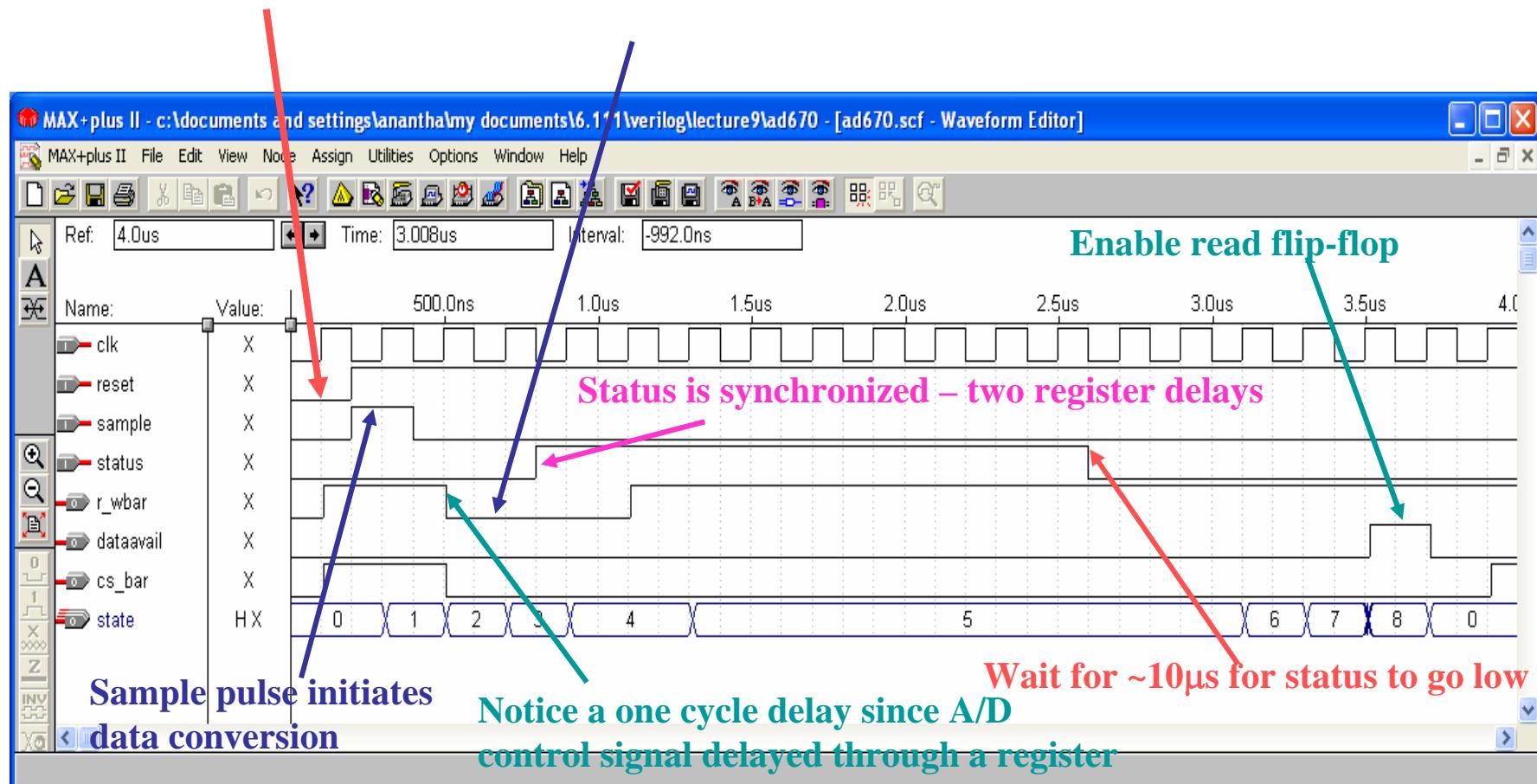r_w_b must stay low for at least 3 cycles (@ 100ns period) –
Don't need 3 cycles if you use the 1.8432MHz clock





Flash A/D Converter

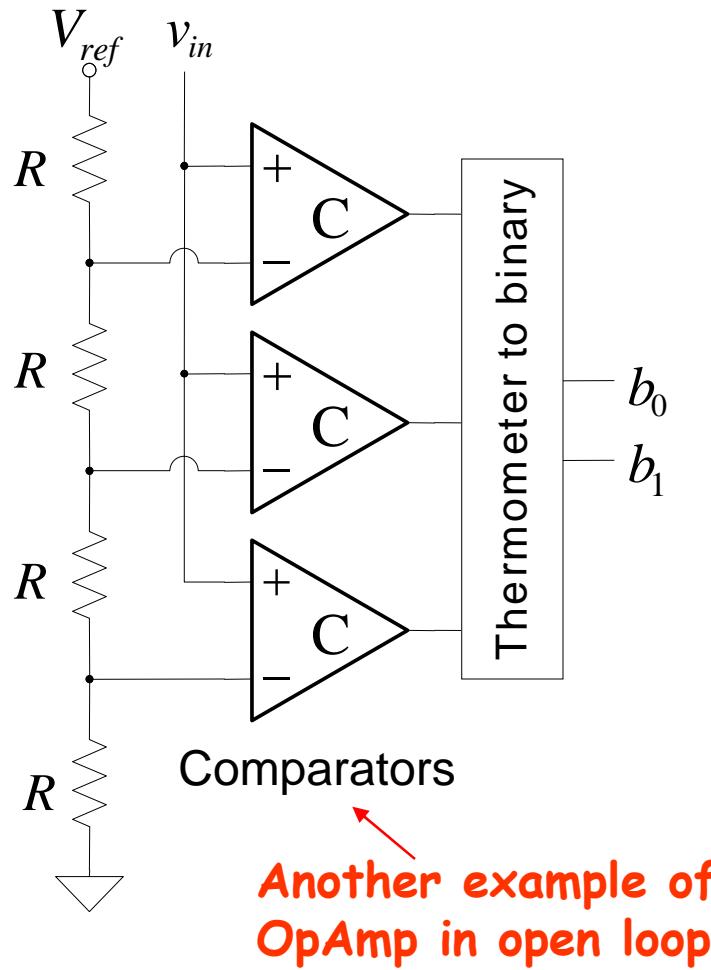

- Brute-force A/D conversion
- Simultaneously compare the analog value with every possible reference value
- Fastest method of A/D conversion
- Size scales exponentially with precision (requires 2^N comparators)

AD 775 - Flash Data Converter

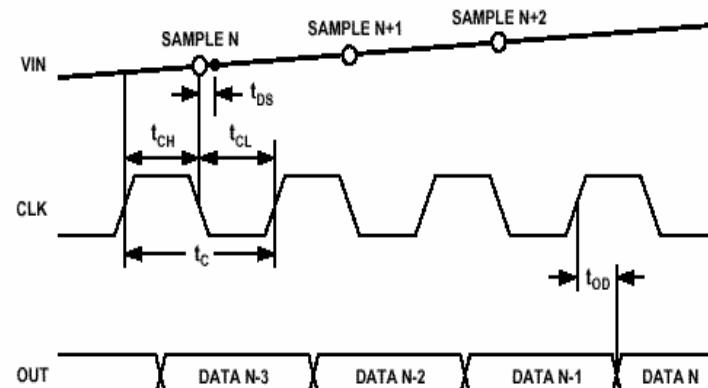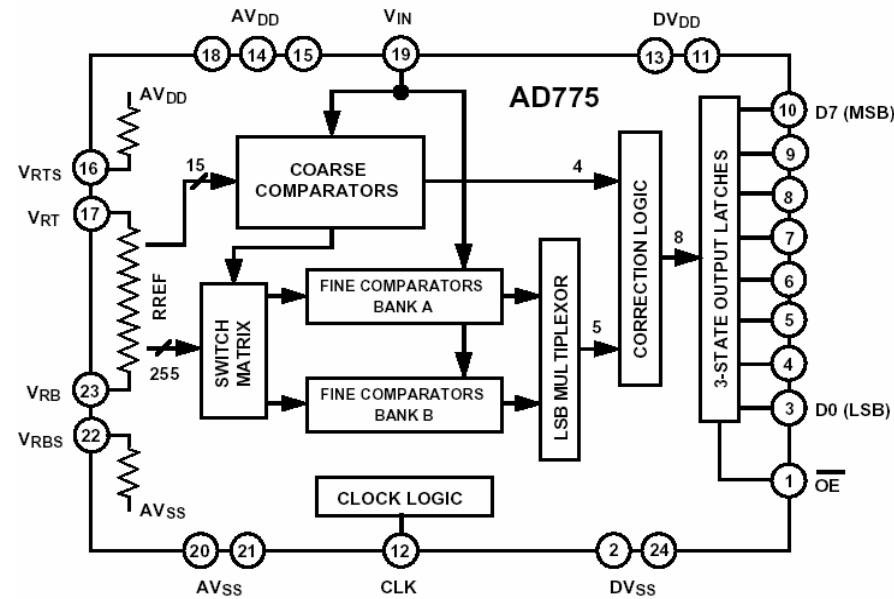


TIMING SPECIFICATIONS


	Symbol	Min	Typ	Max	Units
Maximum Conversion Rate		20	35		MHz
Clock Period	t_c	50			ns
Clock High	t_{CH}	25			ns
Clock Low	t_{CL}	25			ns
Output Delay	t_{OD}		18	30	ns
Pipeline Delay (Latency)				2.5	Clock Cycles
Sampling Delay	t_{DS}		4		ns
Aperture Jitter			30		ps

High Performance Converters: Use Pipelining and Parallelism!

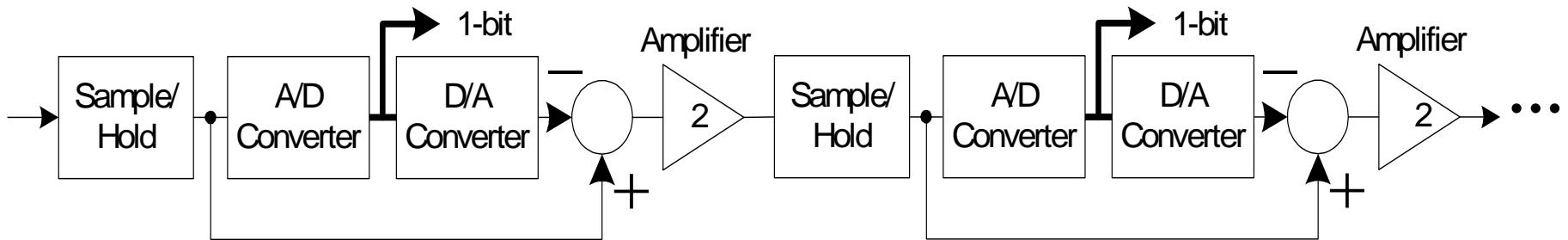Pipelining (used in video rate, RF basestations, etc.)



Parallelism (use many slower A/D's in parallel
to build very high speed A/D converters)

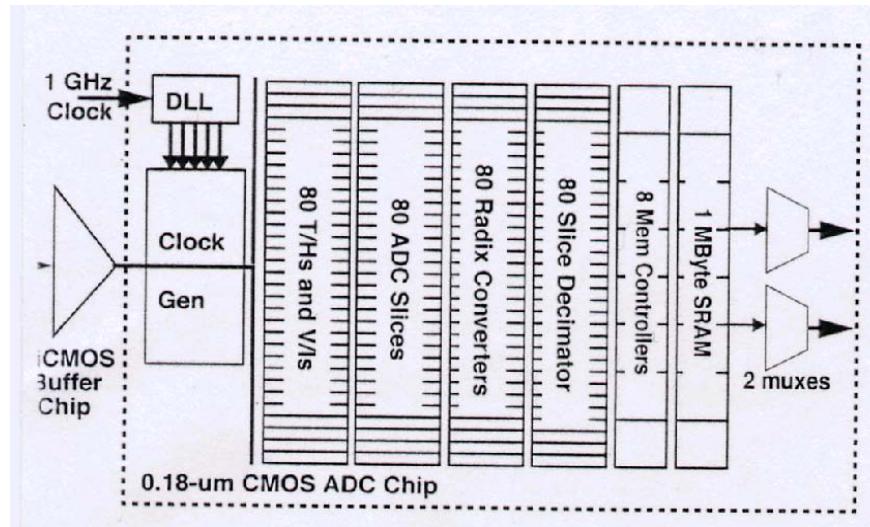

[ISSCC 2003],
Poulton et. al.

20Gsample/sec,
8-bit ADC
from Agilent Labs

Summary of Analog Blocks

- Analog blocks are integral components of any system. Need data converters (analog to digital and digital to analog), analog processing (OpAmps circuits, switched capacitors filters, etc.), power converters (e.g., DC-DC conversion), etc.
- We looked at example interfaces for A/D and D/A converters
 - Make sure you register critical signals (enables, R/W, etc.)
- Analog design incorporate digital principles
 - Glitch free operation using coding
 - Parallelism and Pipelining!
 - More advanced concepts such as calibration