
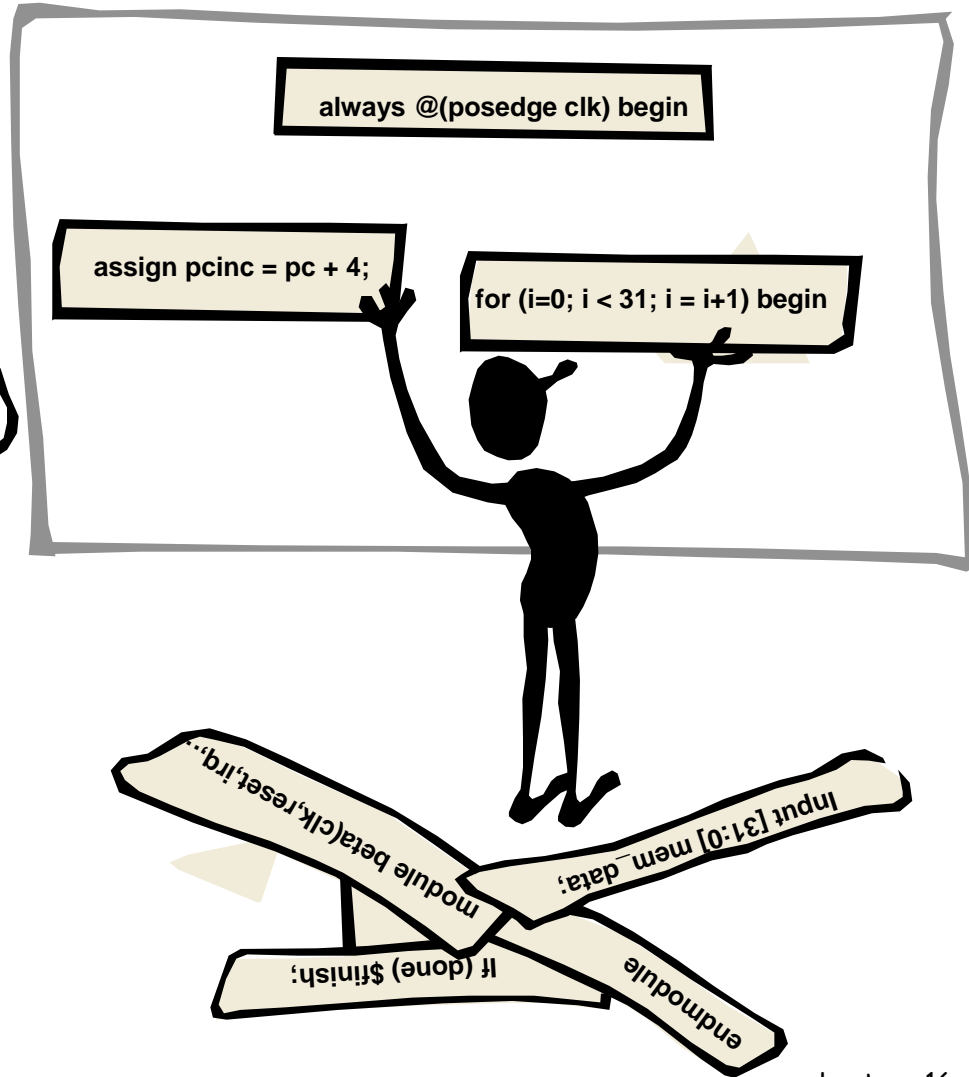



Architecture → Verilog

An Extended Example

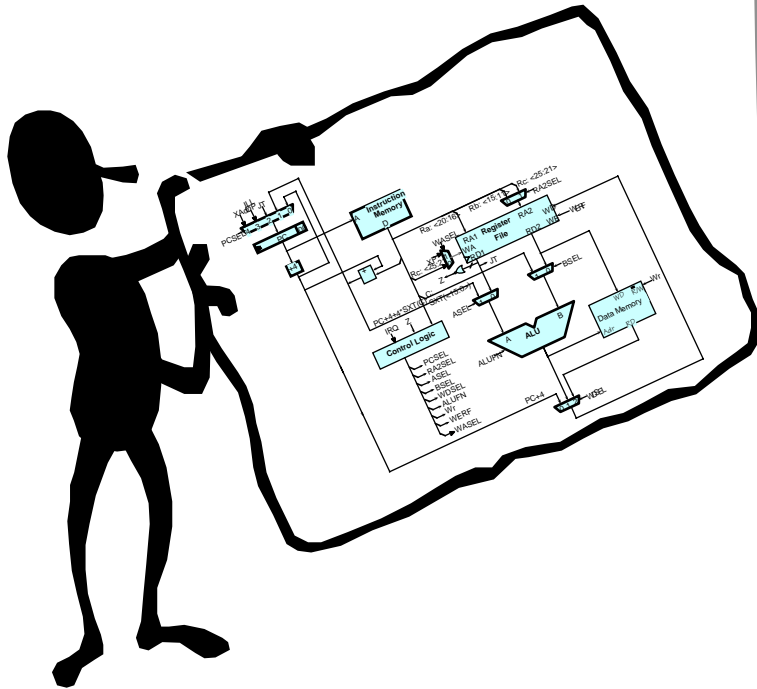

Reprise: Why use an HDL?

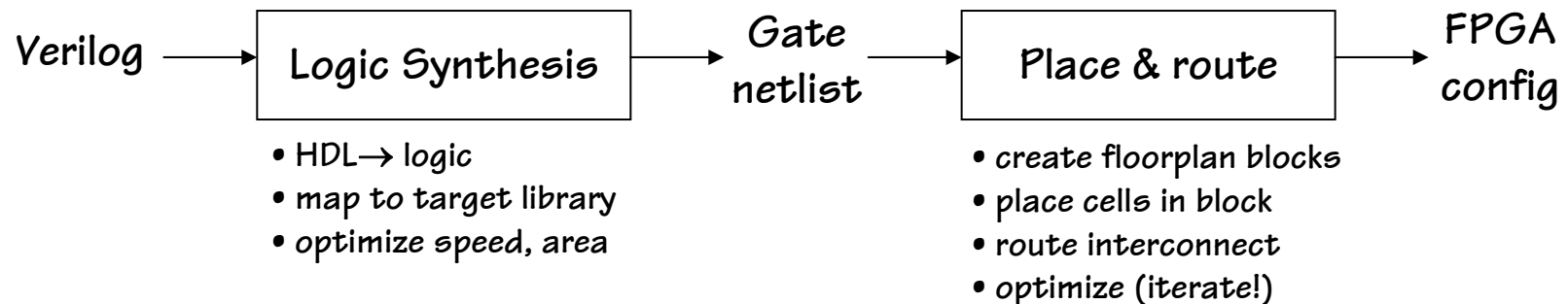- **Want an executable functional specification**
 - Document exact behavior of all the modules and their interfaces
 - Executable models can be tested & refined until they do what you want
- **HDL description is first step in a mostly automated process to build an implementation directly from the behavioral model**



Helping the Tools*

In an ideal world it shouldn't matter how you write the Verilog – optimization in the CAD tools will find the *best solution*. But the world is not ideal (yet...)

- Tools work best on smaller problems
 - Need to partition real problem into pieces for you and the tools (it's hard to think about 1M gates at one time). Decompose large problems into smaller problems and then connect the solutions
 - Hierarchy in Verilog ↔ partitions in physical layout
- Tools use your code as a starting point.
 - Your structure isn't completely eliminated (this is good...)
 - Little optimization will be done between top-level blocks
- Structure of the problem is often important
 - Finding a “good” way to think about the problem is key

Like optimizing compilers for C, tools are good for local optimizations but don't expect them to rewrite your code and change your algorithm. With practice you'll learn what works and what doesn't...

*adapted from a Stanford EE271 lecture by Mark Horowitz

Choosing the right style...

- **Structural Verilog**
 - Use for hierarchy (instantiating other modules)
 - Floorplanning tools often require that modules which include structural verilog not include other styles. In other words the leafs of the hierarchy are dataflow/behavioral modules, all other modules are pure structural verilog.
 - **Dataflow Verilog:** `assign target = expression`
 - Use for (most) combinational logic
 - Avoids problems with activation list omissions
 - **Behavioral Verilog:** `always @(...) begin ... end`
 - Use to model state elements (e.g., registers)
 - Sometimes useful for combinational logic expressed using `for` or `case` statements
 - Simulates much faster than dataflow statements since no waveforms are produced for signals internal to behavioral block. Here's where you can make the tradeoff between simulation speed and debugability.
- These two styles are often mixed in a single module*
-

= vs. <= inside begin ... end

```
module main;  
  reg a,b,clk;
```

```
  initial begin  
    clk = 0; a = 0; b = 1;  
    #10 clk = 1;  
    #10 $display("a=%d b=%d\n",a,b);  
    $finish;  
  end  
endmodule
```

A

```
always @(posedge clk) begin  
  a = b; // blocking assignment  
  b = a; // execute sequentially  
end
```

B

```
always @(posedge clk) begin  
  a <= b; // non-blocking assignment  
  b <= a; // eval all RHSs first  
end
```

C

```
always @(posedge clk) a = b;  
always @(posedge clk) b = a;
```

D

```
always @(posedge clk) a <= b;  
always @(posedge clk) b <= a;
```


E

```
always @(posedge clk) begin  
  a <= b;  
  b = a; // urk! Be consistent!  
end
```


Rule: always change state using <= (e.g., inside always @(posedge clk)...)

Example: the Beta!

Is this 6.004?????

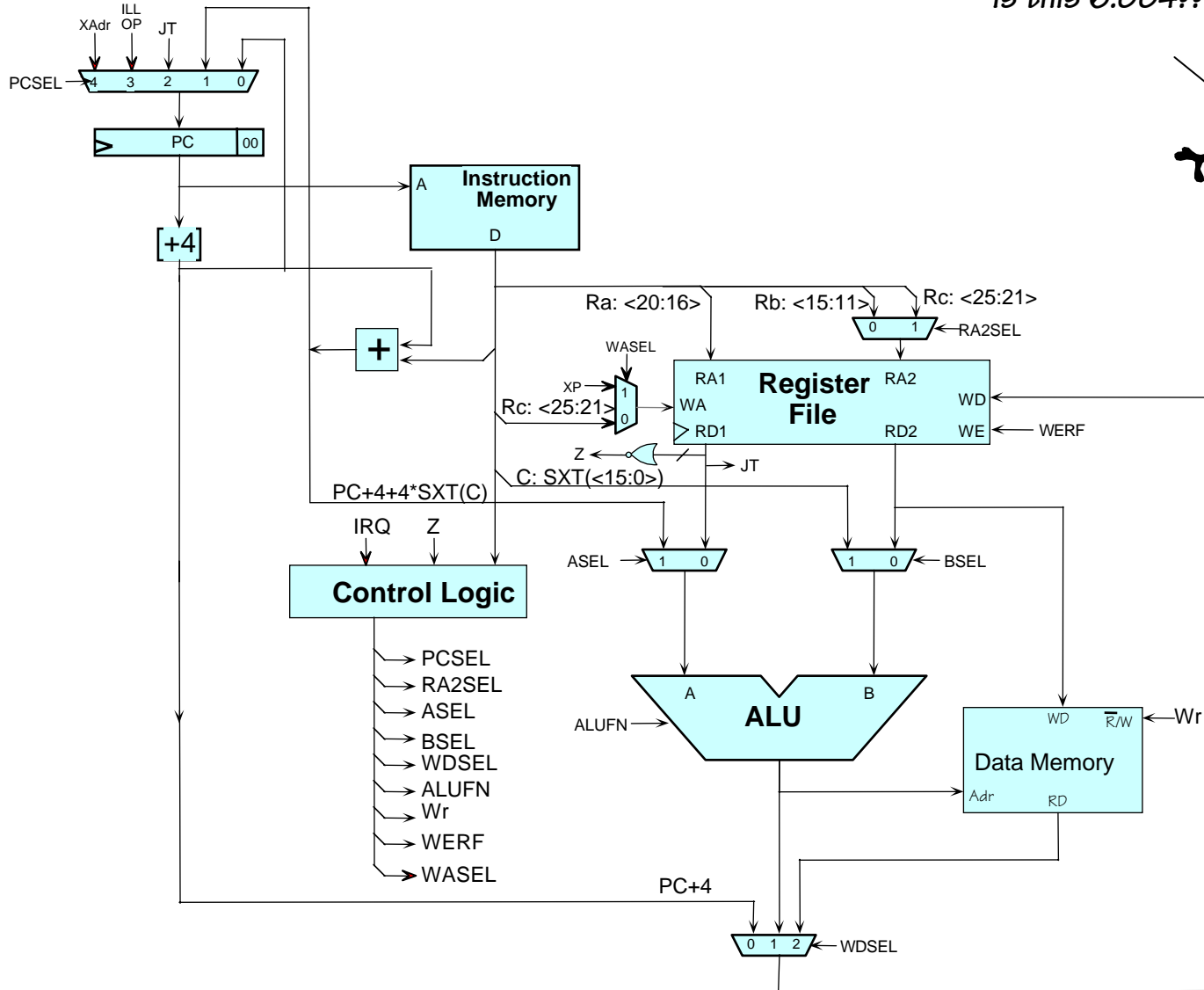


Beta Instructions - I

 

OP(Ra,Rb,Rc): $\text{Reg}[Rc] \leftarrow \text{Reg}[Ra] \text{ op } \text{Reg}[Rb]$

Opcodes:

 ADD (plus), SUB (minus), MUL (multiply), DIV (divided by),
AND (bitwise and), OR (bitwise or), XOR (bitwise exclusive or)
CMPEQ (equal), CMLT (less than), CMPLE (less than or equal) [result = 1 if true, 0 if false]
SHL (left shift), SHR (right shift w/o sign extension), SRA (right shift w/ sign extension)




OPC(Ra,literal,Rc): $\text{Reg}[Rc] \leftarrow \text{Reg}[Ra] \text{ op } \text{SEXT}(\text{literal})$

Opcodes:

ADDC (plus), SUBC (minus), MULC (multiply), DIVC (divided by)
ANDC (bitwise and), ORC (bitwise or), XORC (bitwise exclusive or)
CMPEQC (equal), CMLTC (less than), CMPLEC (less than or equal) [result = 1 if true, 0 if false]
SHLC (left shift), SHRC (right shift w/o sign extension), SRAC (right shift w/ sign extension)

Beta Instructions - II

 

LD(Ra,literal,Rc): $\text{Reg}[\text{Rc}] \leftarrow \text{Mem}[\text{Reg}[\text{Ra}] + \text{SEXT}(\text{literal})]$

ST(Rc,literal,Ra): $\text{Mem}[\text{Reg}[\text{Ra}] + \text{SEXT}(\text{literal})] \leftarrow \text{Reg}[\text{Rc}]$

JMP(Ra,Rc): $\text{Reg}[\text{Rc}] \leftarrow \text{PC} + 4; \text{PC} \leftarrow \text{Reg}[\text{Ra}]$

BEQ/BF(Ra,label,Rc): $\text{Reg}[\text{Rc}] \leftarrow \text{PC} + 4;$
if $\text{Reg}[\text{Ra}] = 0$ then $\text{PC} \leftarrow \text{PC} + 4 + 4 * \text{SEXT}(\text{literal})$

BNE/BT(Ra,label,Rc): $\text{Reg}[\text{Rc}] \leftarrow \text{PC} + 4;$
if $\text{Reg}[\text{Ra}] \neq 0$ then $\text{PC} \leftarrow \text{PC} + 4 + 4 * \text{SEXT}(\text{literal})$


LDR(label,Rc): $\text{Reg}[\text{Rc}] \leftarrow \text{Mem}[\text{PC} + 4 + 4 * \text{SEXT}(\text{literal})]$

Beta Control Logic


	<i>OP</i>	<i>OPC</i>	<i>LD</i>	<i>ST</i>	<i>JMP</i>	<i>BEQ</i>	<i>BNE</i>	<i>LDR</i>	<i>Illop</i>	<i>trap</i>
<i>ALUFN</i>	F(op)	F(op)	"+"	"+"	—	—	—	"A"	—	—
<i>WERF</i>	1	1	1	0	1	1	1	1	1	1
<i>BSEL</i>	0	1	1	1	—	—	—	—	—	—
<i>WDSEL</i>	1	1	2	—	0	0	0	2	0	0
<i>WR</i>	0	0	0	1	0	0	0	0	0	0
<i>RA2SEL</i>	0	—	—	1	—	—	—	—	—	—
<i>PCSEL</i>	0	0	0	0	2	Z ? 1 : 0	Z ? 0 : 1	0	3	4
<i>ASEL</i>	0	0	0	0	—	—	—	1	—	—
<i>WASEL</i>	0	0	0	—	0	0	0	0	1	1

Beta2 (see attached sheet)

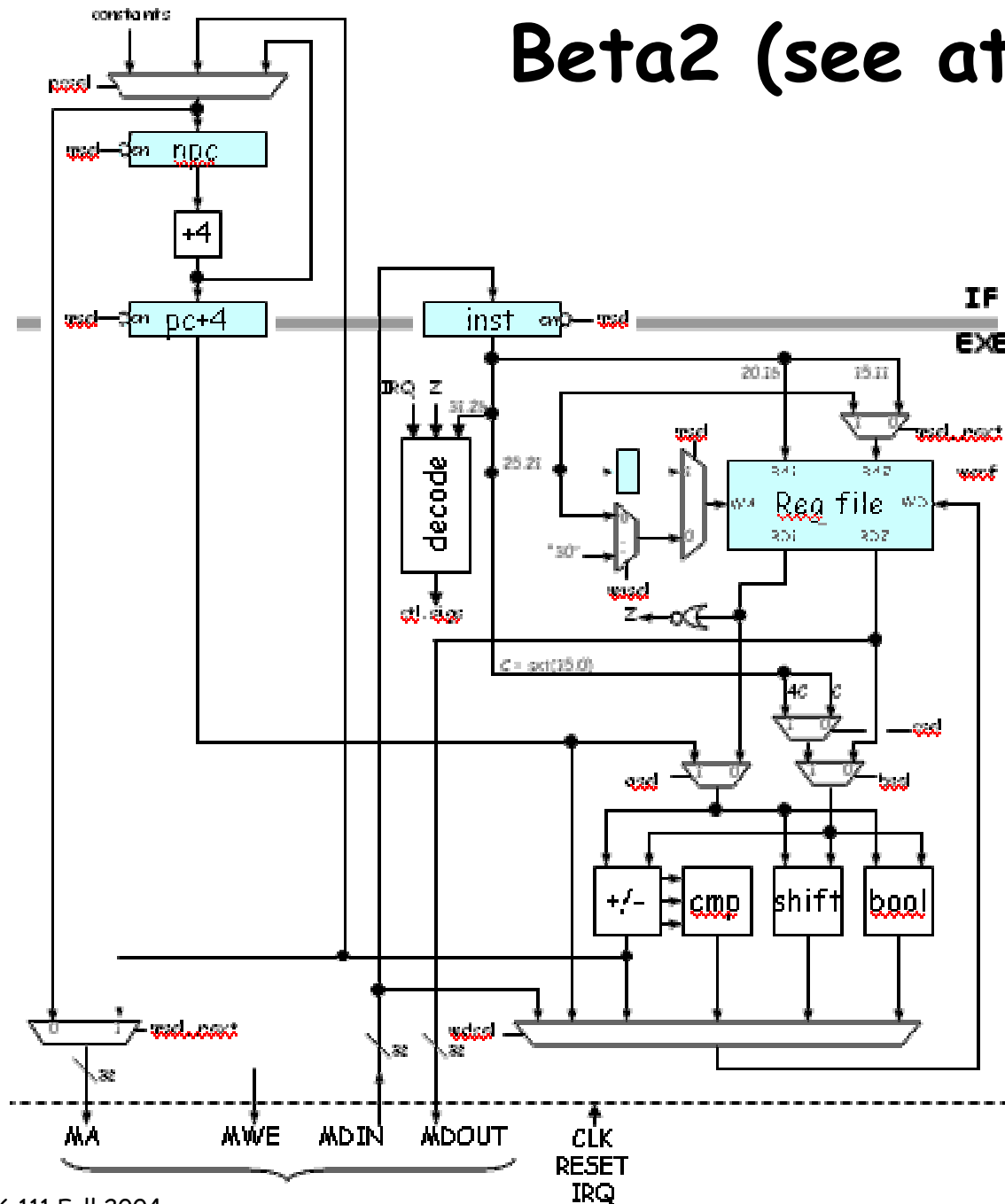- 2-stage pipeline, 1 annuled branch delay slot
- Memory ops (LD, LDR, ST) take two cycle in EXE stage: addr computed in 1st cycle, memory access made in 2nd
- Branch and LDR address arithmetic performed in ALU
- JMP routed thru ALU
- Single memory port shared by inst. fetch and memory access



Xilinx Synchronous Block Memory

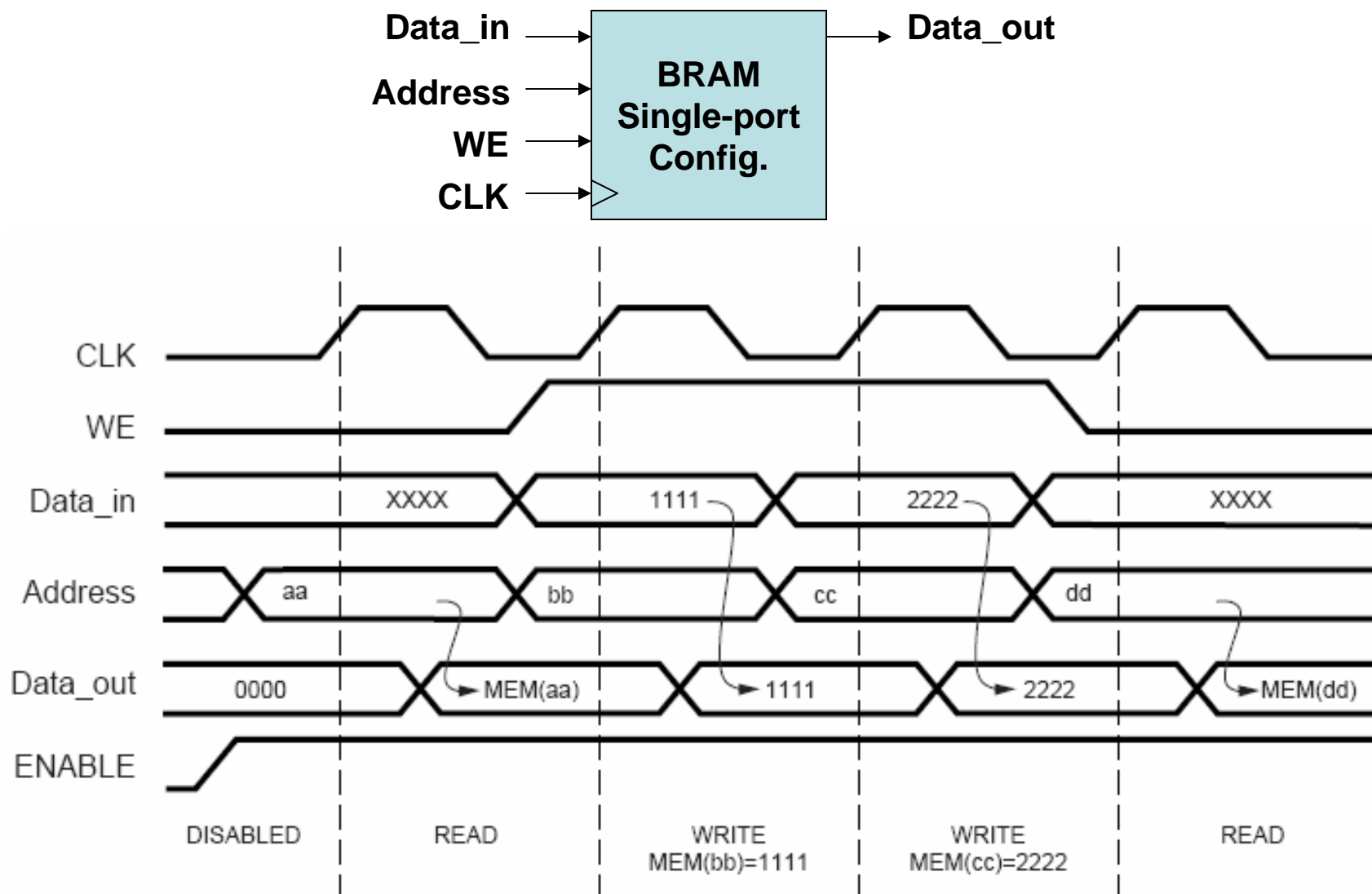


```

100: LD(R31,6004,R2)
104: ADDC(R2,47,R2)
108: ST(R2,44,R31)
10C: XORC(R2,-1,R2)
110: ...
...
6004: 123

```


Instruction Pipeline Diagram

 

* Stalled in pipeline

beta2.v
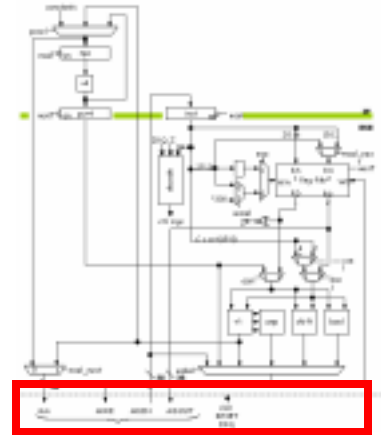
```
module beta2(clk,reset,irq,ma,mdin,mdout,mwe);  
  input  clk,reset,irq;  
  output [31:0] ma,mdout;  
  input  [31:0] mdin;  
  output mwe;
```



```
  // beta2 registers
```

```
  reg [31:0] regfile[31:0];
```

```
  reg [31:0] npc,pc_inc,inst;
```

```
  reg [4:0] rc_save; // needed for second cycle on LD,LDR
```

```
  // internal buses
```

```
  wire [31:0] rd1,rd2,wd,a,b,xb,c,addsub,cmp,shift,boole;
```

```
  // control signals
```

```
  wire wasel,werf,z,asel,bsel,csel;
```


```
  wire addsub_op,cmp_lt,cmp_eq,shift_op
```

```
  wire shift_sxt,boole_and,boole_or;
```

```
  ...
```

```
endmodule
```

PC Logic

 


```
// pc
wire [31:0] npc_inc, npc_next;

assign npc_inc = npc + 4;
assign npc_next = reset ? 32'h80000000 :
    msel ? npc :
    branch ? {npc[31]&addsub[31],
              addsub[30:2], 2'b00} :
    trap ? 32'h80000004 :
    interrupt ? 32'h80000008 :
    npc_inc;

always @ (posedge clk) begin
    npc <= npc_next;    // stall on msel handled above
    if (!msel) pc_inc <= npc_inc;
end
```


Instruction Register & Decode

 

```
// instruction reg
always @ (posedge clk) if (!msel) inst <= mdin;
```

```
// control logic
decode ctl(.clk(clk),.reset(reset),.irq(irq & !npc[31]),
          .z(z),.opcode(inst[31:26]),
          .asel(asel),.bssel(bssel),.csel(csel),
          .wasel(wasel),.werf(werf),.msel(msel),
          .msel_next(msel_next),.mwe(mwe),
          .addsub_op(addsub_op),.cmp_lt(cmp_lt),
          .cmp_eq(cmp_eq),
          .shift_op(shift_op),.shift_sxt(shift_sxt),
          .boole_and(boole_and),.boole_or(boole_or),
          .wd_addsub(wd_addsub),.wd_cmp(wd_cmp),
          .wd_shift(wd_shift),.wd_boole(wd_boole),
          .branch(branch),.trap(trap),
          .interrupt(interrupt));
```

Register File

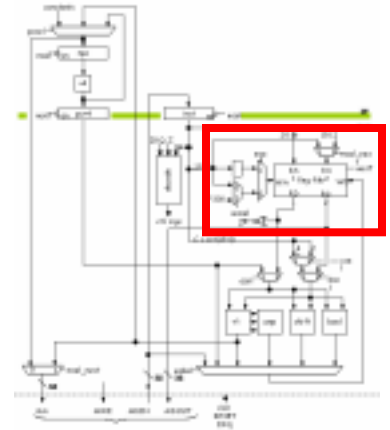

```
// register file
wire [4:0] ra1,ra2,wa;
always @ (posedge clk)
    if (!msel) rc_save <= inst[25:21];

assign ra1 = inst[20:16];
assign ra2 = msel_next ? inst[25:21] : inst[15:11];
assign wa = msel ? rc_save :
            wasel ? 5'd30 : inst[25:21];
assign rd1 = (ra1 == 31) ? 0 : regfile[ra1];
assign rd2 = (ra2 == 31) ? 0 : regfile[ra2];
always @ (posedge clk)
    if (werf) regfile[wa] <= wd;

assign z = ~| rd1;    // used in BEQ/BNE instructions
```


ALU


```
// alu
assign a = asel ? pc_inc : rd1;
assign b = bsel ? c : rd2;
assign c = csel ? {{14{inst[15]}},inst[15:0],2'b00} :
                {{16{inst[15]}},inst[15:0]};

wire addsub_n,addsub_v,addsub_z;
assign xb = {32{addsub_op}} ^ b;
assign addsub = a + xb + addsub_op;
assign addsub_n = addsub[31];
assign addsub_v = (addsub[31] & ~a[31] & ~xb[31]) |
                  (~addsub[31] & a[31] & xb[31]);
assign addsub_z = ~| addsub;


assign cmp[31:1] = 0;
assign cmp[0] = (cmp_lt & (addsub_n ^ addsub_v)) |
                (cmp_eq & addsub_z);

wire [31:0] shift_right;
shift_right sr(shift_sxt,a,b[4:0],shift_right);
assign shift = shift_op ? shift_right : a << b[4:0];

assign boole = boole_and ? (a & b) :
                boole_or ? (a | b) : a ^ b;
```

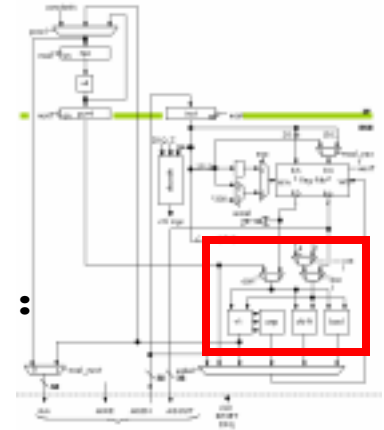

Result Mux, Address Mux

 

```
// result mux, listed in order of speed (slowest first)
```

```
assign wd = msel ? mdin :  
    wd_cmp ? cmp :  
    wd_addsub ? addsub :  
    wd_shift ? shift :  
    wd_boole ? boole :  
    pc_inc;
```


```
// assume synchronous external memory
```

```
assign ma = msel_next ? addsub : npc_next;  
assign mdout = rd2;
```

Control Logic (decode.v)

```
always @ (opcode or z or annul or irq or reset)
begin
    // initial assignments for all control signals
    asel = 1'hx; bsel = 1'hx; csel = 1'hx;
    addsub_op = 1'hx; shift_op = 1'hx; shift_sxt = 1'hx;
    cmp_lt = 1'hx; cmp_eq = 1'hx;
    boole_and = 1'hx; boole_or = 1'hx;
    wasel = 0; mem_next = 0;
    wd_addsub = 0; wd_cmp = 0; wd_shift = 0; wd_boole = 0;
    branch = 0; trap = 0; interrupt = 0;

     if (irq && !reset && !annul) begin
        interrupt = 1;
        wasel = 1;
    end else casez (opcode)
        6'b011000: begin // LD
            asel = 0; bsel = 1; csel = 0;
            addsub_op = 0;
            mem_next = 1;
        end
    end
```



...

Control Logic (cont'd.)

...



```
6'b1?1100: begin // SHL, SHLC
    asel = 0; bsel = opcode[4]; csel = 0;
    shift_op = 0;
    wd_shift = 1;
end
6'b1?1101: begin // SHR, SHRC
    asel = 0; bsel = opcode[4]; csel = 0;
    shift_op = 1; shift_sxt = 0;
    wd_shift = 1;
end
6'b1?1110: begin // SRA, SRAC
    asel = 0; bsel = opcode[4]; csel = 0;
    shift_op = 1; shift_sxt = 1;
    wd_shift = 1;
end
default: begin // illegal opcode
    trap = !annul; wasel = 1;
end

endcase
end // always @ (opcode or ...)
```

Xilinx Spartan-3 Starter Board


TOP

BOTTOM

 
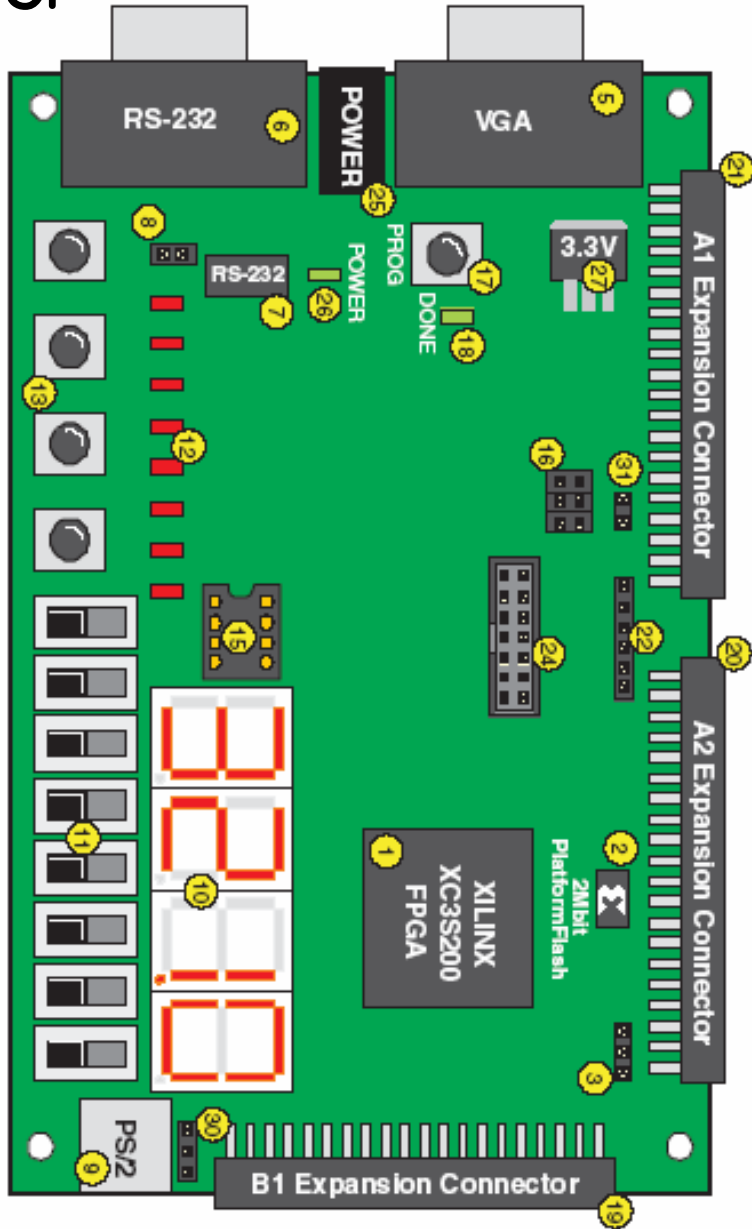


Source: Xilinx Spartan-3 Starter Kit Board User Guide

Xilinx XC3S200 FPGA

 


Beta2 Floorplan

  

BETA2


An implementation of the 6.004 Beta processor with a 2-stage pipeline (IF, EXE) and one annulled branch delay slot. Memory operations (LD/LDR/ST) require two cycles in the EXE stage: the address is computed in the first cycle, the memory access made in the second (during which $m_{sel}=1$ and the IF stage is stalled). Other instructions take a single EXE cycle. Other changes:

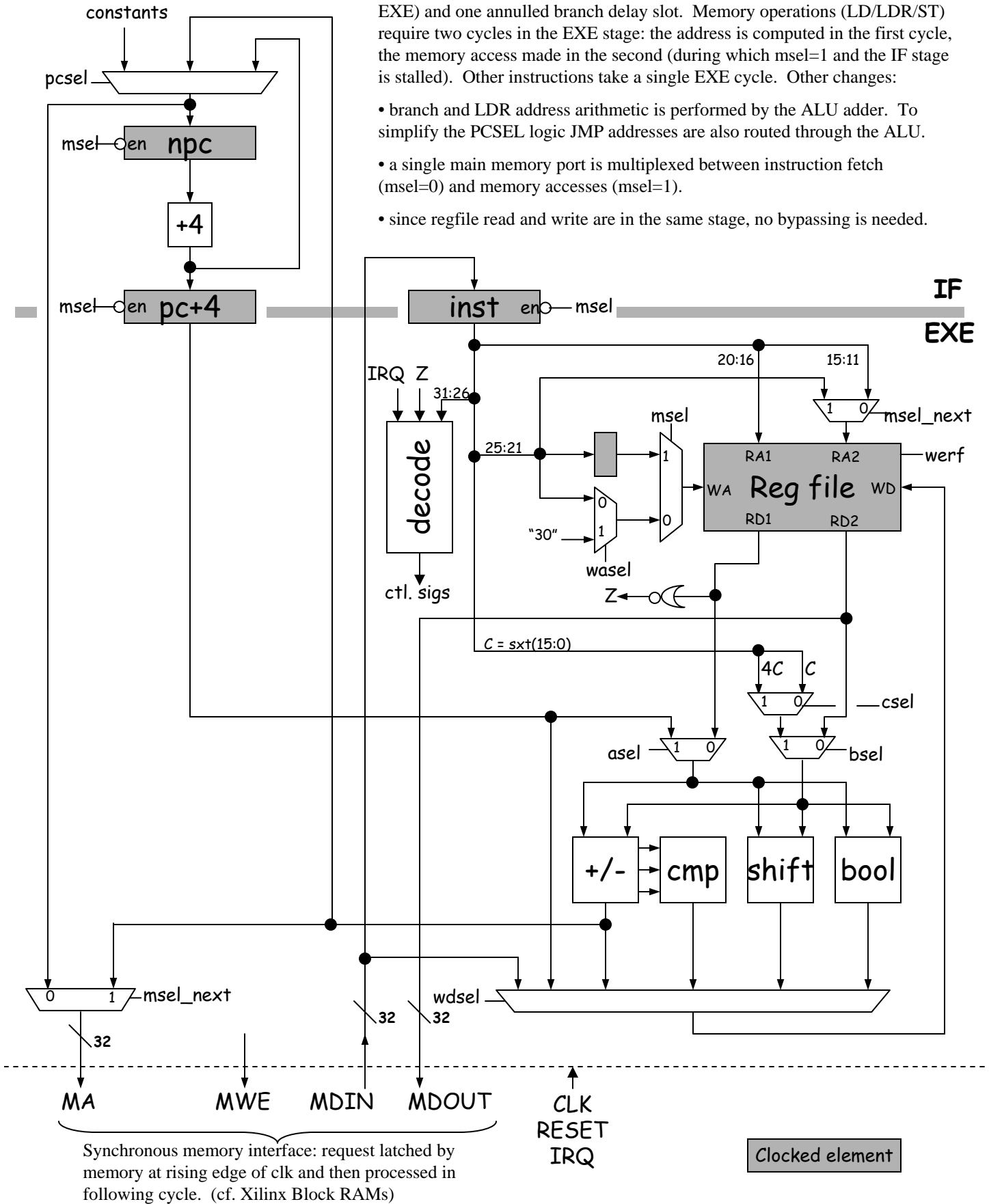- branch and LDR address arithmetic is performed by the ALU adder. To simplify the PCSEL logic JMP addresses are also routed through the ALU.
- a single main memory port is multiplexed between instruction fetch ($m_{sel}=0$) and memory accesses ($m_{sel}=1$).
- since regfile read and write are in the same stage, no bypassing is needed.



Summary of β Instruction Formats


Operate Class:

 

OP(Ra,Rb,Rc): $\text{Reg}[Rc] \leftarrow \text{Reg}[Ra] \text{ op } \text{Reg}[Rb]$

Opcodes: **ADD** (plus), **SUB** (minus), **MUL** (multiply), **DIV** (divided by)
AND (bitwise and), **OR** (bitwise or), **XOR** (bitwise exclusive or)
CMPEQ (equal), **CMPLT** (less than), **CMPLT** (less than or equal) [result = 1 if true, 0 if false]
SHL (left shift), **SHR** (right shift w/o sign extension), **SRA** (right shift w/ sign extension)


Register	Symbol	Usage
R31	R31	Always zero
R30	XP	Exception pointer
R29	SP	Stack pointer
R28	LP	Linkage pointer
R27	BP	Base of frame pointer

 

OPC(Ra,literal,Rc): $\text{Reg}[Rc] \leftarrow \text{Reg}[Ra] \text{ op } \text{SEXT}(\text{literal})$

Opcodes: **ADDC** (plus), **SUBC** (minus), **MULC** (multiply), **DIVC** (divided by)
ANDC (bitwise and), **ORC** (bitwise or), **XORC** (bitwise exclusive or)
CMPEQC (equal), **CMPLTC** (less than), **CMPLTC** (less than or equal) [result = 1 if true, 0 if false]
SHLC (left shift), **SHRC** (right shift w/o sign extension), **SRAC** (right shift w/ sign extension)

Other:

 

LD(Ra,literal,Rc): $\text{Reg}[Rc] \leftarrow \text{Mem}[\text{Reg}[Ra] + \text{SEXT}(\text{literal})]$
ST(Rc,literal,Ra): $\text{Mem}[\text{Reg}[Ra] + \text{SEXT}(\text{literal})] \leftarrow \text{Reg}[Rc]$
JMP(Ra,Rc): $\text{Reg}[Rc] \leftarrow \text{PC} + 4; \text{PC} \leftarrow \text{Reg}[Ra]$
BEQ/BF(Ra,label,Rc): $\text{Reg}[Rc] \leftarrow \text{PC} + 4; \text{if } \text{Reg}[Ra] = 0 \text{ then } \text{PC} \leftarrow \text{PC} + 4 + 4 * \text{SEXT}(\text{literal})$
BNE/BT(Ra,label,Rc): $\text{Reg}[Rc] \leftarrow \text{PC} + 4; \text{if } \text{Reg}[Ra] \neq 0 \text{ then } \text{PC} \leftarrow \text{PC} + 4 + 4 * \text{SEXT}(\text{literal})$
LDR(label,Rc): $\text{Reg}[Rc] \leftarrow \text{Mem}[\text{PC} + 4 + 4 * \text{SEXT}(\text{literal})]$

Opcode Table: (*optional opcodes)

2:0	000	001	010	011	100	101	110	111
5:3	000	001	010	011	100	101	110	111
000								
001								
010								
011	LD	ST		JMP		BEQ	BNE	LDR
100	ADD	SUB	MUL*	DIV*	CMPEQ	CMPLT	CMPLT	CMPLT
101	AND	OR	XOR		SHL	SHR	SRA	
110	ADDC	SUBC	MULC*	DIVC*	CMPEQC	CMPLTC	CMPLTC	CMPLTC
111	ANDC	ORC	XORC		SHLC	SHRC	SRAC	