 


# 6.111 Lecture 6



Today:

1. Blocking vs. non-blocking assignments
2. Single clock synchronous circuits
3. Finite State Machines




# I. Blocking vs. Nonblocking Assignments

Conceptual need for **two kinds of assignment** (in always blocks):

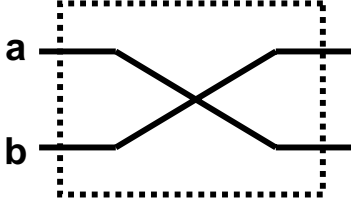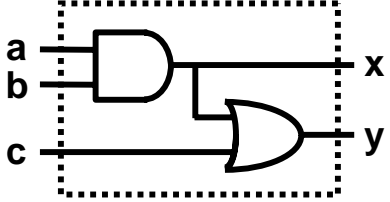		
<p><b>Blocking:</b> Evaluation and assignment are immediate</p>	<del> <math display="block">\begin{array}{l} a = b \\ b = a \end{array}</math> </del>	$\begin{array}{l} x = a \ \& \ b \\ y = x \   \ c \end{array}$
<p><b>Non-Blocking:</b> Assignment is postponed until all r.h.s. evaluations are done</p>	$\begin{array}{l} a \leq b \\ b \leq a \end{array}$	<del> <math display="block">\begin{array}{l} x \leq a \ \&amp; \ b \\ y \leq x \   \ c \end{array}</math> </del>
<p><b>When to use:</b> ( only in always blocks! )</p>	<p>Sequential Circuits</p>	<p>Combinatorial Circuits</p>

# Assignment Styles for Sequential Logic

## *Flip-Flop Based Digital Delay Line*

 

- Will nonblocking and blocking assignments both produce the desired result?


```
module nonblocking(in, clk, out);
  input in, clk;
  output out;
  reg q1, q2, out;
  always @ (posedge clk)
  begin
    q1 <= in;
    q2 <= q1;
    out <= q2;
  end
endmodule
```

```
module blocking(in, clk, out);
  input in, clk;
  output out;
  reg q1, q2, out;
  always @ (posedge clk)
  begin
    q1 = in;
    q2 = q1;
    out = q2;
  end
endmodule
```
 
# Use Nonblocking for Sequential Logic


```
always @ (posedge clk)
begin
  q1 <= in;
  q2 <= q1;
  out <= q2;
end
```

“At each rising clock edge,  $q1$ ,  $q2$ , and  $out$  **simultaneously** receive the old values of  $in$ ,  $q1$ , and  $q2$ .”



```
always @ (posedge clk)
begin
  q1 = in;
  q2 = q1;
  out = q2;
end
```

 “At each rising clock edge,  $q1 = in$ . After that,  $q2 = q1 = in$ ; After that,  $out = q2 = q1 = in$ ; Finally  $out = in$ .”




- Blocking assignments do not reflect the intrinsic behavior of multi-stage sequential logic
- **Guideline: use nonblocking assignments for sequential always blocks**

# Use Blocking for Combinational Logic

## Blocking Behavior

	a	b	c	x	y
(Given) Initial Condition	1	1	0	1	1
a changes; always block triggered	0	1	0	1	1
x = a & b;	0	1	0	0	1
y = x   c;	0	1	0	0	0

```
always @ (a or b or c)
begin
    x = a & b;
    y = x | c;
end
```

 


## Nonblocking Behavior

	a	b	c	x	y	Deferred
(Given) Initial Condition	1	1	0	1	1	
a changes; always block triggered	0	1	0	1	1	
x <= a & b;	0	1	0	1	1	x<=0
y <= x   c;	0	1	0	1	1	x<=0, y<=1
Assignment completion	0	1	0	0	1	


```
always @ (a or b or c)
begin
    x <= a & b;
    y <= x | c;
end
```

- Nonblocking assignments do not reflect the intrinsic behavior of multi-stage combinational logic
- While nonblocking assignments can be hacked to simulate correctly (expand the sensitivity list), it's not elegant
- **Guideline: use blocking assignments for combinational always blocks**

# Implementation for on/off button

 
 
```
module onoff(button,light);  
  input button;  
  output light;  
  reg light;  
  always @ (posedge button)  
  begin  
    light <= ~light;  
  end  
endmodule
```




# II. Single-clock Synchronous Circuits

We'll use Flip Flops and *Registers* – groups of FFs sharing a clock input – in a highly constrained way to build digital systems.
 
## *Single-clock Synchronous Discipline:*


- No combinational cycles
- Single clock signal shared among all clocked devices
- Only care about value of combinational circuits just before rising edge of clock
- Period greater than every combinational delay
- Change saved state after noise-inducing logic transitions have stopped!



# Clocked circuit for on/off button

```
module onoff(clk,button,light);  
  input clk,button;  
  output light;  
  reg light;  
  always @ (posedge clk)  
  begin  
    if (button) light <= ~light;  
  end  
endmodule
```


Does this work  
with a 1Mhz  
CLK?

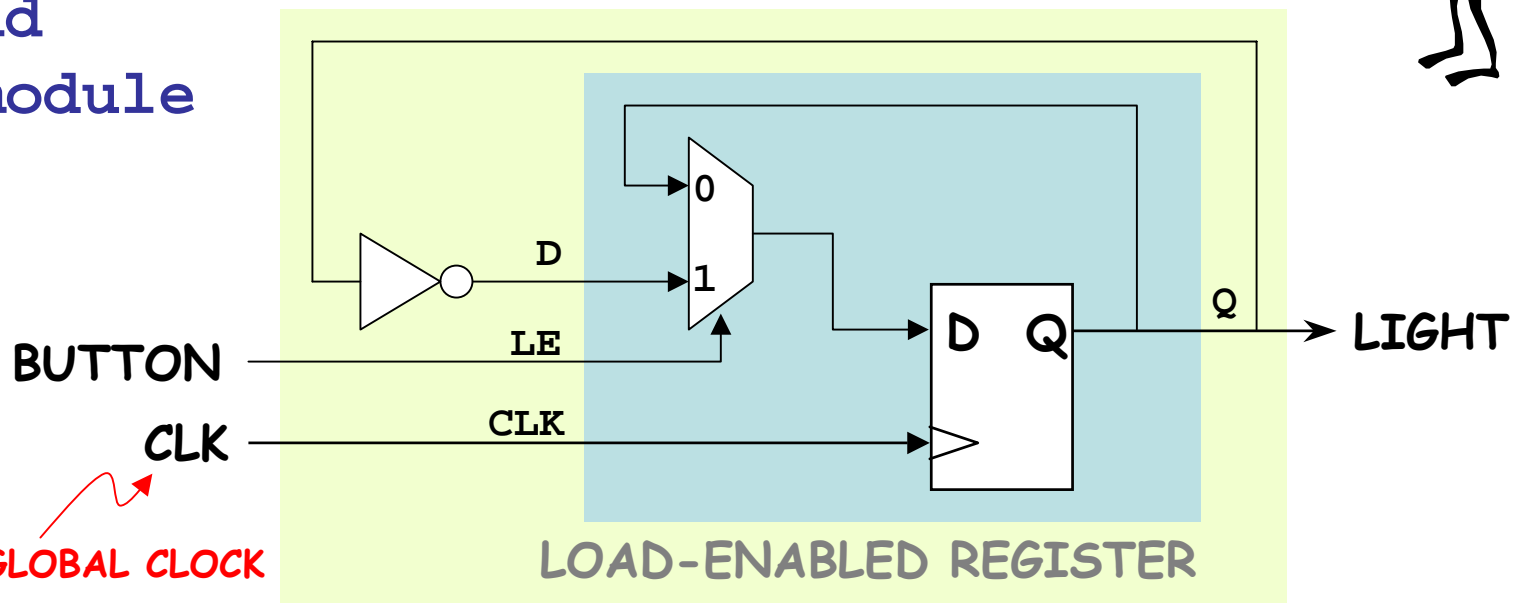




# Asynchronous Inputs in Sequential Systems

What about external signals?

 

*Can't guarantee setup and hold times will be met!*

 When an asynchronous signal causes a setup/hold violation...





**Q: Which cases are problematic?**
  
# Asynchronous Inputs in Sequential Systems

All of them can be, if more than one happens simultaneously within the same circuit.


*Idea: ensure that external signals directly feed exactly one flip-flop*



This prevents the possibility of I and II occurring in different places in the circuit, but what about metastability?
 
# Handling Metastability

- Preventing metastability turns out to be an impossible problem
- High gain of digital devices makes it likely that metastable conditions will resolve themselves quickly
- Solution to metastability: allow time for signals to stabilize




*How many registers are necessary?*

- Depends on many design parameters (clock speed, device speeds, ...)
- In 6.111, a pair of synchronization registers is sufficient

 
# III. Finite State Machines

- Finite State Machines (FSMs) are a useful abstraction for **sequential circuits** with centralized “**states**” of operation
- At each clock edge, combinational logic computes **outputs** and **next state** as a function of **inputs** and **present state**




# Example 1: Light Switch

- State transition diagram

 


- Logic diagram

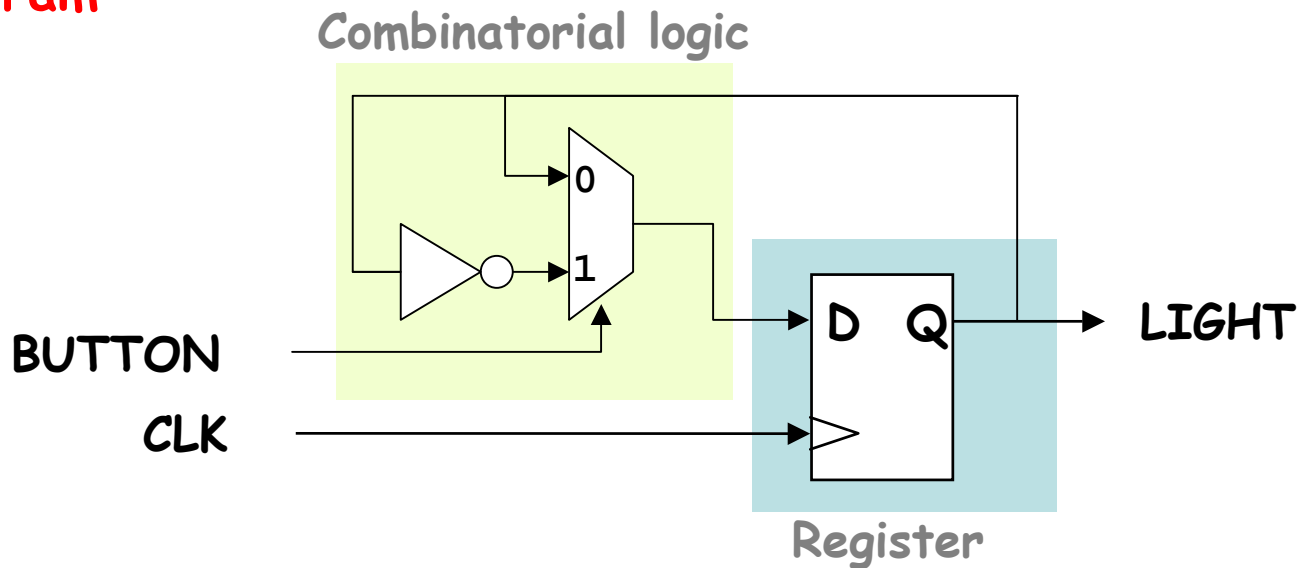


# Two Types of FSMs

Moore and Mealy FSMs : different output generation

- Moore FSM:

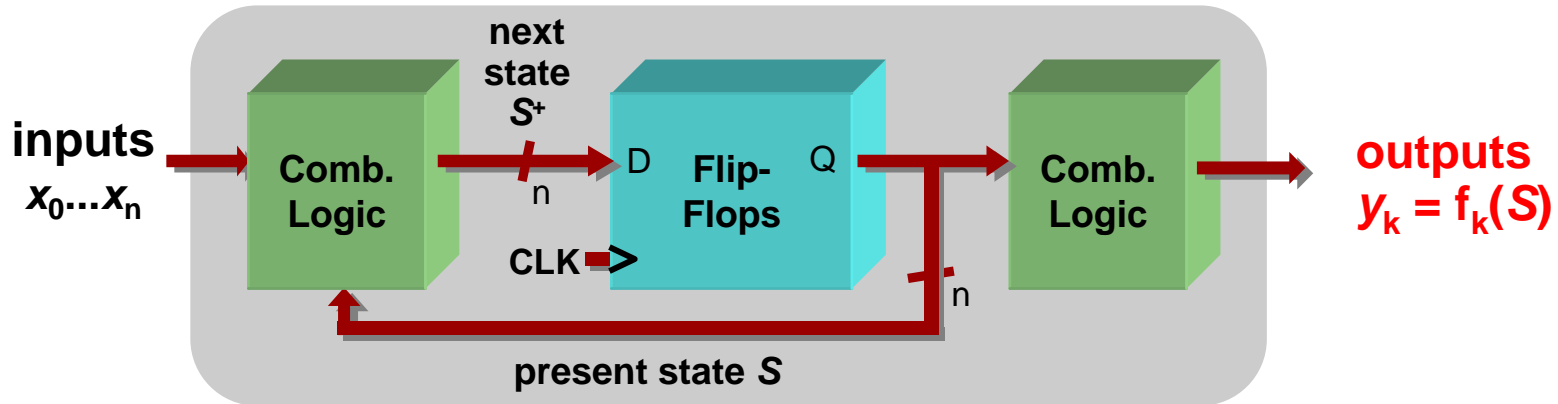


- Mealy FSM:

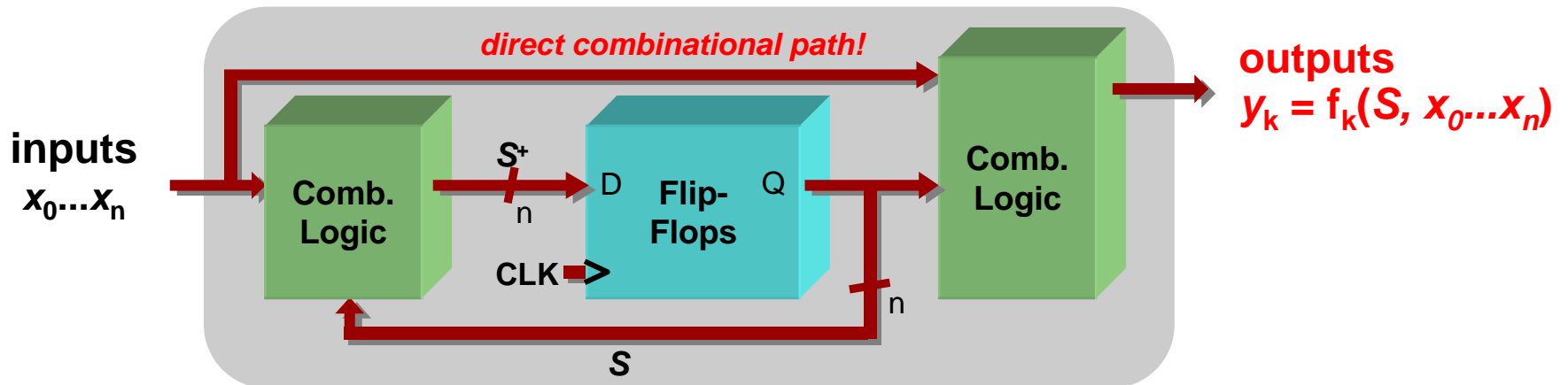

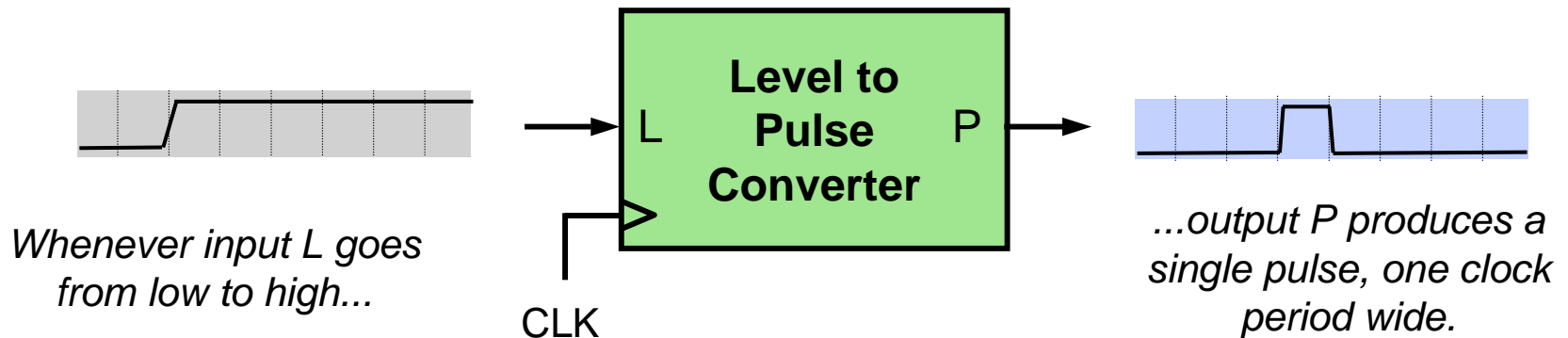
# Design Example: Level-to-Pulse

- A **level-to-pulse converter** produces a single-cycle pulse each time its input goes high.
- It's a synchronous rising-edge detector.
- Sample uses:
  - Buttons and switches pressed by humans for arbitrary periods of time
  - Single-cycle enable signals for counters




# Step 1: State Transition Diagram

- Block diagram of desired system:

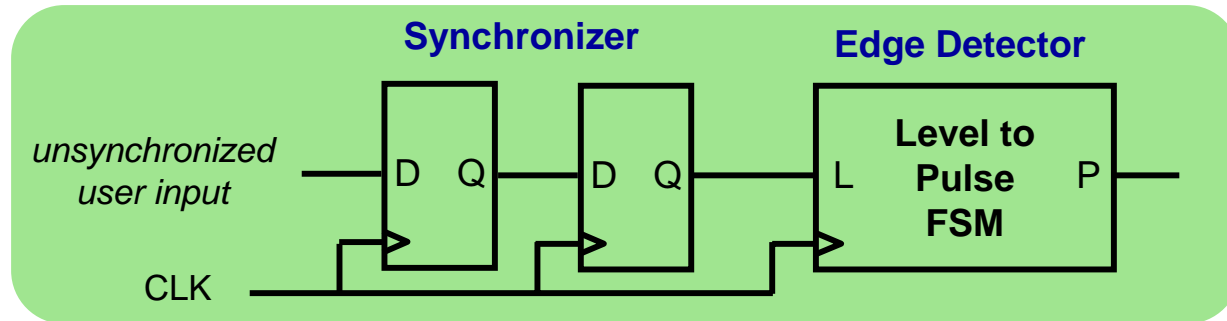

 
- State transition diagram** is a useful FSM representation and design aid:





 
# Step 2: Logic Derivation

Transition diagram is readily converted to a state transition table (just a truth table)




Current State		In	Next State		Out
$S_1$	$S_0$	$L$	$S_1^+$	$S_0^+$	$P$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	1
1	1	0	0	0	0
1	1	1	1	1	0

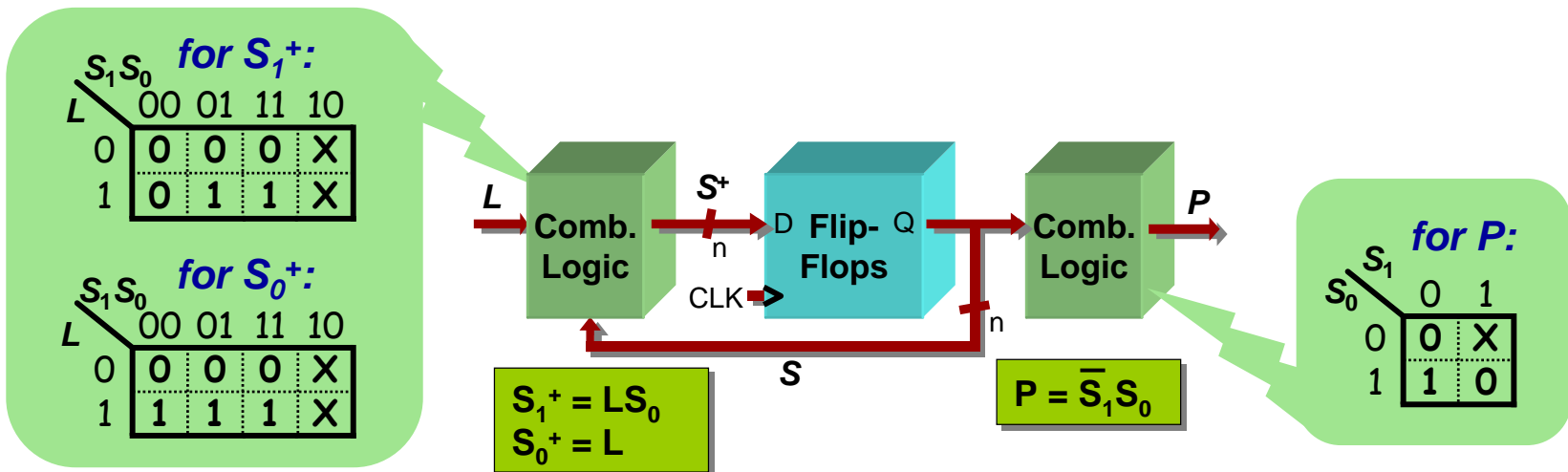
- Combinational logic may be derived using Karnaugh maps




# Moore Level-to-Pulse Converter

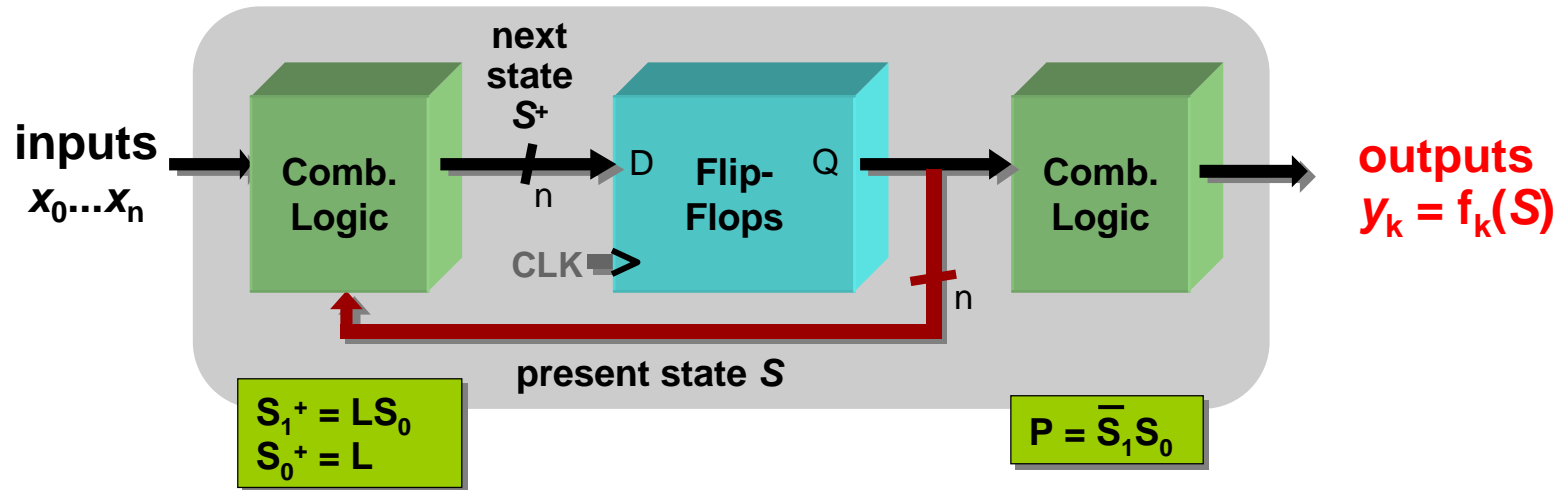

 Moore FSM circuit implementation of level-to-pulse converter:




# Design of a Mealy Level-to-Pulse

 


- Since outputs are determined by state *and* inputs, Mealy FSMs may need fewer states than Moore FSM implementations

 1. When  $L=1$  and  $S=0$ , this output is asserted **immediately** and **until** the state transition occurs (or  $L$  changes).




 2. After the transition to  $S=1$  and as long as  $L$  remains at 1, this output is asserted.




Output transitions immediately.  
State transitions at the clock edge.

# Mealy Level-to-Pulse Converter

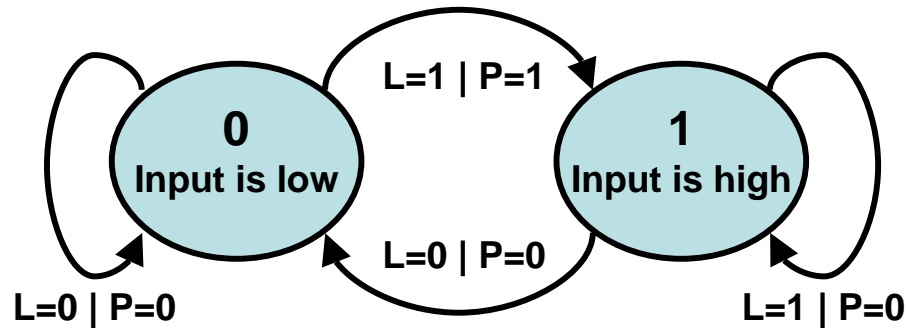

Pres. State	In	Next State	Out
<b>S</b>	<b>L</b>	<b>S<sup>+</sup></b>	<b>P</b>
0	0	0	0
0	1	1	1
1	0	0	0
1	1	1	0

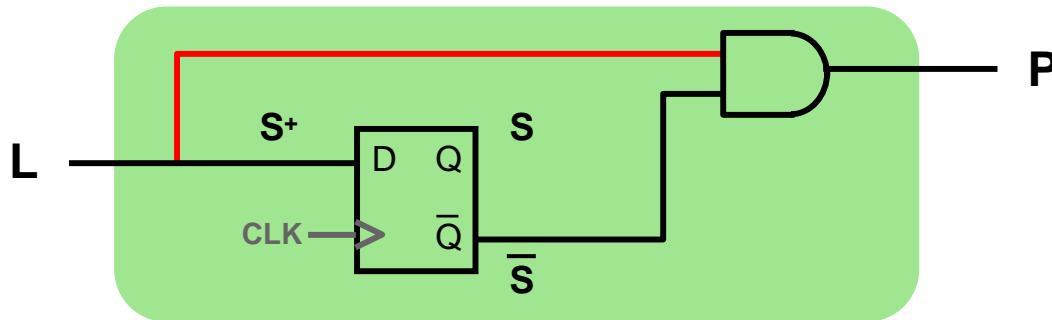Mealy FSM circuit implementation of level-to-pulse converter:




- FSM's state simply remembers the previous value of L
- Circuit benefits from the Mealy FSM's implicit single-cycle assertion of outputs during state transitions


# Moore/Mealy Trade-Offs

- How are they different?
  - Moore: **outputs = f( state )** only
  - Mealy **outputs = f( state *and* input )**
  - Mealy outputs generally occur one cycle earlier than a Moore:

Moore: delayed assertion of P

 

Mealy: immediate assertion of P

 


- Compared to a Moore FSM, a Mealy FSM might...
  - Be more difficult to conceptualize and design
  - Have fewer states

# FSM Timing Requirements


- Timing requirements for FSM are identical to any generic sequential system with feedback

## Minimum Clock Period

 

$$T > T_{cq} + T_{logic} + T_{su}$$

## Minimum Delay

 

$$T_{cd,reg} + T_{cd,logic} > T_{hold}$$

# Summary

- **Assignments in always blocks:**
  - blocking ("`=`") for combinational logic
  - non-blocking ("`<=`") for sequential logic
- **Single-clock Synchronous discipline:**
  - Reliable digital circuits / systems
  - Global clock to edge-triggered registers
- **Finite state machines:**
  - Programmable systems
  - Moore & Mealy

