

Memories: a practical primer

- **The good news: huge selection of technologies**
 - Small & faster vs. large & slower
 - Every year capacities go up and prices go down
 - New kid on the block: high density, fast flash memories
 - Non-volatile, read/write, no moving parts! (robust, efficient)
- **The bad news: perennial system bottleneck**
 - Latencies (access time) haven't kept pace with cycle times
 - Separate technology from logic, so must communicate between silicon, so physical limitations (# of pins, R's and C's and L's) limit bandwidths
 - New hopes: capacitive interconnect, 3D IC's
 - Likely the limiting factor in cost & performance of many digital systems: designers spend a lot of time figuring out how to keep memories running at peak bandwidth
 - "It's the memory, stupid"

Memories in Verilog

- `reg bit; // a single register`
 - `reg [31:0] word; // a 32-bit register`
 - `reg [31:0] array[15:0] // 16 32-bit regs`
- ```
wire [31:0] read_data, write_data;
wire [3:0] index;

// combinational (asynch) read
assign read_data = array[index];

// clocked (synchronous) write
always @ (posedge clock)
 array[index] <= write_data;
```

# Multi-port Memories (aka regfiles)

```
reg [31:0] regfile[31:0]; // 32 32-bit words

// Beta register file: 2 read ports, 1 write
wire [4:0] ra1,ra2,wa;
wire [31:0] rd1,rd2,wd;

assign ra1 = inst[20:16];
assign ra2 = ra2sel ? inst[25:21] : inst[15:11];
assign wa = wasel ? 5'd30 : inst[25:21];

// read ports
assign rd1 = (ra1 == 31) ? 0 : regfile[ra1];
assign rd2 = (ra2 == 31) ? 0 : regfile[ra2];
// write port
always @ (posedge clk)
 if (werf) regfile[wa] <= wd;



assign z = ~| rd1; // used in BEQ/BNE instructions
```

# FPGA memory implementation


- Regular registers in logic blocks
  - Piggy use of resources, but convenient & fast if small
- [Xilinx Vertex II] use the LUTs:
  - Single port: 16x(1,2,4,8), 32x(1,2,4,8), 64x(1,2), 128x1
  - Dual port (1 R/W, 1R): 16x1, 32x1, 64x1
  - Can fake extra read ports by cloning memory: all clones are written with the same addr/data, but each clone can have a different read address
- [Xilinx Vertex II] use block ram:
  - 18K bits: 16Kx1, 8Kx2, 4Kx4  
with parity: 2Kx(8+1), 1Kx(16+2), 512x(32+4)
  - Single or dual port
  - Pipelined (clocked) operations
  - Labkit XCV2V6000: 144 BRAMs, 2952K bits total
  
# Virtex memory configurations



Using LUT resources in configurable logic blocks:



Using BRAMs:

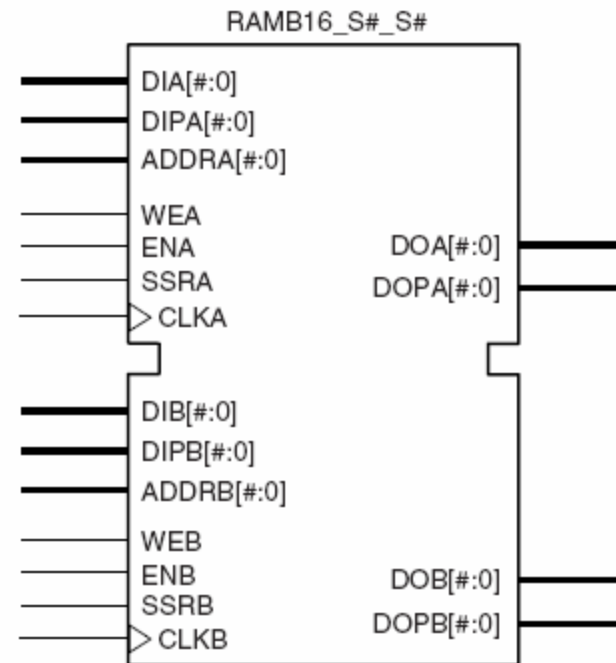


# Xilinx Synchronous Block Memory

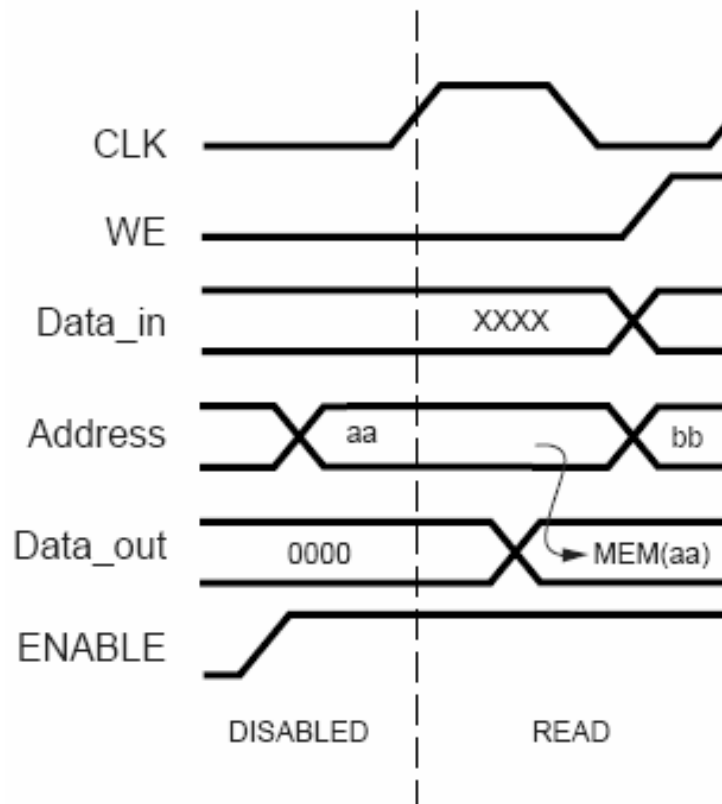 

# Using BRAMs (eg, a 64Kx8 ram)


- From menus: Project → New Source...

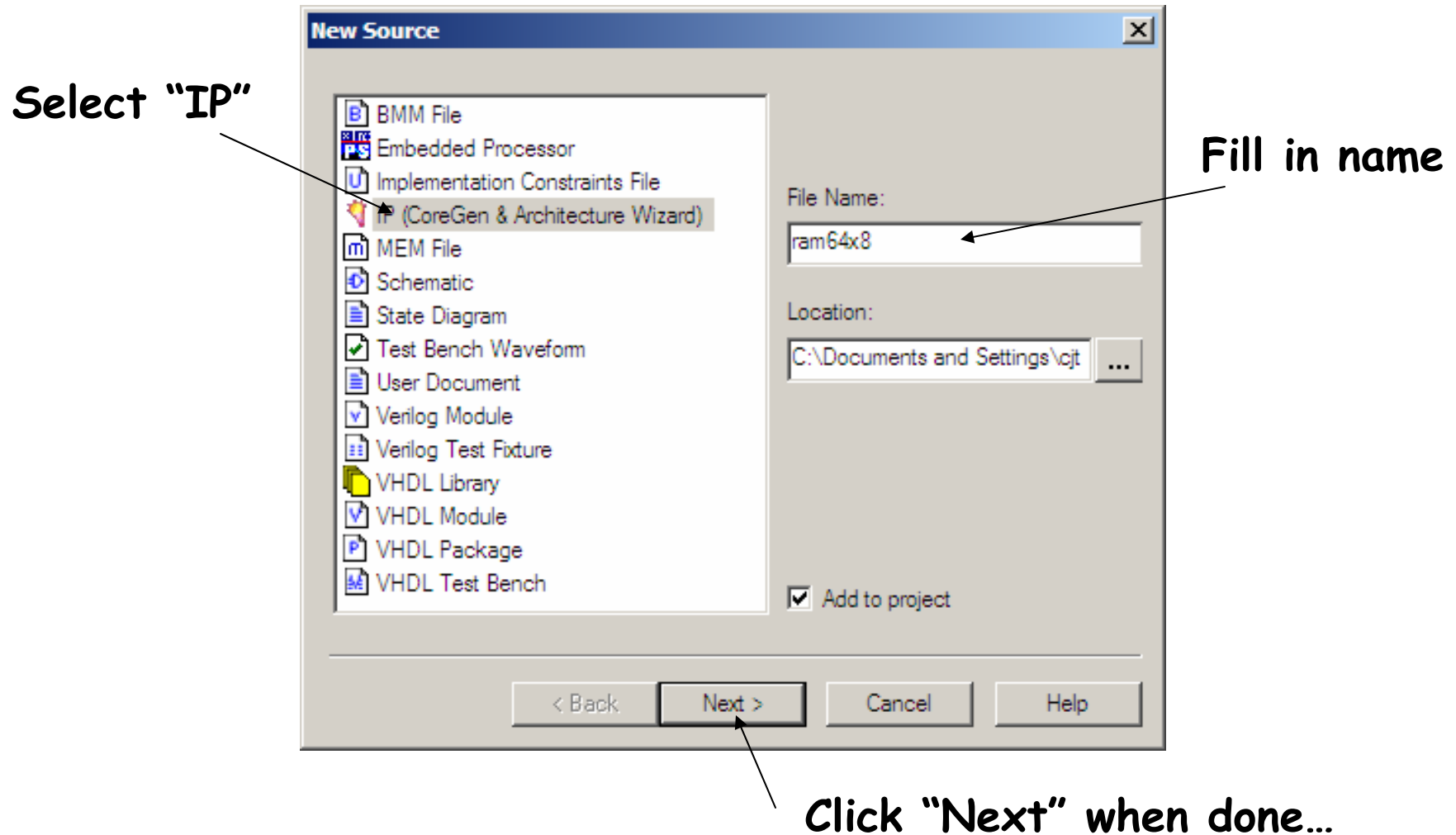

# BRAM Example

Click open folders

Select "Single Port Block Memory"

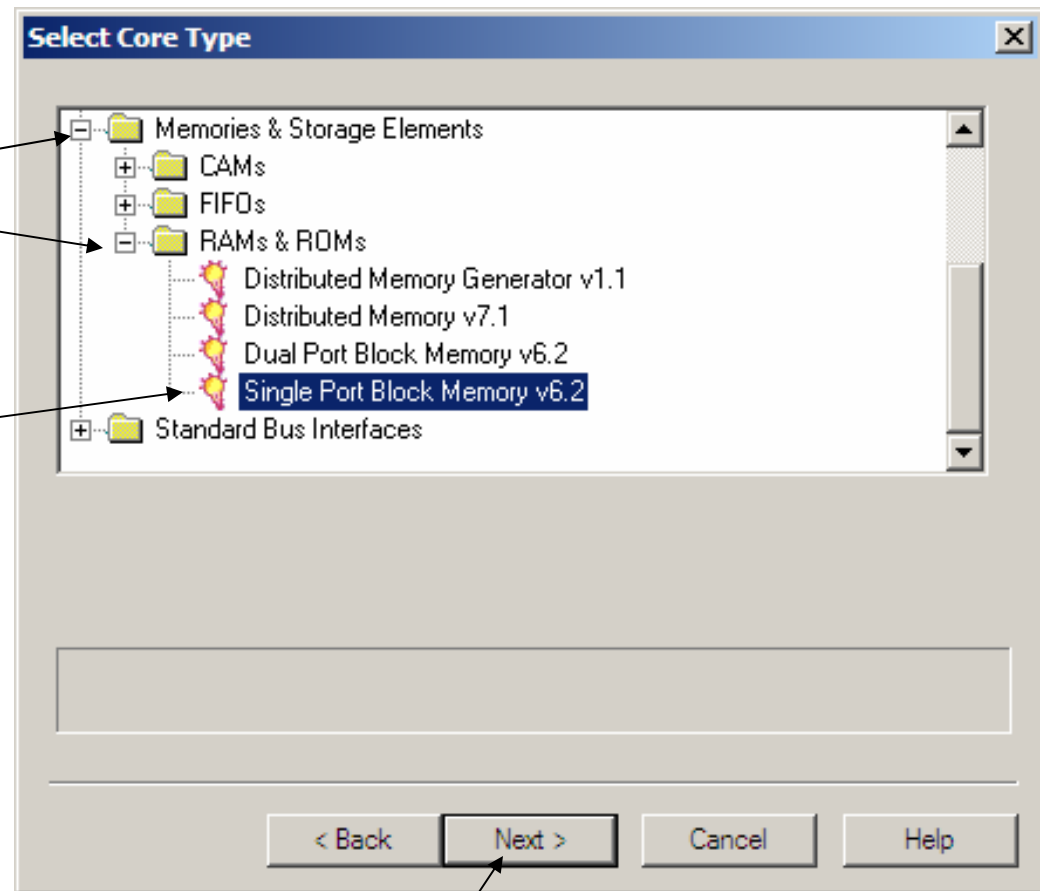

Click "Next" and then "Finish" on next window



# BRAM Example

The screenshot shows the 'Single Port Block Memory' configuration window. On the left, a block diagram of the memory is highlighted in purple, with pins labeled ADDR, DIN, WE, EN, SINIT, ND, CLK, DOUT, RFD, and RDY. The main configuration area on the right includes: 'Component Name' set to 'ram64x8'; 'Port Configuration' with 'Read And Write' selected; 'Memory Size' with 'Width' set to 8 and 'Depth' set to 65536; and 'Write Mode' with 'Read After Write' selected. At the bottom, there are buttons for '<Back', 'Next>', 'Generate', 'Dismiss', 'Data Sheet...', 'Version Info...', and a checkbox for 'Display Core Footprint'. The page number 'Page 1 of 4' is also visible.

Fill in name (again?!)

Select RAM vs ROM


Fill in width & depth

Usually "Read After Write" is what you want

Click "Next" ...
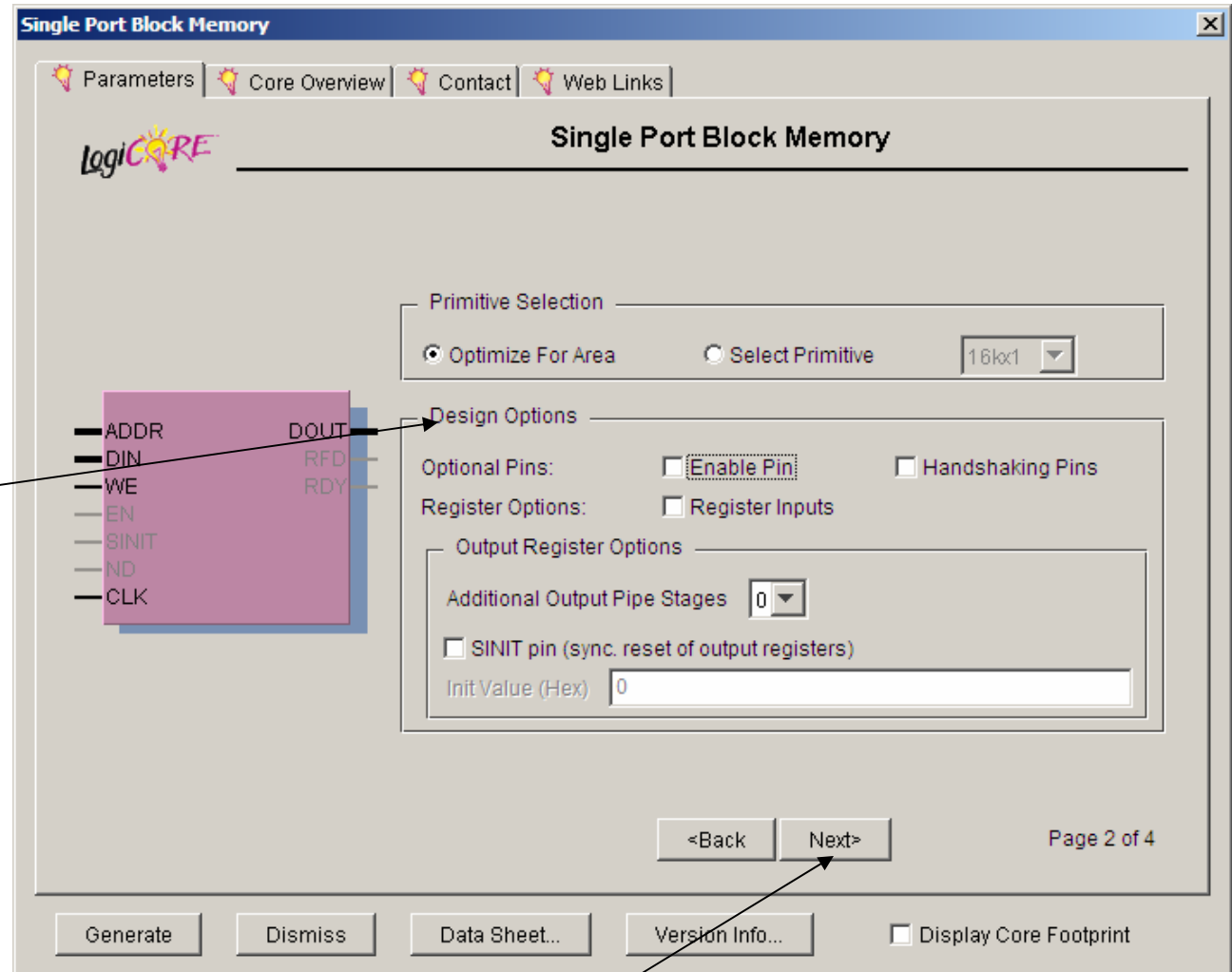
# BRAM Example


Can add extra control pins, but usually not



Click "Next" ...

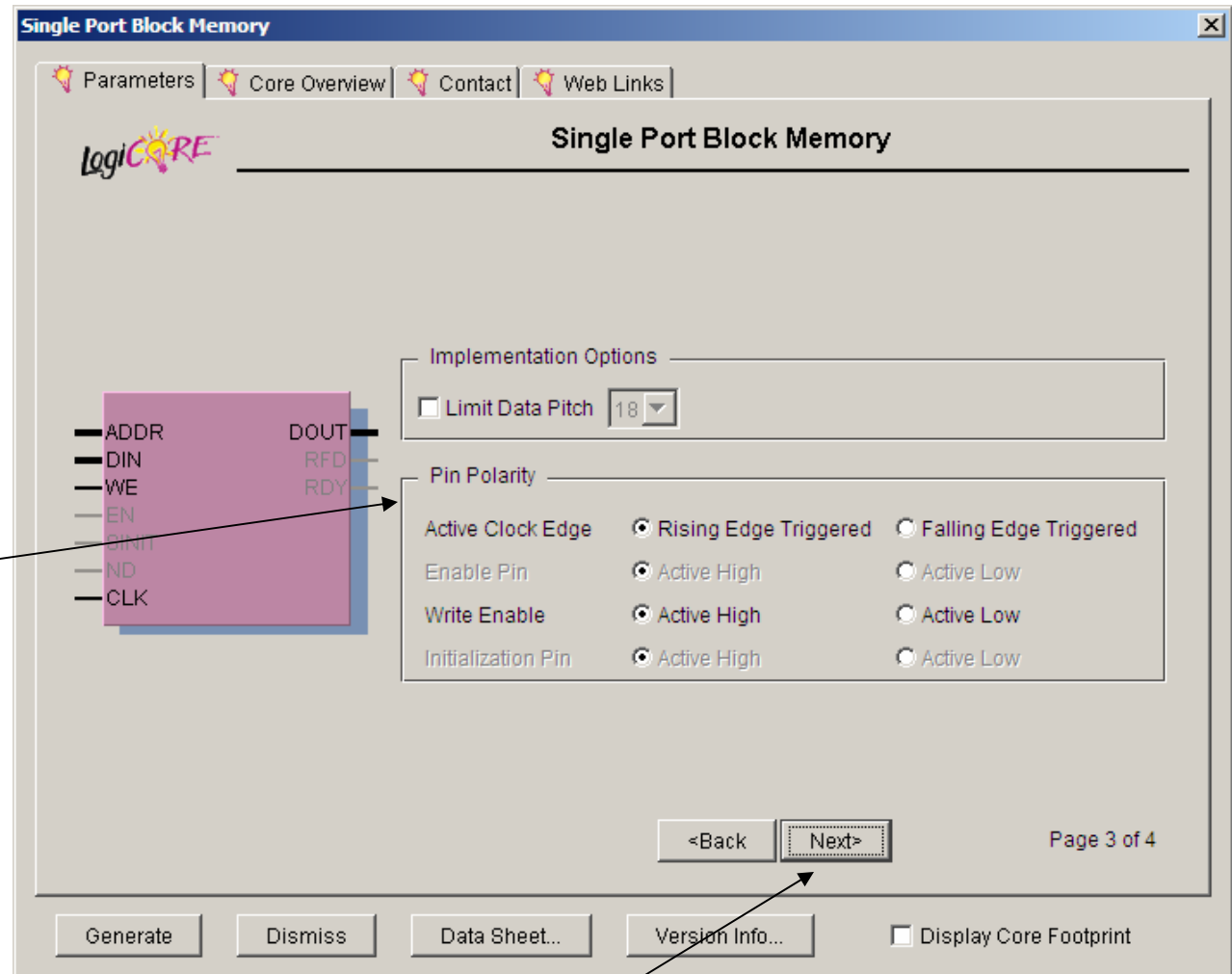
# BRAM Example

Select polarity  
of control pins;  
active high  
default is  
usually just fine



Click "Next" ...

# BRAM Example

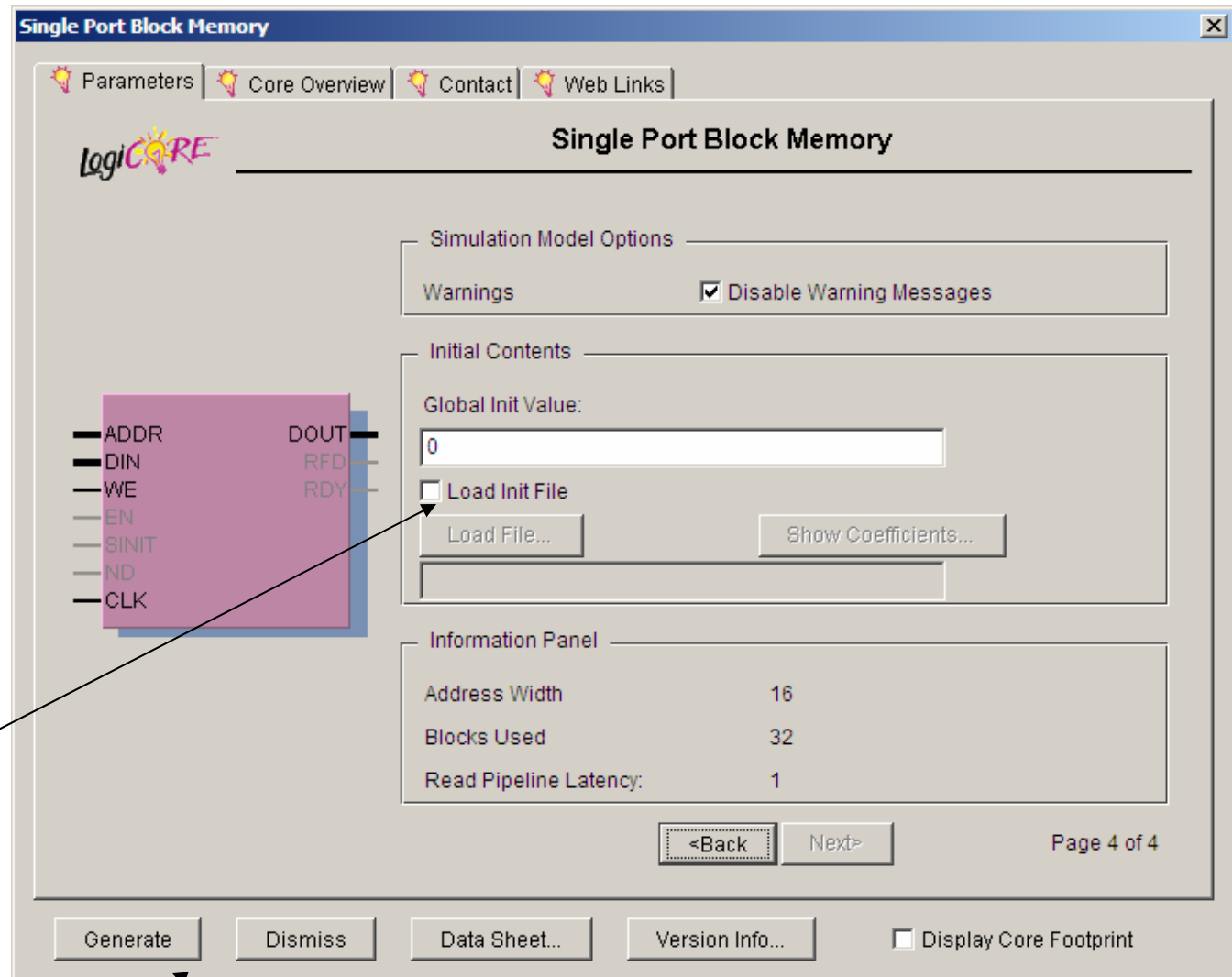

Click to name a .coe file that specifies initial contents (eg, for a ROM)

Click "Generate" to complete

# .coe file format

```
memory_initialization_radix=2;
memory_initialization_vector=
```

```
00000000,
00111110,
01100011,
00000011,
00000011,
00011110,
00000011,
00000011,
01100011,
00111110,
00000000,
00000000,
```

Memory contents with location 0 first, then location 1, etc. You can specify input radix, in this example we're using binary. MSB is on the left, LSB on the right. Unspecified locations (if memory has more locations than given in .coe file) are set to 0.

# Using result in your Verilog

- Look at generated Verilog for module def'n:


```
module ram64x8 (addr,clk,din,dout,we);
 input [15 : 0] addr;
 input clk;
 input [7 : 0] din;
 output [7 : 0] dout;
 input we;
 ...
endmodule
```

- Use to instantiate instances in your code:

```
ram64x8 foo(addr,clk,din,dout,we);
```


# Toward FSM Modularity

- Consider the following abstract FSM:

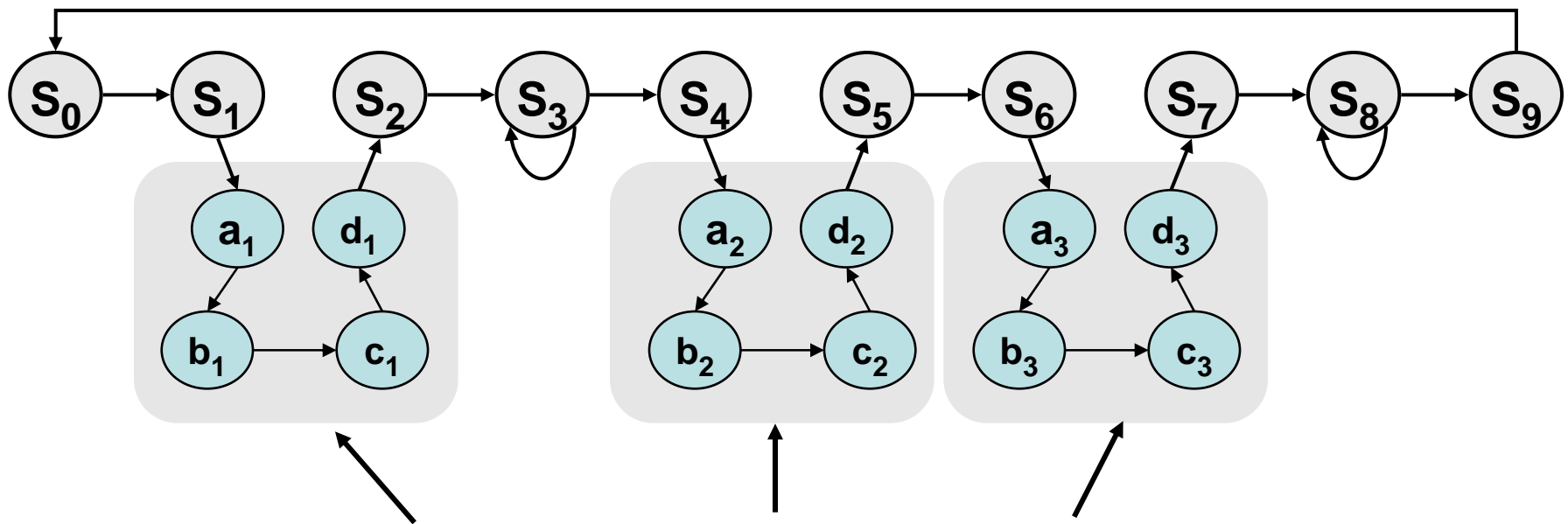

- Suppose that each set of states  $a_x \dots d_x$  is a “sub-FSM” that produces exactly the same outputs.
- Can we simplify the FSM by removing equivalent states?  
*No! The outputs may be the same, but the next-state transitions are not.*
- This situation closely resembles a **procedure call** or **function call** in software...how can we apply this concept to FSMs?


# The Major/Minor FSM Abstraction

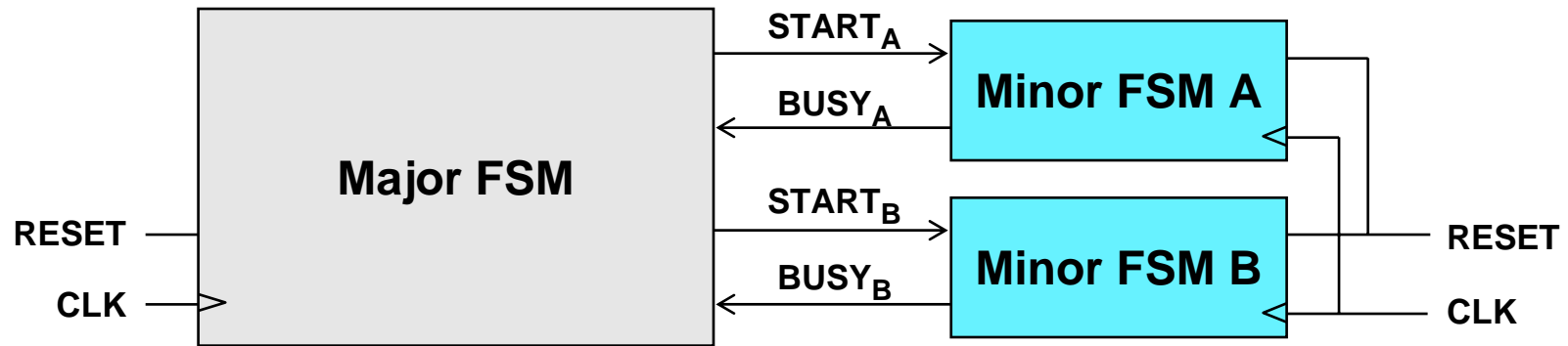

- Subtasks are encapsulated in **minor FSMs** with common reset and clock
- Simple communication abstraction:
  - **START**: tells the minor FSM to begin operation (the call)
  - **BUSY**: tells the major FSM whether the minor is done (the return)
- The major/minor abstraction is great for...
  - Modular designs (*always* a good thing)
  - Tasks that occur often but in different contexts
  - Tasks that require a variable/unknown period of time
  - Event-driven systems




# Inside the Major FSM

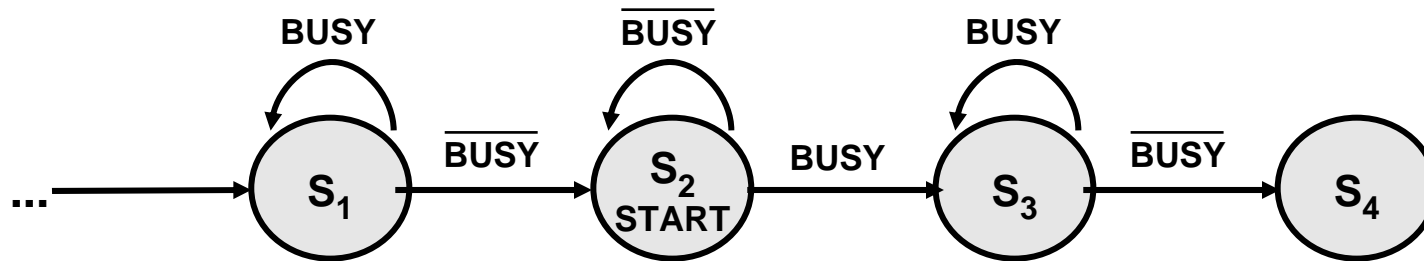

1. Wait until the minor FSM is ready

2. Trigger the minor FSM (and make sure it's started)



3. Wait until the minor FSM is done

 

## Variations:


- Usually don't need both Step 1 and Step 3
- One cycle "done" signal instead of multi-cycle "busy"

# Inside the Minor FSM

 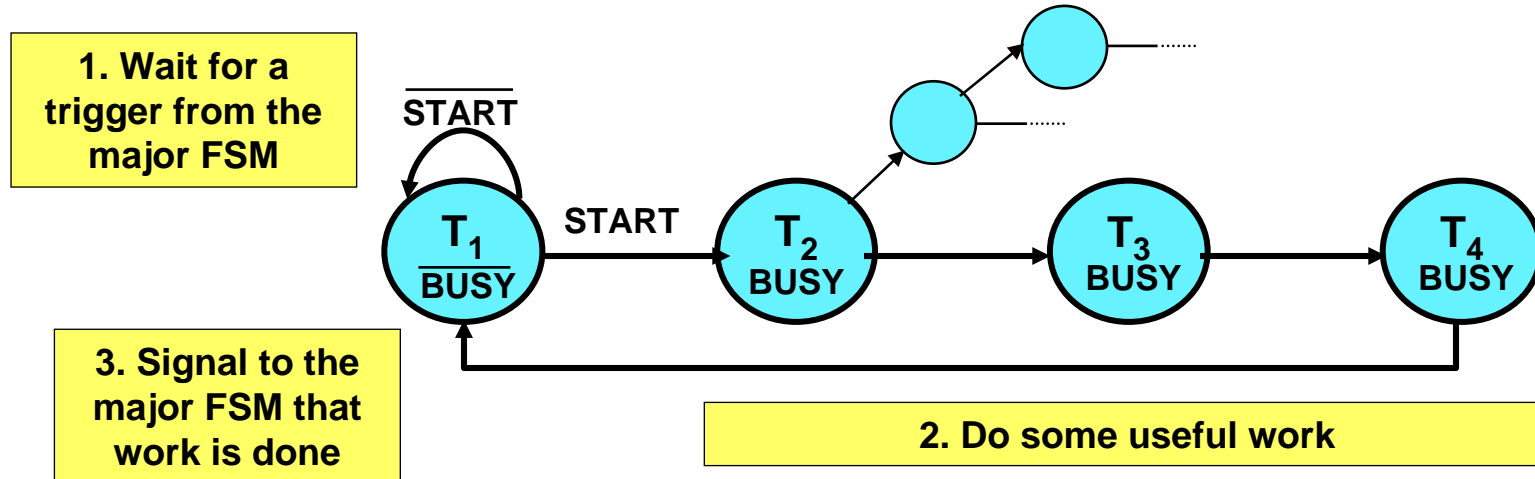

 
# Optimizing the Minor FSM

Good idea: de-assert BUSY one cycle early



 
## Bad idea #1:

T<sub>4</sub> may not immediately return to T<sub>1</sub>




## Bad idea #2:

BUSY never asserts!

 


# A Four-FSM Example


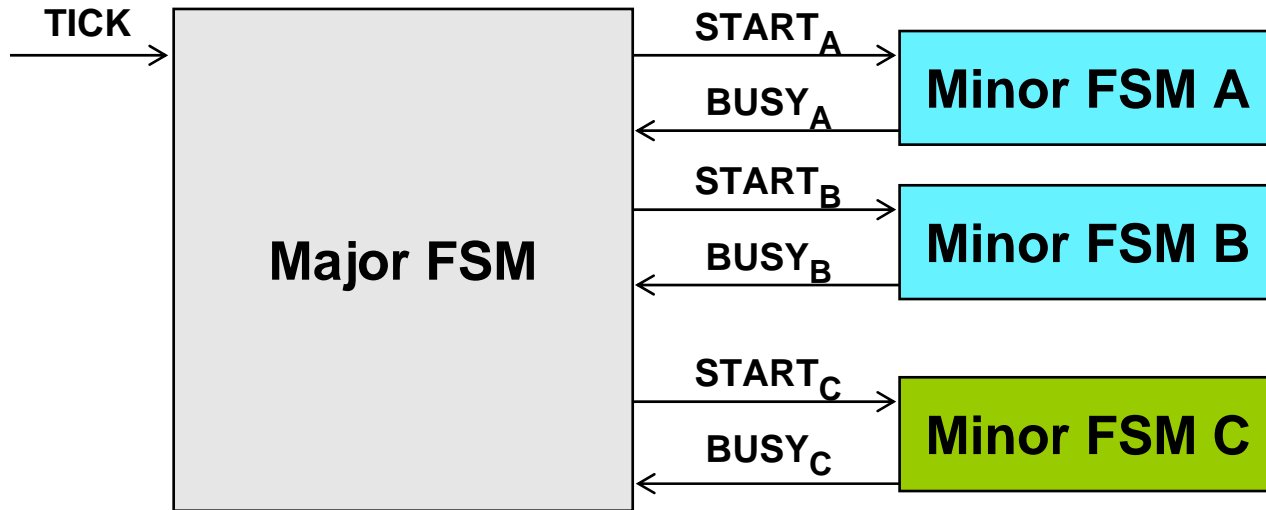


Operating Scenario:

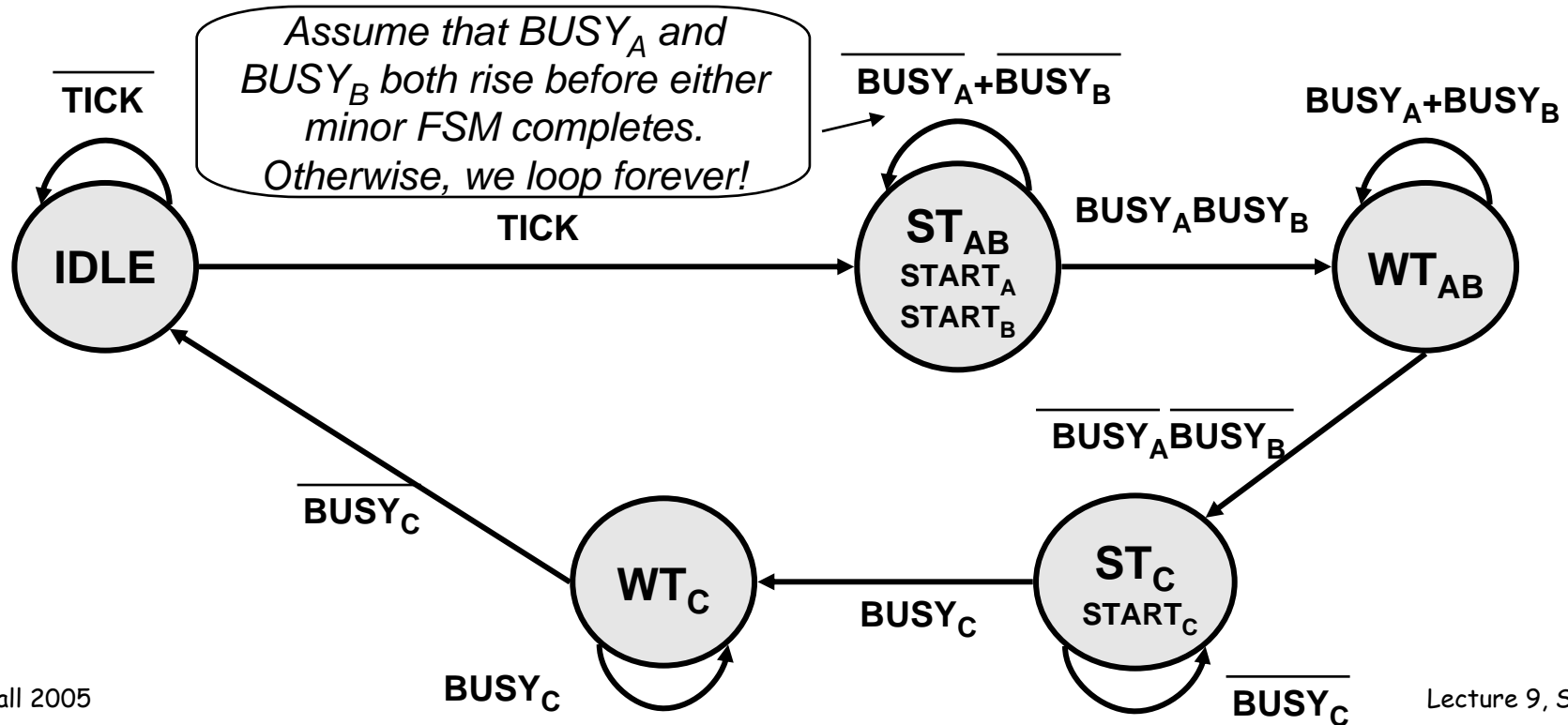- Major FSM is triggered by TICK
- Minors A and B are started simultaneously
- Minor C is started once both A and B complete
- TICKs arriving before the completion of C are ignored




# Four-FSM Sample Waveform

 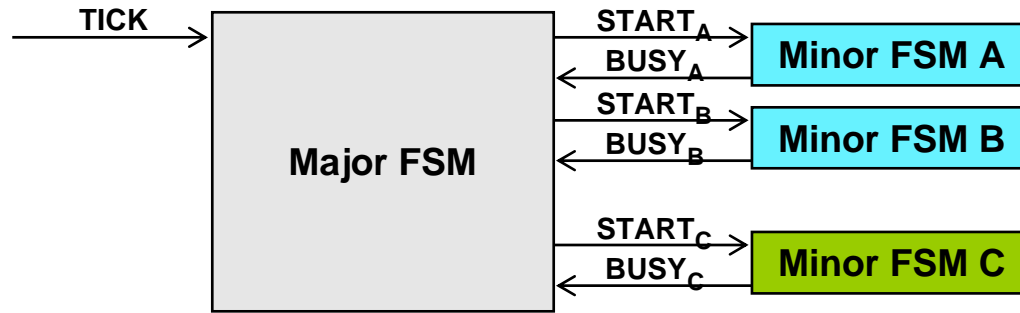
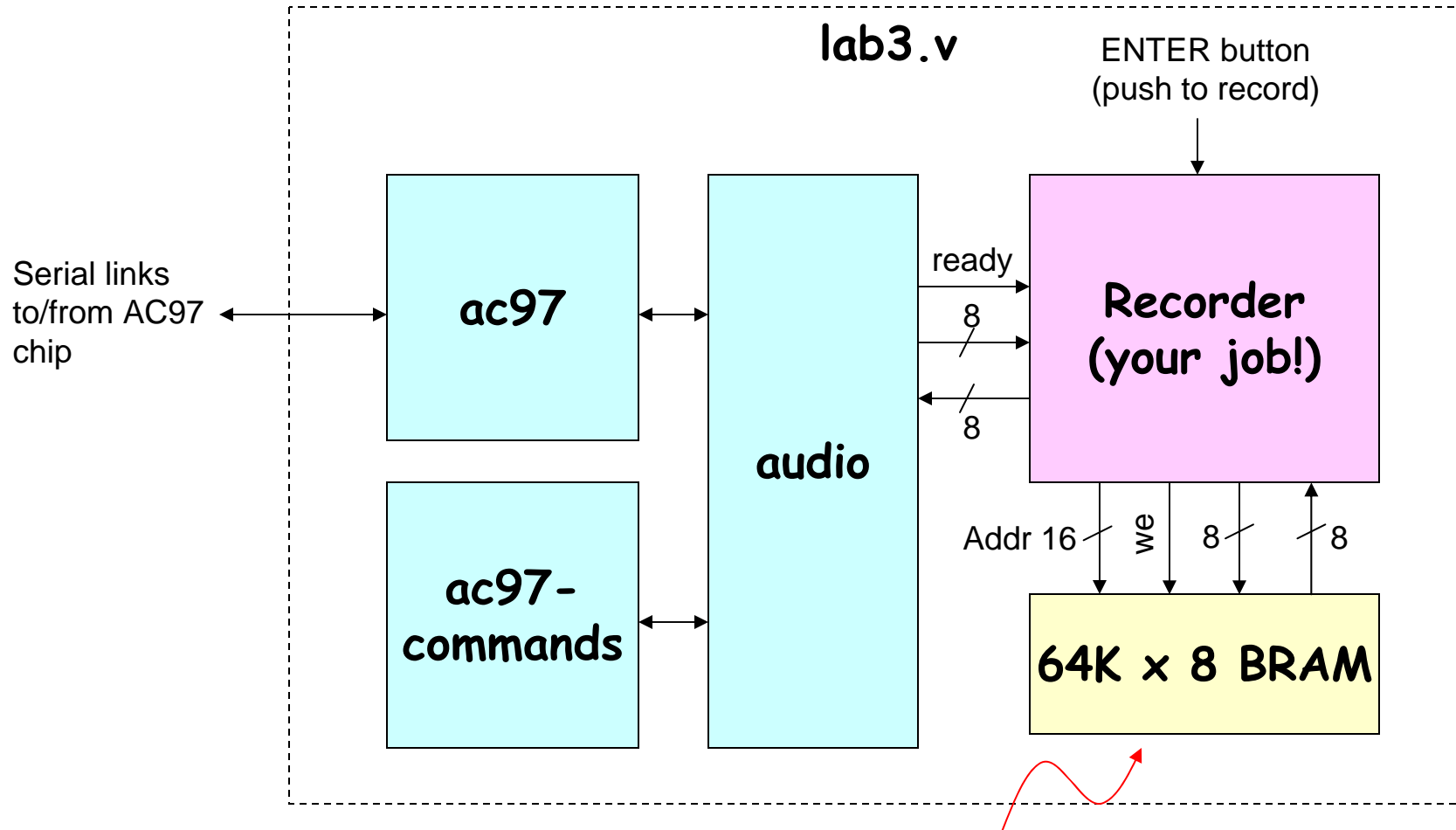
# Lab 3 overview

Assignment: build a voice recorder that uses 8-bit PCM data @ 6KHz



About 11 seconds of speech @ 6KHz

# AC97: PCM data

PCM = pulse code modulation

Sample waveform at fixed intervals, encode results as an N-bit signed number. For our AC97 chip, N = 18.

