



RFID Reader System

Katonio Butler

Akua Nti

15 November 2005

Outline

- Project Goals
- RFID Reader Block Diagram
- Subsystem Block Diagrams
- Division of Labor
- Project Timeline




Project Goals


The principal goal of this project is to successfully design, implement, and test a low-power, low frequency (125 kHz) RFID tag reader for the passive RFID tags in MIT ID cards. The tag reader system, which will be based on the 6.111 Xilinx FPGA labkit, will be accomplished in the following manner:

- Build a transmitter antenna that will produce and send a 125 kHz AM sine wave interrogation signal to an MIT ID card.
- Build a receiver antenna that receives a 62.5 kHz AM sine wave reply signal, amplifies it, converts it to a digital format, and processes it to extract a stream of bits.
- Build a decoder that transforms the data to get identification data (MIT ID number).
- Build a video module that outputs the identification data to a display.

RFID Reader Block Diagram

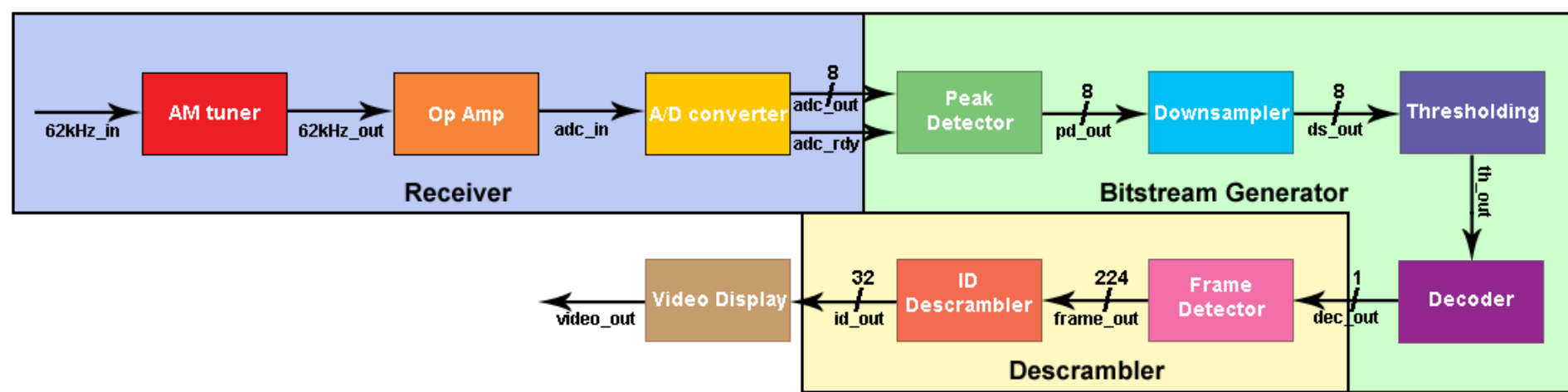


Subsystem Block Diagram: Transmitter

 


- Signal generator creates a constant 125 kHz sine wave
- Antenna transmits signal to transponder in card

Subsystem Block Diagram: Receiver

 


- Amplitude modulated 62.5 kHz signal is received by a tuner, then amplified
- A/D converter module outputs a stream of 8-bit voltage values
- Raises `adc_rdy` when it has a new converted value

 Subsystem Block Diagram: Bitstream Generator



- Peak detector compares latest 3 values of `adc_out` to determine peaks
- Downsampler selects every Nth peak
- Thresholding module converts voltage values to 0 or 1 by comparing to a threshold
- Decoder compares latest 2 values of `th_out` and computes XOR to find transitions

Subsystem Block Diagram: Descrambler

 

- Bitstream from decoder (repeating pattern of values) is input to frame detector
- Frame detector finds beginning of sequence and outputs a frame—the next 224 bits—in parallel
- Descrambler extracts and transforms the 32 bits relevant to the user ID

Division of Labor

Katonio:






- Build 125 kHz AM transmitter
- Design 62.5 kHz receiver
- Code Thresholding module
- Code ID Descrambler module
- Code Video Display Module

Akua:

- Build 62.5 kHz AM receiver
- Code A/D converter
- Code Peak Detection & Downsampler modules
- Code Decoder module
- Code Frame Detector module

Project Timeline: November

November 2005

| Sunday | Monday | Tuesday | Wednesday | Thursday | Friday | Saturday |
|--|--------|--|-----------|--|--|----------|
| | | 1 | 2 | 3 | 4 | 5 |
| 6  | 7 | 8 | 9 | 10 | 11 Veterans Day  | 12 |
| 13 | 14 | 15  | 16 | 17 | 18  | 19 |
| 20 | 21 | 22 | 23 | 24 Thanksgiving Day  | 25 | 26 |
| 27 | 28 | 29 | 30 | | | |

06 November: Project proposal conference

11 November: Block diagram conference

15 November: Project presentation




18 November: Checklist conference

Construction of AM transmitter, AM receiver and A/D module complete

24 November: Completion of Bitstream Generator module

Project Timeline: December

December 2005

| Sunday | Monday | Tuesday | Wednesday | Thursday | Friday | Saturday |
|---------------------|--------|---------|---|----------|---|----------|
| | | | | 1 | 2  | 3 |
| 4 | 5 | 6 | 7 | 8 | 9  | 10 |
| 11 | 12 | 13 | 14  | 15 | 16 | 17 |
| 18 | 19 | 20 | 21 | 22 | 23 | 24 |
| 25 Christmas Day | 26 | 27 | 28 | 29 | 30 | 31 |

02 December: Completion of Descrambler and Display modules

09 December: System testing/debugging

Feature additions (time permitting)

14 December: Final Report due