
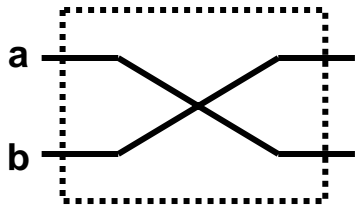
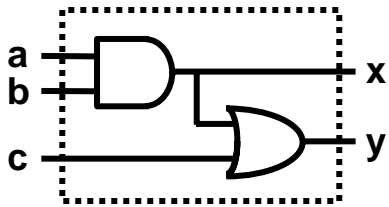


I. Blocking vs. Nonblocking Assignments

Conceptual need for **two kinds of assignment** (in always blocks):

		
<p>Blocking: Evaluation and assignment are immediate</p>	 $\begin{array}{l} a = b \\ b = a \end{array}$ 	$\begin{array}{l} x = a \ \& \ b \\ y = x \ \ c \end{array}$
<p>Non-Blocking: Assignment is postponed until all r.h.s. evaluations are done</p>	$\begin{array}{l} a \leq b \\ b \leq a \end{array}$	 $\begin{array}{l} x \leq a \ \& \ b \\ y \leq x \ \ c \end{array}$
<p>When to use: (only in always blocks!)</p>	<p>Sequential Circuits</p>	<p>Combinatorial Circuits</p>

Assignment Styles for Sequential Logic

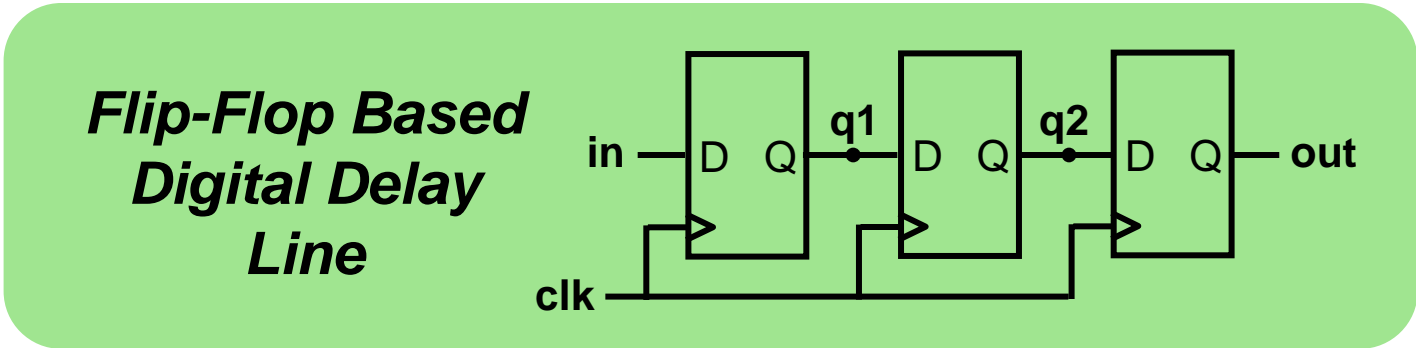

- Will nonblocking and blocking assignments both produce the desired result?


```
module nonblocking(in, clk, out);
  input in, clk;
  output out;
  reg q1, q2, out;
  always @ (posedge clk)
  begin
    q1 <= in;
    q2 <= q1;
    out <= q2;
  end
endmodule
```

```
module blocking(in, clk, out);
  input in, clk;
  output out;
  reg q1, q2, out;
  always @ (posedge clk)
  begin
    q1 = in;
    q2 = q1;
    out = q2;
  end
endmodule
```

Use Nonblocking for Sequential Logic


```
always @ (posedge clk)
begin
    q1 <= in;
    q2 <= q1;
    out <= q2;
end
```

 “At each rising clock edge, $q1$, $q2$, and out **simultaneously receive the old values** of in , $q1$, and $q2$.”



```
always @ (posedge clk)
begin
    q1 = in;
    q2 = q1;
    out = q2;
end
```

 “At each rising clock edge, $q1 = in$. **After that**, $q2 = q1 = in$; **After that**, $out = q2 = q1 = in$; **Finally** $out = in$.”




- Blocking assignments do not reflect the intrinsic behavior of multi-stage sequential logic
- **Guideline: use nonblocking assignments for sequential always blocks**

Use Blocking for Combinational Logic

Blocking Behavior

	a	b	c	x	y
(Given) Initial Condition	1	1	0	1	1
a changes; always block triggered	0	1	0	1	1
x = a & b;	0	1	0	0	1
y = x c;	0	1	0	0	0

```
always @ (a or b or c)
begin
    x = a & b;
    y = x | c;
end
```

 

Nonblocking Behavior

	a	b	c	x	y	Deferred
(Given) Initial Condition	1	1	0	1	1	
a changes; always block triggered	0	1	0	1	1	
x <= a & b;	0	1	0	1	1	x<=0
y <= x c;	0	1	0	1	1	x<=0, y<=1
Assignment completion	0	1	0	0	1	

```
always @ (a or b or c)
begin
    x <= a & b;
    y <= x | c;
end
```


- Nonblocking assignments do not reflect the intrinsic behavior of multi-stage combinational logic
- While nonblocking assignments can be hacked to simulate correctly (expand the sensitivity list), it's not elegant
- **Guideline: use blocking assignments for combinational always blocks**

II. Single-clock Synchronous Circuits

We'll use Flip Flops and *Registers* – groups of FFs sharing a clock input – in a highly constrained way to build digital systems.

Single-clock Synchronous Discipline:

 
- No combinational cycles
- Single clock signal shared among all clocked devices
- Only care about value of combinational circuits just before rising edge of clock
- Period greater than every combinational delay
- Change saved state after noise-inducing logic transitions have stopped!



Clocked circuit for on/off button


```
module onoff(clk,button,light);  
  input clk,button;  
  output light;  
  reg light;  
  always @ (posedge clk)  
  begin  
    if (button) light <= ~light;  
  end  
endmodule
```

Does this work
with a 1Mhz
CLK?

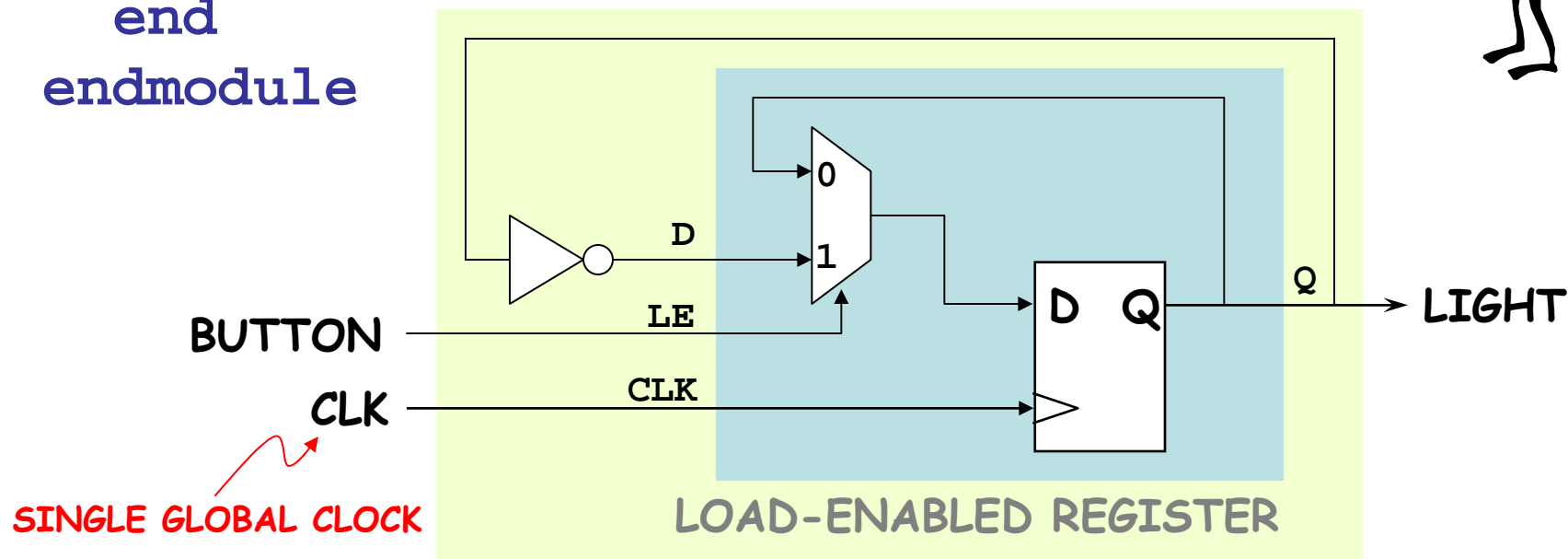


Asynchronous Inputs in Sequential Systems

What about external signals?

 

Can't guarantee setup and hold times will be met!

 When an asynchronous signal causes a setup/hold violation...



Transition is missed on first clock cycle, but caught on next clock cycle.

Transition is caught on first clock cycle.



Output is metastable for an indeterminate amount of time.

Q: Which cases are problematic?

Asynchronous Inputs in Sequential Systems

All of them can be, if more than one happens simultaneously within the same circuit.

  
Idea: ensure that external signals directly feed exactly one flip-flop



This prevents the possibility of I and II occurring in different places in the circuit, but what about metastability?

Handling Metastability

 - Preventing metastability turns out to be an impossible problem
- High gain of digital devices makes it likely that metastable conditions will resolve themselves quickly
- Solution to metastability: allow time for signals to stabilize




How many registers are necessary?

- Depends on many design parameters (clock speed, device speeds, ...)
- In 6.111, a pair of synchronization registers is sufficient


III. Finite State Machines

- Finite State Machines (FSMs) are a useful abstraction for **sequential circuits** with centralized “**states**” of operation
- At each clock edge, combinational logic computes **outputs** and **next state** as a function of **inputs** and **present state**

 


Example 1: Light Switch

- State transition diagram

 


- Logic diagram

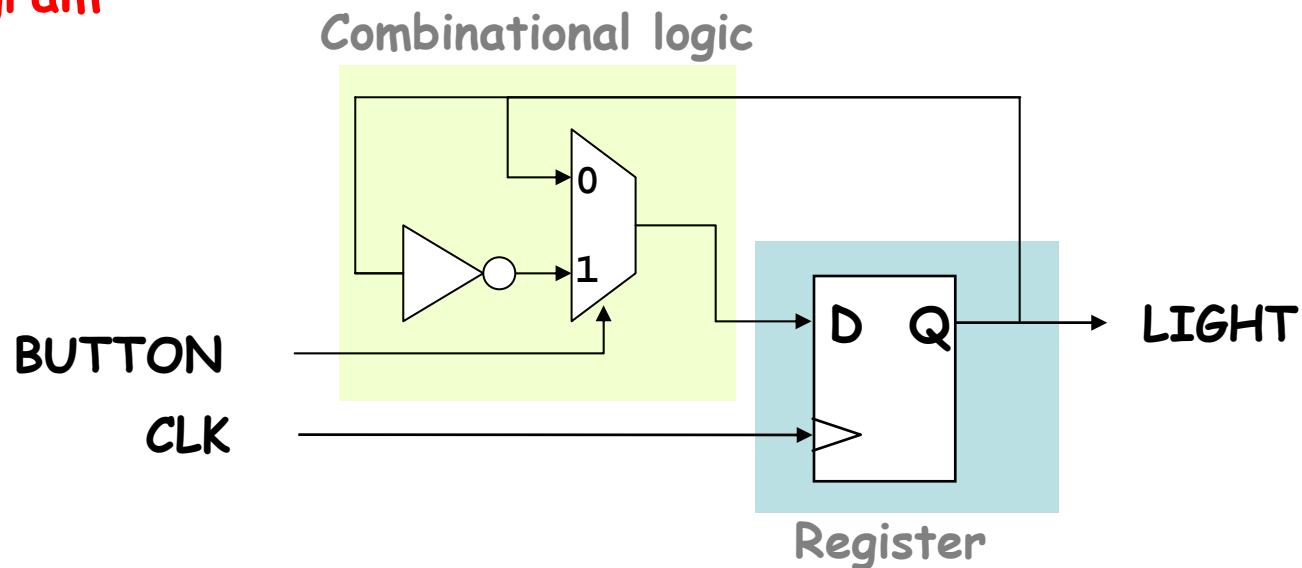

Example 2: 4-bit Counter

- Logic diagram

 


- Verilog

4-bit counter

```
module counter(clk, count);  
  input clk;  
  output [3:0] count;  
  reg [3:0] count;  
  
  always @ (posedge clk) begin  
    count <= count+1;  
  end  
endmodule
```

Example 2: 4-bit Counter

- Logic diagram

 

- Verilog

4-bit counter with enable

```
module counter(clk,enb,count);  
  input clk,enb;  
  output [3:0] count;  
  reg [3:0] count;  
  
  always @ (posedge clk) begin  
    count <= enb ? count+1 : count;  
  end  
endmodule
```


Could I use the following instead?

```
if (enb) count <= count+1;
```



Example 2: 4-bit Counter

- Logic diagram

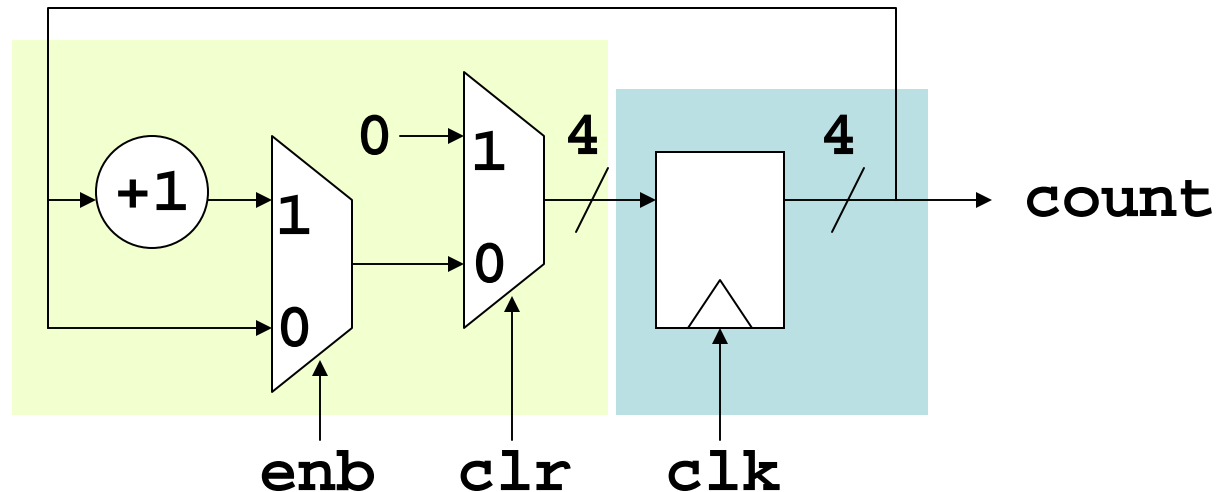

- Verilog

4-bit counter with enable and synchronous clear

```
module counter(clk,enb,clr,count);  
  input  clk,enb,clr;  
  output [3:0] count;  
  reg [3:0] count;  
  
  always @ (posedge clk) begin  
    count <= clr ? 4'b0 : (enb ? count+1 : count);  
  end  
endmodule
```


*Isn't this a lot like
Exercise 1 in Lab 2?*




Two Types of FSMs

Moore and Mealy FSMs : different output generation

- Moore FSM:

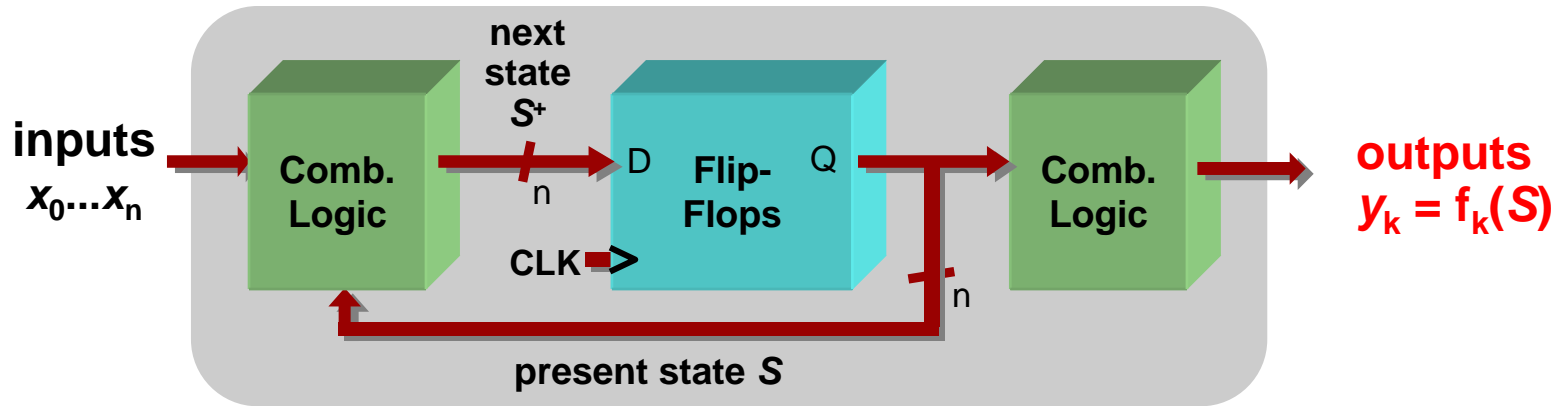


- Mealy FSM:

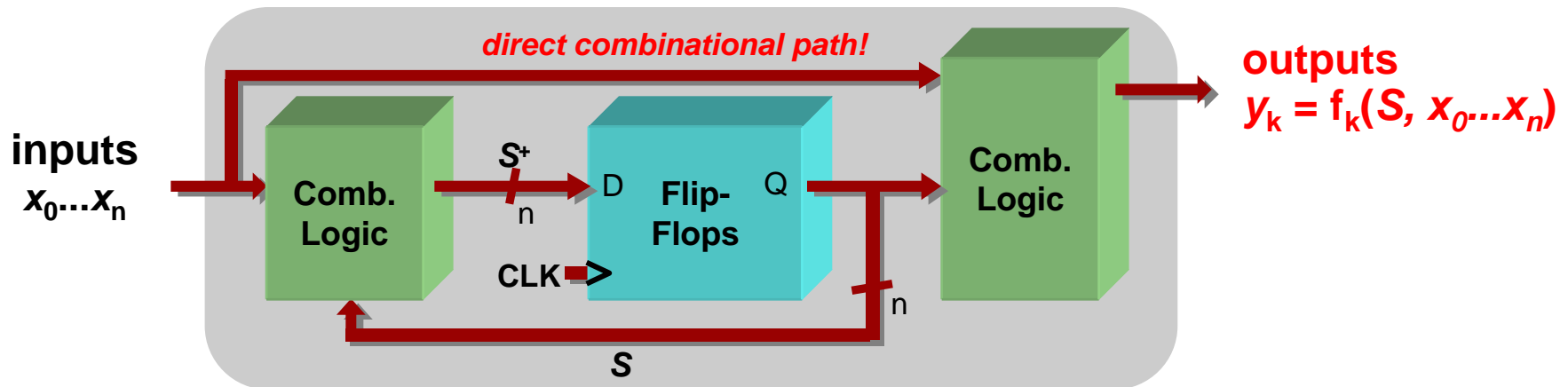


Design Example: Level-to-Pulse

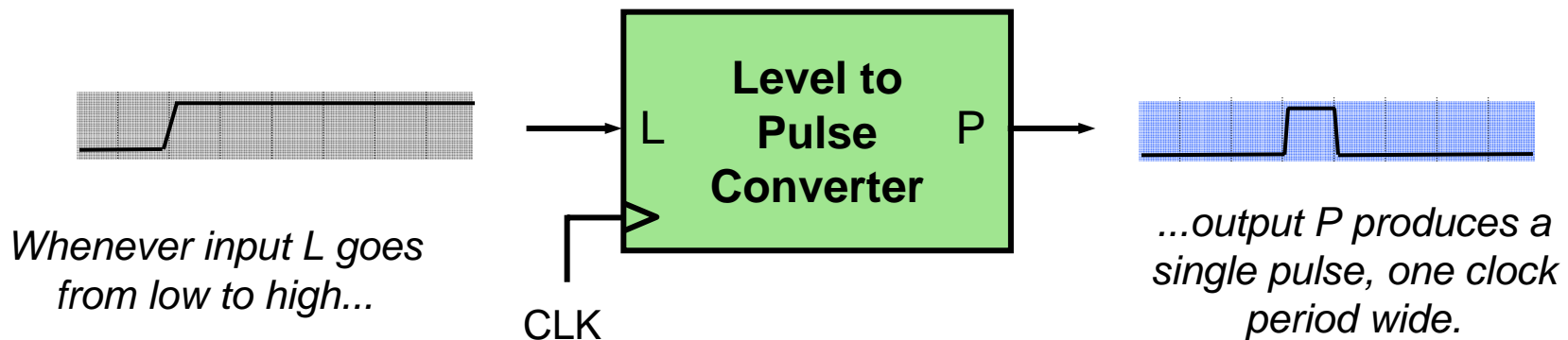- A **level-to-pulse converter** produces a single-cycle pulse each time its input goes high.
- It's a synchronous rising-edge detector.
- Sample uses:
 - Buttons and switches pressed by humans for arbitrary periods of time
 - Single-cycle enable signals for counters




Step 1: State Transition Diagram

- Block diagram of desired system:

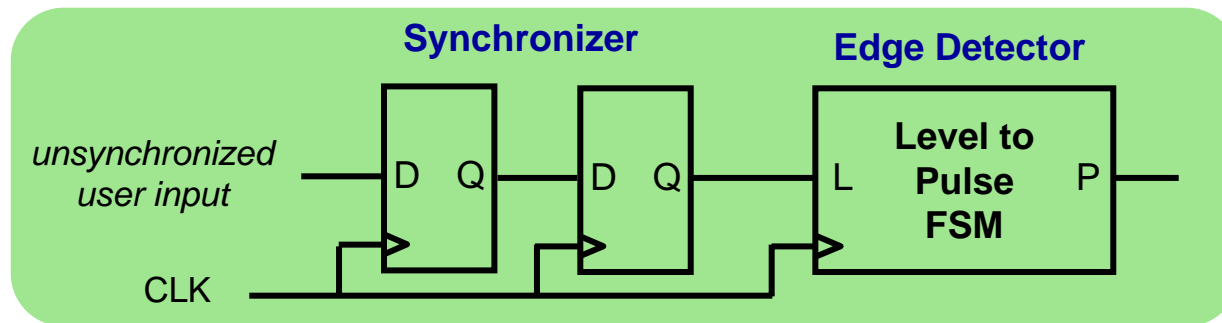


 - State transition diagram** is a useful FSM representation and design aid:




Step 2: Logic Derivation

 Transition diagram is readily converted to a state transition table (just a truth table)




Current t State		In	Next State		Out
S_1	S_0	L	S_1^+	S_0^+	P
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	1
1	1	0	0	0	0
1	1	1	1	1	0

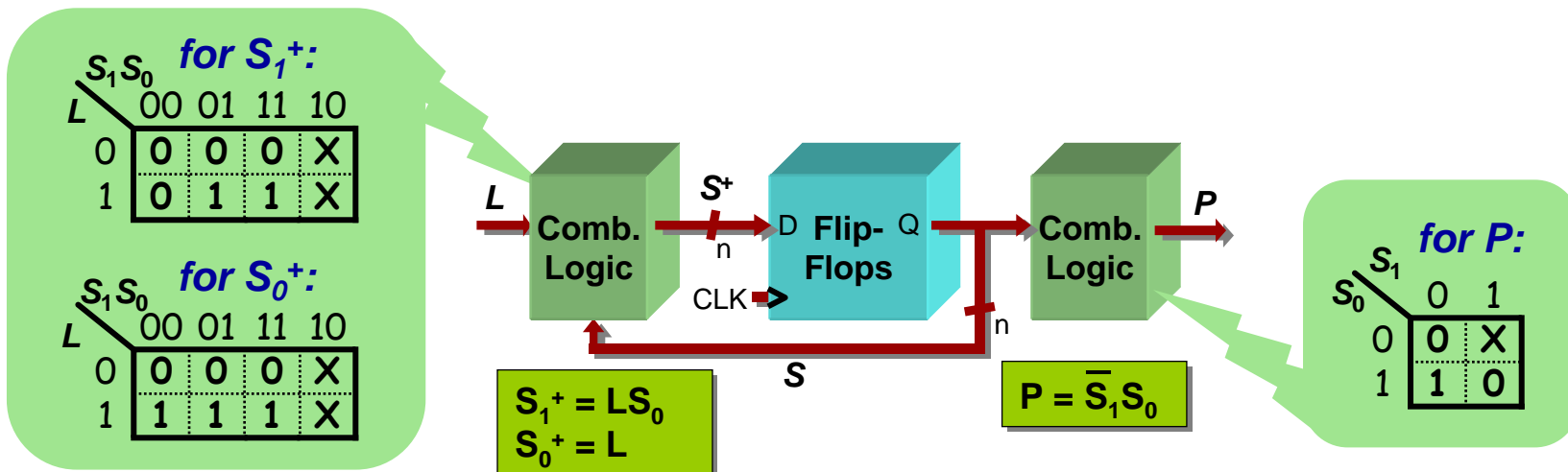
- Combinational logic may be derived using Karnaugh maps




Moore Level-to-Pulse Converter

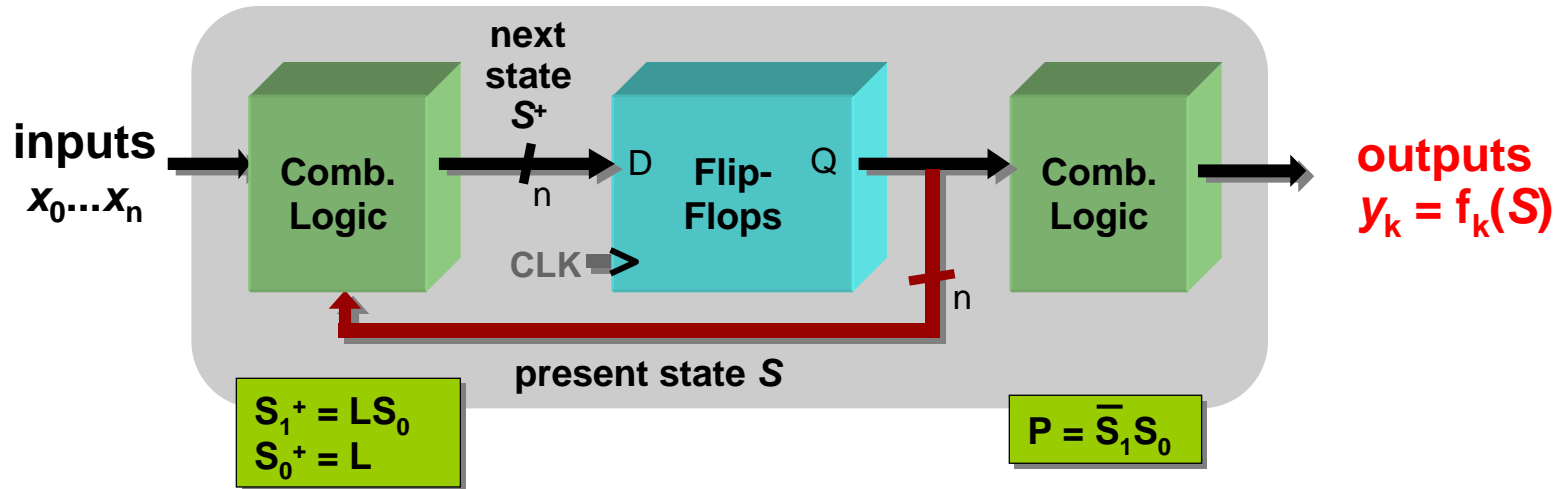

 
Moore FSM circuit implementation of level-to-pulse converter:




Design of a Mealy Level-to-Pulse

 

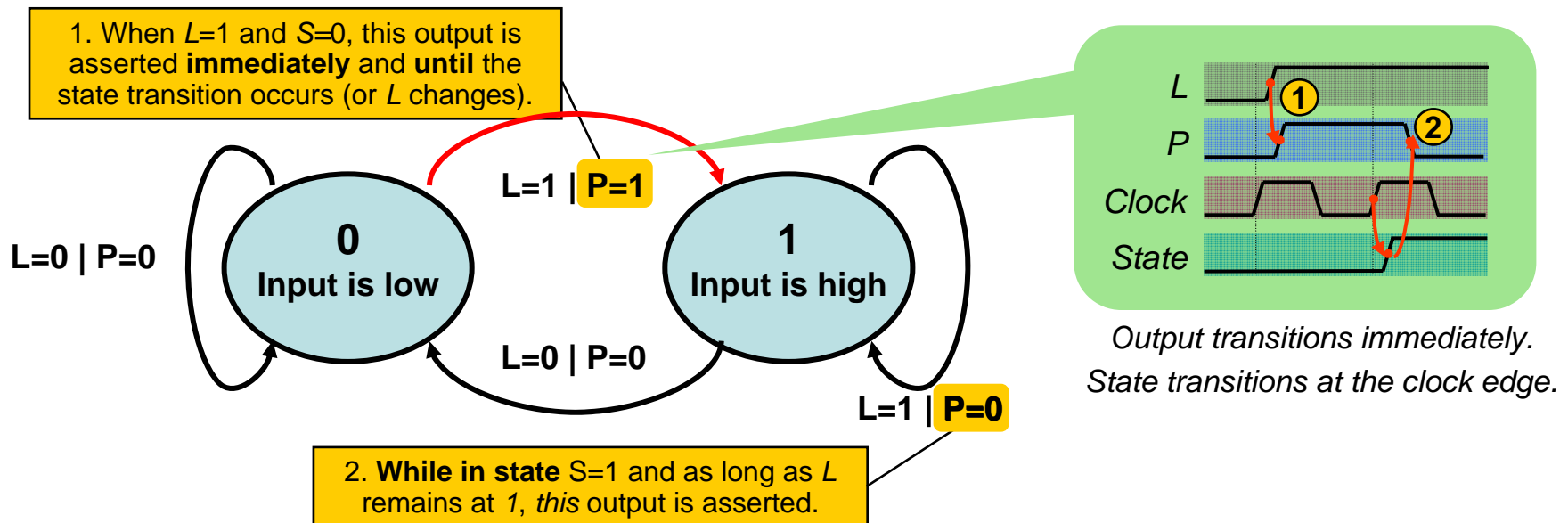- Since outputs are determined by state *and* inputs, Mealy FSMs may need fewer states than Moore FSM implementations




Mealy Level-to-Pulse Converter

 

Pres. State	In	Next State	Out
S	L	S⁺	P
0	0	0	0
0	1	1	1
1	0	0	0
1	1	1	0


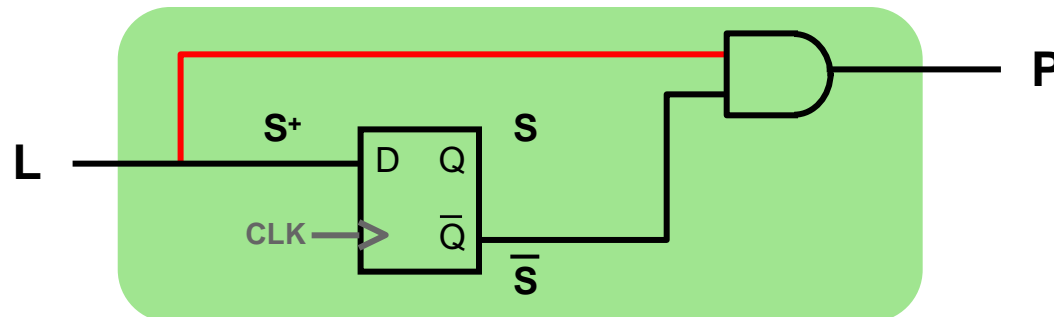
Mealy FSM circuit implementation of level-to-pulse converter:



- FSM's state simply remembers the previous value of L
- Circuit benefits from the Mealy FSM's implicit single-cycle assertion of outputs during state transitions

Moore/Mealy Trade-Offs

  - How are they different?
 - Moore: **outputs = f(state)** only
 - Mealy **outputs = f(state *and* input)**
 - Mealy outputs generally occur one cycle earlier than a Moore:




- Compared to a Moore FSM, a Mealy FSM might...
 - Be more difficult to conceptualize and design
 - Have fewer states

FSM Timing Requirements


- Timing requirements for FSM are identical to any generic sequential system with feedback

Minimum Clock Period

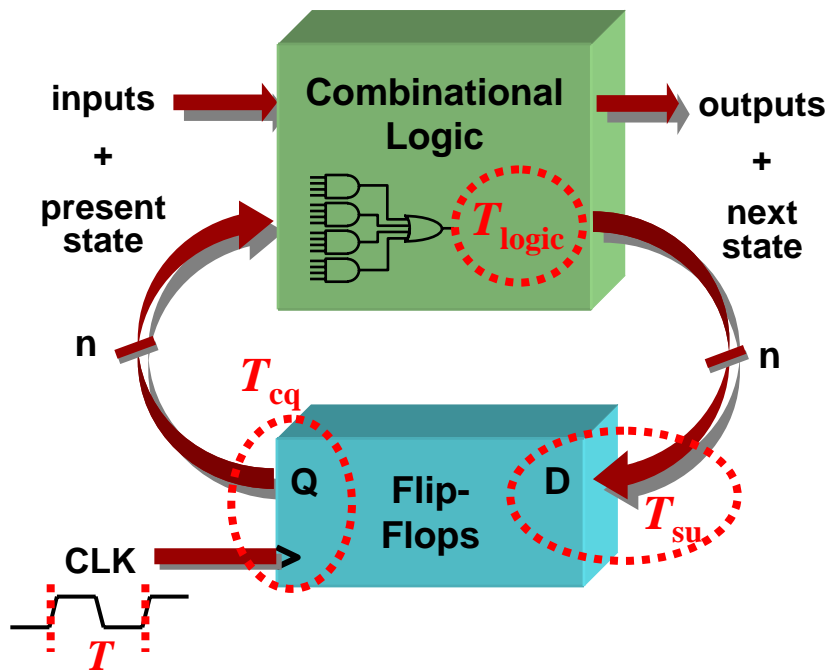

$$T > T_{cq} + T_{logic} + T_{su}$$

Minimum Delay

 

$$T_{cd,reg} + T_{cd,logic} > T_{hold}$$

Summary

- Assignments in always blocks:
 - blocking ("`=`") for combinational logic
 - non-blocking ("`<=`") for sequential logic
- **Single-clock Synchronous discipline:**
 - Reliable digital circuits / systems
 - Global clock to edge-triggered registers
- **Finite state machines:**
 - Programmable systems
 - Moore & Mealy

