 


6.111 Lecture 12

Today: Arithmetic: Addition & Subtraction

1. Binary representation
2. Addition and subtraction
3. Speed: Ripple-Carry
4. Carry-bypass adder
5. Carry-lookahead adder



Acknowledgements:

- R. Katz, "Contemporary Logic Design", Addison Wesley Publishing Company, Reading, MA, 1993. (Chapter 5)
- J. Rabaey, A. Chandrakasan, B. Nikolic, "Digital Integrated Circuits: A Design Perspective" Prentice Hall, 2003.
- Kevin Atkinson, Alice Wang, Rex Min

1. Binary Representation of Numbers

How to represent negative numbers?



- Three common schemes:
 - sign-magnitude, ones complement, twos complement
- Sign-magnitude: MSB = 0 for positive, 1 for negative
 - Range: $-(2^{N-1} - 1)$ to $+(2^{N-1} - 1)$
 - **Two representations** for zero: 0000... & 1000...
 - **Simple multiplication but complicated addition/subtraction**
- Ones complement: if N is positive then its negative is \bar{N}
 - Example: 0111 = 7, 1000 = -7
 - Range: $-(2^{N-1} - 1)$ to $+(2^{N-1} - 1)$
 - **Two representations** for zero: 0000... & 1111...
 - Subtraction is addition followed by ones complement

Negative Numbers: Twos Complement

Twos complement = bitwise complement + 1

0111 → 1000 + 1 = 1001 = -7
 1001 → 0110 + 1 = 0111 = +7

  - Asymmetric range
- Only one representation for zero
- Simple addition and subtraction
- Most common representation



“sign bit”

Range: -2^{N-1} to $2^{N-1} - 1$

“decimal” point

Twos Complement: Examples & Properties

- 4-bit examples:

4	0100	-4	1100	4	0100	-4	1100
<u>+ 3</u>	<u>0011</u>	<u>+ (-3)</u>	<u>1101</u>	<u>- 3</u>	<u>1101</u>	<u>+ 3</u>	<u>0011</u>
7	0111	-7	11001	1	10001	-1	1111

[Katz'93, chapter 5]

- 8-bit twos complement example:

$$11010110 = -2^7 + 2^6 + 2^4 + 2^2 + 2^1 = -128 + 64 + 16 + 4 + 2 = -42$$

- With twos complement representation for signed integers, the same binary addition procedure works for adding both signed and unsigned numbers.

- By moving the implicit location of "decimal" point, we can represent fractions too:

$$1101.0110 = -2^3 + 2^2 + 2^0 + 2^{-2} + 2^{-3} = -8 + 4 + 1 + 0.25 + 0.125 = -2.25$$

2. Binary Addition & Subtraction

Addition:


Here's an example of binary addition as one might do it by "hand":

Adding two N-bit numbers produces an (N+1)-bit result


$$\begin{array}{r} 1101 \\ + 0101 \\ \hline 10010 \end{array}$$

Carries from previous column

 We've already built the circuit that implements one column:



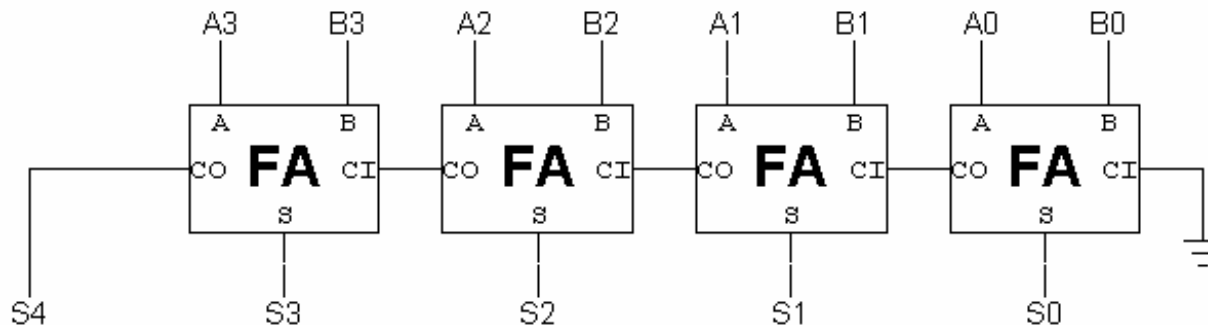So we can quickly build a circuit to add two 4-bit numbers...



"Ripple-carry adder"


Subtraction: $A - B = A + (-B)$

Using 2's complement representation: $-B = \sim B + 1$

\sim = bit-wise complement



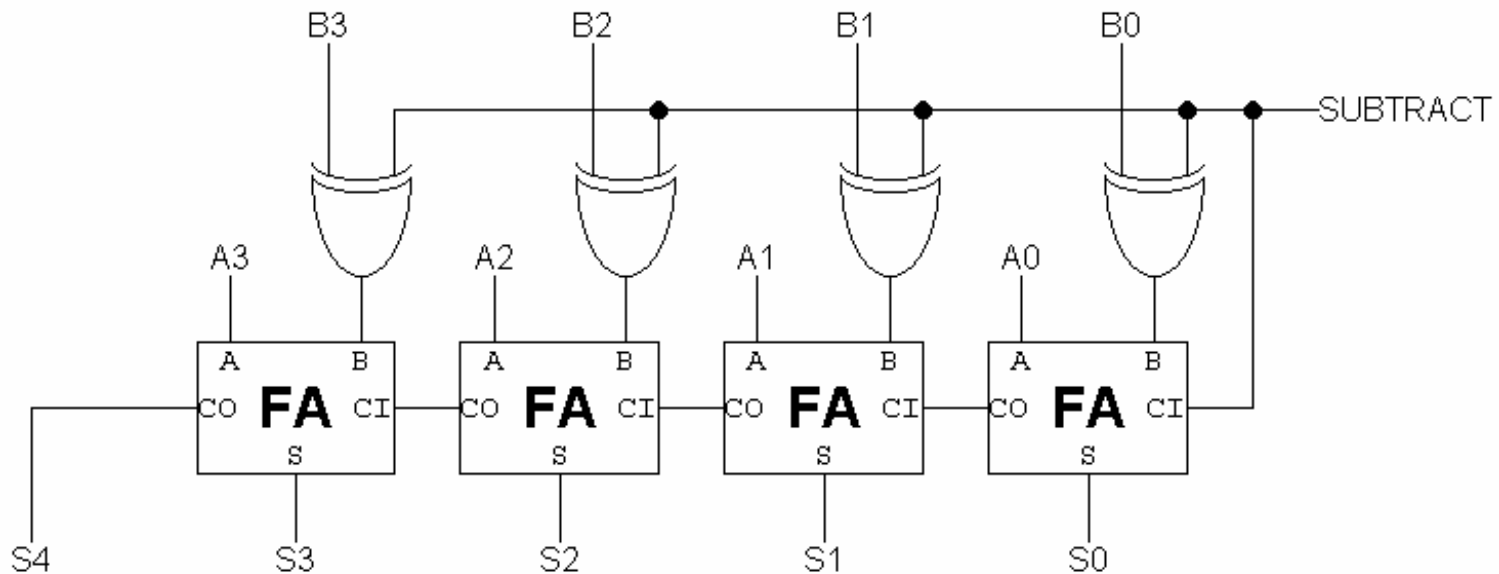So let's build an arithmetic unit that does both addition and subtraction. Operation selected by *control input*:



Condition Codes

Besides the sum, one often wants four other bits of information from an arithmetic unit:

Z (zero): result is = 0

big NOR gate

N (negative): result is < 0

S_{N-1}

C (carry): indicates an add in the most significant position produced a carry, e.g., 1111 + 0001

from last FA

V (overflow): indicates that the answer has too many bits to be represented correctly by the result width, e.g., 0111 + 0111

$$V = A_{N-1}B_{N-1}\overline{S_{N-1}} + \overline{A_{N-1}}\overline{B_{N-1}}S_{N-1}$$

$$V = COUT_{N-1} \oplus CIN_{N-1}$$

To compare A and B, perform A-B and use condition codes:


Signed comparison:

LT	$N \oplus V$
LE	$Z + (N \oplus V)$
EQ	Z
NE	$\sim Z$
GE	$\sim (N \oplus V)$
GT	$\sim (Z + (N \oplus V))$

Unsigned comparison:

LTU	C
LEU	$C + Z$
GEU	$\sim C$
GTU	$\sim (C + Z)$

3. Speed: t_{PD} of Ripple-carry Adder

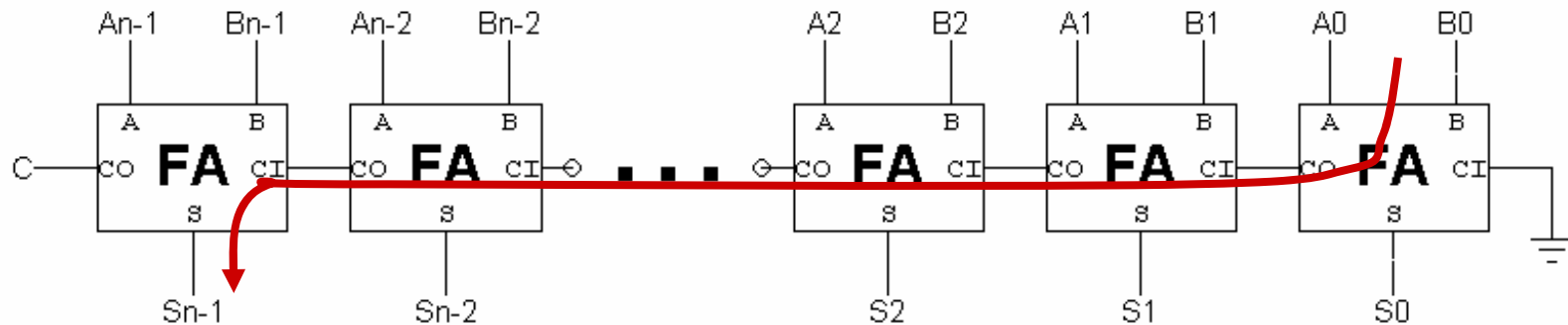

Worse-case path: carry propagation from LSB to MSB, e.g., when adding 11...111 to 00...001.


$$t_{PD} = (N-1) \underbrace{(t_{PD,OR} + t_{PD,AND})}_{CI \text{ to } CO} + \underbrace{t_{PD,XOR}}_{CI_{N-1} \text{ to } S_{N-1}} \approx \Theta(N)$$

$$t_{adder} = (N-1)t_{carry} + t_{sum}$$

$\Theta(N)$ is read "order N" : means that the latency of our adder grows at worst in proportion to the number of bits in the operands.

Faster carry logic

 Let's see if we can improve the speed by rewriting the equations for C_{OUT} :



$$\begin{aligned}C_{OUT} &= AB + AC_{IN} + BC_{IN} \\ &= AB + (A + B)C_{IN} \\ &= \mathbf{G} + \mathbf{P} C_{IN}\end{aligned}$$

generate propagate

where $G = AB$ and
 $P = A + B$

$$\text{Generate } (G) = AB$$

$$\text{Propagate } (P) = A \oplus B$$


$$C_o(G, P) = G + PC_i$$

$$S(G, P) = P \oplus C_i$$


Actually, P is usually defined as $P = A \oplus B$ which won't change C_{OUT} but will allow us to express S as a simple function :

$$S = P \oplus C_{IN}$$

Virtex II Adder Implementation


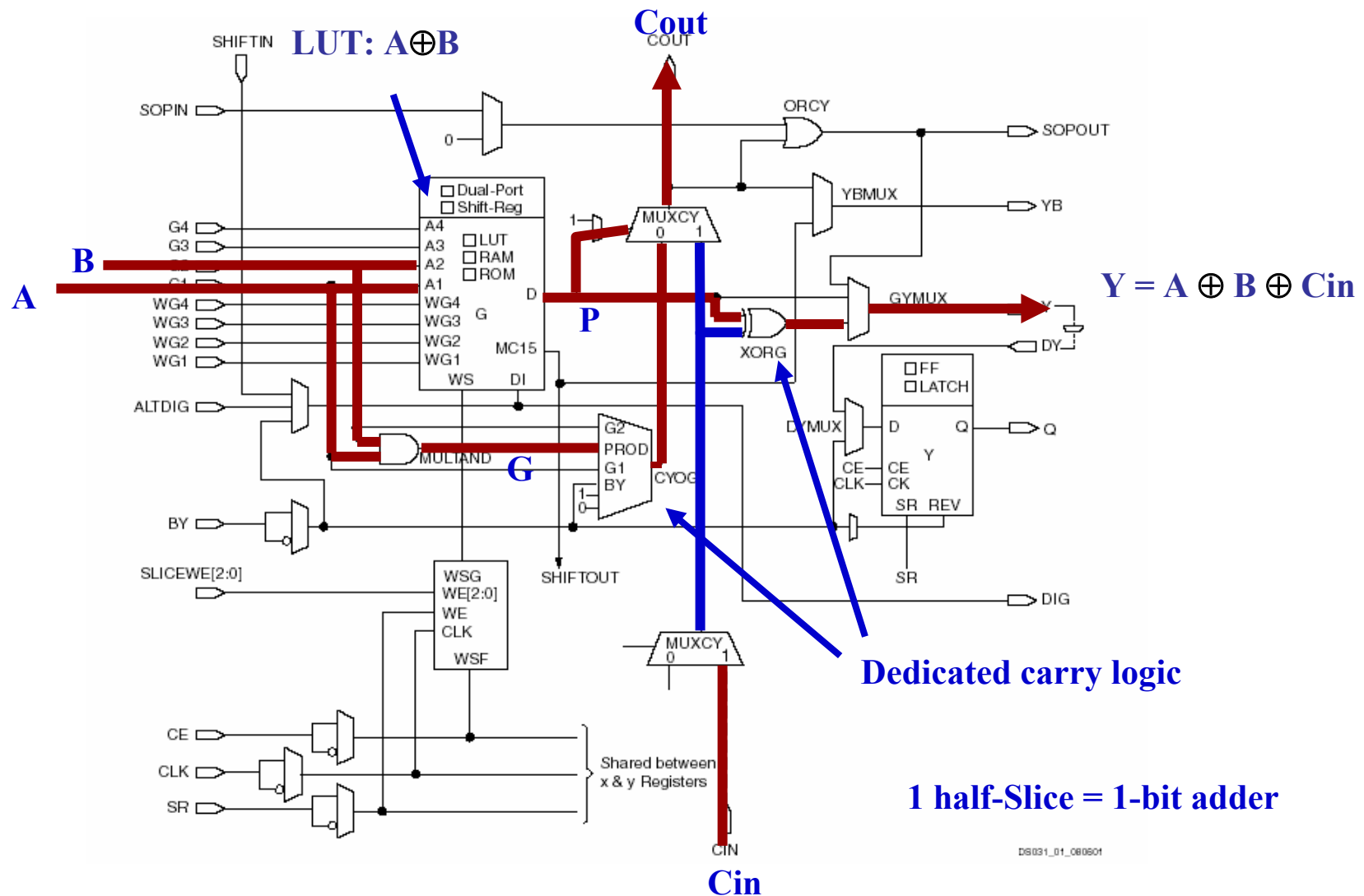


Virtex II Carry Chain

 



1 CLB = 4 Slices = 2, 4-bit adders

64-bit Adder: 16 CLBs

  


CLBs must be in same column

4. Carry Bypass Adder

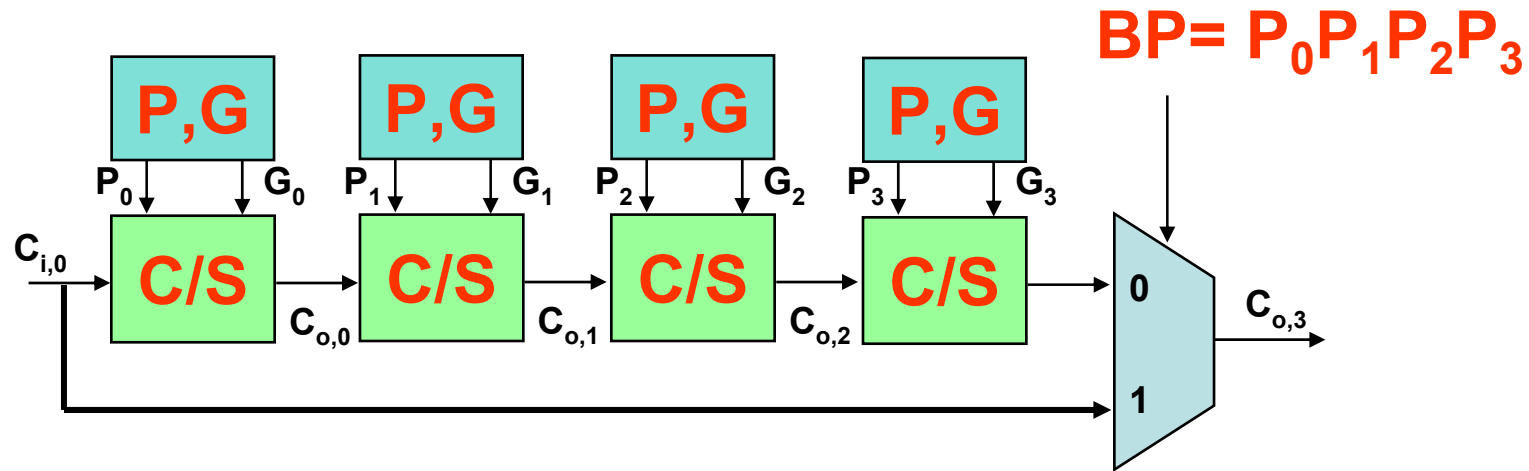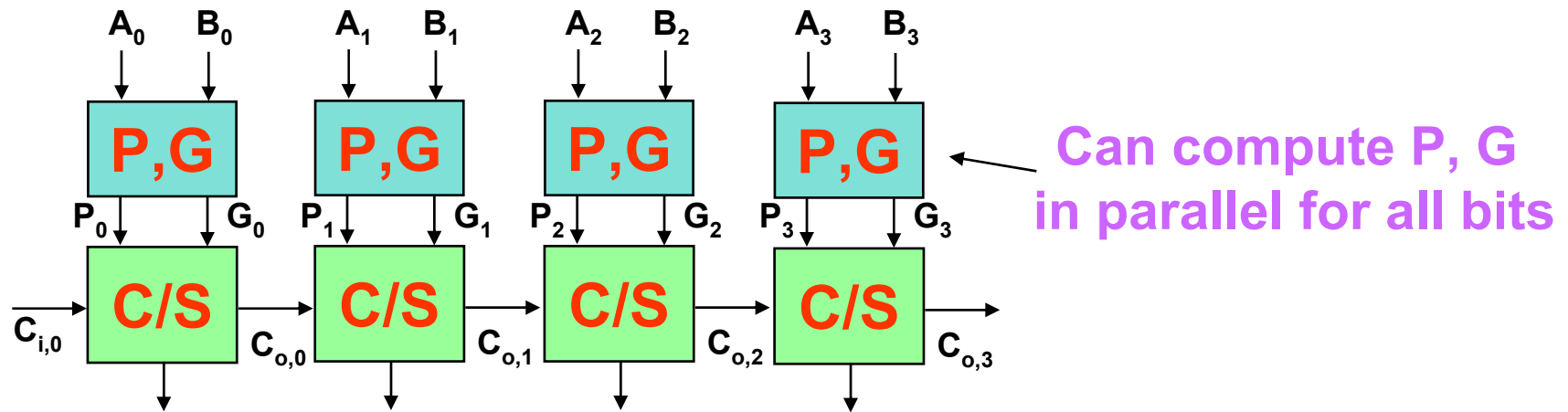

Key Idea: if $(P_0 P_1 P_2 P_3)$ then $C_{o,3} = C_{i,0}$

16-bit Carry Bypass Adder

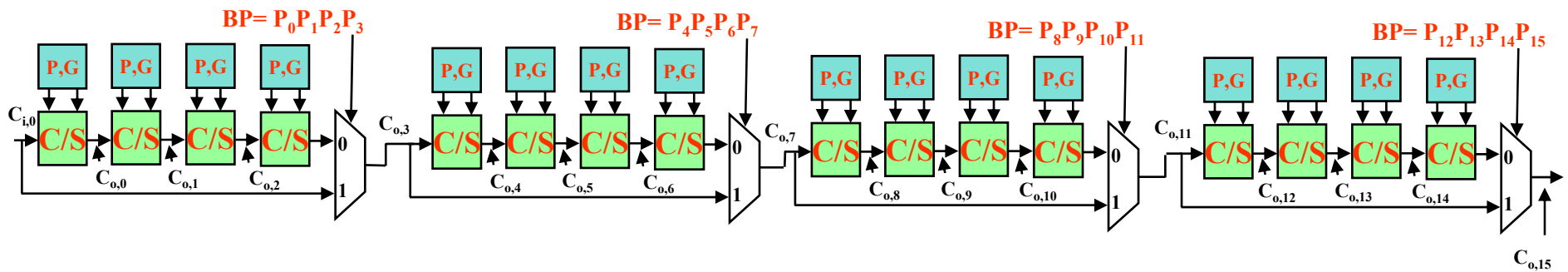

What is the worst case propagation delay for the 16-bit adder?


Assume the following for delay each gate:

P, G from A, B: 1 delay unit

P, G, C_i to C_o or Sum for a C/S: 1 delay unit

2:1 mux delay: 1 delay unit

Critical Path Analysis

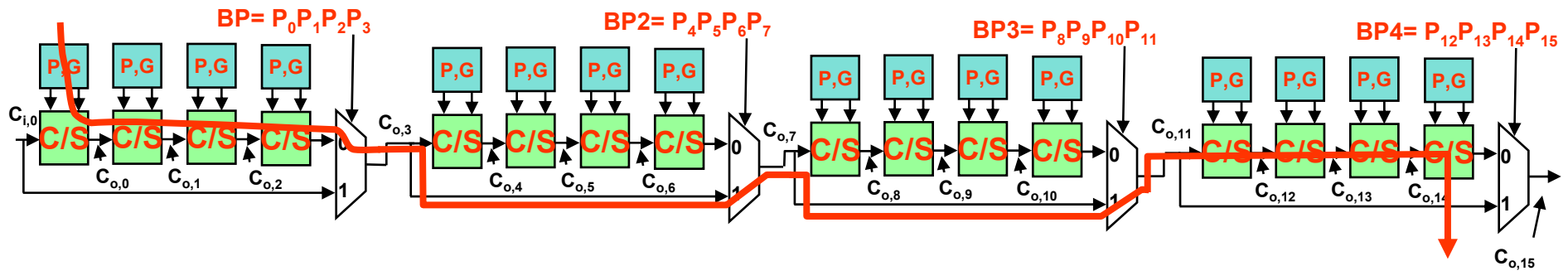

For the second stage, is the critical path:


BP2 = 0 or BP2 = 1 ?

**Message: Timing Analysis is Very Tricky –
Must Carefully Consider Data Dependencies For
False Paths**

Carry Bypass vs Ripple Carry

Ripple Carry: $t_{\text{adder}} = (N-1) t_{\text{carry}} + t_{\text{sum}}$

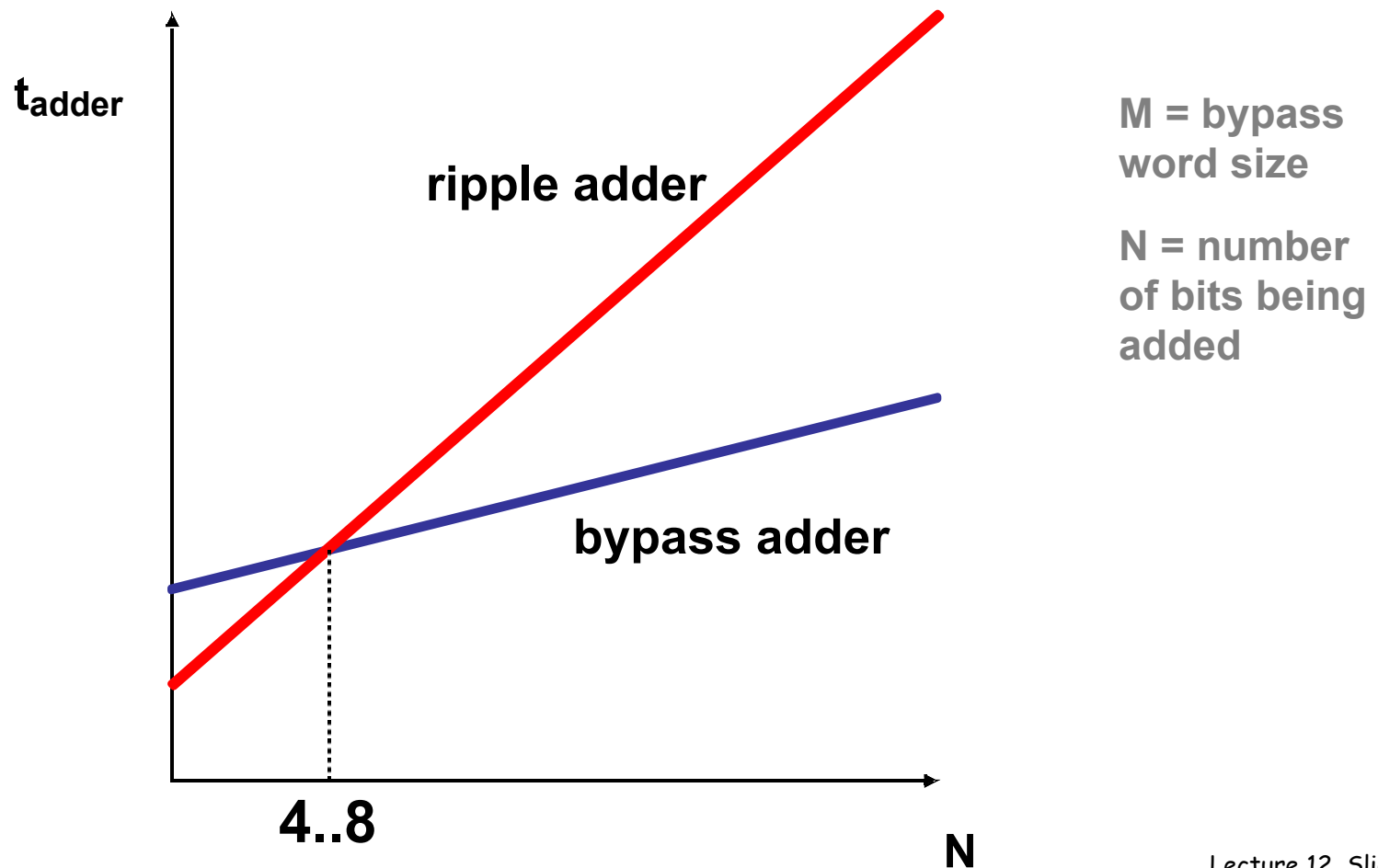Carry Bypass: $t_{\text{adder}} = 2(M-1) t_{\text{carry}} + t_{\text{sum}} + (N/M-1) t_{\text{bypass}}$



5. Carry Lookahead Adder (CLA)

- Recall that $C_{OUT} = G + P C_{IN}$ where $G = AB$ and $P = A \oplus B$
- For adding two N-bit numbers:





$$\begin{aligned}C_N &= G_{N-1} + P_{N-1}C_{N-1} \\ &= G_{N-1} + P_{N-1}G_{N-2} + P_{N-1}P_{N-2}C_{N-2} \\ &= G_{N-1} + P_{N-1}G_{N-2} + P_{N-1}P_{N-2}G_{N-3} + \dots + P_{N-1} \dots P_0 C_{IN}\end{aligned}$$

C_N in only 3 gate delays* :
1 for P/G generation, 1 for ANDs, 1 for final OR

*assuming gates with N inputs



- Idea: pre-compute all carry bits combinatorially

Carry Lookahead Circuits

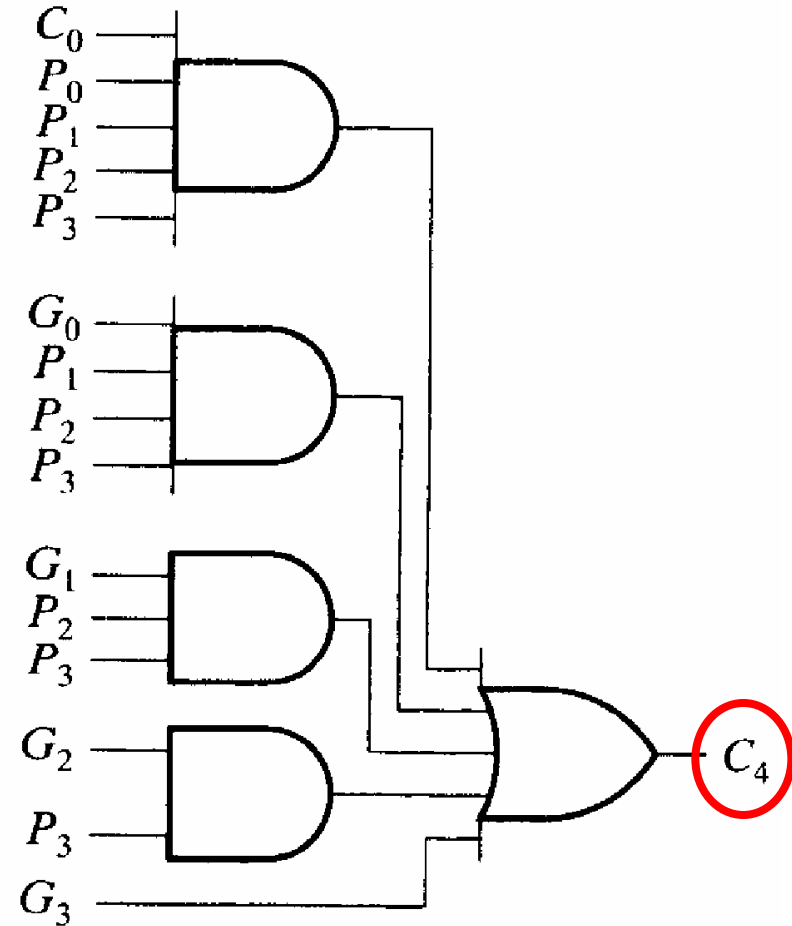   

The 74182 Carry Lookahead Unit

74182 carry lookahead unit

  

Active low example:

$$\begin{aligned}
 C_{n+x} &= \overline{\overline{G_0 \cdot P_0} + \overline{G_0 \cdot C_n}} \\
 &= \overline{\overline{G_0 \cdot P_0} \cdot \overline{G_0 \cdot C_n}} \\
 &= (G_0 + P_0) \cdot (G_0 + C_n) = G_0 + P_0 C_n
 \end{aligned}$$

$$C_4 = G_{3:0} + P_{3:0} C_n$$

$$C_{n+y} = C_8 = G_{7:4} + P_{7:4} G_{3:0} + P_{7:4} P_{3:0} C_{i,0} = G_{7:0} + P_{7:0} C_n$$

$$\begin{aligned}
 C_{n+z} = C_{12} &= G_{11:8} + P_{11:8} G_{7:4} + P_{11:8} P_{7:4} G_{3:0} + P_{11:8} P_{7:4} P_{3:0} C_n \\
 &= G_{11:0} + P_{11:0} C_n
 \end{aligned}$$

- high speed carry lookahead generator
- used with 74181 to extend carry lookahead beyond 4 bits
- correctly handles the carry polarity of the 181

Block Generate and Propagate

G and P can be computed for groups of bits (instead of just for individual bits). This allows us to choose the maximum fan-in we want for our logic gates and then build a hierarchical carry chain using these equations:


$$C_{J+1} = G_{IJ} + P_{IJ}C_I$$

$$G_{IK} = G_{J+1,K} + P_{J+1,K} G_{IJ}$$

$$P_{IK} = P_{IJ} P_{J+1,K}$$


"generate a carry from bits I thru K if it is generated in the high-order ($J+1, K$) part of the block or if it is generated in the low-order (I, J) part of the block and then propagated thru the high part"

where $I < J$ and $J+1 < K$

 


P/G generation

1st level of lookahead

 


Hierarchical building block

8-bit CLA (P/G generation)

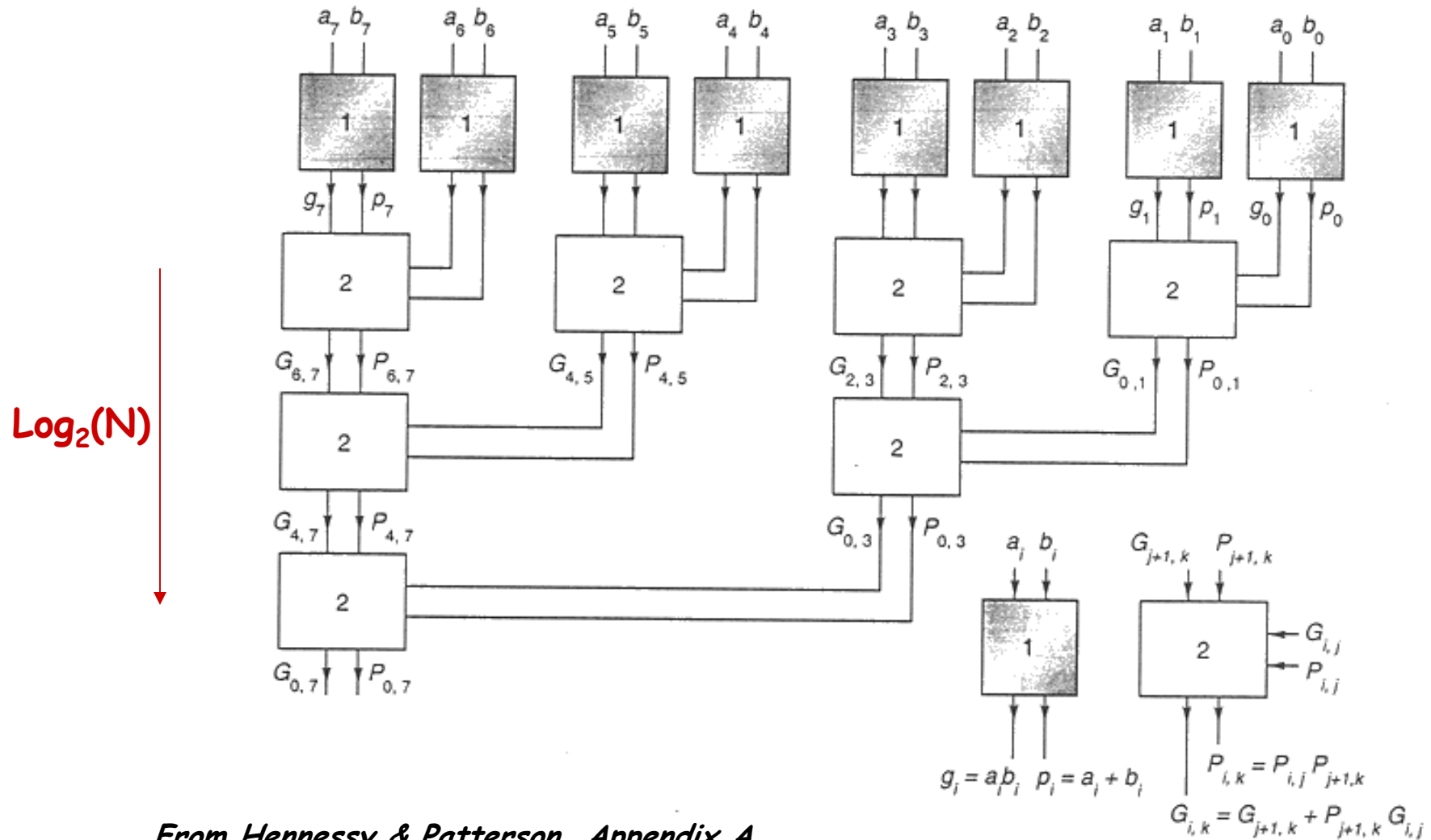


From Hennessy & Patterson, Appendix A

8-bit CLA (carry generation)

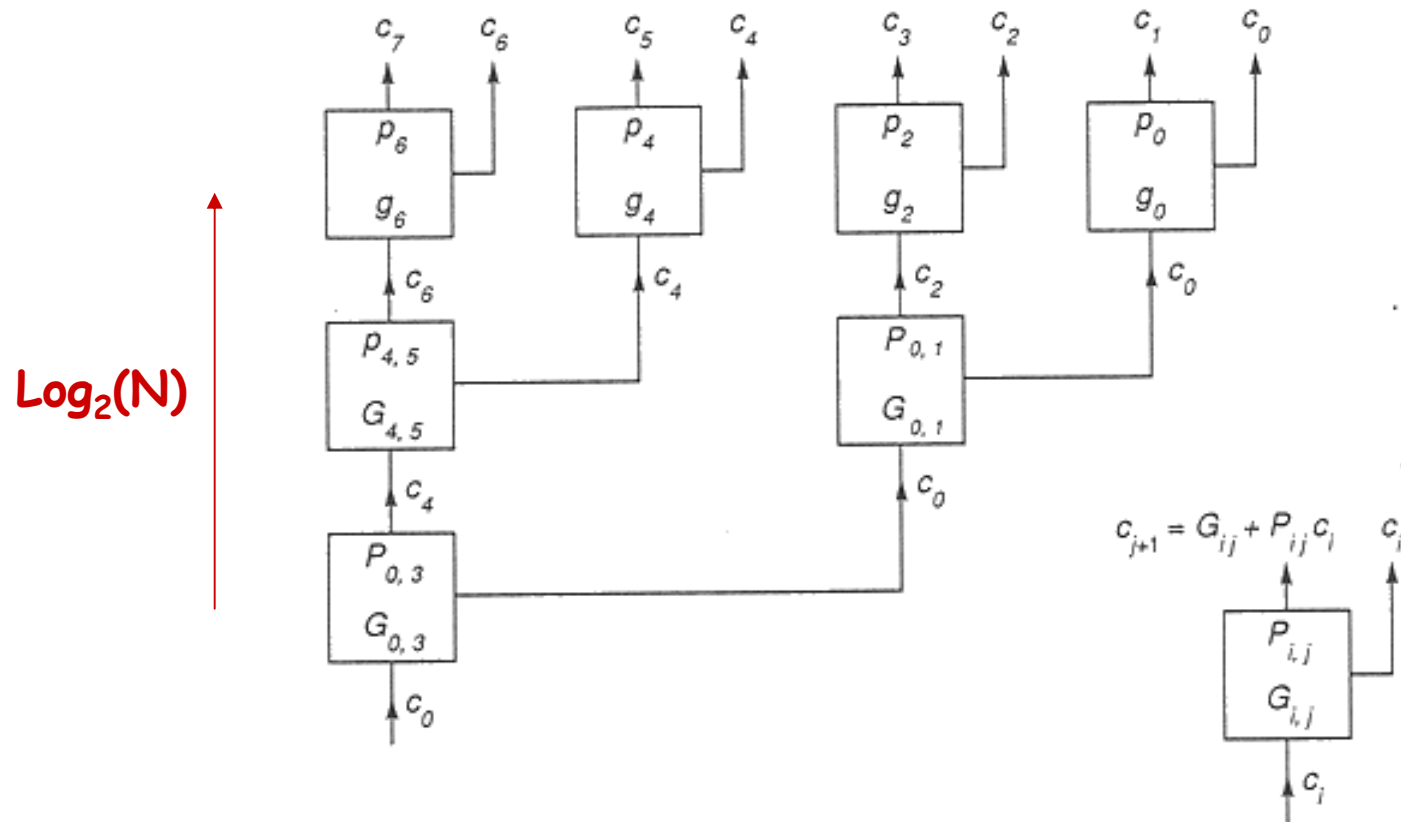


8-bit CLA (complete)

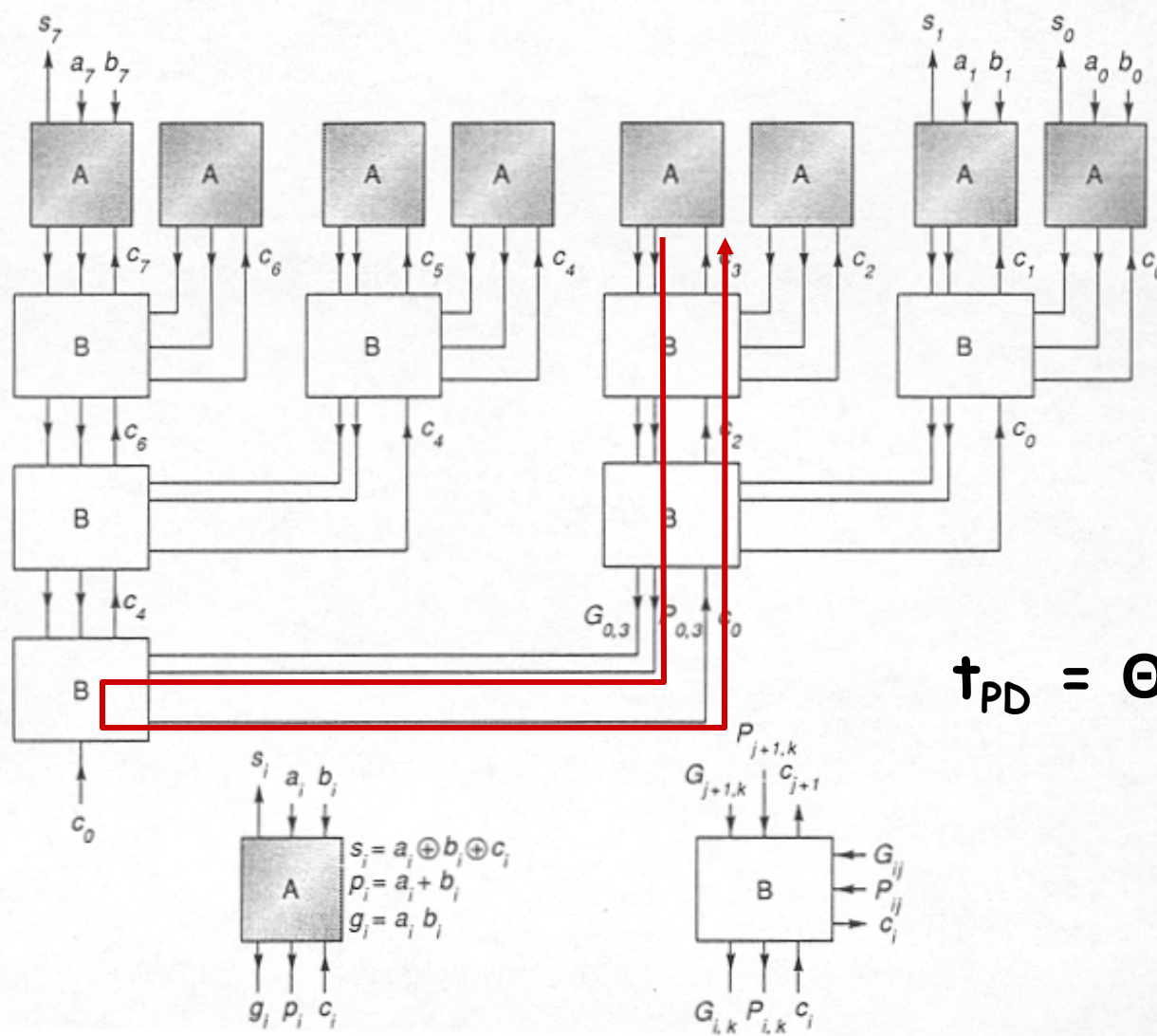

$$t_{PD} = \Theta(\log(N))$$

Summary

 


- Negative numbers:**

- Twos Complement $-B = \bar{B} + 1$
- Addition & Subtraction use same adder

- Ripple Carry Adder:**

 - $t_{\text{adder}} = (N-1) t_{\text{carry}} + t_{\text{sum}}$



- Carry Bypass Adder:**

- $t_{\text{adder}} \approx (M-1) t_{\text{carry}} + t_{\text{sum}} + (N/M-1) t_{\text{bypass}}$

- Carry Lookahead Adder:**

- $t_{\text{adder}} \approx 2 \log_2(N) t_{\text{pg}}$

