 


The Last Lecture!


1. Schedule
2. FSM++
3. FGPA's @ Home



Schedule Reminders

- Fri, 10/27: Lab #5 checkoff by 5pm
- Mon, 10/30: upload CI-M Final Version by 5pm
upload Project Abstract by 5pm
- Wed, 11/01: Quiz, 7:30p - 9:30p, 50-340
- Fri, 11/03: complete proposal meeting with TA
upload Project Proposal by 5pm
- Fri, 11/10: complete block diagram meeting with TA
- M, Tu, W : 15min design presentations
11/12-15 schedule TBA (we'll email you!)
please upload slides to website
- Fri, 11/17: upload Project Checklist by 5pm
- M, Tu, W : project presentations & videotaping
12/11-13 schedule TBA (we'll email you!)
- Wed, 12/13: upload Final Project Report by 5pm
(sorry, no extensions possible!)


Digital Systems = FSMs + Datapath

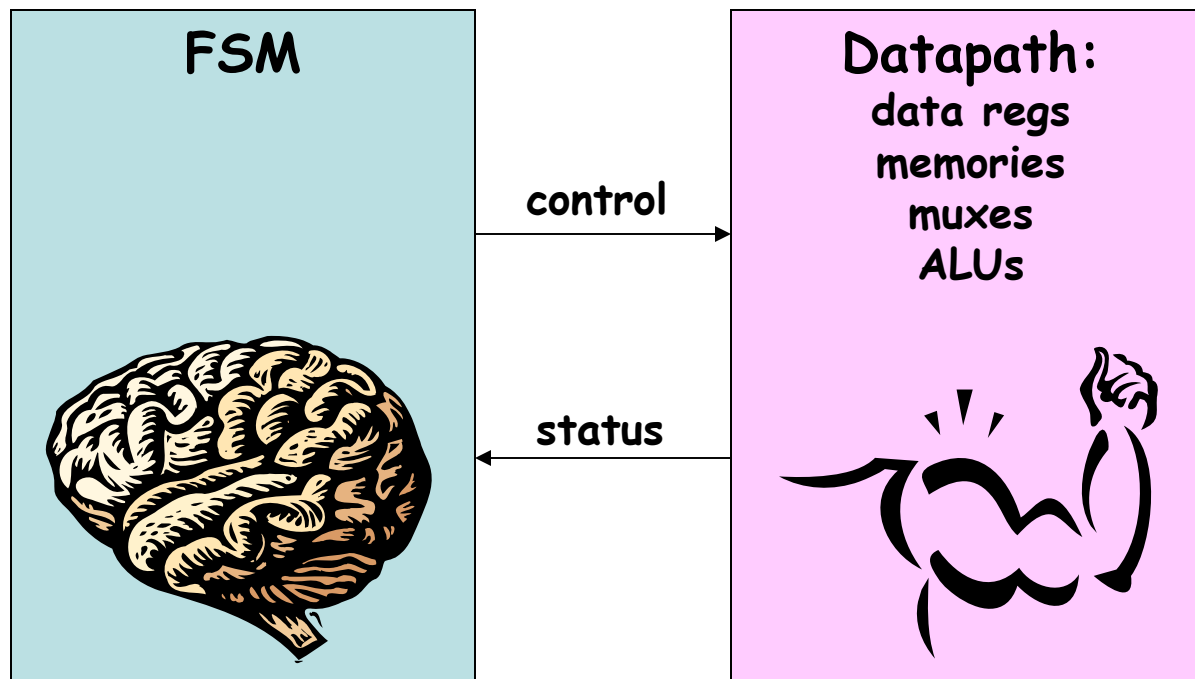


But what if my FSM has hundreds or thousands of states? That's a BIG case statement!

Microsequencers

Step 1: use a counter for the state

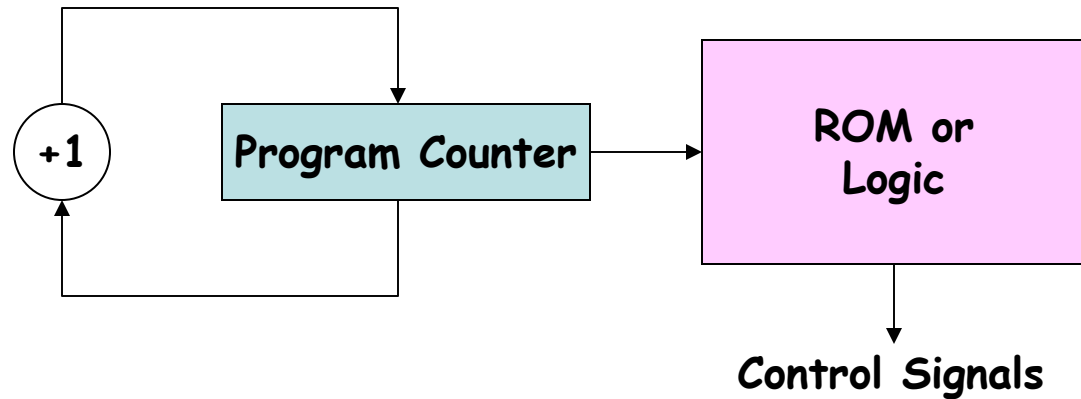


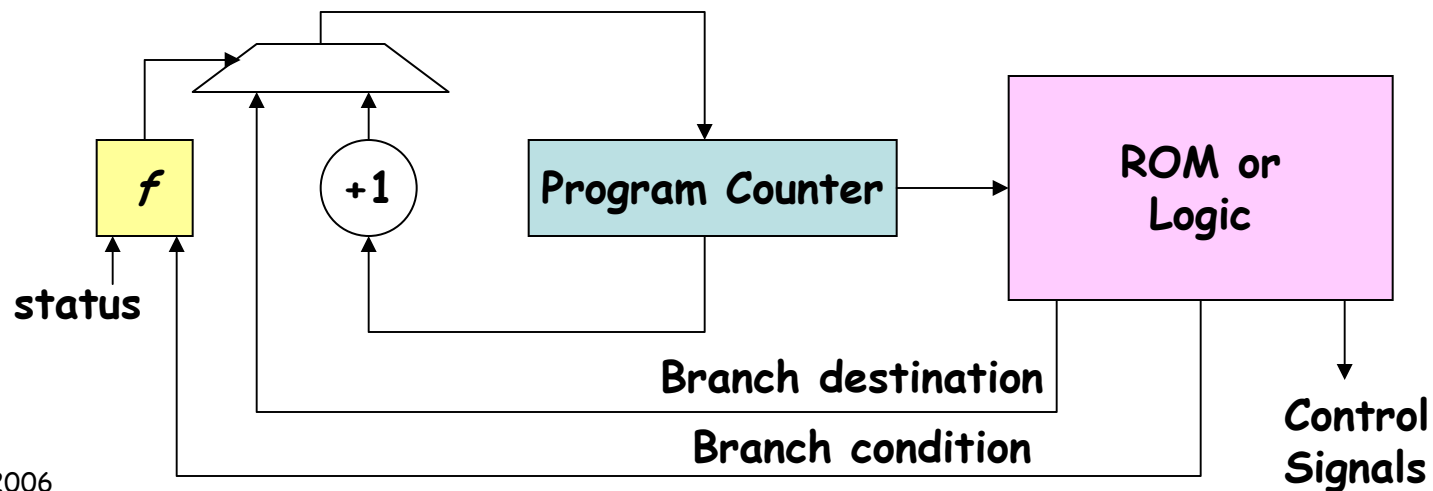Step 2: add a conditional branch mechanism




Microsequencers (cont'd.)

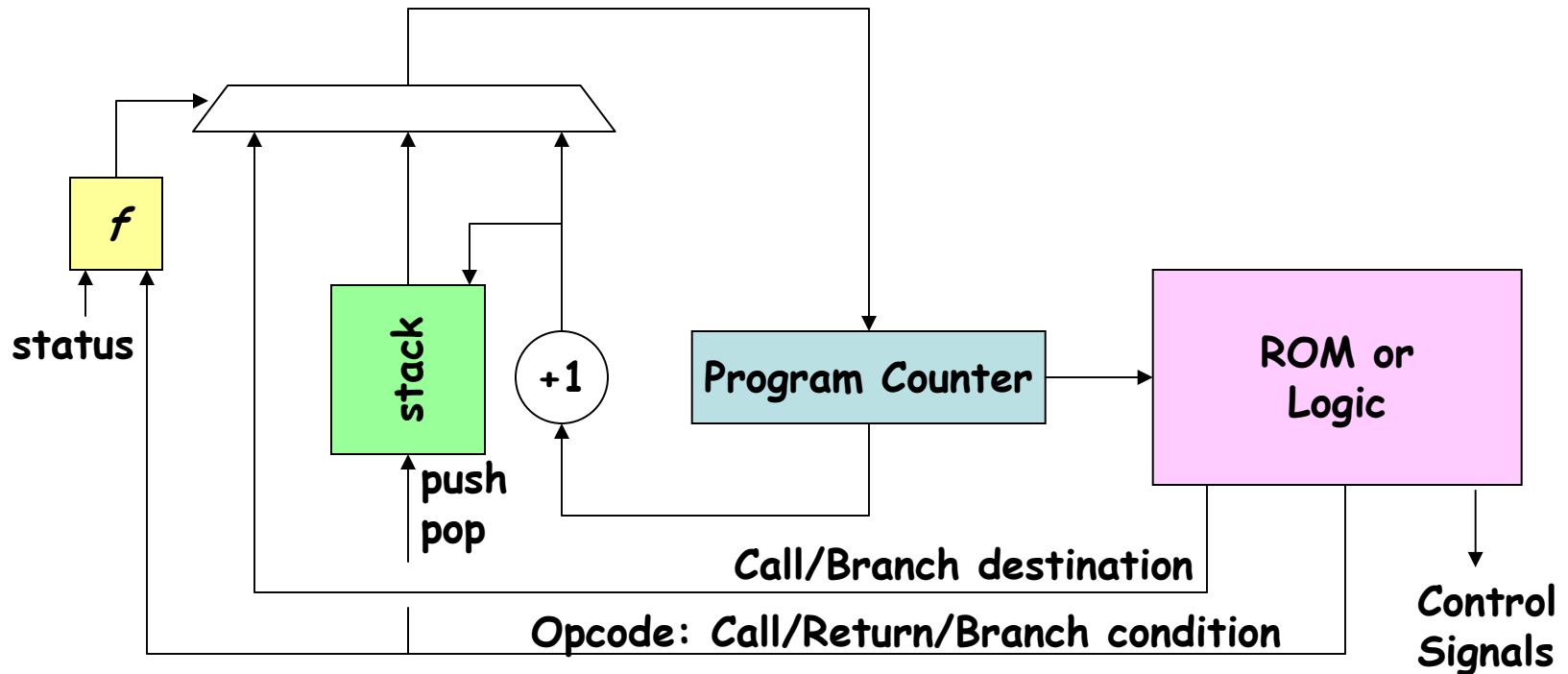Step 3: add a (small) call/return stack to support "subroutines"



Subroutine call: select destination as new PC, push PC+1 onto stack
Subroutine return: select top of stack as new PC, pop stack

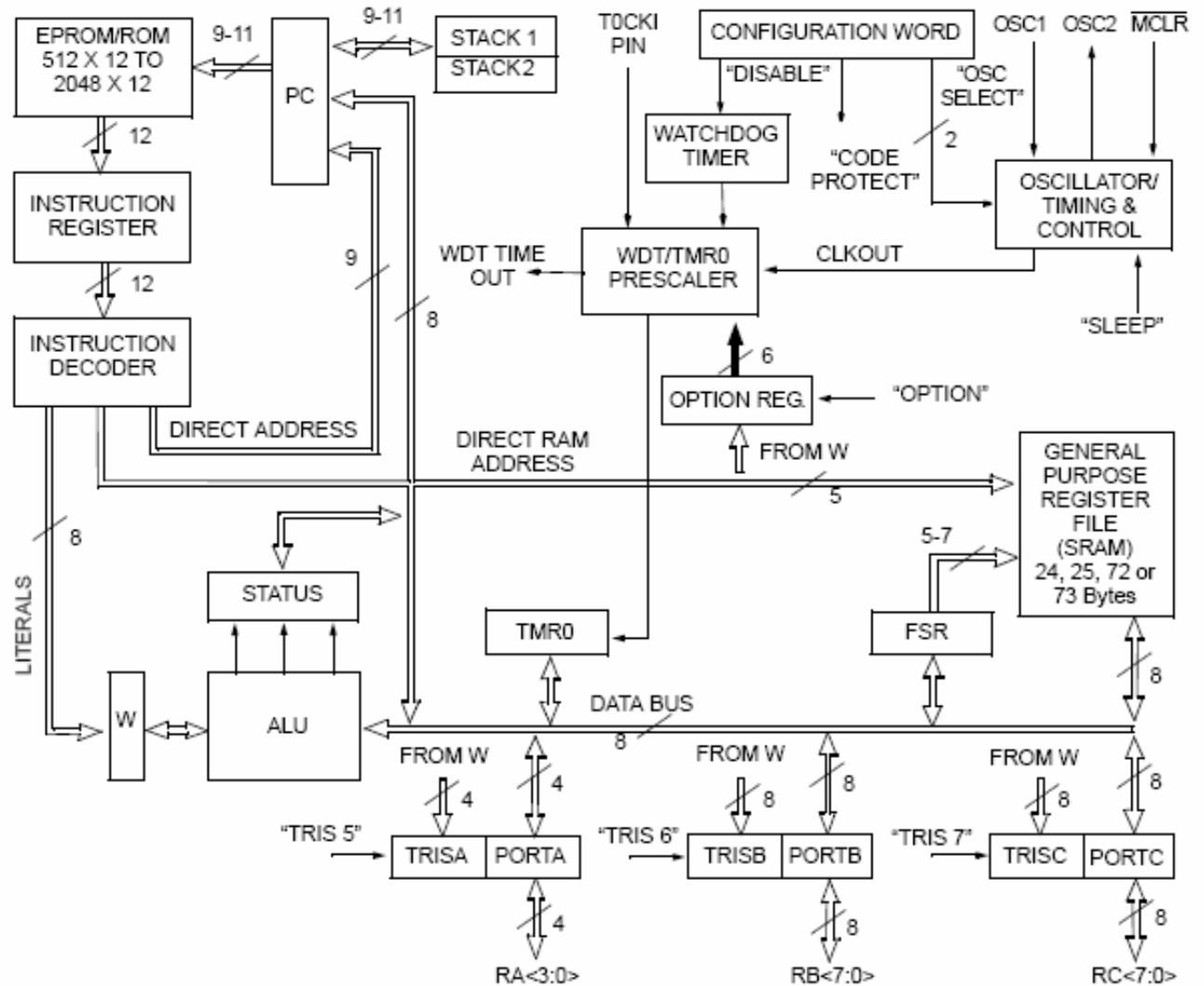PIC Processor: Microsequencer + general-purpose datapath



PIC Instruction Set

Mnemonic, Operands	Description	Cycles	12-Bit Opcode			Status Affected
			MSb		LSb	
ADDWF f,d	Add W and f	1	0001	11df	ffff	C,DC,Z
ANDWF f,d	AND W with f	1	0001	01df	ffff	Z
CLRF f	Clear f	1	0000	011f	ffff	Z
CLRW -	Clear W	1	0000	0100	0000	Z
COMF f,d	Complement f	1	0010	01df	ffff	Z
DECf f,d	Decrement f	1	0000	11df	ffff	Z
DECFSZ f,d	Decrement f, Skip if 0	1 ⁽²⁾	0010	11df	ffff	None
INCF f,d	Increment f	1	0010	10df	ffff	Z
INCFSZ f,d	Increment f, Skip if 0	1 ⁽²⁾	0011	11df	ffff	None
IORWF f,d	Inclusive OR W with f	1	0001	00df	ffff	Z
MOVF f,d	Move f	1	0010	00df	ffff	Z
MOVWF f	Move W to f	1	0000	001f	ffff	None
NOP -	No Operation	1	0000	0000	0000	None
RLF f,d	Rotate left f through Carry	1	0011	01df	ffff	C
RRF f,d	Rotate right f through Carry	1	0011	00df	ffff	C
SUBWF f,d	Subtract W from f	1	0000	10df	ffff	C,DC,Z
SWAPF f,d	Swap f	1	0011	10df	ffff	None
XORWF f,d	Exclusive OR W with f	1	0001	10df	ffff	Z
BIT-ORIENTED FILE REGISTER OPERATIONS						
BCF f,b	Bit Clear f	1	0100	bbbb	ffff	None
BSF f,b	Bit Set f	1	0101	bbbb	ffff	None
BTFSC f,b	Bit Test f, Skip if Clear	1 ⁽²⁾	0110	bbbb	ffff	None
BTFSS f,b	Bit Test f, Skip if Set	1 ⁽²⁾	0111	bbbb	ffff	None
LITERAL AND CONTROL OPERATIONS						
ANDLW k	AND literal with W	1	1110	kkkk	kkkk	Z
CALL k	Call subroutine	2	1001	kkkk	kkkk	None
CLRWDT k	Clear Watchdog Timer	1	0000	0000	0100	\overline{TO} , \overline{PD}
GOTO k	Unconditional branch	2	101k	kkkk	kkkk	None
IORLW k	Inclusive OR Literal with W	1	1101	kkkk	kkkk	Z
MOVLW k	Move Literal to W	1	1100	kkkk	kkkk	None
OPTION k	Load OPTION register	1	0000	0000	0010	None
RETLW k	Return, place Literal in W	2	1000	kkkk	kkkk	None
SLEEP -	Go into standby mode	1	0000	0000	0011	\overline{TO} , \overline{PD}
TRIS f	Load TRIS register	1	0000	0000	0fff	None
XORLW k	Exclusive OR Literal to W	1	1111	kkkk	kkkk	Z

PIC Example: Verilog

```
// PIC core
wire [9:0] pc;
wire [11:0] idata;
wire [3:0] porta;
wire [7:0] portb;
pic16c5x pic(.clk(clk),.reset(reset),
            .pc(pc),.idata(idata),           // instruction memory
            .port_a_out(an[3:0]),           // digit select
            .port_b_out(segment[7:0]),      // display segments
            .port_c_in(sw[7:0])             // slide switches
            );
defparam pic.PCMSB = 9;    // 1024 inst locations

// PIC program memory (1024 x 12): test.pic
test pgm({1'b0,pc},~clk,idata);
```


PIC Example: test.pic


```
sw      equ h'0018'
digit  equ h'0019'
count  equ h'001A'
Start   movlw  0
        tris   PORTA      ; ports A and B are outputs
        tris   PORTB
        movlw  h'ff'
        tris   PORTC      ; port C are inputs
        movlw  h'f'
        movwf  PORTA
        clrf   count

Loop
        movlw  h'f'
        movwf  PORTA
        movf   PORTC,0     ; read switches into W
        movwf  sw
        andlw  h'f'        ; keep low 4 bits
        call   Segments
        movwf  PORTB      ; set up segments
        movlw  h'e'
        movwf  PORTA      ; turn on AN[0]


buzz1
        decfsz count,1    ; display this digit for a while
        goto  buzz1
        ...
```

A "Real" Processor: the Beta!

Is this 6.004?????

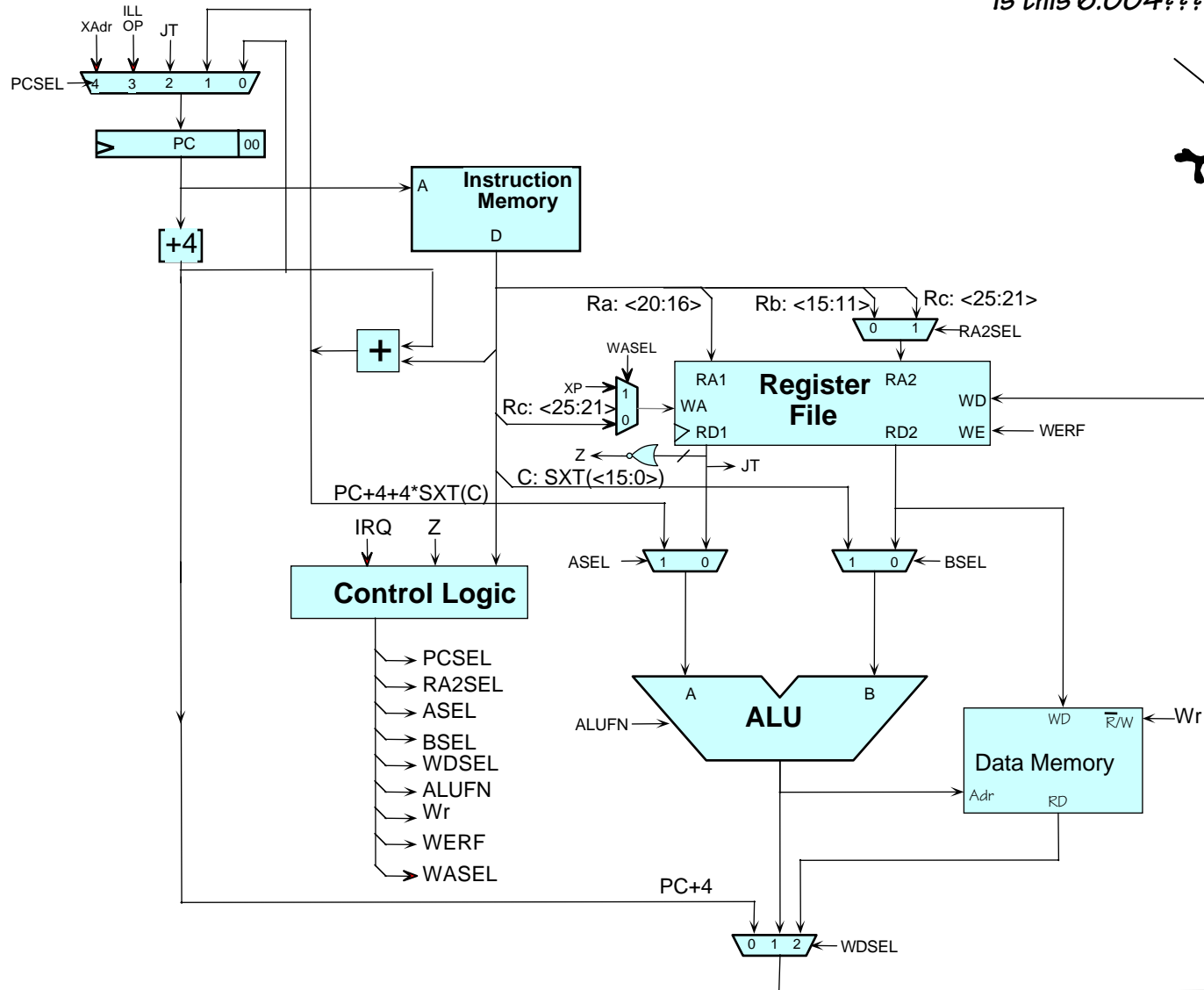


Beta Instructions - I

 

OP(Ra,Rb,Rc): $\text{Reg}[Rc] \leftarrow \text{Reg}[Ra] \text{ op } \text{Reg}[Rb]$

Opcodes:

 ADD (plus), SUB (minus), MUL (multiply), DIV (divided by),
AND (bitwise and), OR (bitwise or), XOR (bitwise exclusive or)
CMPEQ (equal), CMLT (less than), CMPLE (less than or equal) [result = 1 if true, 0 if false]
SHL (left shift), SHR (right shift w/o sign extension), SRA (right shift w/ sign extension)




OPC(Ra,literal,Rc): $\text{Reg}[Rc] \leftarrow \text{Reg}[Ra] \text{ op } \text{SEXT}(\text{literal})$

Opcodes:

ADDC (plus), SUBC (minus), MULC (multiply), DIVC (divided by)
ANDC (bitwise and), ORC (bitwise or), XORC (bitwise exclusive or)
CMPEQC (equal), CMLTC (less than), CMPLEC (less than or equal) [result = 1 if true, 0 if false]
SHLC (left shift), SHRC (right shift w/o sign extension), SRAC (right shift w/ sign extension)

Beta Instructions - II

 

LD(Ra,literal,Rc): $\text{Reg}[\text{Rc}] \leftarrow \text{Mem}[\text{Reg}[\text{Ra}] + \text{SEXT}(\text{literal})]$

ST(Rc,literal,Ra): $\text{Mem}[\text{Reg}[\text{Ra}] + \text{SEXT}(\text{literal})] \leftarrow \text{Reg}[\text{Rc}]$

JMP(Ra,Rc): $\text{Reg}[\text{Rc}] \leftarrow \text{PC} + 4; \text{PC} \leftarrow \text{Reg}[\text{Ra}]$

BEQ/BF(Ra,label,Rc): $\text{Reg}[\text{Rc}] \leftarrow \text{PC} + 4;$
if $\text{Reg}[\text{Ra}] = 0$ then $\text{PC} \leftarrow \text{PC} + 4 + 4 * \text{SEXT}(\text{literal})$

BNE/BT(Ra,label,Rc): $\text{Reg}[\text{Rc}] \leftarrow \text{PC} + 4;$
if $\text{Reg}[\text{Ra}] \neq 0$ then $\text{PC} \leftarrow \text{PC} + 4 + 4 * \text{SEXT}(\text{literal})$


LDR(label,Rc): $\text{Reg}[\text{Rc}] \leftarrow \text{Mem}[\text{PC} + 4 + 4 * \text{SEXT}(\text{literal})]$

Beta Control Logic


	<i>OP</i>	<i>OPC</i>	<i>LD</i>	<i>ST</i>	<i>JMP</i>	<i>BEQ</i>	<i>BNE</i>	<i>LDR</i>	<i>Illop</i>	<i>trap</i>
<i>ALUFN</i>	F(op)	F(op)	"+"	"+"	—	—	—	"A"	—	—
<i>WERF</i>	1	1	1	0	1	1	1	1	1	1
<i>BSEL</i>	0	1	1	1	—	—	—	—	—	—
<i>WDSEL</i>	1	1	2	—	0	0	0	2	0	0
<i>WR</i>	0	0	0	1	0	0	0	0	0	0
<i>RA2SEL</i>	0	—	—	1	—	—	—	—	—	—
<i>PCSEL</i>	0	0	0	0	2	Z ? 1 : 0	Z ? 0 : 1	0	3	4
<i>ASEL</i>	0	0	0	0	—	—	—	1	—	—
<i>WASEL</i>	0	0	0	—	0	0	0	0	1	1

Beta2 (see attached sheet)

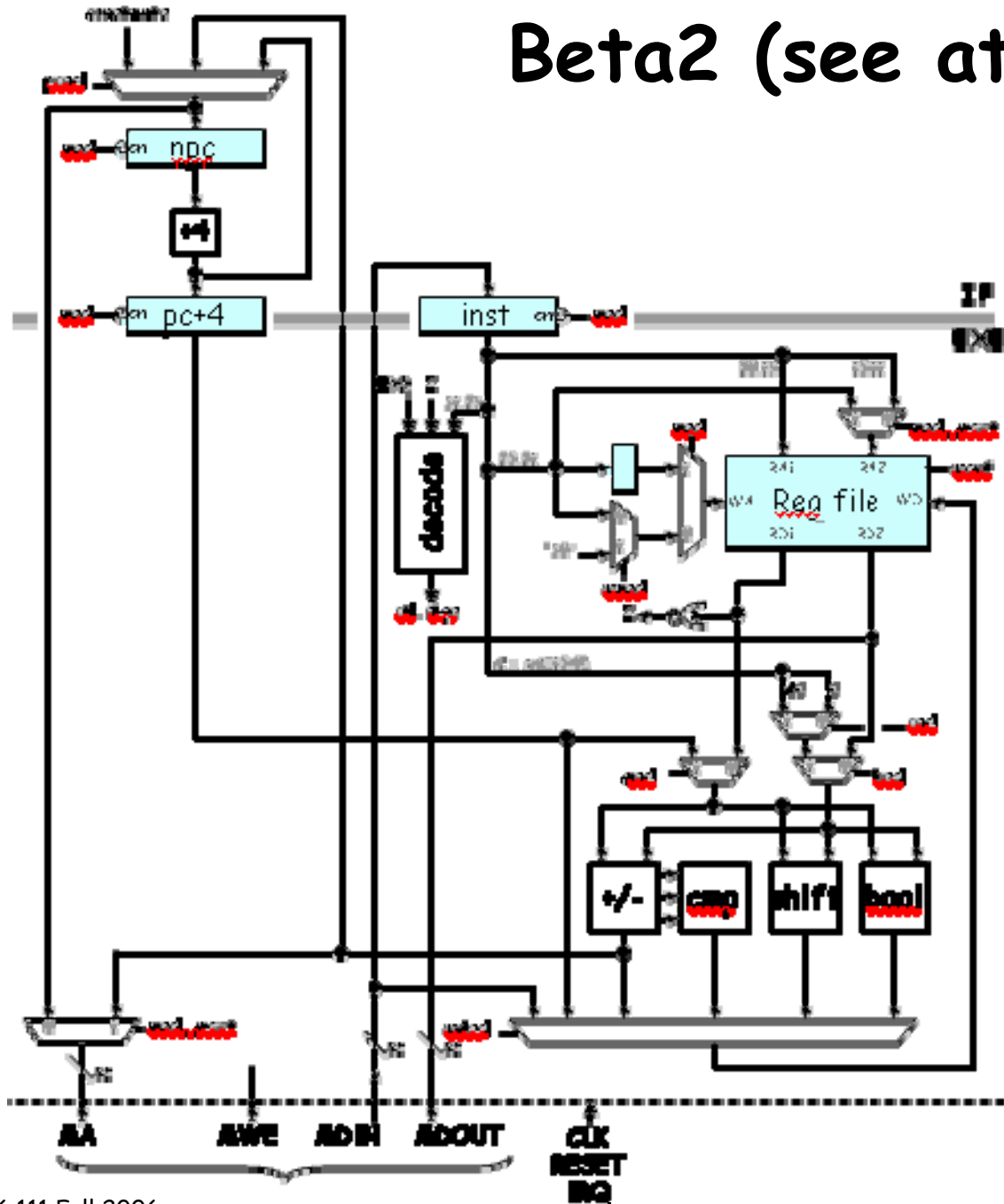- 2-stage pipeline, 1 annuled branch delay slot
- Memory ops (LD, LDR, ST) take two cycle in EXE stage: addr computed in 1st cycle, memory access made in 2nd
- Branch and LDR address arithmetic performed in ALU
- JMP routed thru ALU
- Single memory port shared by inst. fetch and memory access



Xilinx Synchronous Block Memory

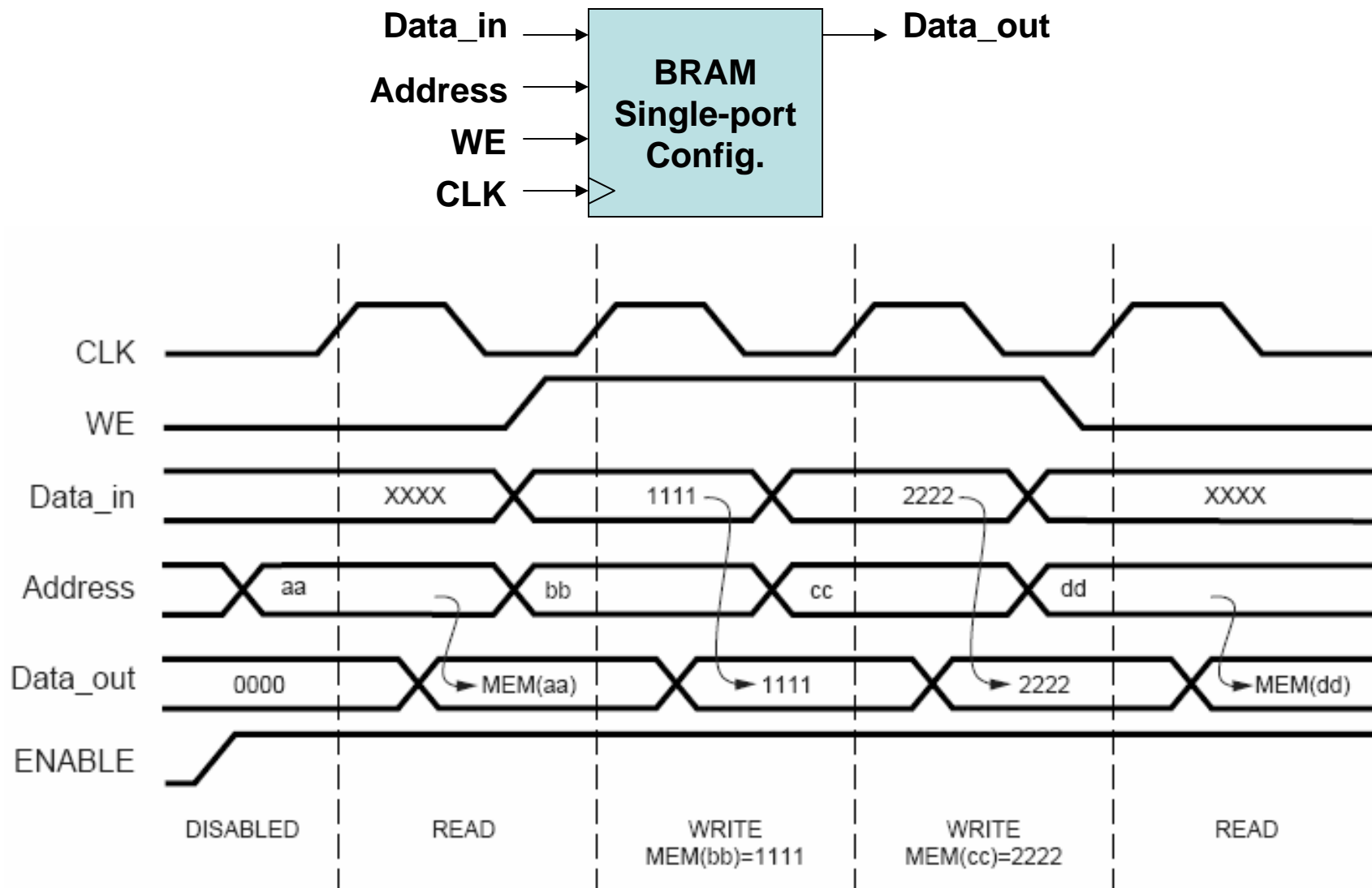


```

100: LD(R31,6004,R2)
104: ADDC(R2,47,R2)
108: ST(R2,44,R31)
10C: XORC(R2,-1,R2)
110: ...
...
6004: 123

```

Instruction Pipeline Diagram

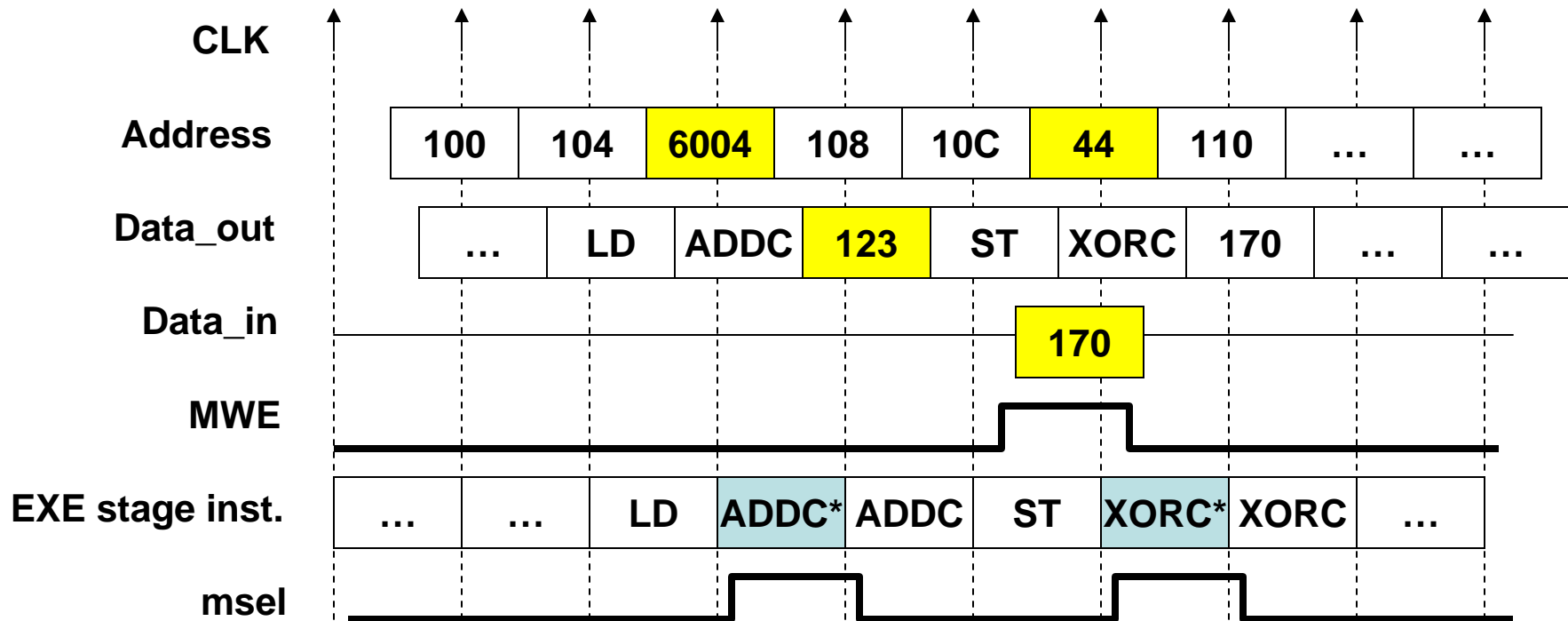

* Stalled in pipeline


beta2.v

```
module beta2(clk,reset,irq,ma,mdin,mdout,mwe);
  input  clk,reset,irq;
  output [31:0] ma,mdout;
  input  [31:0] mdin;
  output mwe;


  // beta2 registers
  reg [31:0] regfile[31:0];
  reg [31:0] npc,pc_inc,inst;
  reg [4:0] rc_save; // needed for second cycle on LD,LDR

  // internal buses
  wire [31:0] rd1,rd2,wd,a,b,xb,c,addsub,cmp,shift,boole;

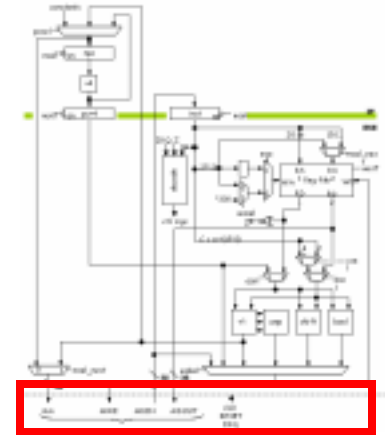  // control signals
  wire wasel,werf,z,asel,bsel,csel;
  wire addsub_op,cmp_lt,cmp_eq,shift_op
  wire shift_sxt,boole_and,boole_or;
  ...
endmodule
```



PC Logic

 


```
// pc
wire [31:0] npc_inc, npc_next;

assign npc_inc = npc + 4;
assign npc_next = reset ? 32'h80000000 :
    msel ? npc :
    branch ? {npc[31]&addsub[31],
              addsub[30:2], 2'b00} :
    trap ? 32'h80000004 :
    interrupt ? 32'h80000008 :
    npc_inc;

always @ (posedge clk) begin
    npc <= npc_next;    // stall on msel handled above
    if (!msel) pc_inc <= npc_inc;
end
```

Instruction Register & Decode

 

```
// instruction reg
always @ (posedge clk) if (!msel) inst <= mdin;
```


```
// control logic
decode ctl(.clk(clk),.reset(reset),.irq(irq & !npc[31]),
          .z(z),.opcode(inst[31:26]),
          .asel(asel),.bssel(bssel),.csel(csel),
          .wasel(wasel),.werf(werf),.msel(msel),
          .msel_next(msel_next),.mwe(mwe),
          .addsub_op(addsub_op),.cmp_lt(cmp_lt),
          .cmp_eq(cmp_eq),
          .shift_op(shift_op),.shift_sxt(shift_sxt),
          .boole_and(boole_and),.boole_or(boole_or),
          .wd_addsub(wd_addsub),.wd_cmp(wd_cmp),
          .wd_shift(wd_shift),.wd_boole(wd_boole),
          .branch(branch),.trap(trap),
          .interrupt(interrupt));
```

Register File

```
// register file
wire [4:0] ra1,ra2,wa;
always @ (posedge clk)
    if (!msel) rc_save <= inst[25:21];

assign ra1 = inst[20:16];
assign ra2 = msel_next ? inst[25:21] : inst[15:11];
assign wa = msel ? rc_save :
           wasel ? 5'd30 : inst[25:21];
assign rd1 = (ra1 == 31) ? 0 : regfile[ra1];
assign rd2 = (ra2 == 31) ? 0 : regfile[ra2];
always @ (posedge clk)
    if (werf) regfile[wa] <= wd;

assign z = ~| rd1;    // used in BEQ/BNE instructions
```

 

ALU


```
// alu
assign a = asel ? pc_inc : rd1;
assign b = bsel ? c : rd2;
assign c = csel ? {{14{inst[15]}},inst[15:0],2'b00} :
                {{16{inst[15]}},inst[15:0]};

wire addsub_n,addsub_v,addsub_z;
assign xb = {32{addsub_op}} ^ b;
assign addsub = a + xb + addsub_op;
assign addsub_n = addsub[31];
assign addsub_v = (addsub[31] & ~a[31] & ~xb[31]) |
                  (~addsub[31] & a[31] & xb[31]);
assign addsub_z = ~| addsub;


assign cmp[31:1] = 0;
assign cmp[0] = (cmp_lt & (addsub_n ^ addsub_v)) |
                (cmp_eq & addsub_z);

wire [31:0] shift_right;
shift_right sr(shift_sxt,a,b[4:0],shift_right);
assign shift = shift_op ? shift_right : a << b[4:0];

assign boole = boole_and ? (a & b) :
                boole_or ? (a | b) : a ^ b;
```

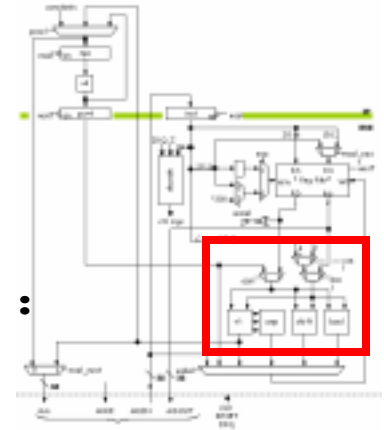

Result Mux, Address Mux

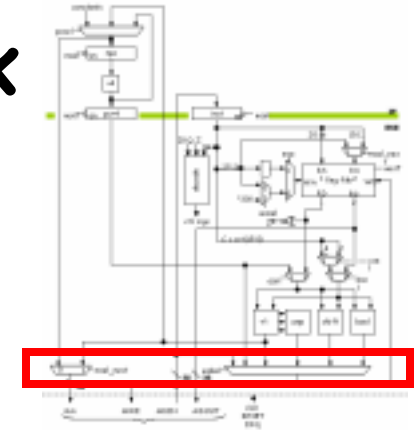

```
// result mux, listed in order of speed (slowest first)
```

```
assign wd = msel ? mdin :  
    wd_cmp ? cmp :  
    wd_addsub ? addsub :  
    wd_shift ? shift :  
    wd_boole ? boole :  
    pc_inc;
```


```
// assume synchronous external memory
```

```
assign ma = msel_next ? addsub : npc_next;  
assign mdout = rd2;
```

Control Logic (decode.v)

```
always @ (opcode or z or annul or irq or reset)
begin
    // initial assignments for all control signals
    asel = 1'hx; bsel = 1'hx; csel = 1'hx;
    addsub_op = 1'hx; shift_op = 1'hx; shift_sxt = 1'hx;
    cmp_lt = 1'hx; cmp_eq = 1'hx;
    boole_and = 1'hx; boole_or = 1'hx;
    wasel = 0; mem_next = 0;
    wd_addsub = 0; wd_cmp = 0; wd_shift = 0; wd_boole = 0;
    branch = 0; trap = 0; interrupt = 0;

     if (irq && !reset && !annul) begin
        interrupt = 1;
        wasel = 1;
    end else casez (opcode)
        6'b011000: begin // LD
            asel = 0; bsel = 1; csel = 0;
            addsub_op = 0;
            mem_next = 1;
        end
    end
```



...


Control Logic (cont'd.)

...



```
6'b1?1100: begin // SHL, SHLC
    asel = 0; bsel = opcode[4]; csel = 0;
    shift_op = 0;
    wd_shift = 1;
end
6'b1?1101: begin // SHR, SHRC
    asel = 0; bsel = opcode[4]; csel = 0;
    shift_op = 1; shift_sxt = 0;
    wd_shift = 1;
end
6'b1?1110: begin // SRA, SRAC
    asel = 0; bsel = opcode[4]; csel = 0;
    shift_op = 1; shift_sxt = 1;
    wd_shift = 1;
end
default: begin // illegal opcode
    trap = !annul; wasel = 1;
end

endcase
end // always @ (opcode or ...)
```


Xilinx XC3S200 FPGA

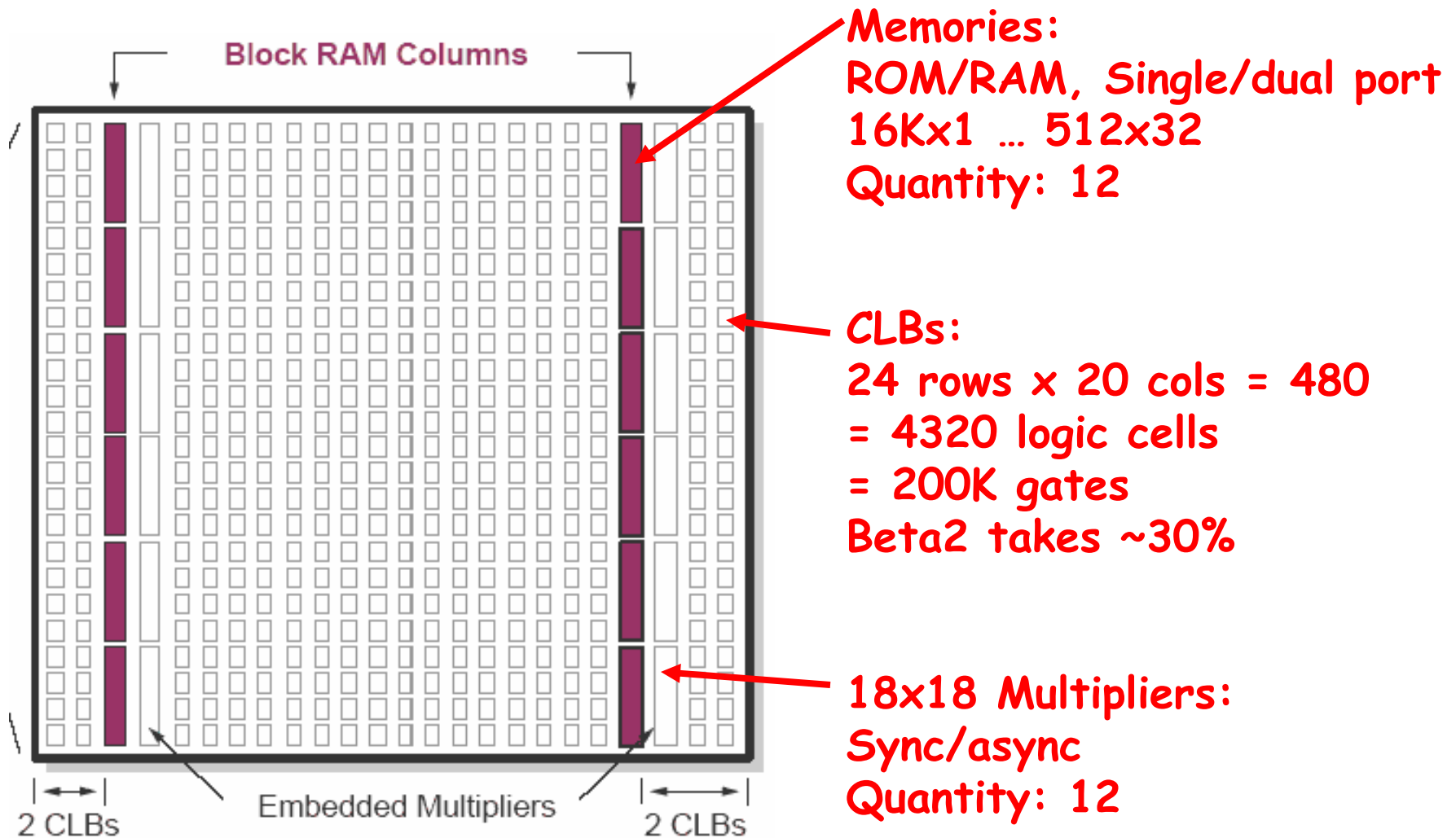


Beta2 Floorplan

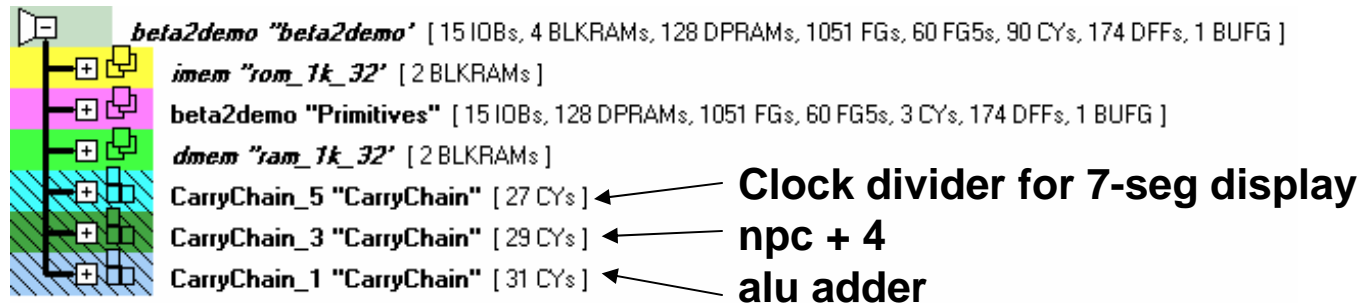 


FPGAs @ Home

- **6.111 labkit: the Lexus of FPGA protoboards**
 - XC2V6000 (76032 logic cells, 2.5 Mbits BRAM)
- **Two affordable alternatives (lots more out there)**
 - **Spartan-3 Starter Board (www.digilentinc.com)**
 - \$99 = Spartan XC3S200 (4320 logic cells, 216 Kbits BRAM)
 - \$119 = Spartan XC3S400 (8064 logic cells, 288 Kbits BRAM)
 - \$149 = Spartan XC3S1000 (17480 logic cells, 432 Kbits BRAM)
 - Switches, buttons, leds, 4-digit display
 - 1Mbyte 10ns SRAM
 - PS2, serial port, 8-color VGA, 3 expansion connectors
 - **XSA-3S1000 @ \$199 (www.xess.com)**
 - Spartan XC3S1000 (17480 logic cells, 432 Kbits BRAM)
 - Switches, buttons, 1-digit display
 - 32Mbyte SDRAM, 2Mbyte Flash
 - PS2, 512-color VGA
 - 80-pin expansion connector (protoboard friendly)


Xilinx Spartan-3 Starter Board

 


Spartan-3 Starter Board Diagram

 

XSA-3S1000

 

XSA-3S1000 Block Diagram

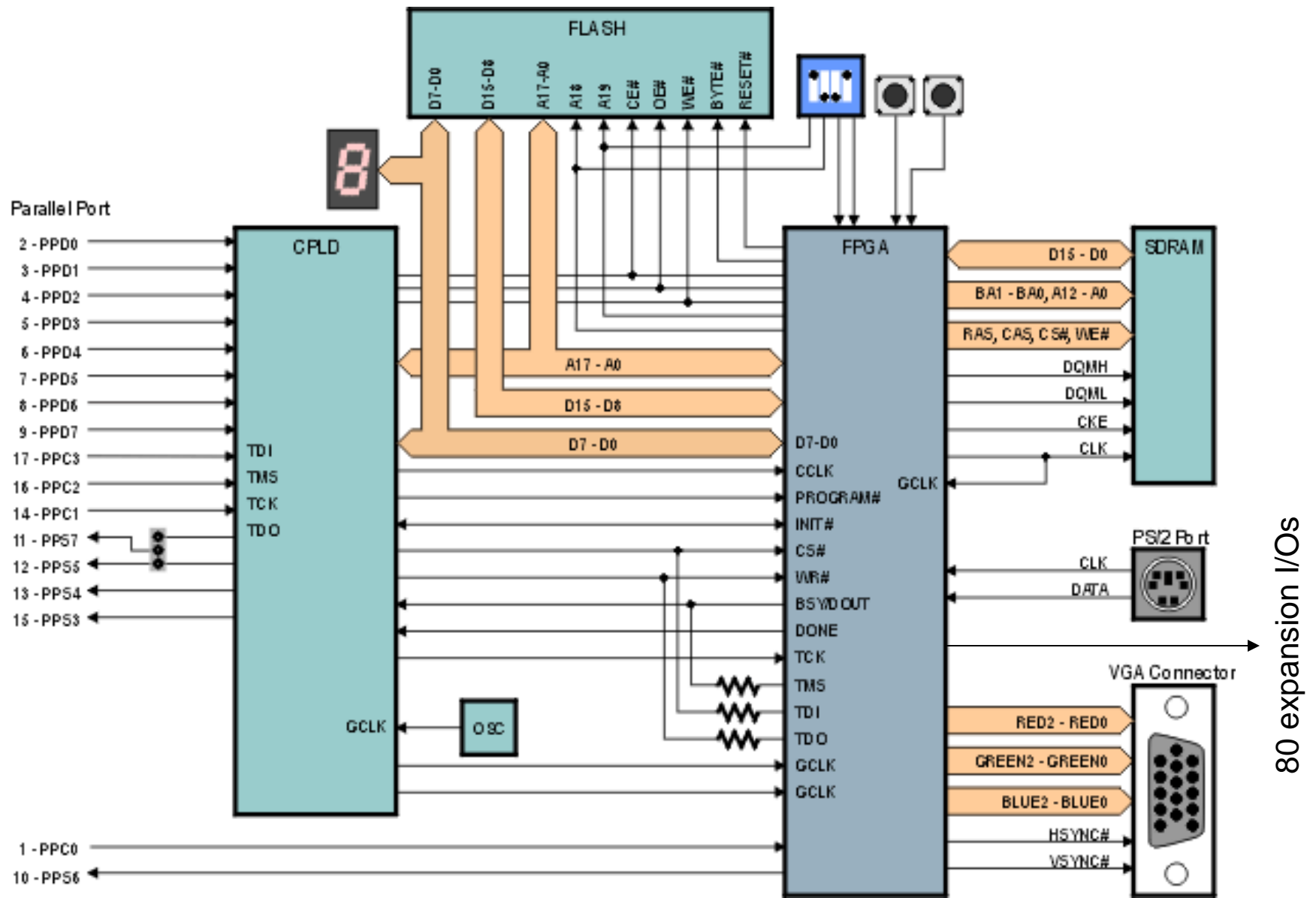

FPGA Software

- Xilinx ISE Web-pack
 - Free!
 - Windows 2000/XP, Red Hat Enterprise Linux 3
 - Supports subset of Xilinx FPGAs (but covers the chips used in the boards listed on the previous slide)
 - No IP Wizard, but
 - You can build memories, logic “by hand” using available components (eg, RAMB16_Sxx) and appropriate defparams or attribute assignments - see Xilinx documentation
 - A **lot** of very good design info in Xilinx App Notes (on-line)
 - Wimpy simulator
 - Need computer with parallel port to connect programming cable for boards listed on the previous slide
OR use Digilent USB cable for Digilent Boards