

MASSACHUSETTS INSTITUTE OF TECHNOLOGY  
DEPARTMENT OF ELECTRICAL ENGINEERING AND COMPUTER SCIENCE

**6.111 Introductory Digital Systems Laboratory**  
Fall 2006

**Midterm Exam: November 1, 2006**

<i>Name</i>  <b>SOLUTIONS</b>	<i>Score</i> <i>(out of 100)</i>
-------------------------------------	-------------------------------------


This is a closed book exam. Calculators can be used (but I don't think you'll need one).

Please write your answers legibly in the spaces provided. You can use the backs of the pages for scratch work.

<b>Problem</b>	<b>Score</b>
<b>#1</b>	
<b>#2</b>	
<b>#3</b>	
<b>#4</b>	

 **Problem 1. (30 Points)**

A state transition diagram for a 4-state FSM is shown below. The FSM has two one-bit inputs (A and B) and three one-bit outputs (F, L and R). The current state is represented as a two-bit value  $S_1S_0$ .



- (A) (16 Points) Please neatly fill in the truth table for the FSM's combinational logic below: using  $S_1$ ,  $S_0$ , A and B as the inputs, and using next\_ $S_1$ , next\_ $S_0$ , F, L and R as the outputs.

$S_1$	$S_0$	A	B	next_ $S_1$	next_ $S_0$	F	L	R
0	0	0	0	0	0	1	0	0
0	0	0	1	0	1	1	0	0
0	0	1	0	0	1	1	0	0
0	0	1	1	0	1	1	0	0
0	1	0	0	1	0	0	1	0
0	1	0	1	0	1	0	1	0
0	1	1	0	0	1	0	1	0
0	1	1	1	0	1	0	1	0
1	0	0	0	1	0	1	0	1
1	0	0	1	1	1	1	0	1
1	0	1	0	1	0	1	0	1
1	0	1	1	1	1	1	0	1
1	1	0	0	1	0	1	1	0
1	1	0	1	1	1	1	1	0
1	1	1	0	0	1	1	1	0
1	1	1	1	0	1	1	1	0

- (B) (14 Points) Give minimal sum-of-product expressions for next\_ $S_1$  and next\_ $S_0$ . Hint: Use Karnaugh maps (you can use the backs of the exam pages for scratch work).

**Minimal sum-of-products expression for next\_ $S_1$ :**  $S_1\bar{S}_0 + S_1\bar{A} + S_0\bar{A}\bar{B}$

**Minimal sum-of-products expression for next\_ $S_0$ :**  $B + \bar{S}_1A + S_0A$

## Problem 2. (20 Points)

Hoping to get a head start on her final project, Vera Log downloaded the following Verilog module from the net. It's supposed to implement a 4-bit two's complement adder using the propagate and generate signals Vera learned about in lecture.

```
module adder4(a,b,cin,s,cout);
    input [3:0] a,b;
    input cin;
    output [3:0] s;

    wire [3:0] a,b,s,c,p,g;
    wire cout;

    always @ (a or b) begin
        g <= a & b;
        p <= a ^ b;
        c <= g | (p & {c[2:0],cin});
        s <= p | {c[2:0],cin};
        cout <= c[3];
    end
endmodule
```

After a quick glance Vera sees that the module has many Verilog and logic errors and is hoping someone knowledgeable will fix it up. Help Vera out by rewriting the module, correcting the errors as you go.

**Rewrite the module below, correcting all the errors.**


```
module adder4(a,b,cin,s,cout);
    input [3:0] a,b;
    input cin;
    output [3:0] s;
    output cout;

    wire [3:0] a,b; // this declaration is not needed...
    reg [3:0] s,c,p,g;
    reg cout;

    always @ (a or b or cin) begin
        g = a & b;
        p = a ^ b;
        c = g | (p & {c[2:0],cin});
        s = p ^ {c[2:0],cin};
        cout = c[3];
    end
endmodule
```
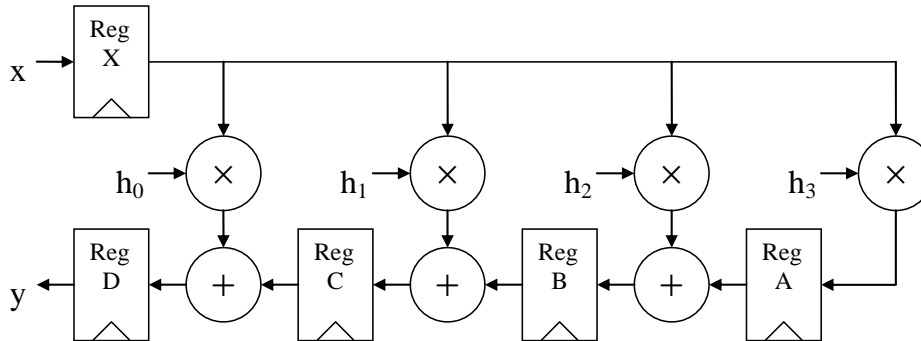
### Problem 3. (25 Points)

The schematic below implements a 4-tap FIR filter in its transposed form. The incoming data ( $x$ ) is a stream of 16-bit two's complement numbers and the coefficients are 10-bit two's complement numbers.



- (A) (6 Points) What are the minimum and maximum possible values for a coefficient?

**Minimum coefficient value: -512**  
**Maximum coefficient value: 511**

- (B) (5 Points) One of the coefficients has the value -42. What's the appropriate binary representation for this value?

**Appropriate binary representation for coefficient of -42: 1111010110**

- (C) (8 Points) Indicate the appropriate width in bits for each of the registers A – D assuming that we don't want to lose any arithmetic precision (i.e., we don't want to round, shift or truncate any of the intermediate results or the final answer).

**Most positive value for  $y = 4 * (-32768) * (-512)$ .**  
**Most negative value for  $y = 4 * (32767) * (-512)$ .**  
**Only need 28 bits for final value to represent actual range of output values.**

**Width of Register A: 26**  
**Width of Register B: 27**  
**Width of Register C: 28**  
**Width of Register D: 28 or 29**

- (D) (6 Points) What's the minimum clock period for which the circuit will still work correctly given the following timing specifications for the components:

component	$t_{CD}$	$t_{PD}$	$t_{SETUP}$	$t_{HOLD}$
Register	0.7ns	1.1ns	0.6ns	0.4ns
Adder	0.2ns	2.1ns	--	--
Multiplier	0.2ns	4.5ns	--	--

**Minimum clock period: 8.3ns**

#### Problem 4. (25 Points)

Consider the following Verilog module that iteratively computes the square root of an 8-bit integer value.

```
module sqrt(clk,data,start,answer,done);
    input clk,start;
    input [7:0] data;
    output [3:0] answer;
    output done;

    reg [3:0] answer;
    reg busy;
    reg [1:0] bit;

    wire [3:0] trial;
    assign trial = answer | (1 << bit); // << is left shift

    always @ (posedge clk) begin
        if (busy) begin
            if (bit == 0) busy <= 0;
            else bit <= bit - 1;
            if (trial*trial <= data) answer <= trial;
        end
        else if (start) begin
            busy <= 1;
            answer <= 0;
            bit <= 3;
        end
    end

    assign done = ~busy;
endmodule
```

Please neatly complete the timing diagram below as the module computes the square root of 169.

