 


# Welcome to 6.111!

## Introductory Digital Systems Laboratory



Handouts:

**Info form (yellow)**

Course Calendar

Lecture slides

Lectures:

Chris Terman

TAs:

Roberto Carli


Brian Schmidt

Alessandro Yamhure

Lab guru:

Gim Hom
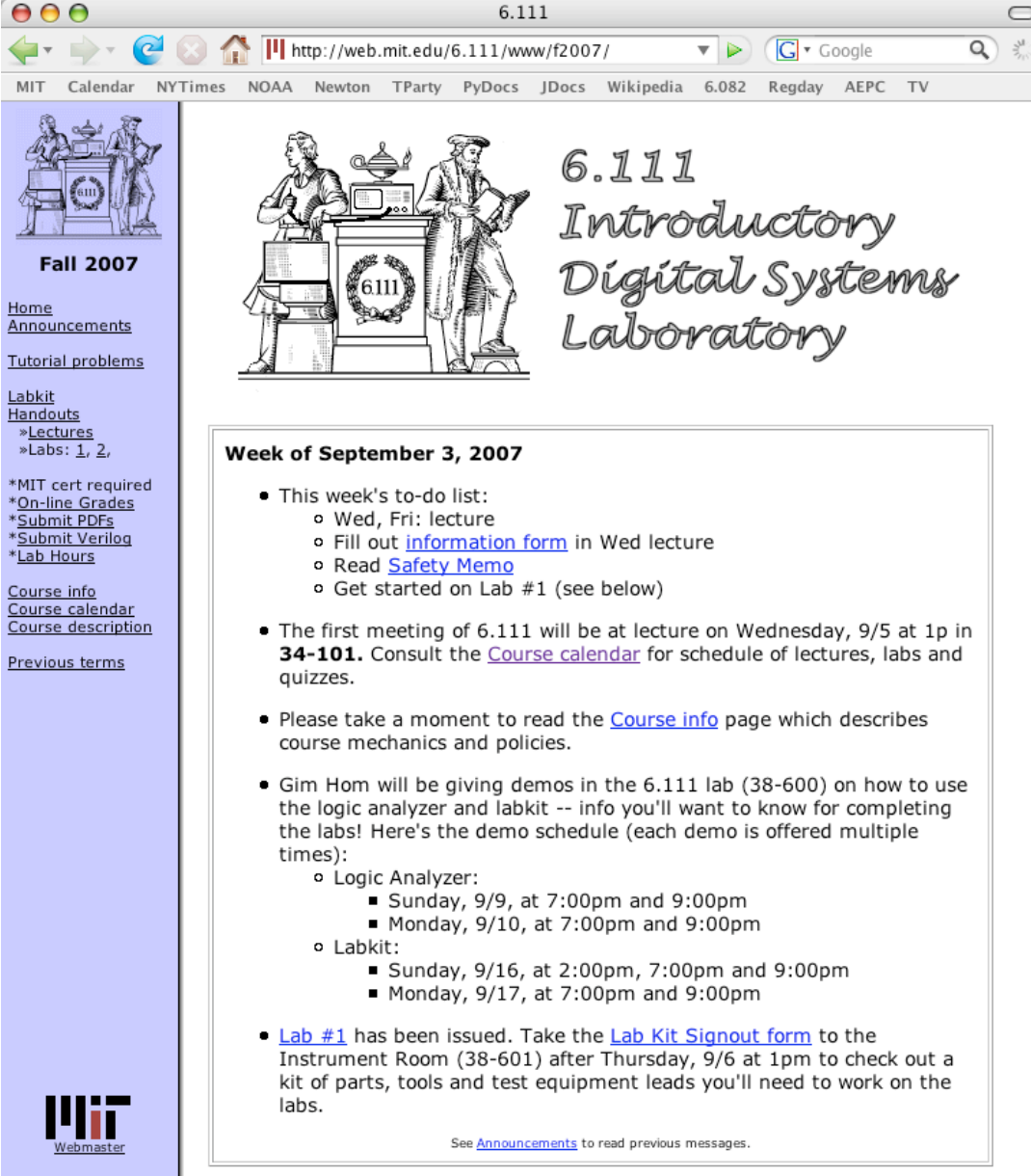
# Course Website (<http://mit.edu/6.111>)



6.111  
Introductory  
Digital Systems  
Laboratory

**Week of September 3, 2007**

- This week's to-do list:
  - Wed, Fri: lecture
  - Fill out [information form](#) in Wed lecture
  - Read [Safety Memo](#)
  - Get started on Lab #1 (see below)
- The first meeting of 6.111 will be at lecture on Wednesday, 9/5 at 1p in **34-101**. Consult the [Course calendar](#) for schedule of lectures, labs and quizzes.
- Please take a moment to read the [Course info](#) page which describes course mechanics and policies.
- Gim Hom will be giving demos in the 6.111 lab (38-600) on how to use the logic analyzer and labkit -- info you'll want to know for completing the labs! Here's the demo schedule (each demo is offered multiple times):
  - Logic Analyzer:
    - Sunday, 9/9, at 7:00pm and 9:00pm
    - Monday, 9/10, at 7:00pm and 9:00pm
  - Labkit:
    - Sunday, 9/16, at 2:00pm, 7:00pm and 9:00pm
    - Monday, 9/17, at 7:00pm and 9:00pm
- [Lab #1](#) has been issued. Take the [Lab Kit Signout form](#) to the Instrument Room (38-601) after Thursday, 9/6 at 1pm to check out a kit of parts, tools and test equipment leads you'll need to work on the labs.

See [Announcements](#) to read previous messages.

MIT  
Webmaster

# 6.111 Goals

- **Fundamentals of logic design**
  - combinational and sequential blocks
- **System integration with multiple components**
  - FPGAs, memories, discrete components, etc.
- **Learn a Hardware Description Language (Verilog)**
- **Interfacing issues with analog components**
  - ADC, DAC, sensors, etc.
- **Understand different design methodologies**
- **Understand different design metrics**
  - component/gate count and implementation area, switching speed, energy dissipation and power
- **Design & implement a substantial digital system**
- **Have fun!**

# Labs: learning the ropes

- **Lab 1**
  - Experiment with gates, design & implement some logic
  - Learn about lab equipment in the Digital Lab (38-600):  
oscilloscopes and logic analyzers
- **Lab 2**
  - Introduction to Verilog & the labkit
- **Lab 3**
  - Design and implement a Finite State Machine (FSM)
  - Use Verilog to program an FPGA
  - Report and its revision will be evaluated for CI-M
- **Lab 4**
  - Design a complicated system with multiple FSMs (Major/Minor FSM)
  - Voice recorder using AC97 codec and SRAMs
- **Lab 5**
  - Video circuits: a simple Pong game


# Final Project

- Done in groups of two (or sometimes three)
- Open ended
- You and the staff negotiate a project proposal
  - Must emphasize digital concepts, but inclusion of analog interfaces (e.g., data converters, sensors or motors) common and often desirable
  - Proposal Conference, several Design Reviews
- Design presentation to staff
- Staff will provide help with project definition and scope, design, debugging, and testing
- It is extremely difficult for a student to receive an A without completing the final project

# Evaluation


- **Midterm (10/31): 20%**
- **Labs: 30%**
  - Labs 1 & 2: 3%, Lab 3: 6%, Labs 4 & 5: 9%
- **CI-M paper: 10%**
- **Final Project: 40%**
  - Deadlines and participation: 5%
  - Quality and organization of presentation and report: 5%
  - Complexity, innovation and risk: 10%
  - Problem definition: 2%
  - Architecture: 3%
  - Design (modularity, Verilog): 5%
  - Functionality: 10%
- A large number of students do "A" level work and are, indeed, rewarded with a grade of "A". The corollary to this is that, since average performance levels are so high, punting any part of the subject can lead to a disappointing grade.

# Why Digital? A Thought Experiment

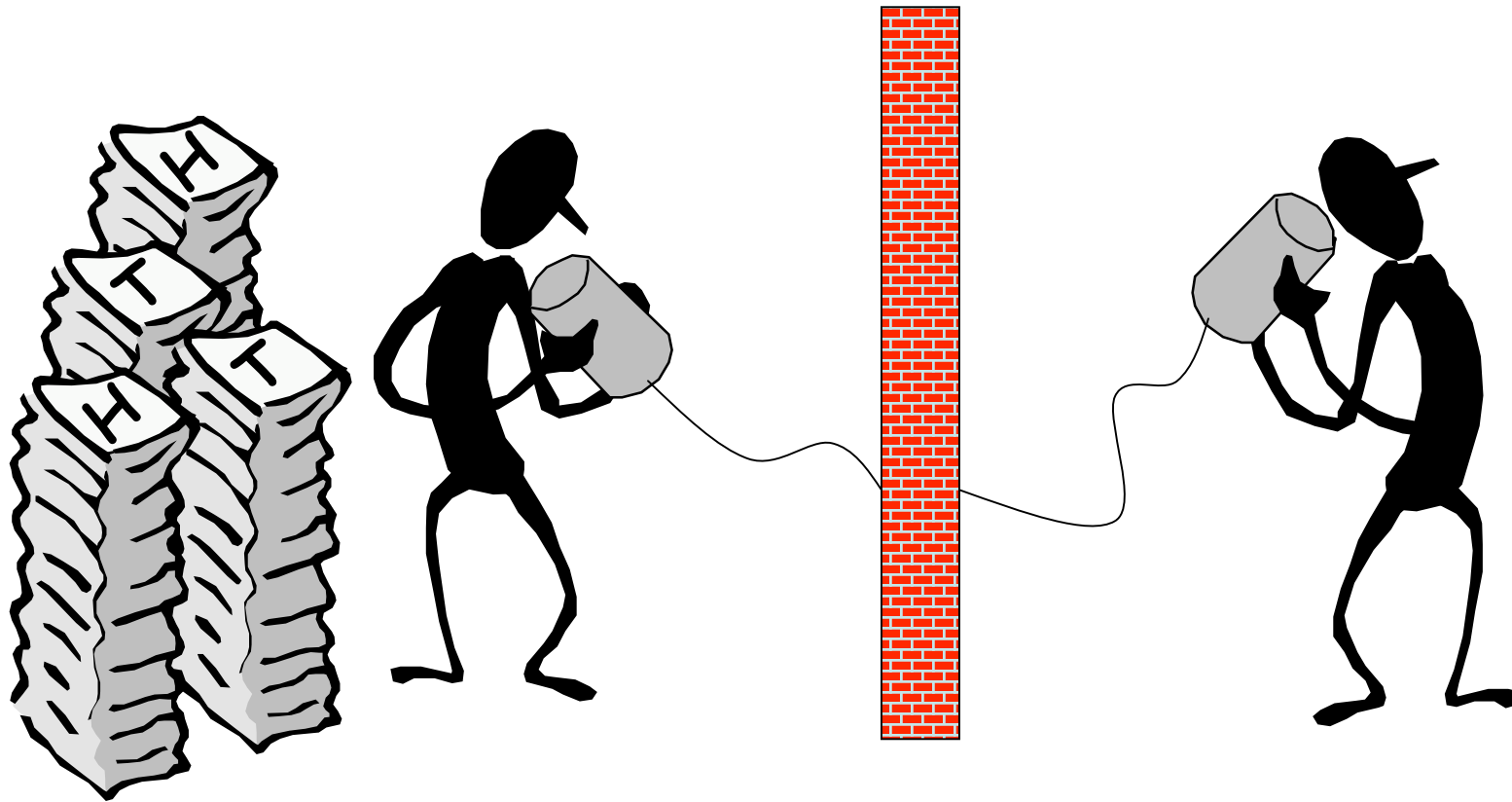

**Goal: transmit results of 100 coin flips**

# Experiment #1: Analog Encoding

 

100 coin flips  $\rightarrow 2^{100}$  possibilities

Transmit voltage  $N/2^{100}$  for possibility #N

Required voltage resolution =  $1/2^{100} = \sim 8e-31$  volts



**impossible to reliably transmit/receive voltages with required resolution**



# Rethink basic system architecture


- Noise and inaccuracy are inevitable; we can't reliably transmit/receive/manipulate "infinite" information-- we must **design our system to tolerate some amount of error** if it is to process information reliably.
- A system is a structure that is guaranteed to exhibit a specified behavior, assuming all of its (imperfect) components obey their specified behaviors.

## **CONTRACTS!**


How is this achieved?

Every system component will have clear obligations and responsibilities. If contracts are violated all bets are off.

# Digital Signaling

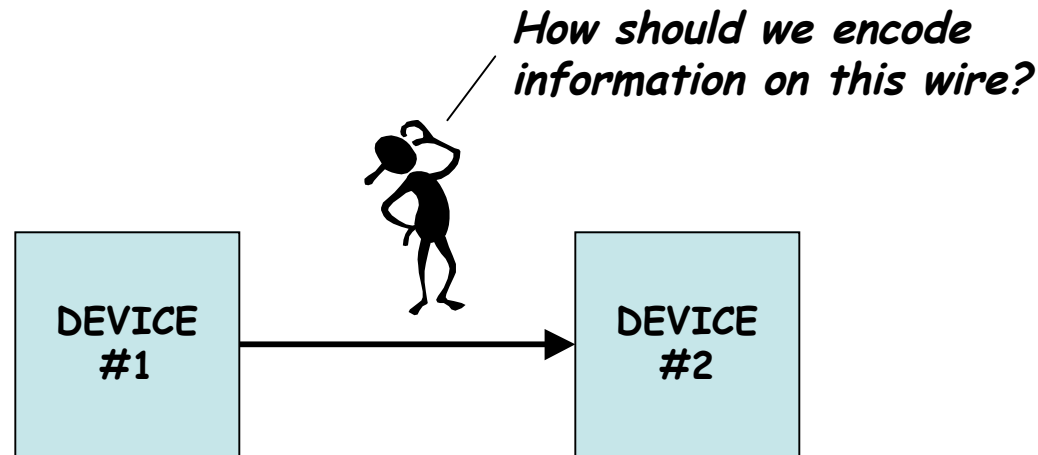


 We can encode information using voltages, currents, frequency, phase, etc. A common choice is to use a **voltage encoding** and a **binary (0/1) signaling** scheme




# Digital Signaling II


Encoding Attempt #2:

 

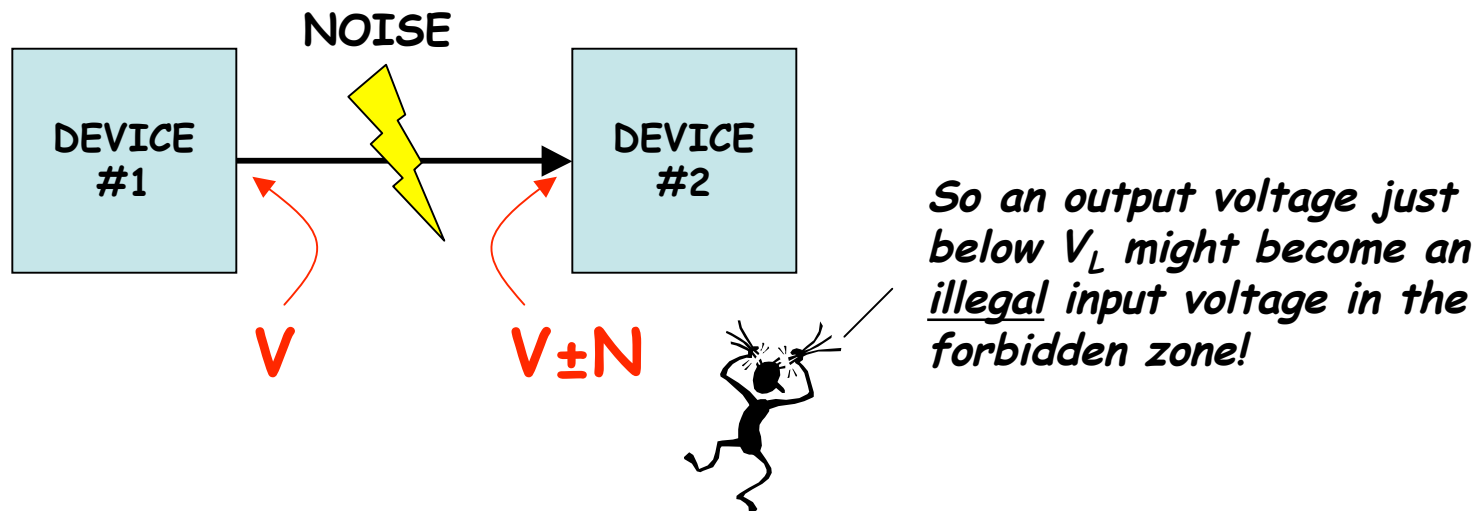This avoids "close calls", but now we have to consider noise (i.e. unavoidable perturbations to our signaling voltage)




# Big Idea: Noise Margins

 


*Let's leave room for bad things to happen! So we'll design devices restore marginally valid input signals. They must accept marginal inputs and provide unquestionable outputs (i.e., to leave room for noise).*

OUTPUTS:

 

INPUTS:

 

**Noise Margins**

# Using Voltages Digitally

Digital input:  $V_{IN} < V_{IL}$  or  $V_{IN} > V_{IH}$

Digital output:  $V_{OUT} < V_{OL}$  or  $V_{OUT} > V_{OH}$

Noise margins:  $V_{OL} < V_{IL} < V_{IH} < V_{OH}$

Where  $V_{OL}$ ,  $V_{IL}$ ,  $V_{IH}$  and  $V_{OH}$  are part of the specification for a particular family of digital components.


Challenges: if one lowers the supply voltage to save power and increase speed of transitions, the noise margin also decreases.

# Sample DC (signaling) Specification

I/O Standard	$V_{IL}$		$V_{IH}$		$V_{OL}$	$V_{OH}$	$I_{OL}$	$I_{OH}$
	V, Min	V, Max	V, Min	V, Max	V, Max	V, Min	mA	mA
LVTTL	-0.3	0.8	2.0	3.45	0.4	2.4	Note(3)	Note(3)
LVC MOS33, LVDCI33	-0.3	0.8	2.0	3.45	0.4	$V_{CCO} - 0.4$	Note(3)	Note(3)
LVC MOS25, LVDCI25	-0.3	0.7	1.7	$V_{CCO} + 0.3$	0.4	$V_{CCO} - 0.4$	Note(3)	Note(3)
LVC MOS18, LVDCI18	-0.3	35% $V_{CCO}$	65% $V_{CCO}$	$V_{CCO} + 0.3$	0.45	$V_{CCO} - 0.45$	Note(4)	Note(4)
LVC MOS15, LVDCI15	-0.3	35% $V_{CCO}$	65% $V_{CCO}$	$V_{CCO} + 0.3$	25% $V_{CCO}$	75% $V_{CCO}$	Note(4)	Note(4)
LVC MOS12	-0.3	35% $V_{CCO}$	65% $V_{CCO}$	$V_{CCO} + 0.3$	25% $V_{CCO}$	75% $V_{CCO}$	Note(6)	Note(6)
PCI33_3 <sup>(5)</sup>	-0.2	30% $V_{CCO}$	50% $V_{CCO}$	$V_{CCO}$	10% $V_{CCO}$	90% $V_{CCO}$	Note(5)	Note(5)
PCI66_3 <sup>(5)</sup>	-0.2	30% $V_{CCO}$	50% $V_{CCO}$	$V_{CCO}$	10% $V_{CCO}$	90% $V_{CCO}$	Note(5)	Note(5)
PCI-X <sup>(5)</sup>	-0.2	35% $V_{CCO}$	50% $V_{CCO}$	$V_{CCO}$	10% $V_{CCO}$	90% $V_{CCO}$	Note(5)	Note(5)

Source: Xilinx Virtex 5 Datasheet

# Experiment #2: Digital Encoding

 


100 coin flips → one transmission for each flip

➡ But when does receiver make measurements?  
Is  "HT" or "HHHTTT"?

# A Digital Processing Element

- A *combinational device* is a circuit element that has
  - one or more digital *inputs*
  - one or more digital *outputs*
  - a *functional specification* that details the value of each output for every possible combination of valid input values
  - a *timing specification* consisting (at minimum) of an upper bound  $t_{pd}$  on the required time for the device to compute the specified output values from an arbitrary set of stable, valid input values

Static discipline

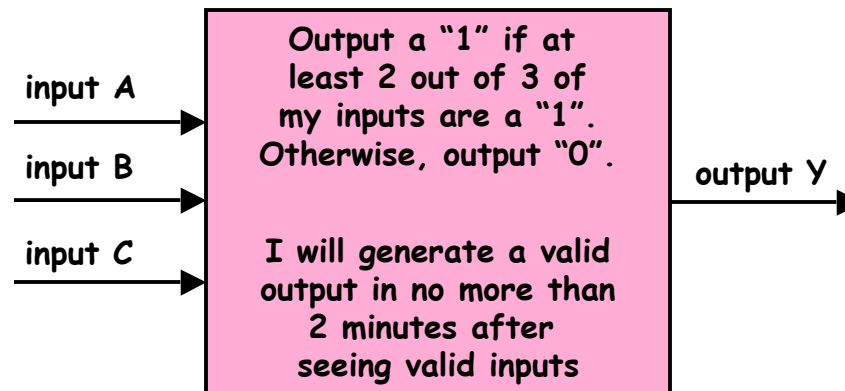




# Why have processing blocks?

- The goal of modular design:
 
## ABSTRACTION


- What does that mean anyway:
  - Rules simple enough for a 6-3 to follow...
  - Understanding BEHAVIOR without knowing IMPLEMENTATION
  - Predictable composition of functions
  - Tinker-toy assembly
  - Guaranteed behavior under REAL WORLD circumstances



# A Combinational Digital System

- A set of interconnected elements is a *combinational device* if
  - each circuit element is a combinational device
  - every input is connected to exactly one output or a constant (eg, some vast supply of 0's and 1's)
  - the circuit contains no directed cycles
- Why is this true?
  - Given an acyclic circuit meeting the above constraints, we can derive functional and timing specs for the input/output behavior from the specs of its components!
  - We'll see lots of examples soon. But first, we need to build some combinational devices to work with...

# Example device: An Inverter

 

0  $\rightarrow$   $\neg$  1

1  $\rightarrow$   $\neg$  0



**Voltage Transfer Characteristic:**  
Plot of  $V_{OUT}$  vs.  $V_{IN}$  where each measurement is taken after any transients have died out.

*Note: VTC does not tell you anything about how fast a device is—it measures static behavior not dynamic behavior*

Static Discipline requires that we avoid the shaded regions aka “forbidden zones”), which correspond to *valid* inputs but *invalid* outputs. Net result: combinational devices must have **GAIN > 1** and be **NONLINEAR**.





$$\frac{\partial V_{OUT}}{\partial V_{IN}}$$

# Combinational Device Wish List

  


- ✓ Design our system to tolerate some amount of error
  - ⇒ Add positive noise margins
  - ⇒ VTC: gain > 1 & nonlinearity
- ✓ Lots of gain ⇒ big noise margin
- ✓ Cheap, small
- ✓ Changing voltages will require us to dissipate power, but if no voltages are changing, we'd like zero power dissipation
- ✓ Want to build devices with useful functionality (what sort of operations do we want to perform?)

# Wishes Granted: CMOS

 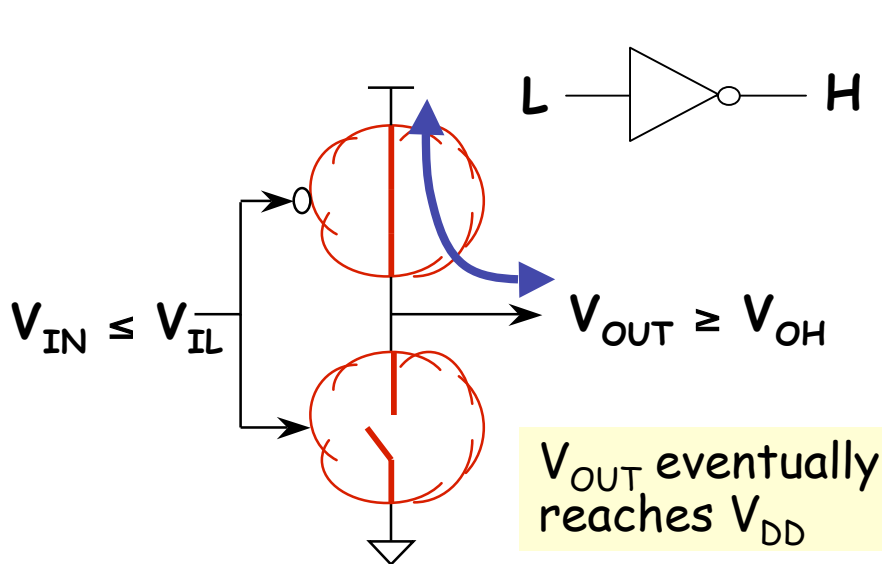  

 
# Digital Integrated Circuits

IBM photomicrograph ( $\text{SiO}_2$  has been removed!)





# CMOS Forever!?

 

# Summary

- Use voltages to encode information
- “Digital” encoding
  - valid voltage levels for representing “0” and “1”
  - forbidden zone avoids mistaking “0” for “1” and vice versa
- Noise
  - Want to tolerate real-world conditions: NOISE.
  - Key: tougher standards for output than for input
  - devices must have gain and have a non-linear VTC
- Combinational devices
  - Each logic family has Tinkertoy-set simplicity, modularity
  - predictable composition: “parts work → whole thing works”
  - static discipline
    - digital inputs, outputs; restore marginal input voltages
    - complete functional spec
    - valid inputs lead to valid outputs in bounded time