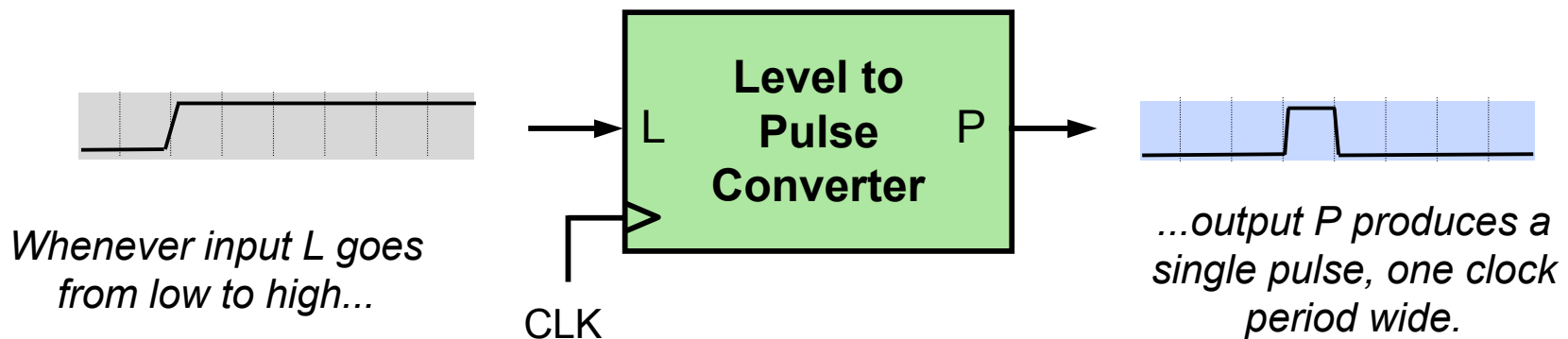



Design Example: Level-to-Pulse

- A **level-to-pulse converter** produces a single-cycle pulse each time its input goes high.
- It's a synchronous rising-edge detector.
- Sample uses:
 - Buttons and switches pressed by humans for arbitrary periods of time
 - Single-cycle enable signals for counters




Step 1: State Transition Diagram

- Block diagram of desired system:

 


 - State transition diagram** is a useful FSM representation and design aid:




Step 2: Logic Derivation

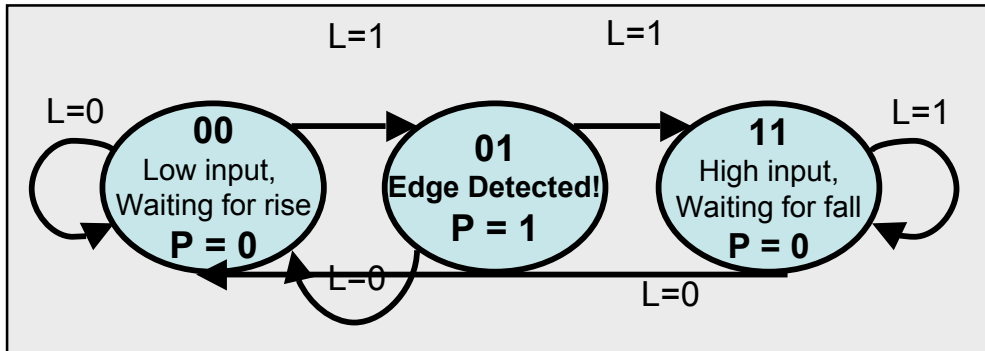Transition diagram is readily converted to a state transition table (just a truth table)




Current t State		In	Next State		Out
S_1	S_0	L	S_1^+	S_0^+	P
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	1
1	1	0	0	0	0
1	1	1	1	1	0

 
- Combinational logic may be derived using Karnaugh maps




Moore Level-to-Pulse Converter

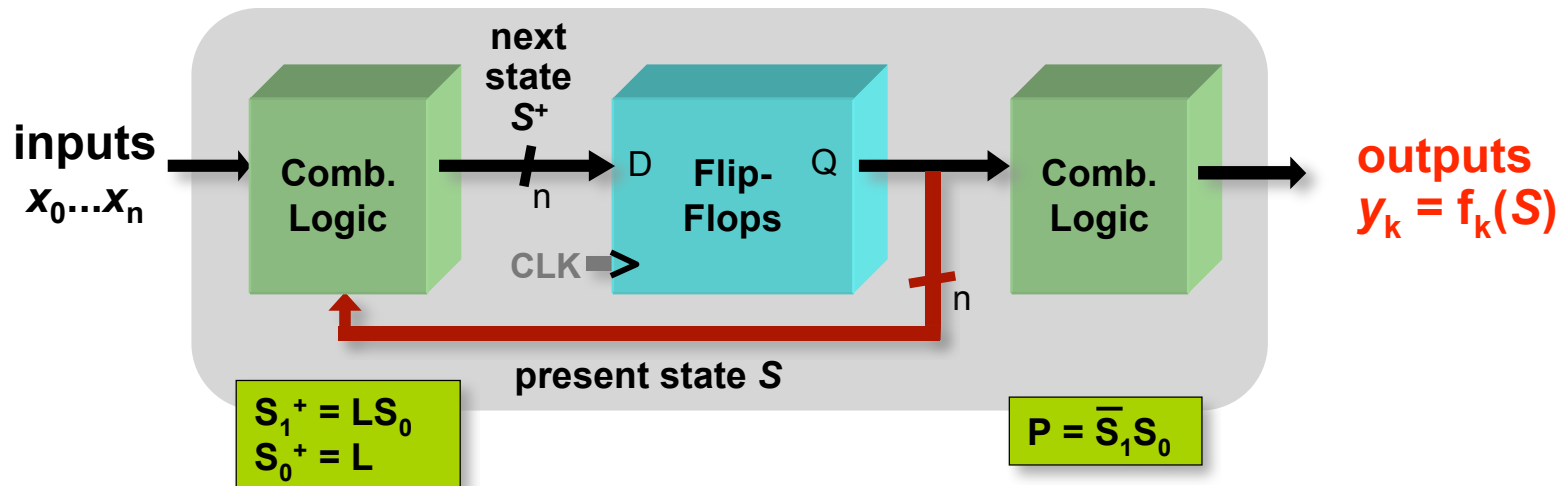

 
Moore FSM circuit implementation of level-to-pulse converter:




Design of a Mealy Level-to-Pulse

 

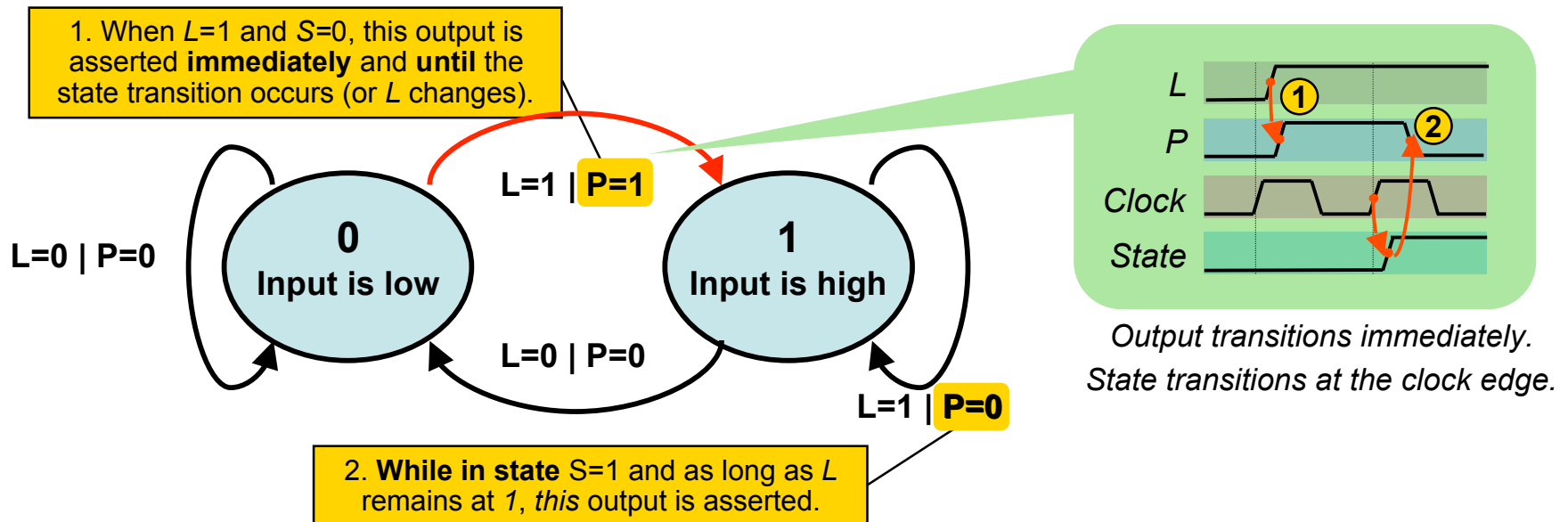- Since outputs are determined by state *and* inputs, Mealy FSMs may need fewer states than Moore FSM implementations




Mealy Level-to-Pulse Converter

 

Pres. State	In	Next State	Out
S	L	S⁺	P
0	0	0	0
0	1	1	1
1	0	0	0
1	1	1	0


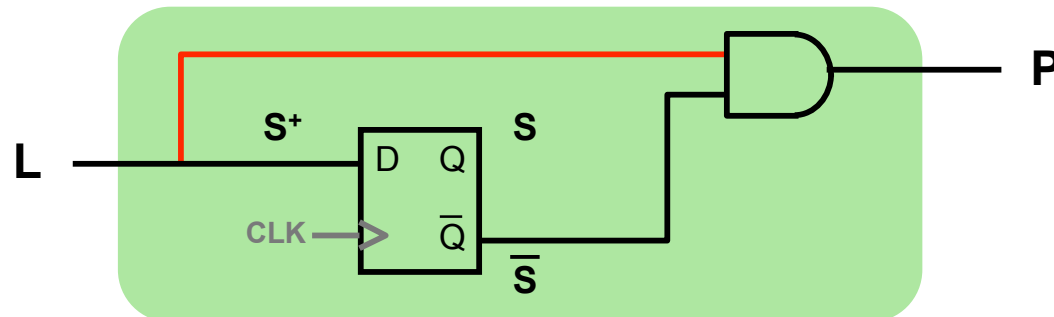
Mealy FSM circuit implementation of level-to-pulse converter:



- FSM's state simply remembers the previous value of L
- Circuit benefits from the Mealy FSM's implicit single-cycle assertion of outputs during state transitions


Moore/Mealy Trade-Offs

  - How are they different?
 - Moore: **outputs = f(state)** only
 - Mealy **outputs = f(state and input)**
 - Mealy outputs generally occur one cycle earlier than a Moore:



- Compared to a Moore FSM, a Mealy FSM might...
 - Be more difficult to conceptualize and design
 - Have fewer states

Light Switch Revisited

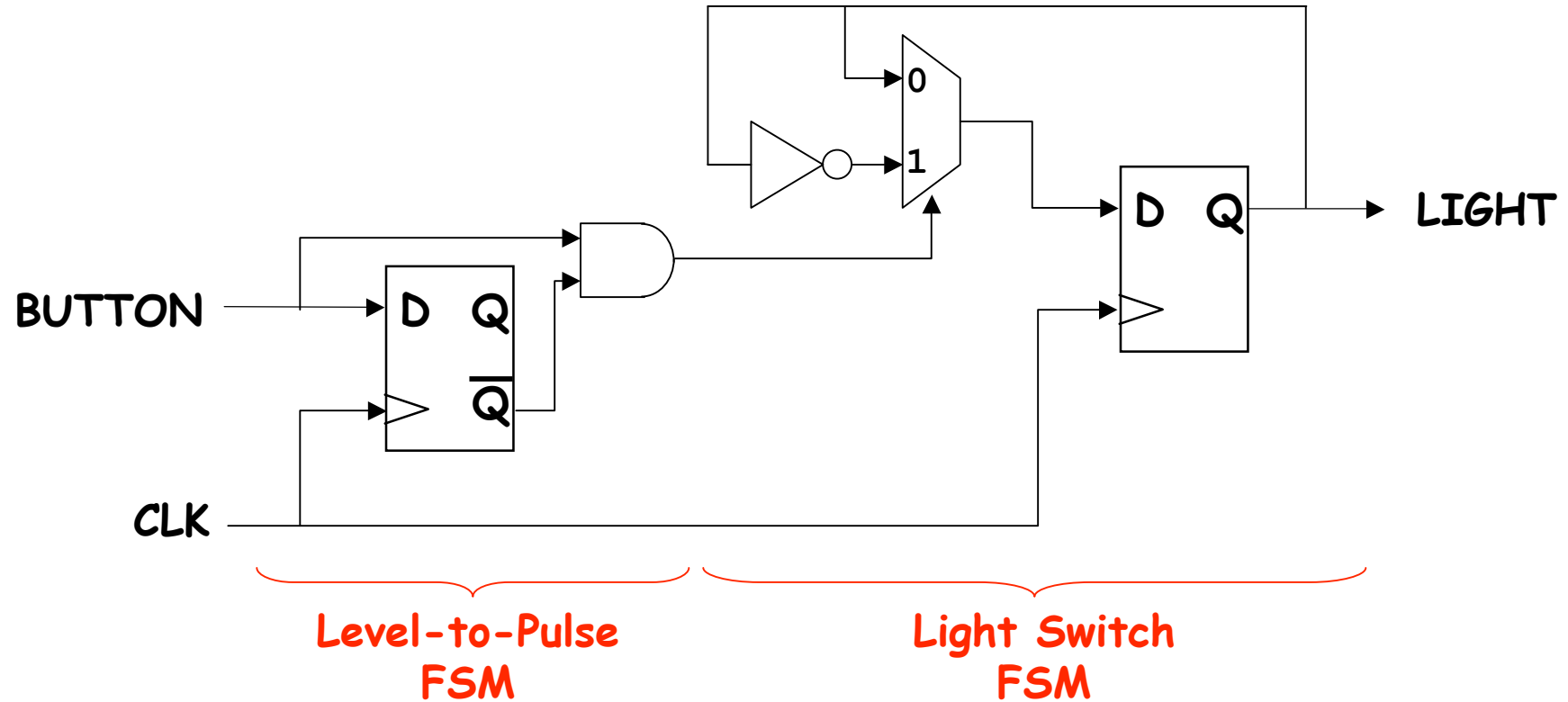

FSM Example

GOAL:


Build an electronic combination lock with a reset button, two number buttons (0 and 1), and an unlock output. The combination should be **01011**.




STEPS:

1. Design lock FSM (block diagram, state transitions)
2. Write Verilog module(s) for FSM

Step 1A: Block Diagram

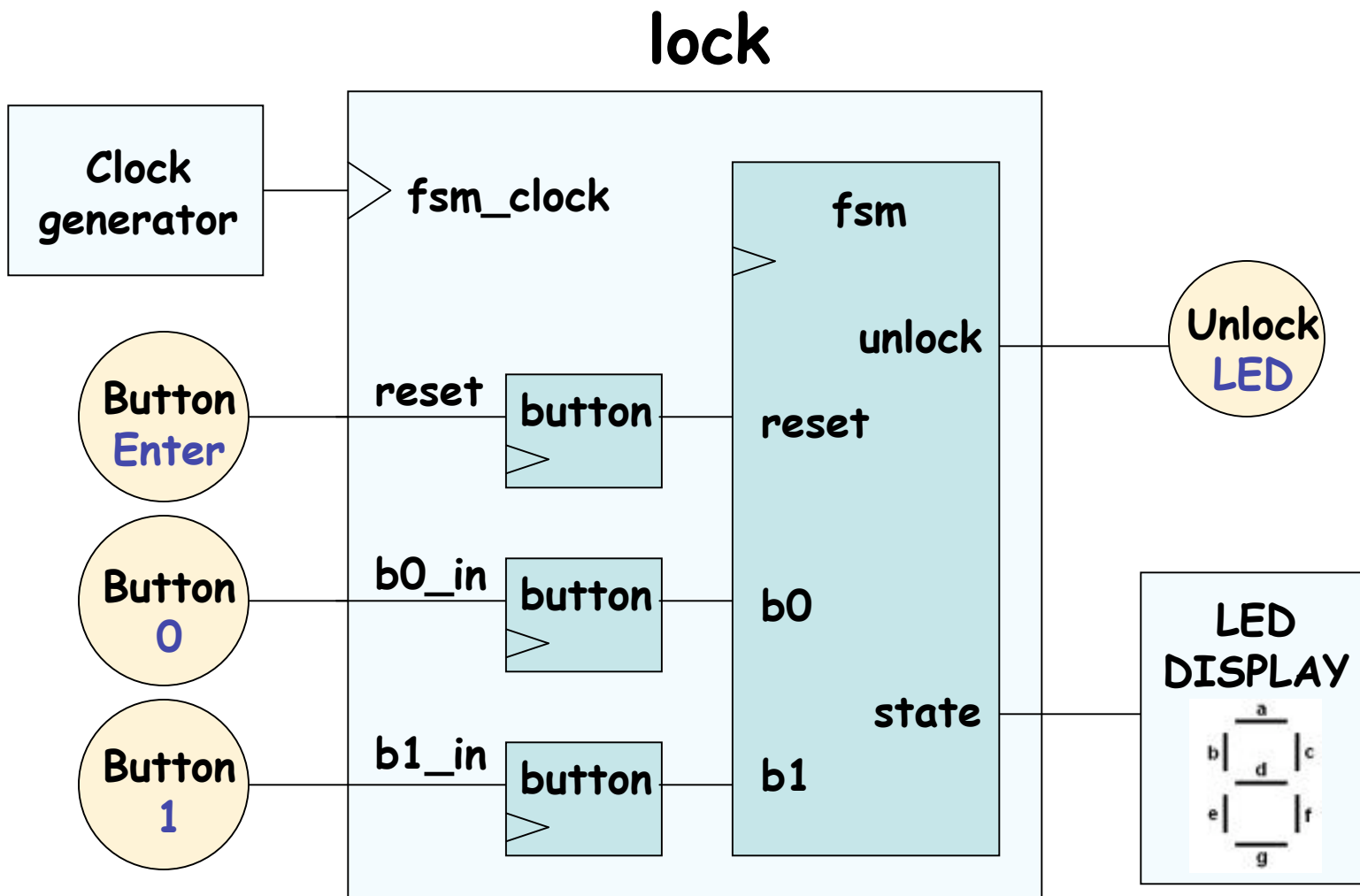

Step 1B: State transition diagram

 

Step 2: Write Verilog

```
module lock(clk,reset_in,b0_in,b1_in,out);  
  
    input clk,reset,b0_in,b1_in;  
    output out;  
  
    // synchronize push buttons, convert to pulses  
  
    // implement state transition diagram  
    reg [2:0] state,next_state;  
    always @ (*) begin  
        // combinational logic!  
        next_state = ???;  
    end  
    always @ (posedge clk) state <= next_state;  
  
    // generate output  
    assign out = ???;  
  
    // debugging?  
endmodule
```


Step 2A: Synchronize buttons

```
// button -- push button synchronizer and level-to-pulse converter
// OUT goes high for one cycle of CLK whenever IN makes a
// low-to-high transition.
```

```
module button(clk,in,out);
  input clk;
  input in;
  output out;

  reg r1,r2,r3;
  always @ (posedge clk)
  begin
    r1 <= in;      // first reg in synchronizer
    r2 <= r1;      // second reg in synchronizer, output is in sync!
    r3 <= r2;      // remembers previous state of button
  end

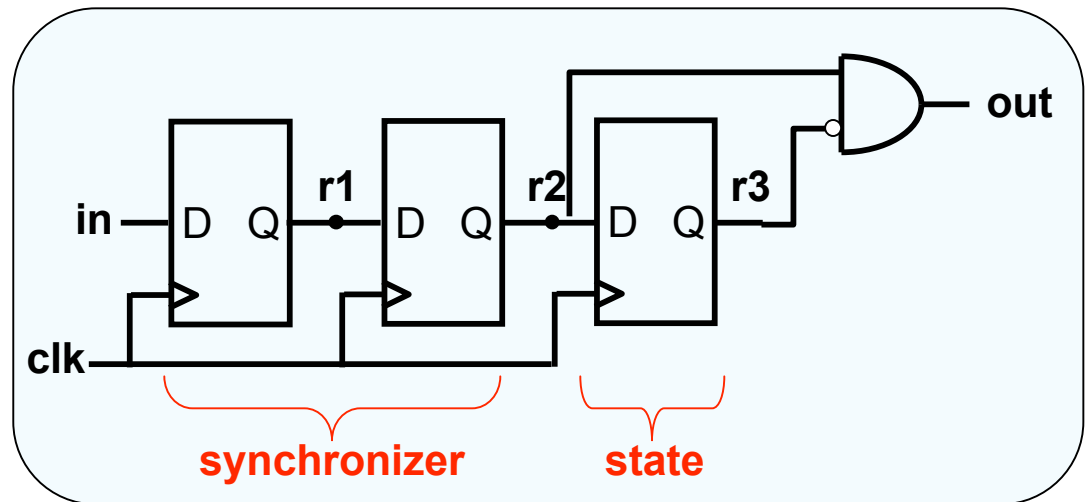  // rising edge = old value is 0, new value is 1
  assign out = ~r3 & r2;
endmodule
```



Step 2B: state transition diagram

```

parameter S_RESET = 0; // state assignments
parameter S_0 = 1;
parameter S_01 = 2;
parameter S_010 = 3;
parameter S_0101 = 4;
parameter S_01011 = 5;

```

```

reg [2:0] state, next_state;
always @ (*) begin

```

```

// implement state transition diagram

```

```

if (reset) next_state = S_RESET;

```

```

else case (state)

```

```

    S_RESET: next_state = b0 ? S_0      : b1 ? S_RESET : state;

```

```

    S_0:      next_state = b0 ? S_0      : b1 ? S_01     : state;

```

```

    S_01:     next_state = b0 ? S_010    : b1 ? S_RESET  : state;

```

```

    S_010:    next_state = b0 ? S_0      : b1 ? S_0101   : state;

```

```

    S_0101:   next_state = b0 ? S_010    : b1 ? S_01011  : state;

```

```

    S_01011:  next_state = b0 ? S_0      : b1 ? S_RESET  : state;

```

```

    default:  next_state = S_RESET; // handle unused states

```

```

endcase

```

```


end

```

```

always @ (posedge clk) state <= next_state;

```

 

Step 2C: generate output

```
// it's a Moore machine! Output only depends on current state
```

```
assign out = (state == S_01011);
```

Step 2D: debugging?

```
// hmmm. What would be useful to know? Current state?
```

```
assign hex_display = {1'b0,state[2:0]};
```

Step 2: final Verilog implementation

```
module lock(clk,reset_in,b0_in,b1_in,out, hex_display);

    input clk,reset,b0_in,b1_in;
    output out; output[3:0] hex_display;


    wire reset, b0, b1; // synchronize push buttons, convert to pulses
    button b_reset(clk,reset_in,reset);
    button b_0(clk,b0_in,b0);
    button b_1(clk,b1_in,b1);

    parameter S_RESET = 0; parameter S_0 = 1; // state assignments
    parameter S_01 = 2; parameter S_010 = 3;
    parameter S_0101 = 4; parameter S_01011 = 5;


    reg [2:0] state,next_state;
    always @ (*) begin // implement state transition diagram
        if (reset) next_state = S_RESET;
        else case (state)
            S_RESET: next_state = b0 ? S_0 : b1 ? S_RESET : state;
            S_0: next_state = b0 ? S_0 : b1 ? S_01 : state;
            S_01: next_state = b0 ? S_010 : b1 ? S_RESET : state;
            S_010: next_state = b0 ? S_0 : b1 ? S_0101 : state;
            S_0101: next_state = b0 ? S_010 : b1 ? S_01011 : state;
            S_01011: next_state = b0 ? S_0 : b1 ? S_RESET : state;
            default: next_state = S_RESET; // handle unused states
        endcase
    end
    always @ (posedge clk) state <= next_state;
    assign out = (state == S_01011); // assign output: Moore machine
    assign hex_display = {1'b0,state}; // debugging
endmodule
```


Where should CLK come from?

 - Option 1: external crystal
 - Stable, known frequency, typically 50% duty cycle
- Option 2: internal signals
 - Option 2A: output of combinational logic



 - No! If inputs to logic change, output may make several transitions before settling to final value → several rising edges, not just one! Hard to design away output glitches...
- Option 2B: output of a register
 - Okay, but timing of CLK2 won't line up with CLK1



Summary

- Modern digital system design:
 - Hardware description language → FPGA / ASIC

- **Toolchain:**

- Design Entry → Synthesis → Implementation
- Simulate

- **New Labkit:**

- Black-box peripherals
- Almost all functionality is programmed in!
- How to generate video?
Synchronize systems?
Create/Digitize Audio?
Serial & communications?

