 


The Last Lecture!


1. Schedule
2. FSM++
3. FGPA's @ Home



Schedule Reminders

- Fri, 10/26: Lab #5 checkoff by 5pm
- Mon, 10/29: upload Project Abstract by 5pm
- Wed, 10/31: Quiz, 7:30p - 9:30p, 34-101
- Fri, 11/03: mandatory writing workshop, 1p, 34-101
complete proposal meeting with mentor
upload Project Proposal by 5pm
- Fri, 11/10: upload CI-M final version by 5pm
complete block diagram meeting w/ mentor
- Tu, W, Th: 15min design presentations
11/12-15 schedule TBA (we'll email you!)
please upload slides to website
- Fri, 11/16: upload Project Checklist by 5pm
- M, Tu, W : project presentations & videotaping
12/10-12 schedule TBA (we'll email you!)
- Wed, 12/12: upload Final Project Report by 5pm
(sorry, no extensions possible!)


Digital Systems = FSMs + Datapath

 


But what if my FSM has hundreds or thousands of states? That's a BIG case statement!

Microsequencers

Step 1: use a counter for the state

 


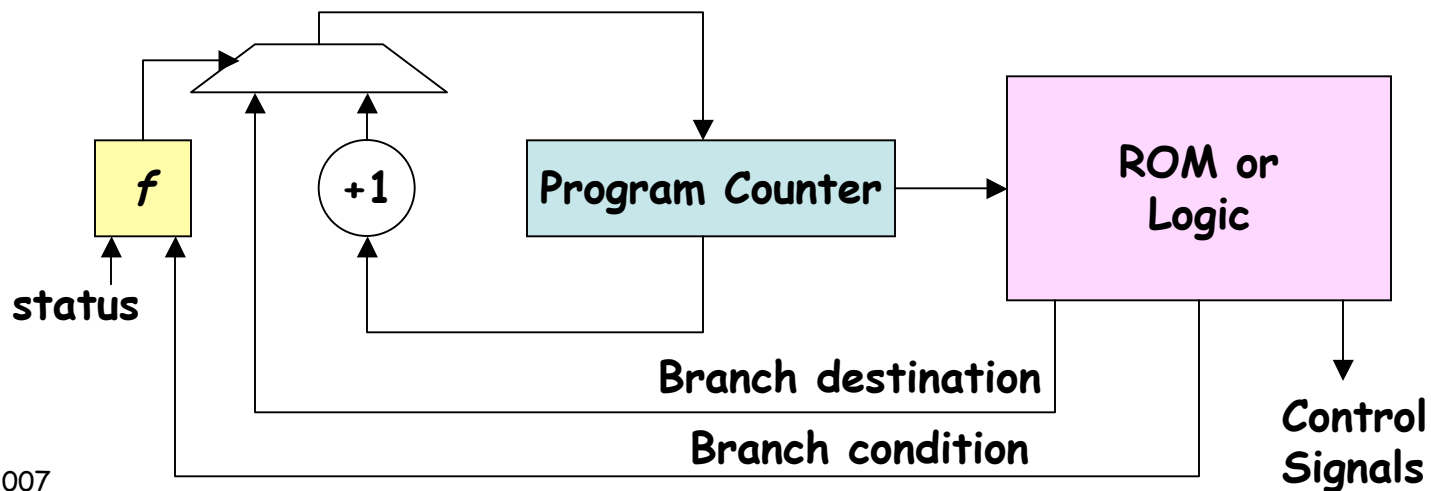Step 2: add a conditional branch mechanism




Microsequencers (cont'd.)

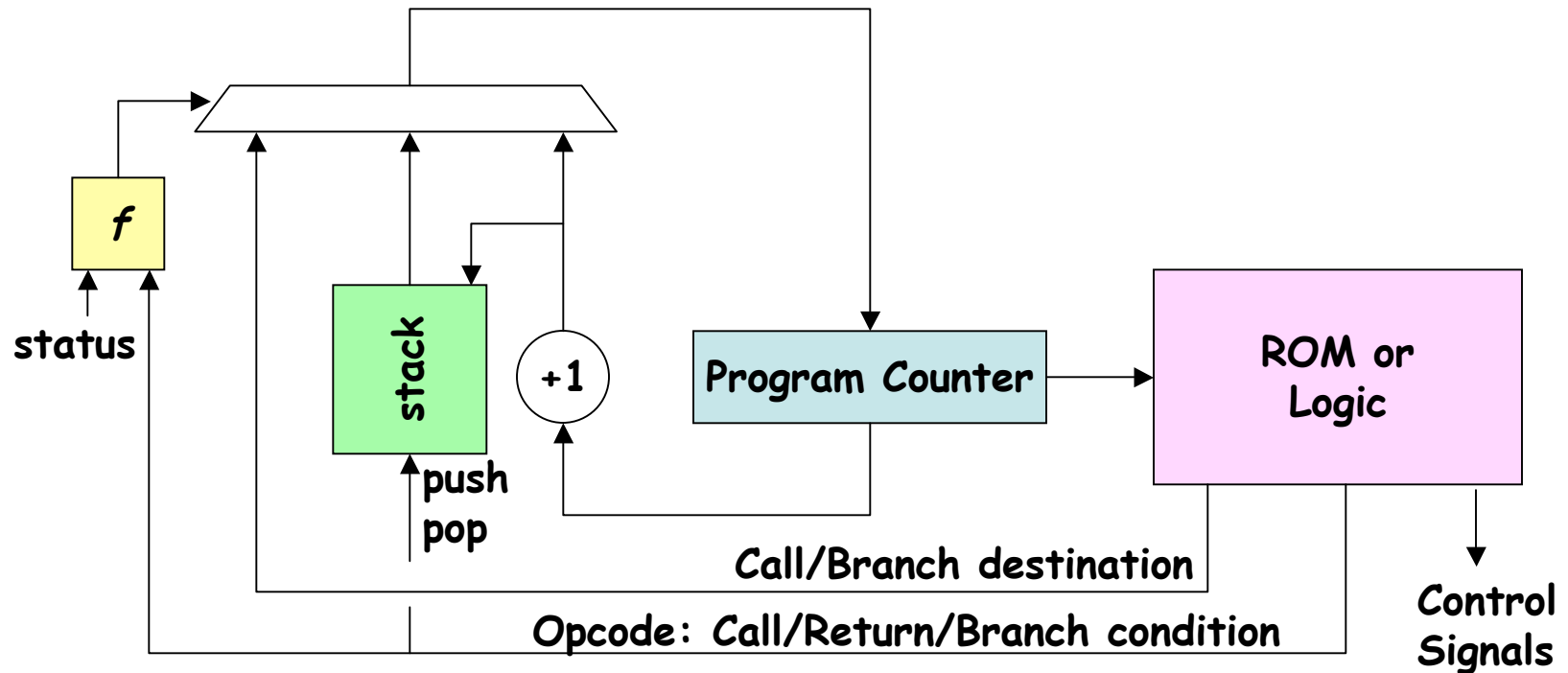Step 3: add a (small) call/return stack to support "subroutines"



Subroutine call: select destination as new PC, push PC+1 onto stack
Subroutine return: select top of stack as new PC, pop stack

Xilinx PicoBlaze™

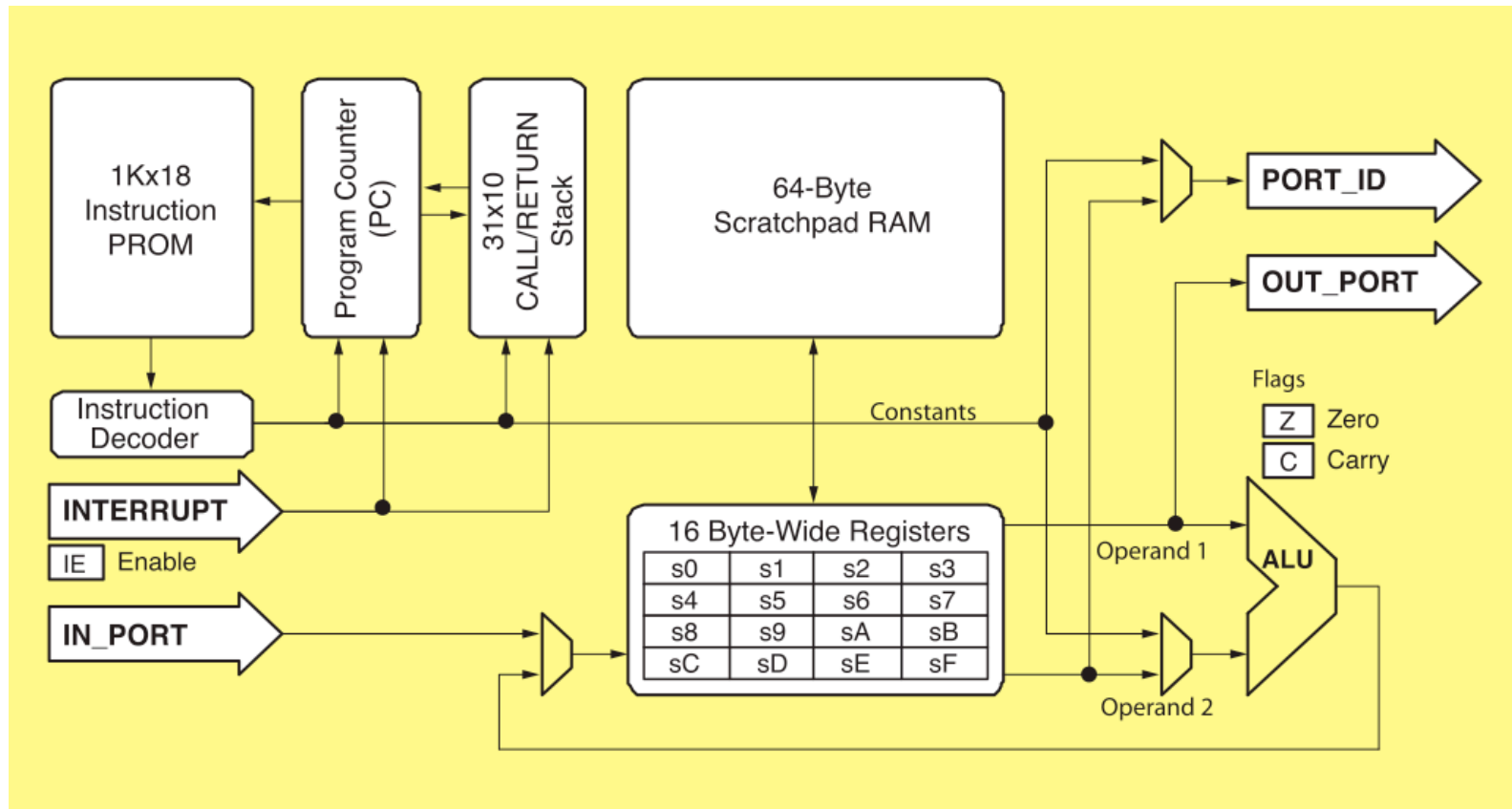


- **8-bit data path**
- **internal memory**
 - 1K 18-bit insts
 - 31-locn stack
 - 16 8-bit registers
 - 64-locn local mem
- **external 8-bit ports**
 - 256 in, 256 out
- **small: only 96 slices + inst mem**
- **fast: 2 cycles/inst [IF→EXE]**
200MHz (100MIPS) on labkit

PicoBlaze Instructions


Conditional and unconditional flow of control



 8-bit ALU:
 $\langle r1 \rangle \langle op \rangle = \langle r2 \rangle$
 $\langle r1 \rangle \langle op \rangle = \text{const}$



Access to 64-locn local mem

 

Interrupt management

<u>Program Control</u>	<u>Logical</u>	<u>Arithmetic</u>
JUMP aaa	LOAD sX,kk	ADD sX,kk
JUMP Z,aaa	AND sX,kk	ADDCY sX,kk
JUMP NZ,aaa	OR sX,kk	SUB sX,kk
JUMP C,aaa	XOR sX,kk	SUBCY sX,kk
JUMP NC,aaa	TEST sX,kk	COMPARE sX,kk
	LOAD sX,sY	ADD sX,sY
CALL aaa	AND sX,sY	ADDCY sX,sY
CALL Z,aaa	OR sX,sY	SUB sX,sY
CALL NZ,aaa	XOR sX,sY	SUBCY sX,sY
CALL C,aaa	TEST sX,sY	COMPARE sX,sY
CALL NC,aaa		
	<u>Shift and Rotate</u>	<u>Storage</u>
RETURN	SR0 sX	FETCH sX,ss
RETURN Z	SR1 sX	FETCH sX,(sY)
RETURN NZ	SRX sX	STORE sX,ss
RETURN C	SRA sX	STORE sX,(sY)
RETURN NC	RR sX	
	SL0 sX	<u>Interrupt</u>
	SL1 sX	RETURNI ENABLE
	SLX sX	RETURNI DISABLE
	SLA sX	ENABLE INTERRUPT
	RL sX	DISABLE INTERRUPT
<u>Input/Output</u>		
INPUT sX,pp		
INPUT sX,(sY)		
OUTPUT sX,pp		
OUTPUT sX,(sY)		


Access to external devices




All instructions execute in 2 clock cycles

A "Real" Processor: the Beta!

Is this 6.004??????

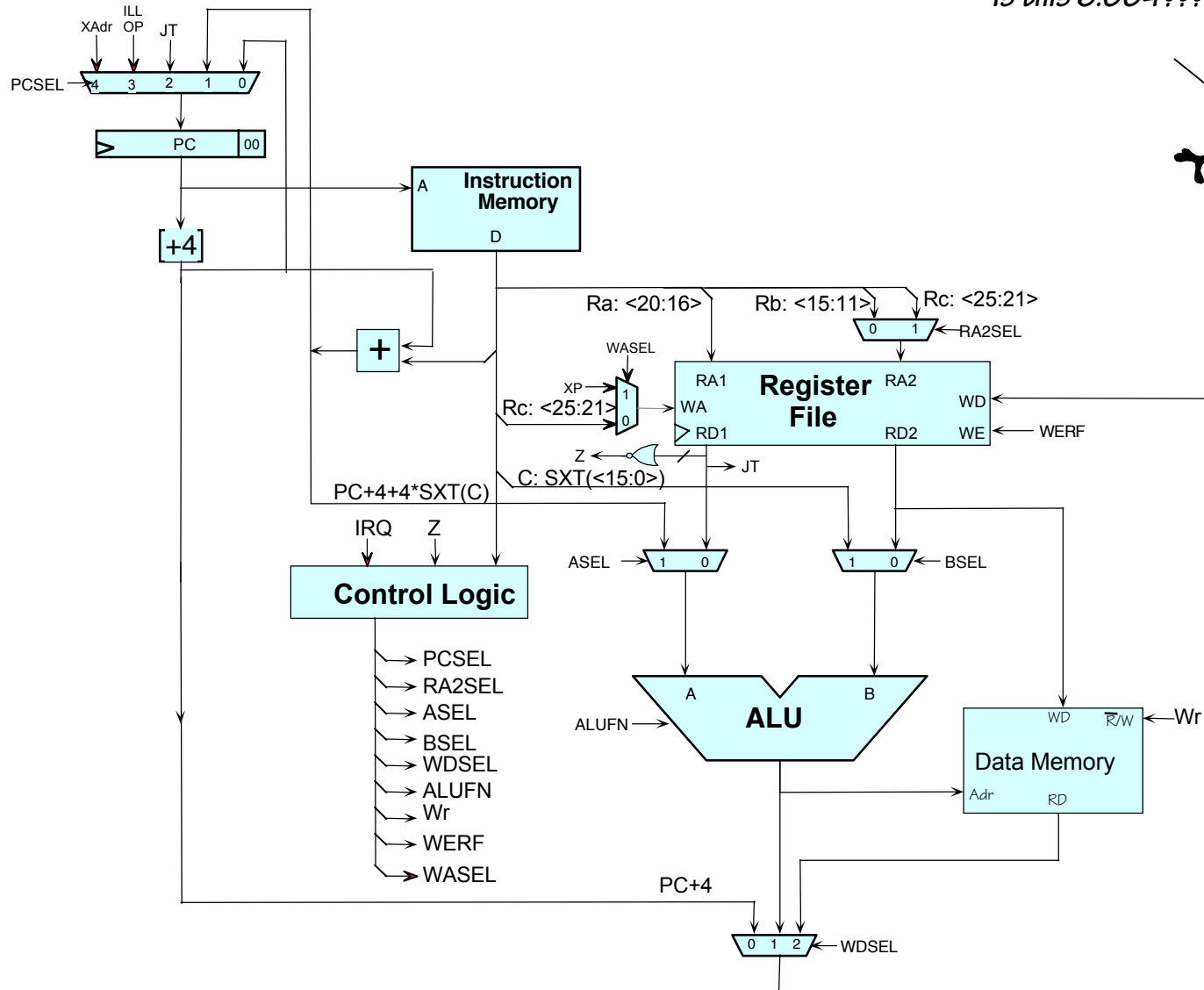


Beta Instructions - I

 

OP(Ra,Rb,Rc): $\text{Reg}[Rc] \leftarrow \text{Reg}[Ra] \text{ op } \text{Reg}[Rb]$

Opcodes:

 ADD (plus), SUB (minus), MUL (multiply), DIV (divided by),
AND (bitwise and), OR (bitwise or), XOR (bitwise exclusive or)
CMPEQ (equal), CMPLT (less than), CMPLE (less than or equal) [result = 1 if true, 0 if false]
SHL (left shift), SHR (right shift w/o sign extension), SRA (right shift w/ sign extension)




OPC(Ra,literal,Rc): $\text{Reg}[Rc] \leftarrow \text{Reg}[Ra] \text{ op } \text{SEXT}(\text{literal})$

Opcodes:

ADDC (plus), SUBC (minus), MULC (multiply), DIVC (divided by)
ANDC (bitwise and), ORC (bitwise or), XORC (bitwise exclusive or)
CMPEQC (equal), CMPLTC (less than), CMPLEC (less than or equal) [result = 1 if true, 0 if false]
SHLC (left shift), SHRC (right shift w/o sign extension), SRAC (right shift w/ sign extension)

Beta Instructions - II

 

LD(Ra,literal,Rc): $\text{Reg}[\text{Rc}] \leftarrow \text{Mem}[\text{Reg}[\text{Ra}] + \text{SEXT}(\text{literal})]$

ST(Rc,literal,Ra): $\text{Mem}[\text{Reg}[\text{Ra}] + \text{SEXT}(\text{literal})] \leftarrow \text{Reg}[\text{Rc}]$

JMP(Ra,Rc): $\text{Reg}[\text{Rc}] \leftarrow \text{PC} + 4; \text{PC} \leftarrow \text{Reg}[\text{Ra}]$

BEQ/BF(Ra,label,Rc): $\text{Reg}[\text{Rc}] \leftarrow \text{PC} + 4;$
if $\text{Reg}[\text{Ra}] = 0$ then $\text{PC} \leftarrow \text{PC} + 4 + 4 * \text{SEXT}(\text{literal})$

BNE/BT(Ra,label,Rc): $\text{Reg}[\text{Rc}] \leftarrow \text{PC} + 4;$
if $\text{Reg}[\text{Ra}] \neq 0$ then $\text{PC} \leftarrow \text{PC} + 4 + 4 * \text{SEXT}(\text{literal})$


LDR(label,Rc): $\text{Reg}[\text{Rc}] \leftarrow \text{Mem}[\text{PC} + 4 + 4 * \text{SEXT}(\text{literal})]$

Beta Control Logic


	<i>OP</i>	<i>OPC</i>	<i>LD</i>	<i>ST</i>	<i>JMP</i>	<i>BEQ</i>	<i>BNE</i>	<i>LDR</i>	<i>I/lop</i>	<i>trap</i>
<i>ALUFN</i>	F(op)	F(op)	"+"	"+"	—	—	—	"A"	—	—
<i>WERF</i>	1	1	1	0	1	1	1	1	1	1
<i>BSEL</i>	0	1	1	1	—	—	—	—	—	—
<i>WDSEL</i>	1	1	2	—	0	0	0	2	0	0
<i>WR</i>	0	0	0	1	0	0	0	0	0	0
<i>RA2SEL</i>	0	—	—	1	—	—	—	—	—	—
<i>PCSEL</i>	0	0	0	0	2	Z ? 1 : 0	Z ? 0 : 1	0	3	4
<i>ASEL</i>	0	0	0	0	—	—	—	1	—	—
<i>WASEL</i>	0	0	0	—	0	0	0	0	1	1

Beta2 (see attached sheet)

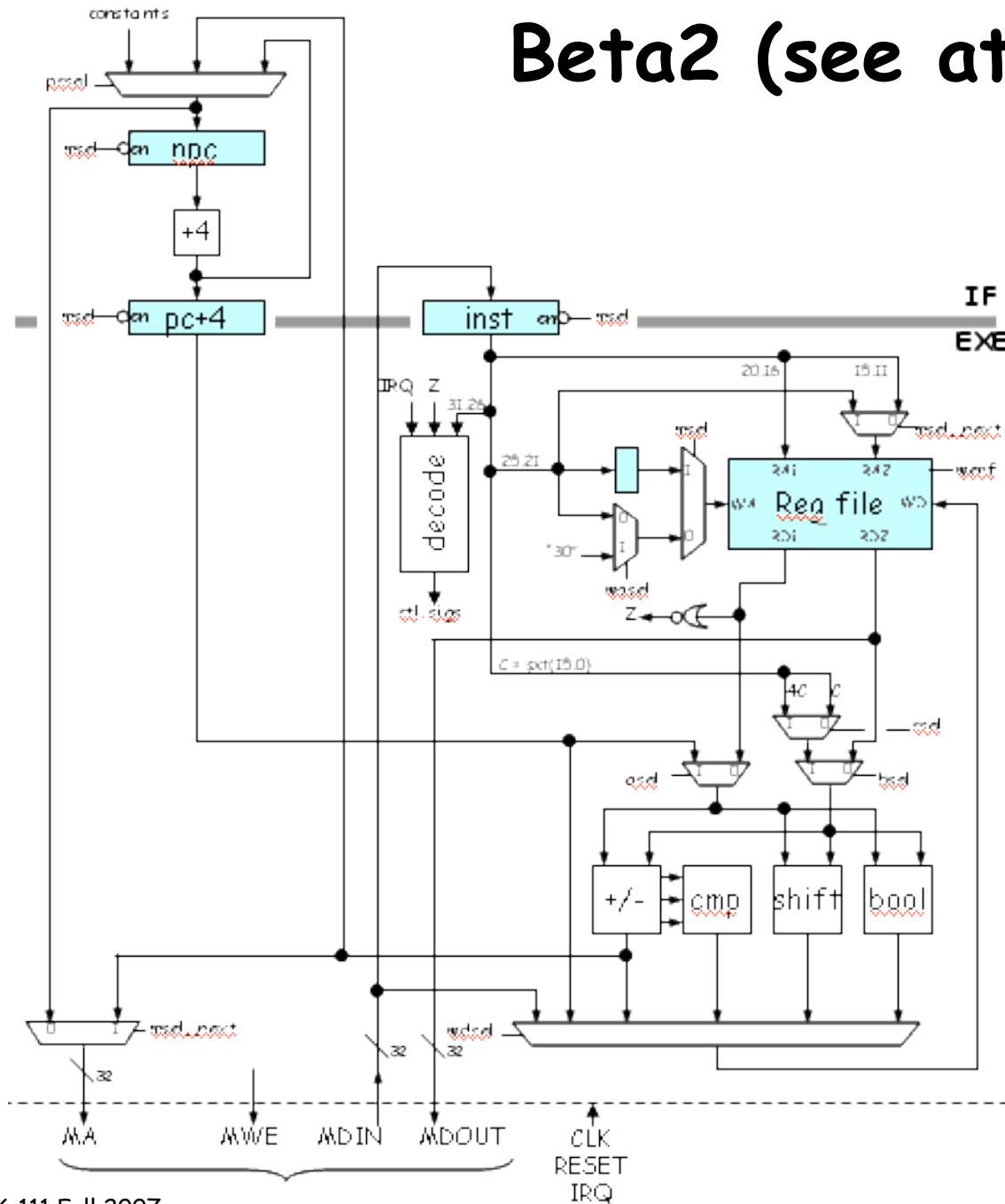- 2-stage pipeline, 1 annuled branch delay slot
- Memory ops (LD, LDR, ST) take two cycle in EXE stage: addr computed in 1st cycle, memory access made in 2nd
- Branch and LDR address arithmetic performed in ALU
- JMP routed thru ALU
- Single memory port shared by inst. fetch and memory access




Xilinx Synchronous Block Memory

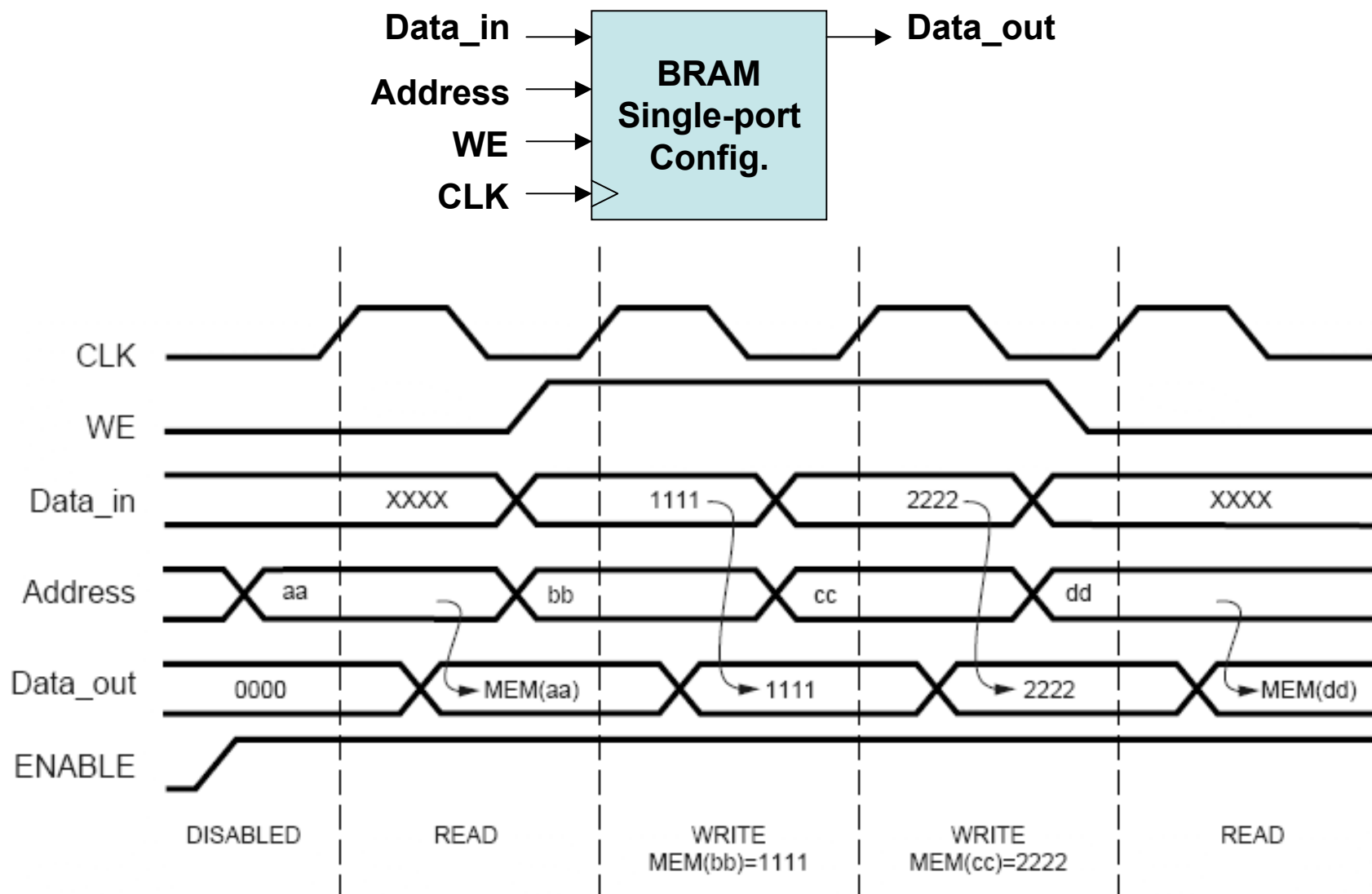

100: LD (R31, 6004, R2)
 104: ADDC (R2, 47, R2)
 108: ST (R2, 44, R31)
 10C: XORC (R2, -1, R2)
 110: ...
 ...
 6004: 123

Instruction Pipeline Diagram

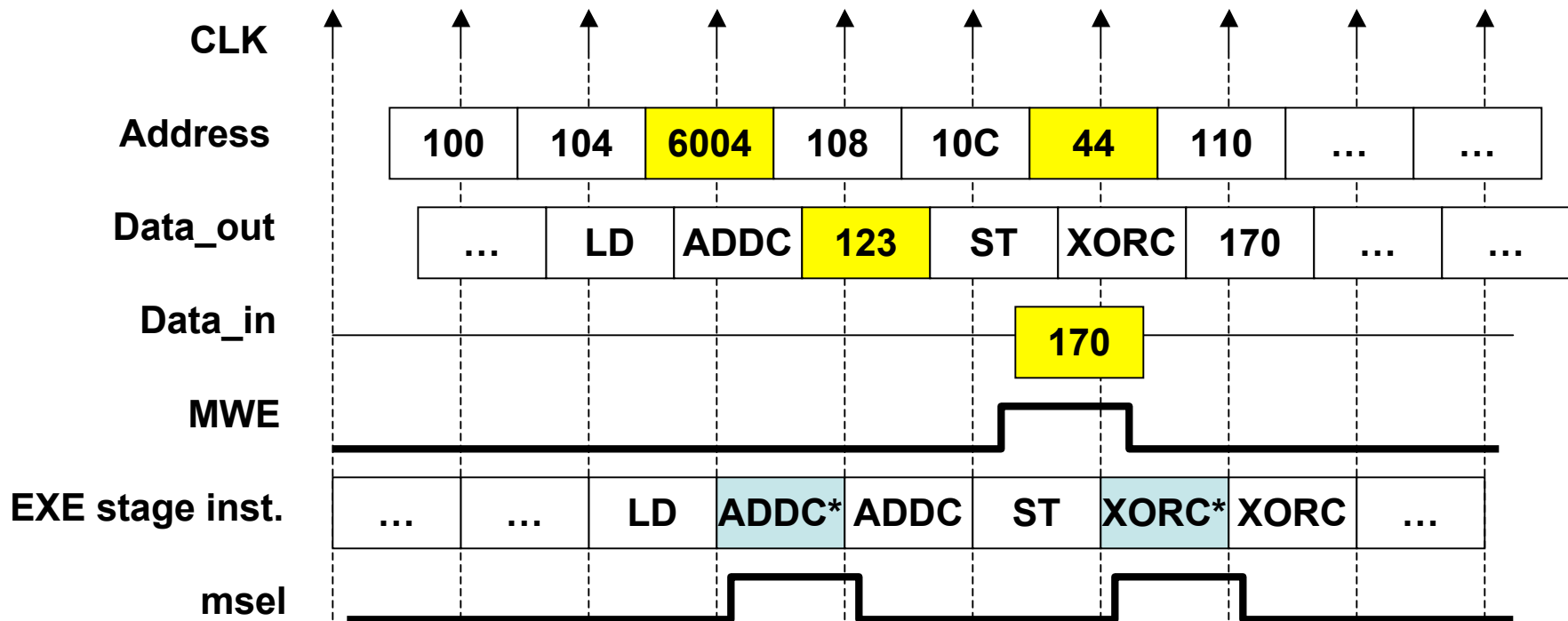

* Stalled in pipeline


beta2.v

```
module beta2 (clk, reset, irq, ma, mdin, mdout, mwe) ;
  input clk, reset, irq;
  output [31:0] ma, mdout;
  input [31:0] mdin;
  output mwe;


  // beta2 registers
  reg [31:0] regfile[31:0];
  reg [31:0] npc, pc_inc, inst;
  reg [4:0] rc_save; // needed for second cycle on LD, LDR

  // internal buses
  wire [31:0] rd1, rd2, wd, a, b, xb, c, addsub, cmp, shift, boole;

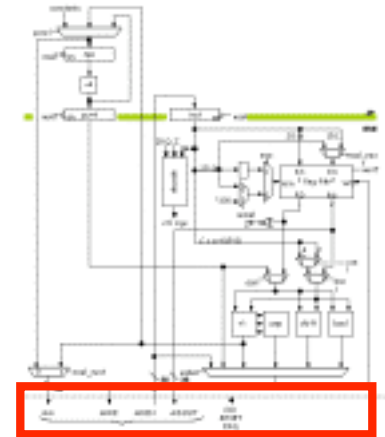  // control signals
  wire wasel, werf, z, asel, bsel, csel;
  wire addsub_op, cmp_lt, cmp_eq, shift_op
  wire shift_sxt, boole_and, boole_or;
  ...
endmodule
```



PC Logic

 


```
// pc
wire [31:0] npc_inc, npc_next;

assign npc_inc = npc + 4;
assign npc_next = reset ? 32'h80000000 :
    msel ? npc :
    branch ? {npc[31]&addsub[31],
              addsub[30:2], 2'b00} :
    trap ? 32'h80000004 :
    interrupt ? 32'h80000008 :
    npc_inc;

always @ (posedge clk) begin
    npc <= npc_next;    // stall on msel handled above
    if (!msel) pc_inc <= npc_inc;
end
```


Instruction Register & Decode

 

```
// instruction reg
always @ (posedge clk) if (!msel) inst <= mdin;
```


```
// control logic
decode ctl(.clk(clk), .reset(reset), .irq(irq & !npc[31]),
    .z(z), .opcode(inst[31:26]),
    .asel(asel), .bse1(bse1), .cse1(cse1),
    .wase1(wase1), .werf(werf), .mse1(mse1),
    .mse1_next(mse1_next), .mwe(mwe),
    .addsub_op(addsub_op), .cmp_lt(cmp_lt),
    .cmp_eq(cmp_eq),
    .shift_op(shift_op), .shift_sxt(shift_sxt),
    .boole_and(boole_and), .boole_or(boole_or),
    .wd_addsub(wd_addsub), .wd_cmp(wd_cmp),
    .wd_shift(wd_shift), .wd_boole(wd_boole),
    .branch(branch), .trap(trap),
    .interrupt(interrupt));
```

Register File

```
// register file
wire [4:0] ra1,ra2,wa;
always @ (posedge clk)
    if (!msel) rc_save <= inst[25:21];

assign ra1 = inst[20:16];
assign ra2 = msel_next ? inst[25:21] : inst[15:11];
assign wa = msel ? rc_save :
           wasel ? 5'd30 : inst[25:21];
assign rd1 = (ra1 == 31) ? 0 : regfile[ra1];
assign rd2 = (ra2 == 31) ? 0 : regfile[ra2];
always @ (posedge clk)
    if (werf) regfile[wa] <= wd;

assign z = ~| rd1;    // used in BEQ/BNE instructions
```

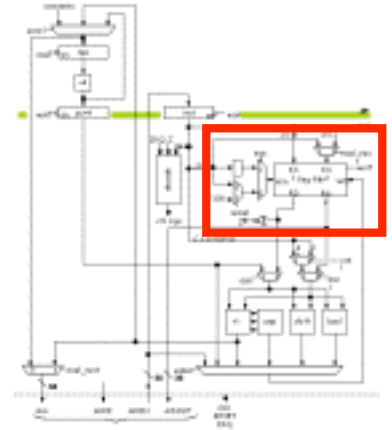

ALU


```
// alu
assign a = asel ? pc_inc : rd1;
assign b = bsel ? c : rd2;
assign c = csel ? {{14{inst[15]}},inst[15:0],2'b00} :
               {{16{inst[15]}},inst[15:0]};

wire addsub_n,addsub_v,addsub_z;
assign xb = {32{addsub_op}} ^ b;
assign addsub = a + xb + addsub_op;
assign addsub_n = addsub[31];
assign addsub_v = (addsub[31] & ~a[31] & ~xb[31]) |
                  (~addsub[31] & a[31] & xb[31]);
assign addsub_z = ~| addsub;


assign cmp[31:1] = 0;
assign cmp[0] = (cmp_lt & (addsub_n ^ addsub_v)) |
                (cmp_eq & addsub_z);

wire [31:0] shift_right;
shift_right sr(shift_sxt,a,b[4:0],shift_right);
assign shift = shift_op ? shift_right : a << b[4:0];

assign boole = boole_and ? (a & b) :
               boole_or ? (a | b) : a ^ b;
```

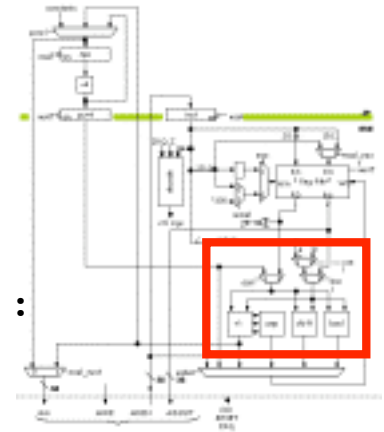

Result Mux, Address Mux

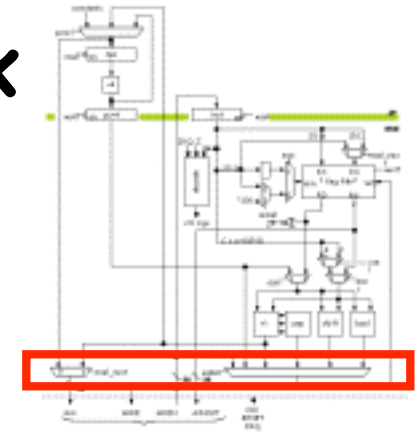

// result mux, listed in order of speed (slowest first)

```
assign wd = msel ? mdin :  
    wd_cmp ? cmp :  
    wd_addsub ? addsub :  
    wd_shift ? shift :  
    wd_boole ? boole :  
    pc_inc;
```


// assume synchronous external memory

```
assign ma = msel_next ? addsub : npc_next;  
assign mdout = rd2;
```

Control Logic (decode.v)

```
always @ (opcode or z or annul or irq or reset)
begin
    // initial assignments for all control signals
    asel = 1'hx; bsel = 1'hx; csel = 1'hx;
    addsub_op = 1'hx; shift_op = 1'hx; shift_sxt = 1'hx;
    cmp_lt = 1'hx; cmp_eq = 1'hx;
    boole_and = 1'hx; boole_or = 1'hx;
    wasel = 0; mem_next = 0;
    wd_addsub = 0; wd_cmp = 0; wd_shift = 0; wd_boole = 0;
    branch = 0; trap = 0; interrupt = 0;

     if (irq && !reset && !annul) begin
        interrupt = 1;
        wasel = 1;
    end else casez (opcode)
        6'b011000: begin // LD
            asel = 0; bsel = 1; csel = 0;
            addsub_op = 0;
            mem_next = 1;
        end
    end
```




Control Logic (cont'd.)

...


```
6'b1?1100: begin // SHL, SHLC
    asel = 0; bsel = opcode[4]; csel = 0;
    shift_op = 0;
    wd_shift = 1;
end
6'b1?1101: begin // SHR, SHRC
    asel = 0; bsel = opcode[4]; csel = 0;
    shift_op = 1; shift_sxt = 0;
    wd_shift = 1;
end
6'b1?1110: begin // SRA, SRAC
    asel = 0; bsel = opcode[4]; csel = 0;
    shift_op = 1; shift_sxt = 1;
    wd_shift = 1;
end
default: begin // illegal opcode
    trap = !annul; wasel = 1;
end





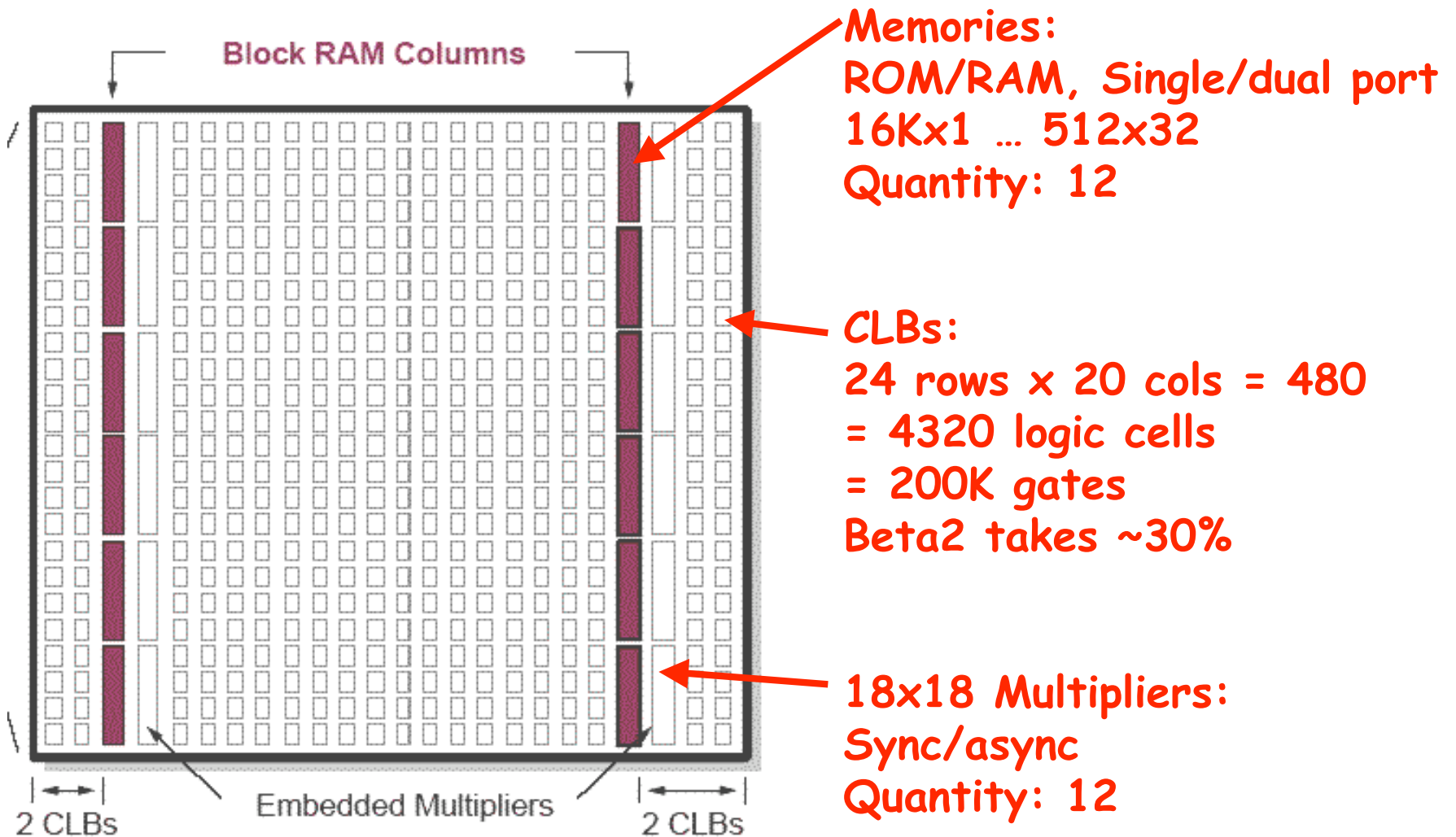


endcase
end // always @ (opcode or ...)
```

 Xilinx XC3S200 FPGA



Beta2 Floorplan




-  *beta2demo "beta2demo"* [15 IOBs, 4 BLKRAMs, 128 DPRAMs, 1051 FGs, 60 FG5s, 90 CYs, 174 DFFs, 1 BUFG]
-  *imem "rom_1k_32"* [2 BLKRAMs]
-  *beta2demo "Primitives"* [15 IOBs, 128 DPRAMs, 1051 FGs, 60 FG5s, 3 CYs, 174 DFFs, 1 BUFG]
-  *dmem "ram_1k_32"* [2 BLKRAMs]
-  CarryChain_5 "CarryChain" [27 CYs] ← Clock divider for 7-seg display
-  CarryChain_3 "CarryChain" [29 CYs] ← npc + 4
-  CarryChain_1 "CarryChain" [31 CYs] ← alu adder


FPGAs @ Home

- **6.111 labkit: the Lexus of FPGA protoboards**
 - XC2V6000 (76032 logic cells, 2.5 Mbits BRAM)
- **Two affordable alternatives (lots more out there)**
 - **Nexys2 Board (www.digilentinc.com)**
 - \$99 = Spartan 3E-500 (10476 logic cells, 360 Kbits BRAM)
 - Switches, buttons, leds, 4-digit display
 - 16Mbyte flash, 16Mbyte SDRAM
 - USB2 slave (power, programming, 8-bit host data stream)
 - PS2, serial port, 256-color VGA, 4 expansion connectors
 - **XSA-3S1000 @ \$199 (www.xess.com)**
 - Spartan XC3S1000 (17480 logic cells, 432 Kbits BRAM)
 - Switches, buttons, 1-digit display
 - 32Mbyte SDRAM, 2Mbyte Flash
 - PS2, 512-color VGA
 - 80-pin expansion connector (protoboard friendly)


Digilent Nexys2 Board

 


Nexys2 Diagram

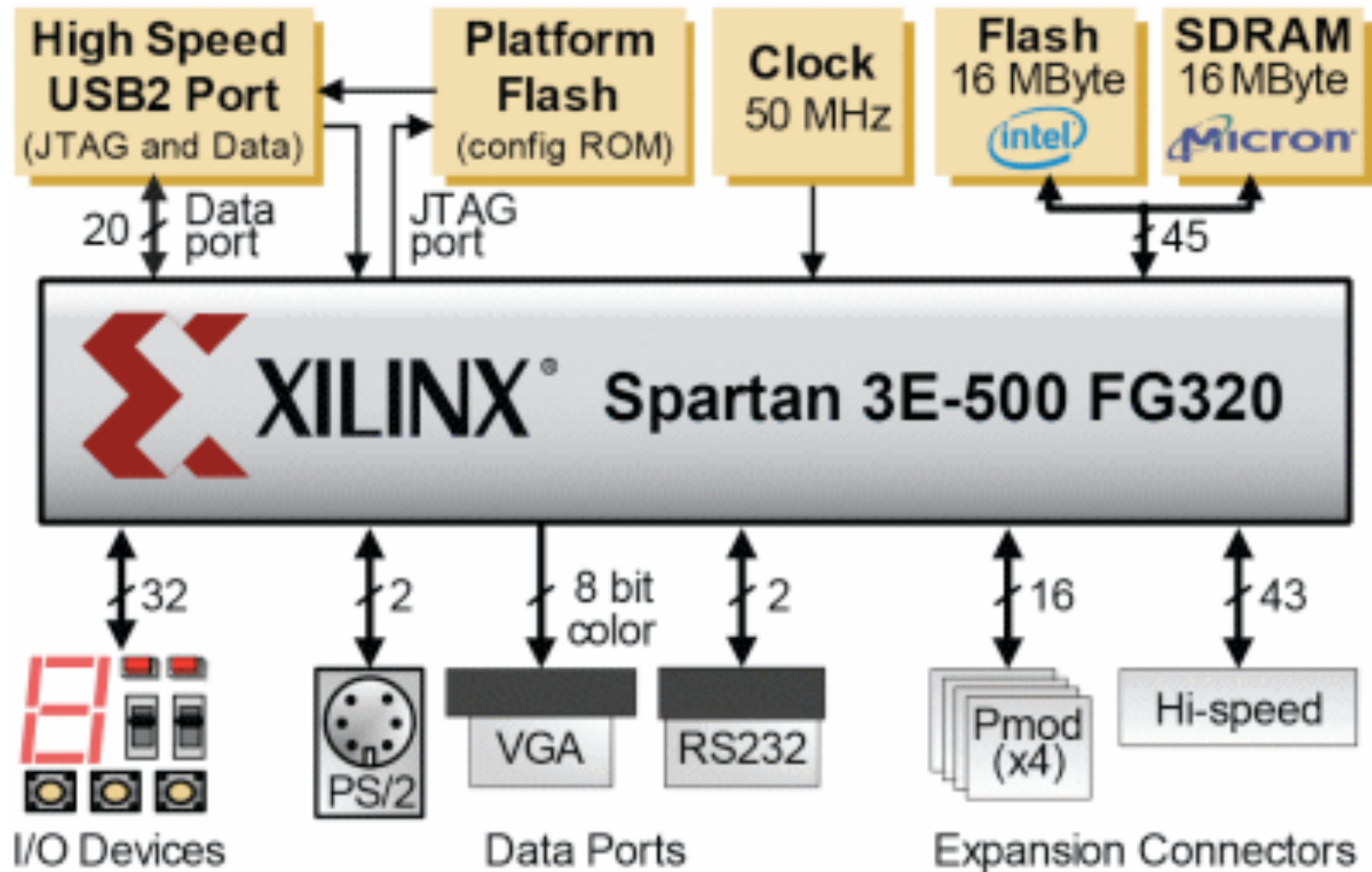

XSA-3S1000

 

XSA-3S1000 Block Diagram

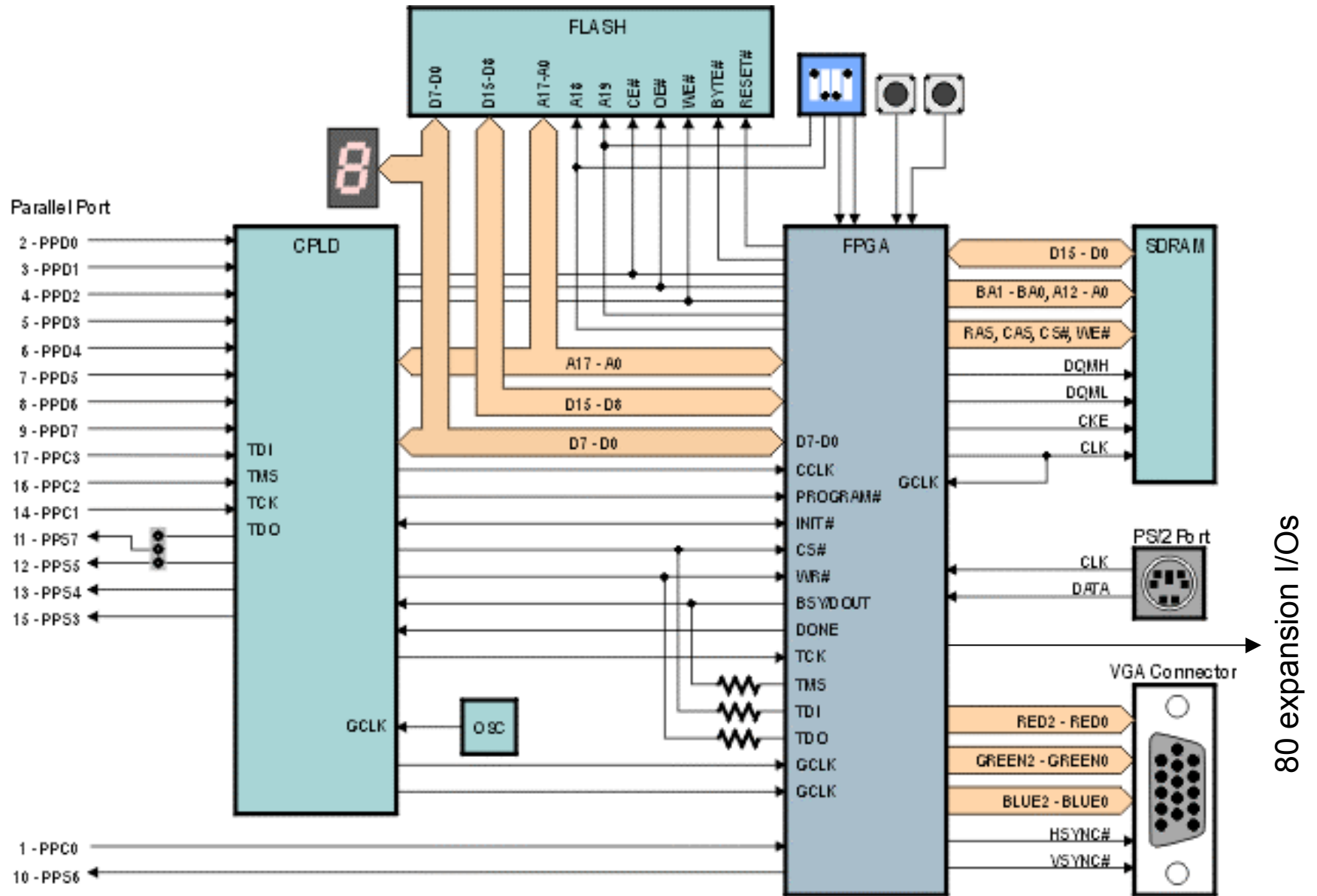

FPGA Software

- **Xilinx ISE Web-pack**
 - Free!
 - Windows 2000/XP, Red Hat Enterprise Linux 3
 - Supports subset of Xilinx FPGAs (but covers the chips used in the boards listed on the previous slide)
 - No IP Wizard, but
 - You can build memories, logic “by hand” using available components (eg, RAMB16_Sxx) and appropriate defparams or attribute assignments - see Xilinx documentation
 - A **lot** of very good design info in Xilinx App Notes (on-line)
 - Built-in simulator
 - Need computer with parallel port to connect programming cable for boards listed on the previous slide
OR use Digilent USB cable for Digilent Boards